



Chapter 5

Logic Design with **Behavioral Models** of Combinational and Sequential Logic



Contents

- Verilog models based on Boolean equations
- More general and abstract style of modeling for combinational and sequential logic
- More general sequential machines consisting of a datapath and a control unit designed by ASM and ASMD
- **ASM** :Algorithmic State Machine
- **ASMD**: Algorithmic State Machine and Datapath



5.1 Behavioral Modeling

- Behavioral modeling is **the predominant descriptive style used by industry**, enabling the design of massive chips
- Behavioral modeling describes **the functionality of a design** —that is: **what the designed circuit will do, not how to build it in hardware**
- Propagation delays **are not included in the behavioral model of the circuit, are considered by the synthesis tool**



Behavioral modeling

- (1) rapidly **create a behavioral prototype** of a design (without binding it to hardware detail)
- (2) **verify its functionality**
- (3) use a synthesis tool to **optimize and map** the design into a selected physical technology, **subject to constraints on timing and/or area**
- Focusing the designer's **attention on the functionality** that is to be implemented ,rather than on individual logic gates and their interconnections
- Provides the freedom to explore **alternatives and tradeoffs before committing a design to production**



Behavioral Modeling

- A much easier way to write testbenches
- Also good for more abstract models of circuits
 - **Easier to write**
 - **Simulates faster**
 - **More flexible**
- Verilog succeeded in part because it allowed both the model and the testbench to be described together




5.2 Data Types for Behavioral Modeling

- Two main data types: **nets and registers**
- *Net variables* **act like wires** in a physical circuits and establish connectivity between designed objects
- *Register variables* **act like variables** in ordinary procedural languages-they **store information while the program executes**
- **Use mainly the net type *wire* and the register types *reg* and *integer* in synthesis**
- A ***wire*** and a ***reg*** have a default size of 1 bit
- An ***integer*** is automatically fixed at the word length ,at least 32 bit



Nets

 - **Physical connections** between structural entities.
- As the driver changes its value, Verilog automatic propagates the value onto a net.
- **Default value is z if no drivers are connected to net**
An undriven wire defaults to a value of Z (high impedance).





Registers

- Registers represent **abstract storage elements**.
- A register holds its value until a new value is assigned to it.
- Registers are used extensively **in behavior modeling and in applying stimuli**.
- **Default value is X.**



Type of Registers

- **reg**
 - Unsigned integer variable of varying bit width
- **integer**
 - Signed integer variable, 32-bit wide. Arithmetic operations produce 2's complement results.
- **real**
 - Signed floating point variable, double precision
- **time**
 - Unsigned integer variable, 64-bit wide.
- **Do not confuse register data type with structural storage element (e.g. D-type FF)**



Choosing the Correct Data Types

- An **input** or **inout** port must be a net.
- An **output** port can be a register or net data type.
- A signal assigned a value in a procedural block must be a register data type.



Common Mistakes in Choosing Data Types

- Make a procedural assignment to a net
wire [7:0] databus;
always @(read or addr) databus=read ? mem[addr] : 'bz;
Illegal left-hand-side assignment
- Connect a register to an instance output
reg myreg;
and (myreg, net1, net2);
Illegal output port specification
- Declare a module **input** port as a register
input myinput;
reg myinput;
Incompatible declaration



Assignments

- Drive values into nets and registers.
- There are two basic forms of assignment
 - Continuous assignment, assigns values to net
 - Procedural assignment, assigns values to register
- Basic form
 - `<left_hand_side> = <right_hand_side>`



Continuous Assignment


- **Another way to describe combinational function**
 - Convenient for logical or datapath specifications
 - wire [8:0] sum;
wire [7:0] a, b;
wire carryin;
assign sum = a + b + carryin;
- Define bus widths
- Continuous assignment:
permanently sets the value of sum to be a+b+carryin
- Recomputed when a, b, or carryin changes



Continuous Assignment

- Any changes in the RHS of the continuous assignment are evaluated and the LHS is updated
- Continuous assignment provides a way to model combinational logic.

```
assign #2 out=in;
```

 



Continuous Assignment

- Right hand side can be
 - Expression
 - `assign and_out = a & b;`
 - Value
 - `assign c = 1;`
 - Other net
 - `assign d = e;`
- Type of continuous assignment declaration
 - The net declaration assignment
 - The continuous assignment statement



Net Declaration Assignment

The net declaration assignment

- `<net_type><drive_strength>?<range>?<delay>?<list_of_assignment>;`

```
wire inv_out = ~in;
```



```
wire #10 inv_out = ~in;
```



```
wire (strong0,pull1) and_out = a&b;
```






5.3 Boolean-Equation-Based Behavioral Models of Combinational Logic

- A Boolean equation describes combinational logic by an expression of operations on variables
- Its counterpart in Verilog is the continuous assignment statement
- **A continuous assignment describe implicit combinational logic**
- A continuous assignment is more compact and understandable than a schematic or a netlist of primitives



Example 5.1 A five-input AOI described statement


```
module AOI_5_CA0 (y_out,x_in1, x_in2,x_in3,x_in4,x_in5);  
  input x_in1, x_in2,x_in3,x_in4,x_in5;  
  output y_out;  
  assign y_out=~((x_in1&x_in2)|(x_in3&x_in4&x_in5));  
endmodule
```

 



Ex 5.2 A five-input AOI with *enable* and have a three-state output

```
module AOI_5_CA1
    (y_out,x_in1, x_in2,x_in3,x_in4,x_in5,enable);
    input  x_in1, x_in2,x_in3,x_in4,x_in5,enable;
    output y_out;
    assign
        y_out=enable ? ~((x_in1&x_in2)|(x_in3&x_in4&x_in5)):1'bz
    endmodule
```

 



Continuous Assignment Statement

- `assign <drive_strength>?<delay>?<list_of_assignment>;`
- The continuous assignment statement drive a net that has been previously declared.

```
module MUX2_to_1(out,i0,i1,sel);  
  output out;  
  input i0,i1,sel;  
  
  assign out = (sel) ? i1 : i0;  
  
endmodule
```



Conditional Operation ? :

- Used with various relational operators
provide convenient mechanisms for description of fairly complex logical functions

- Example:

- 'timescale 1ns/100ps

```
Module quad_mux2_1
```

```
    (input[3:0] i0,i1,input s,output[3:0] y);
```

```
    assign y = s ? i1 : i0 ;
```

```
endmodule
```



Example 5.3

- **Continuous assignments** can also be written implicitly and efficiently (**without the keyword assign**) as part of the declaration of a wire.

```
module AOI_5_CA2
```

```
    (y_out,x_in1, x_in2,x_in3,x_in4,x_in5,enable);
```

```
input  x_in1, x_in2,x_in3,x_in4,x_in5,enable;
```

```
output y_out;
```

```
    wire
```


```
    y_out=enable?~((x_in1&x_in2)|(x_in3&x_in4&x_in5)):1'bz
```

```
endmodule
```



 Example 5.4 A two-channel mux with 32-bit datapaths

```
module Mux_2_32_CA (mux_out, data_1, data_0, select);  
    parameter      word_size=32;  
    output          [word_size-1: 0] mux_out;  
    input           [word_size-1: 0] data_1, data_0;  
    input           select;  
    assign mux_out=select? data_1:data_0;  
endmodule
```





5.4 Propagation Delay and Continuous Assignments

- Propagation (inertial) delay can be associated with a continuous assignment
- So that its implicit logic has the same functionality and timing characteristics as its gate-level counterpart




Ex 5.5 an AOI gate structure with unit propagation delays on its implicit gates

```
module AOI_5_CA3 (y_out,x_in1,x_in2,x_in3,x_in4);  
  input   x_in1,x_in2,x_in3,x_in4;  
  output  y_out;  
  wire #1 y1=x_in1&x_in2;    //bitwise and operation  
  wire #1 y2=x_in3&x_in4;  
  wire #1 y_out=~(y1|y2);    // complement the result of  
                               //   bitwise OR operation  
endmodule
```



Ex. schematic of a 2-bit binary comparator(Fig 4.10)

 



Ex 5.6 a 2-bit comparator described by three continuous assignments

```
module compare_2_CA0
```

```
    (A_lt_B,A_gt_b,A_eq_B,A1,A0,B1,B0);
```

```
input   A1,A0,B1,B0;
```

```
output A_lt_B,A_gt_B,A_eq_B;
```

```
assign A_lt_B=(~A1)&B1|(~A1)&(~A0)&B0|(~A0)&B1&B0;
```

```
assign A_gt_B=A1&(~B1)|A0&(~B1)&(B0)|A1&A0&(~B0);
```


```
assign A_eq_B=(~A1)&(~A0)&(~B1)&(~B0)|(~A1)&A0&  
            (~B1)&B0|A1&A0&&B1&B0|A1&(~A0)&B1&(~B0);
```

```
endmodule
```




counterparts of three common descriptions of comb. logic

 - All three descriptions describe level-sensitive behavior—variables are **updated immediately when an input changes**






Verilog Operators

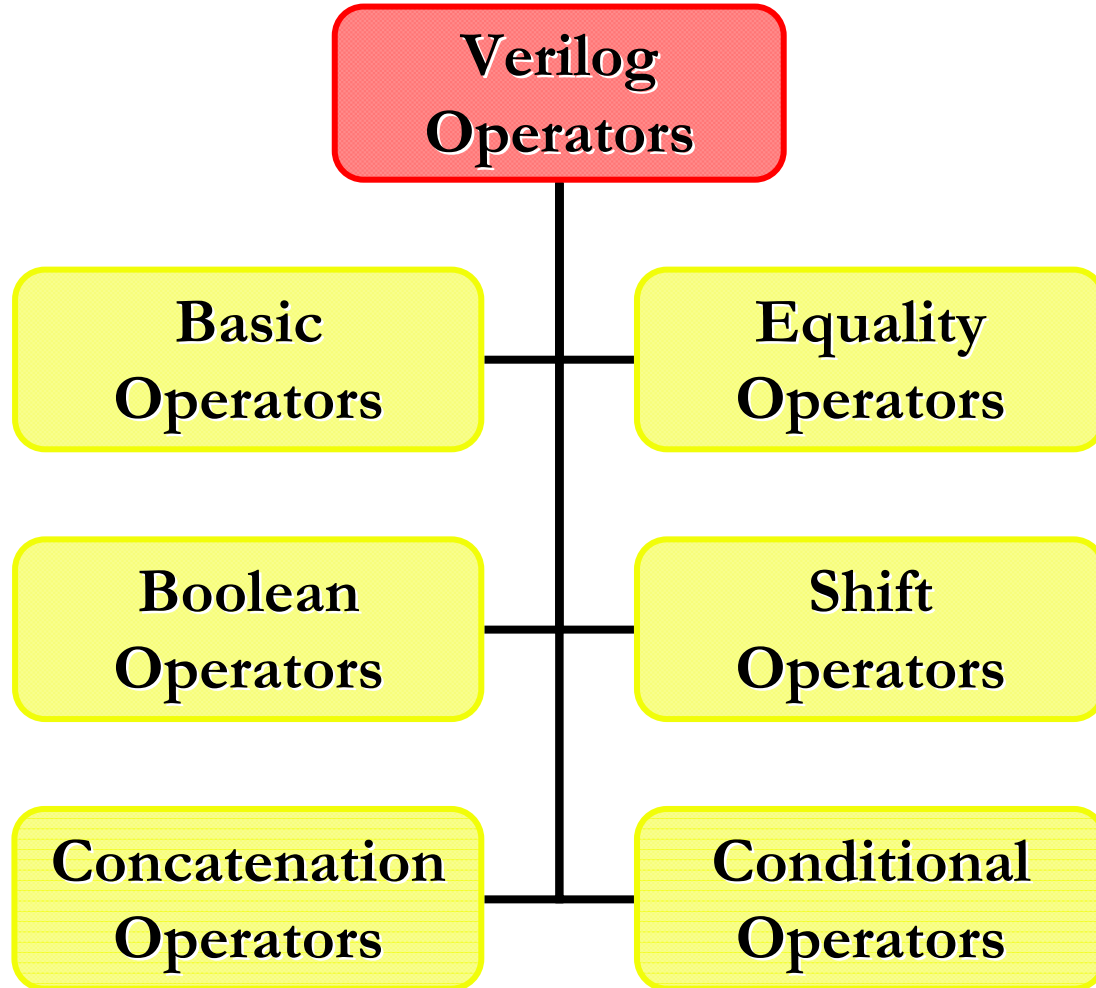



Basic Operators

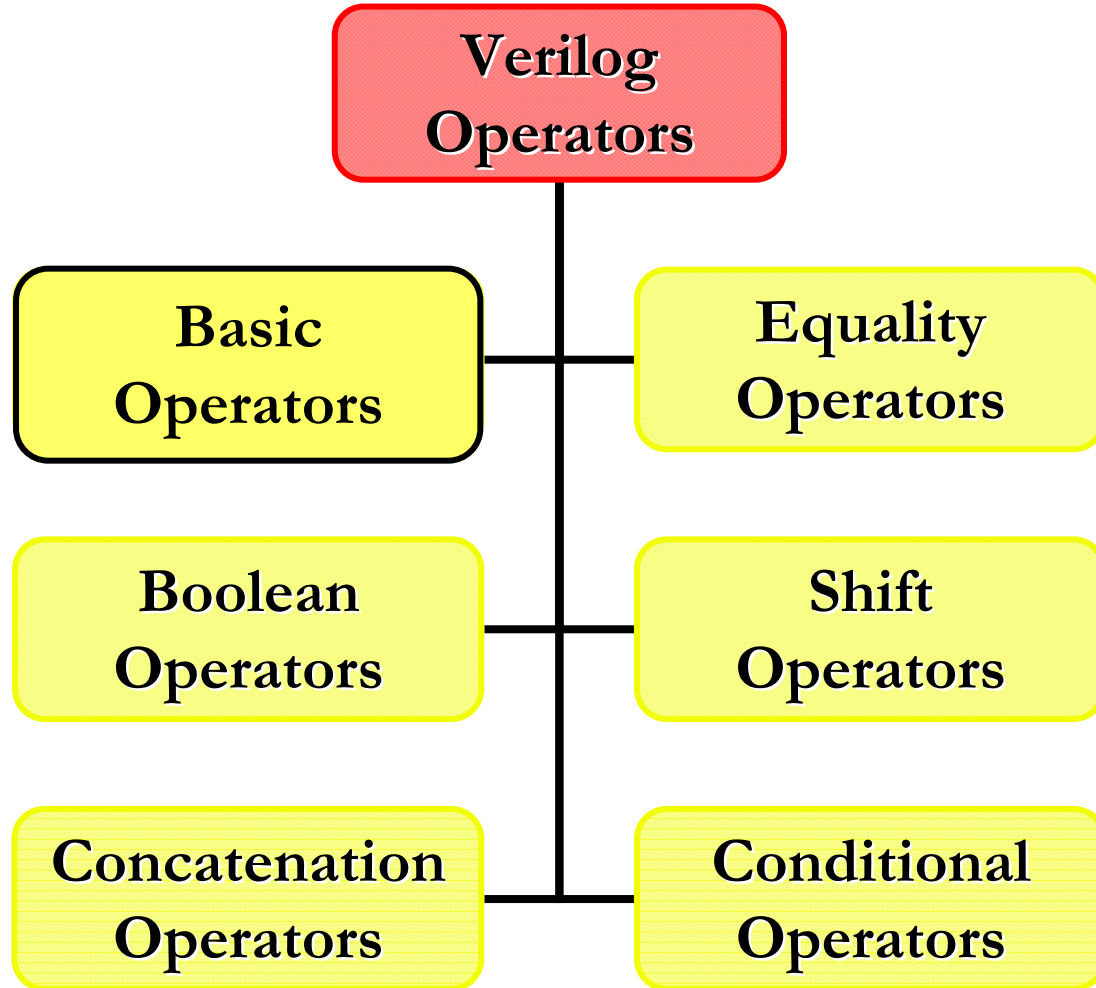



Basic Operators

Basic	OPERATION	DESCRIPTION	RESULT
Arithmetic	+ - * / **	Basic arithmetic	Multi-bit
Relational	> >= < <=	compare	One-bit

- Arithmetic Operations in Verilog take bit, vector, integer and real operands.
- **Basic operators of Verilog are +, -, *, / and **.**
- **An X or a Z value in a bit of either of the operands of a multiplication causes the entire result of the multiply operation to become X.**
- Unary plus (+) and minus (−) are allowed in Verilog. These operators take precedence over other arithmetic operators.
- **If any of the operands of a relational operator contain an X or a Z, then the result becomes X.**




Basic Operators

Example	Results in
$25 * 8'b6$	150
$25 + 8'b7$	32
$25 / 8'b6$	4
$22 \% 7$	1
$8'b10110011 > 8'b0011$	1
$4'b1011 < 10$	0
$4'b1Z10 < 4'b1100$	x
$4'b1x10 < 4'b1100$	x
$4'b1x10 <= 4'b1x10$	x

- Examples of Basic Operations



Equality Operators

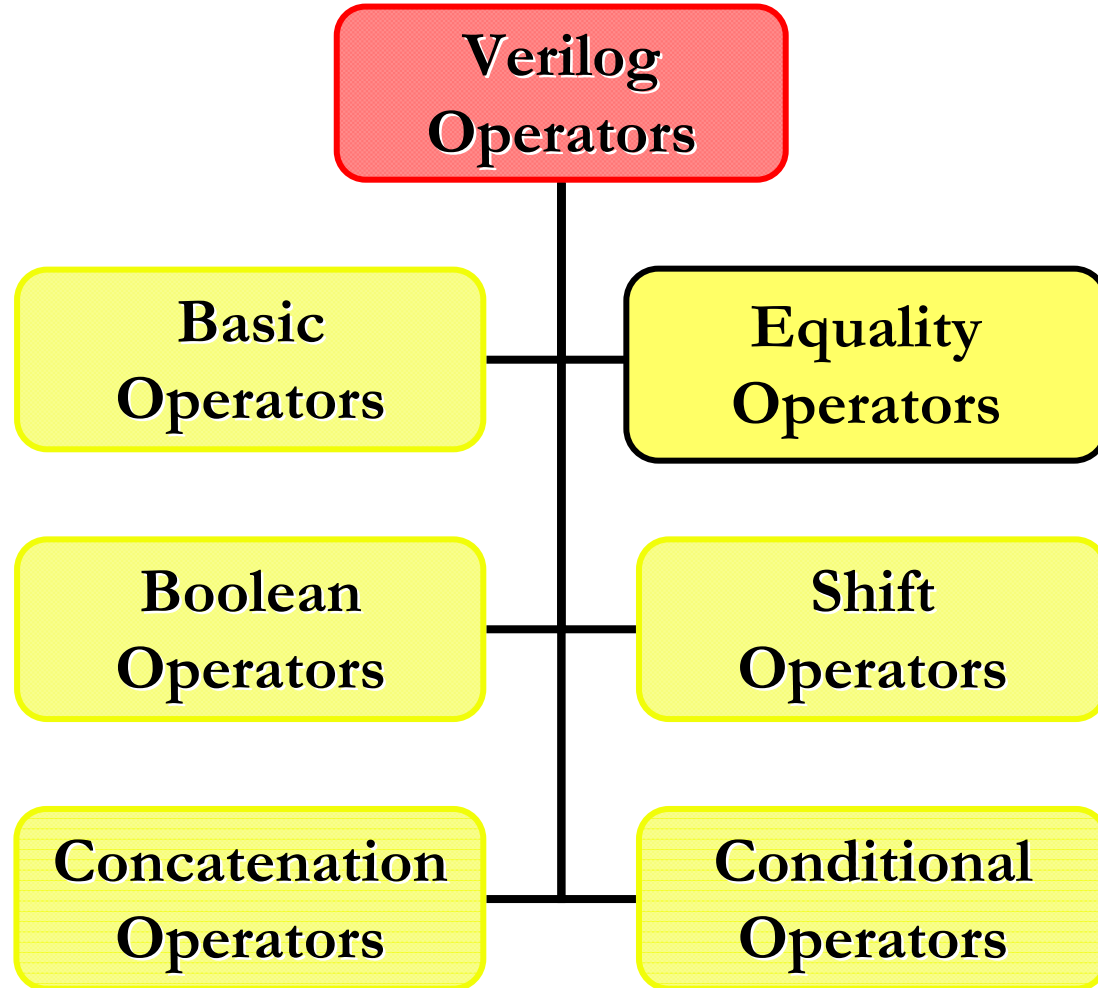



Equality Operators

Equality	OPERATION	DESCRIPTION	RESULT
Logical	== !=	Equality not including Z, X	One-bit
Case	=== !==	Equality including Z, X	One-bit

- Equality operators are categorized into two groups:
- **Logical: Compare their operands for equality (==) or inequality (!=)**
 - Return a one-bit result, 0, 1, or x
 - An X ambiguity arises when an X or a Z occurs in one of the operands.
- **Case: (=== , !==) , Consider X and Z values comparing their operands. The result is always 0 or 1.**




Equality Operators

Example		Results in
8'b10110011	== 8'b10110011	1
8'b1011	== 8'b00001011	1
4'b1100	== 4'b1Z10	0
4'b1100	!= 8'b100X	1
8'b1011	!== 8'b00001011	0
8'b101X	=== 8'b101X	1

- Examples of Equality Operations



Boolean Operators

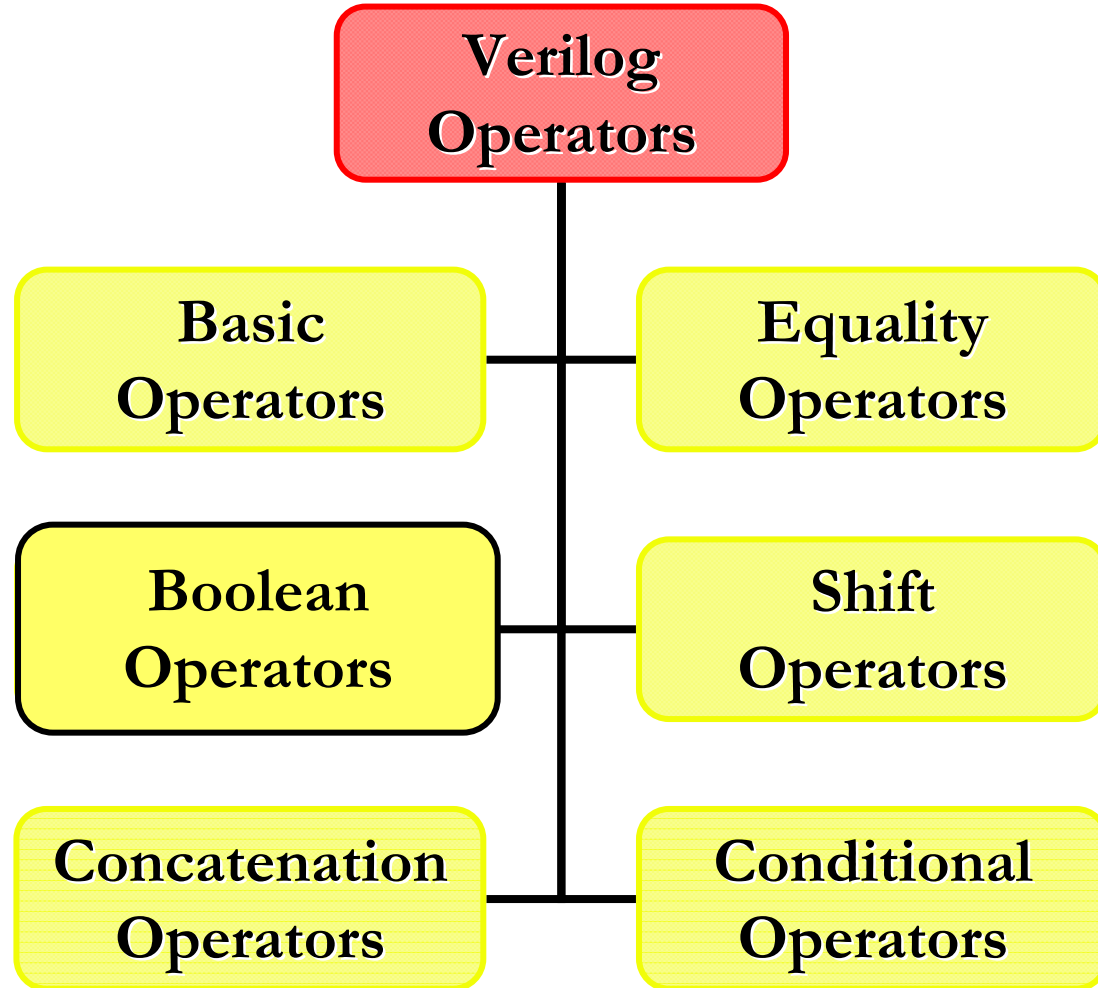



Boolean Operators

Boolean	OPERATION	DESCRIPTION	RESULT
Logical	&& !	Simple logic	One-bit
Bit-wise	~ & ^ ~ ~^	Vector logic operation	One-bit
Reduction	& ~& ~ ^ ^~ ~^	Perform operation on all bits	One-bit

If an X or a Z appears in an operand of a logical operator, an X will result.

The complement operator ~ results in 1 and 0 for 0 and 1 inputs, and X for X and Z inputs.



Boolean Operators

& ^	 ^~	0		1		X		Z	
		0		0		0		0	
0		0	0	0	1	0	x	0	x
		0	1	1	0	x	x	x	x
1		0	1	1	1	x	1	x	1
		1	0	0	1	x	x	x	x
X		0	x	x	1	x	x	x	x
		x	x	x	x	x	x	x	x
Z		0	x	x	1	x	x	x	x
		1	x	x	x	x	x	x	x

- Bit-by-bit Bitwise and Reduction Operators



Boolean Operators


- Complement reduction operations ($\sim\&$, $\sim|$, and \sim^{\wedge}) perform reduction first and then complement the result.

Example	Results in
$8'b01101110 \ \&\& \ 4'b0$	0
$8'b01101110 \ \ 4'b0$	1
$8'b01101110 \ \&\& \ 8'b10010001$	1
$! \ (8'b10010001)$	1
$8'b01101110 \ \& \ 8'bxxzz1100$	$8'b0xx01100$
$8'b01101110 \ \ 8'bxxzz1100$	$8'bx11x1110$
$\sim\& \ (4'b0xz1)$	1
$\sim \ (4'b0xz1)$	0

- Logical, Bit-wise, and Reduction



Shift Operators

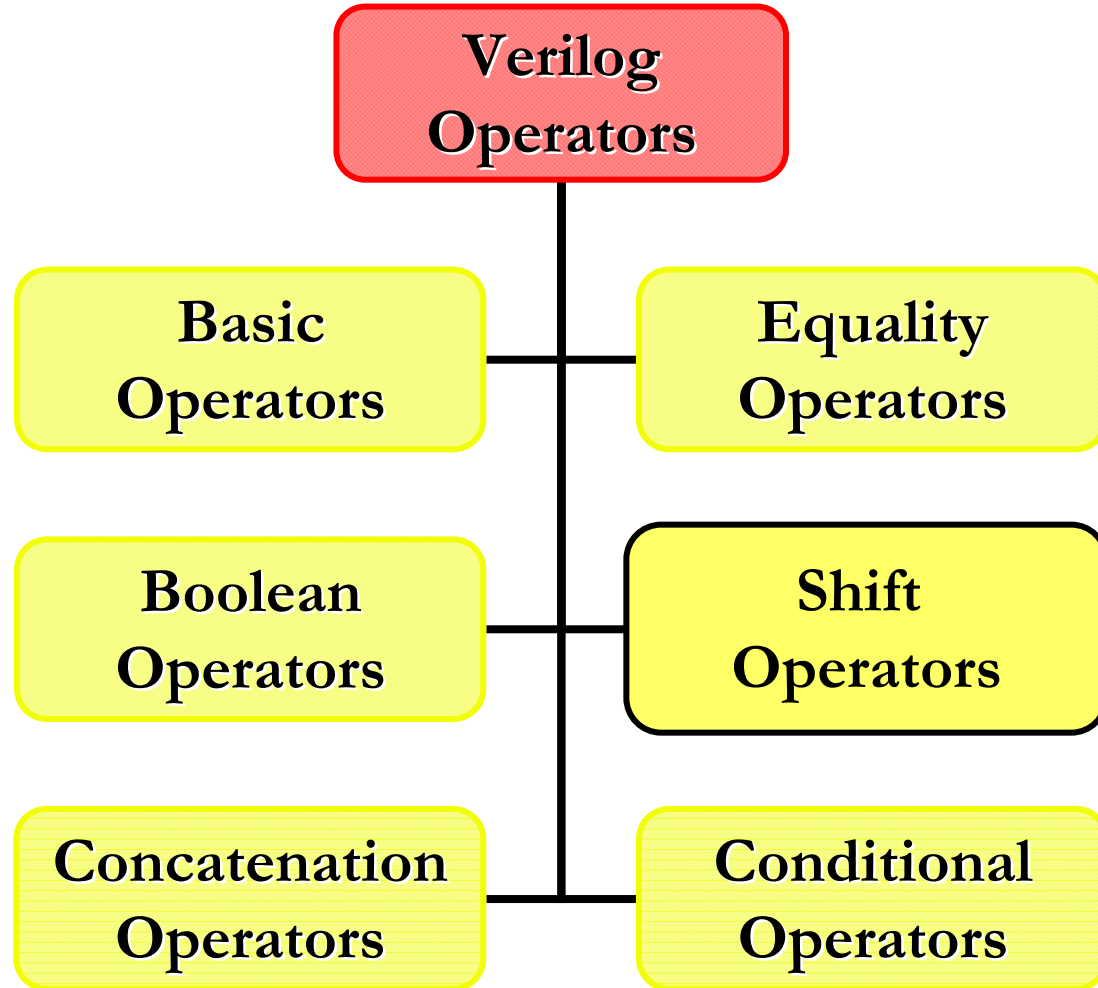



Shift Operators

Shift	OPERATION	DESCRIPTION	RESULT
Logical right	$\gg n$	Zero-fill Shift n places	Multi-bit
Logical left	$\ll n$	Zero-fill Shift n places	Multi-bit
Arithmetic right	$\ggg n$		Multi-bit
Arithmetic left	$\lll n$		Multi-bit

- **Logical shift operators (\gg and \ll for shift right and left) fill the vacated bit positions with zeros.**
- **Fill values for arithmetic shift operators depend on the type of their results being signed or unsigned .**




Shift Operators

Example	Results in
<code>8'b0110_0111 << 3</code>	<code>8'b0011_1000</code>
<code>8'b0110_0111 << 1'bz</code>	<code>8'bxxxx_xxxx</code>
<code>Signed_LHS = 8'b1100_0000>>>2</code>	<code>8'b1111_0000</code>



Concatenation Operators

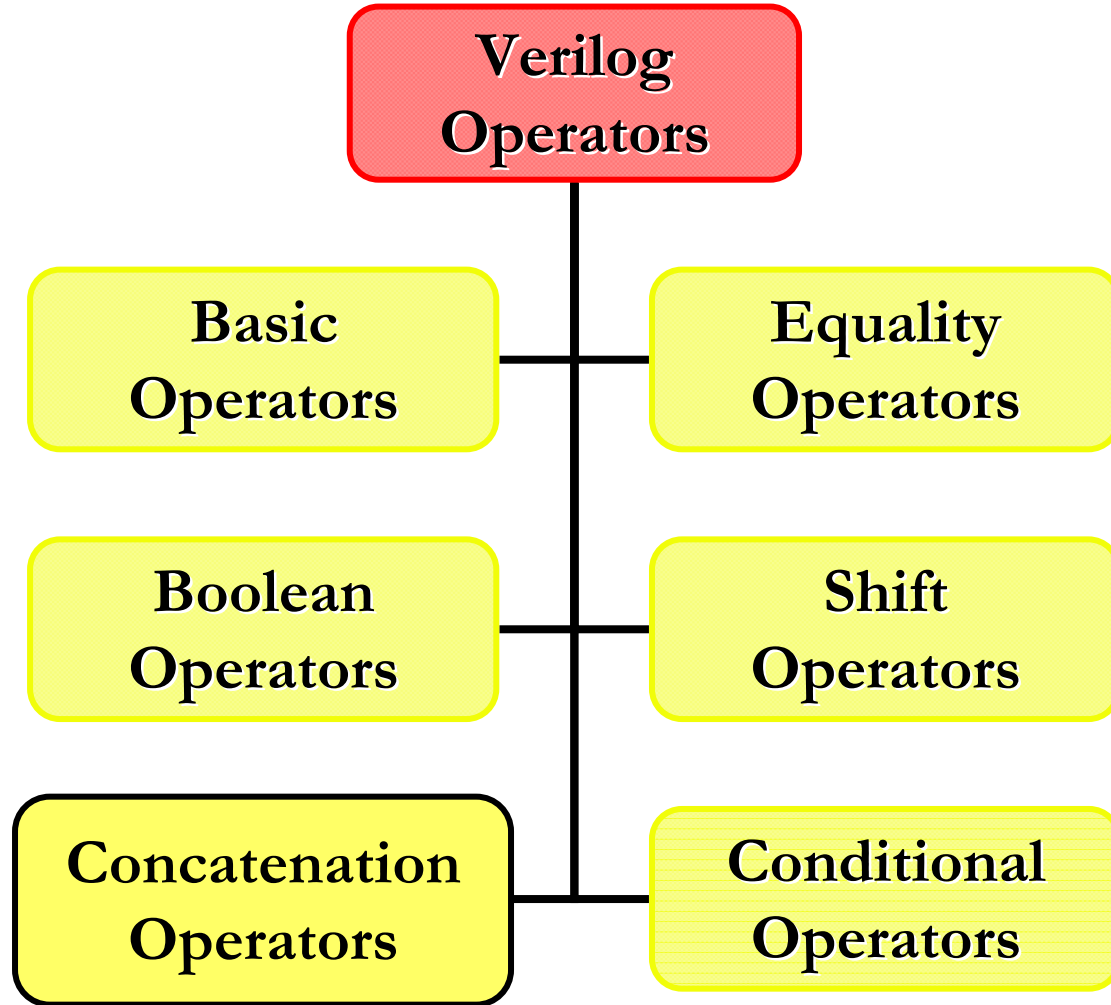



Concatenation Operators

Concat	OPERATION	DESCRIPTION	RESULT
Concatenation	{ }	Join bits	Multi-bit
Replication	{{ }}	Join & replicate	Multi-bit

- The notation used for this operator is a pair of curly brackets **{...}** enclosing all scalars and vectors that are being concatenated.
- If *a* is a 4-bit reg and *aa* is a 6-bit reg, the following assignment places 1101 in *a* and 001001 in *aa*:

$\{a, aa\} = 10'b1101_001001$



Concatenation Operators

- If the `a` and `aa` registers have the values assigned to them above, and `aaa` is a 16-bit reg data type, then the assignment,


$$aaa = \{aa, \{2\{a\}\}, 2'b11\}$$

puts 001001_1101_1101_11 in `aaa`.

- $\{a, 2\{b, c\}, 3\{d\}\}$ is equivalent to:
 $\{a, b, c, b, c, d, d, d\}$
- $\{2'b00, 3\{2'01\}, 2'b11\}$ results in:
10'b0001010111



Conditional Operators

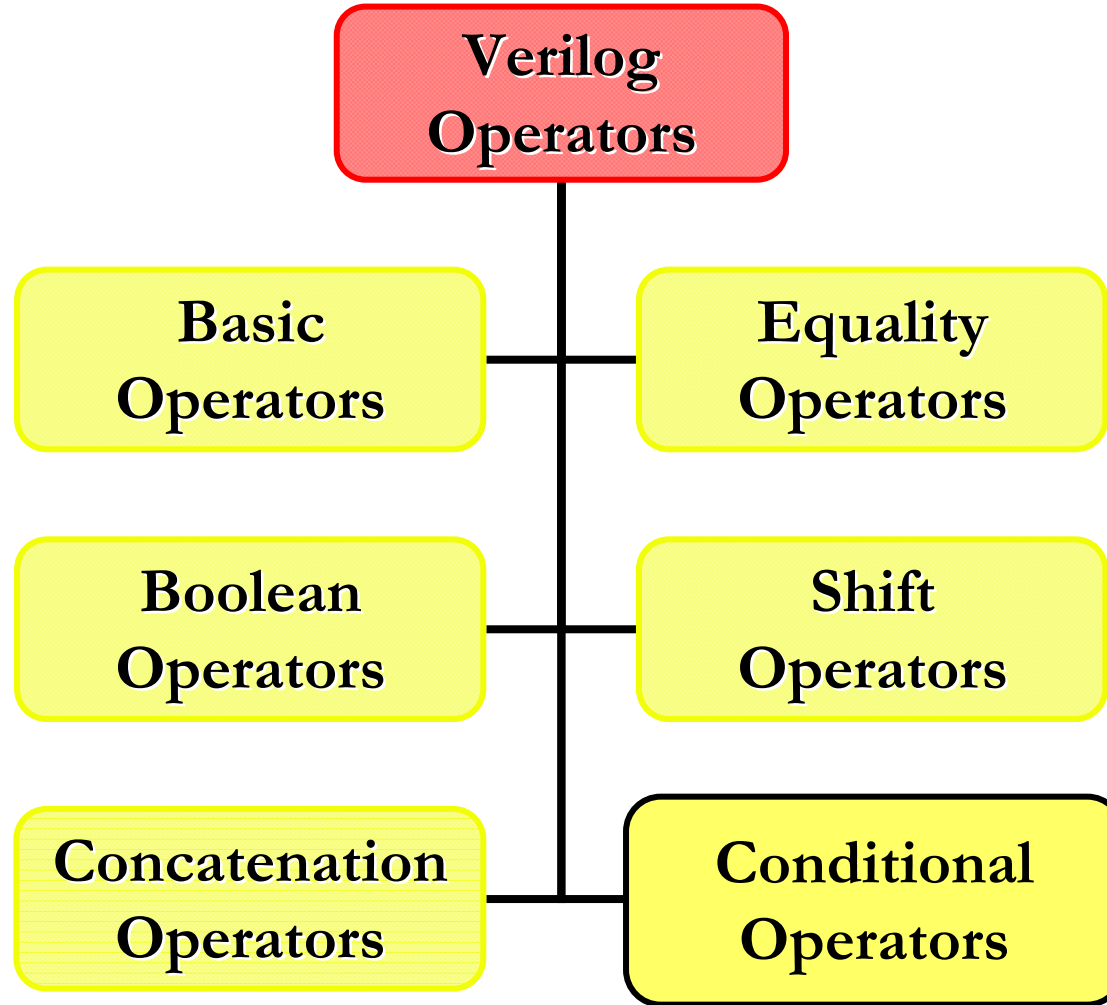



Conditional Operators

- **expression1 ? expression2 : expression3**



...

assign a = (b == c)? 1 : 0;

...

If *expression1* is true, then *expression2* is selected as the result of the operation; otherwise *expression3* is selected.

- If *expression1* is X or Z, both expressions 2 and 3 will be evaluated, and the result becomes the bit-by-bit combination of these two expressions.



Conditional Operators

Example	Results in
1 ? 4'b1100 : 4'b zx0	4'b1100
0 ? 4'b1100 : 4'b1zx0	4'b1zx0
x ? 4'b1100 : 4'b1zx0	4'b1xx0

- Conditional Operators




Precedence of Operators

	Highest
+ - ! ~	
* *	
* / %	
+ -	
<< >> <<< >>>	
< <= > >=	
== != === !==	
& ~ &	
^ ^~ ~^	
~	
& &	
? :	
	Lowest

- Operator Precedence



Precedence of Operators

 

- Precedence Examples



5.5 Latches and Level Sensitive circuits in Verilog

- A set of continuous-assignment statements has **implicit feedback** if a variable in one of the RHS expressions is also the target of an assignment
- Synthesis tool **do not accommodate** this form of feedback
- They support the feedback that is implied by a continuous assignment in which the RHS uses a conditional operator




Example 5.7

A Transparent Latch

```
module Latch_CA (q_out, data_in, enable);  
    output      q_out;  
    input       data_in, enable;  
    assign      q_out=enable? data_in : q_out;  
endmodule
```



The waveforms produced by simulation of Latch_CA

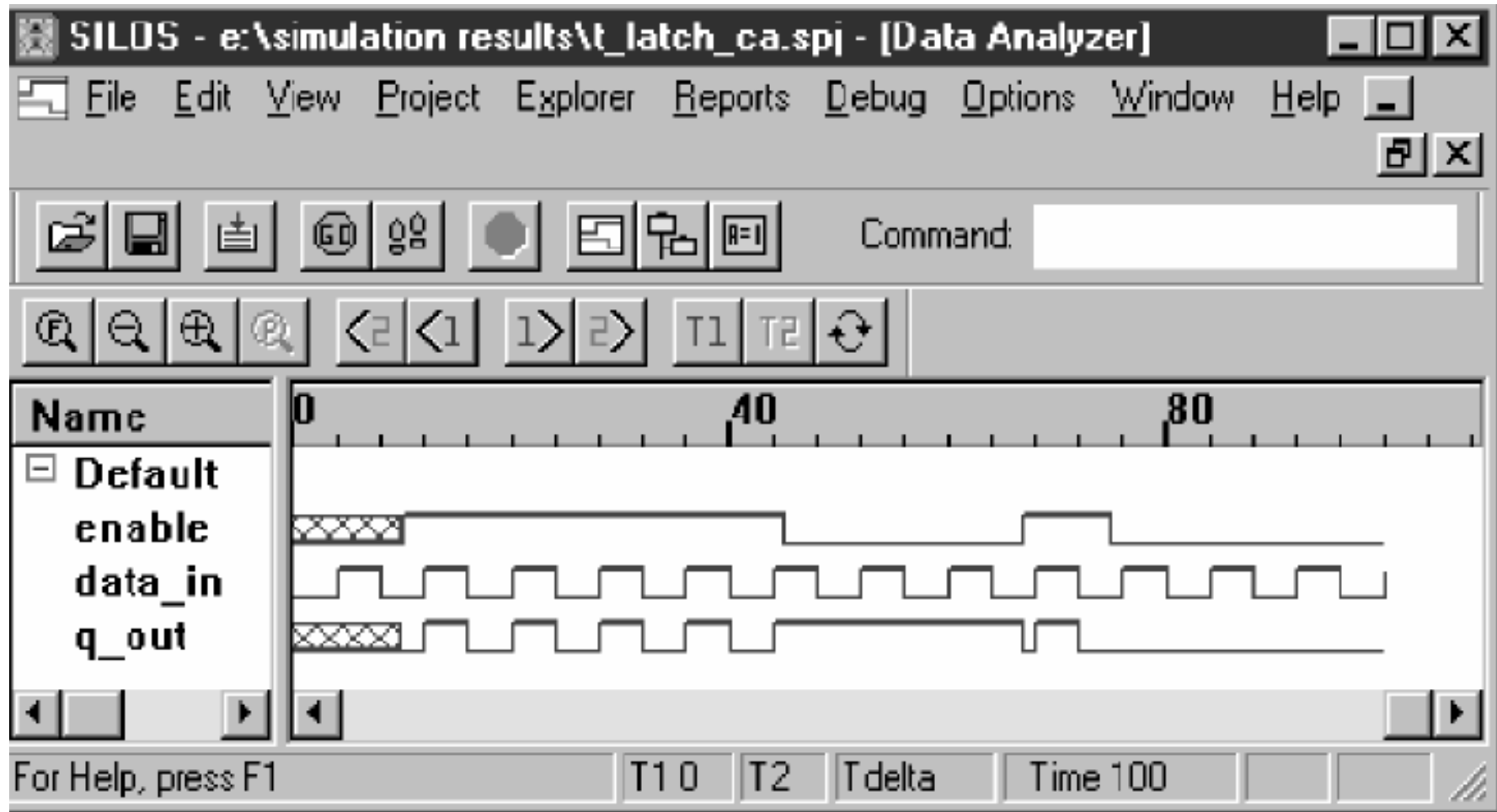




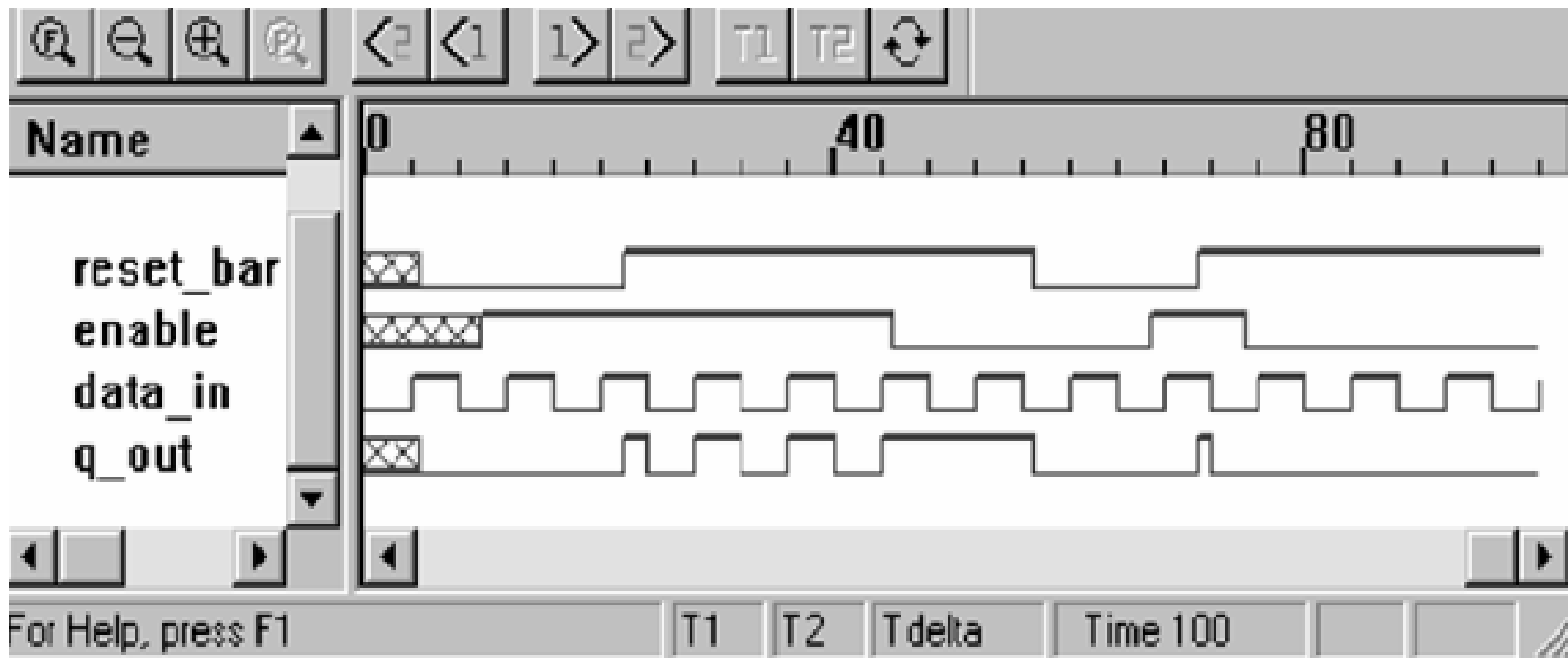Example 5.8 a latch with a nested conditional operator

```
module Latch_Rbar_CA (q_out, data_in, enable, reset);  
  output    q_out;  
  input      data_in, enable, reset;  
  assign    q_out= !reset ? 0 : enable ? Data_in : q_out;  
endmodule
```



The simulation of the latch model Latch_Rbar_CA





Use Continuous assignments

- Convenient for modeling small Boolean expressions, three-state behavior, and transparent latches
- Easy to make mistake when design large Boolean equation models
- Boolean expressions might obscure the functionality of the design



5.6 Cyclic Behavioral Models of Flip-Flops and Latches

- Many digital systems are triggered by a clock
- Verilog uses a cyclic behavior to model edge-sensitive functionality
- **Cyclic behaviors execute procedural statements** to generate the values of variables
- Cyclic behaviors are used to model both level-sensitive and edge-sensitive behavior



Example 5.9

```
module df_behav (q, q_bar, data, set, reset, clk);  
  input      data, set, clk, reset;  
  output     q, q_out;  
  reg        q;  
  assign q_bar=~q;  
  always@ (posedge clk) // flip-flop with synchronous set/reset  
  begin  
    if (reset==0) q<=0;  
    else if (set==0) q<=1;  
    else q<=data;  
  end  
endmodule
```




Clocked Process

- **Clocked Process**

- Sensitive to **a clock** or/and **control signals**

- **Example**


always @(posedge clk or negedge clr)

 

*sensitivity list does not include the **d** input,
only the clock or/and control signals*



Procedural Assignments

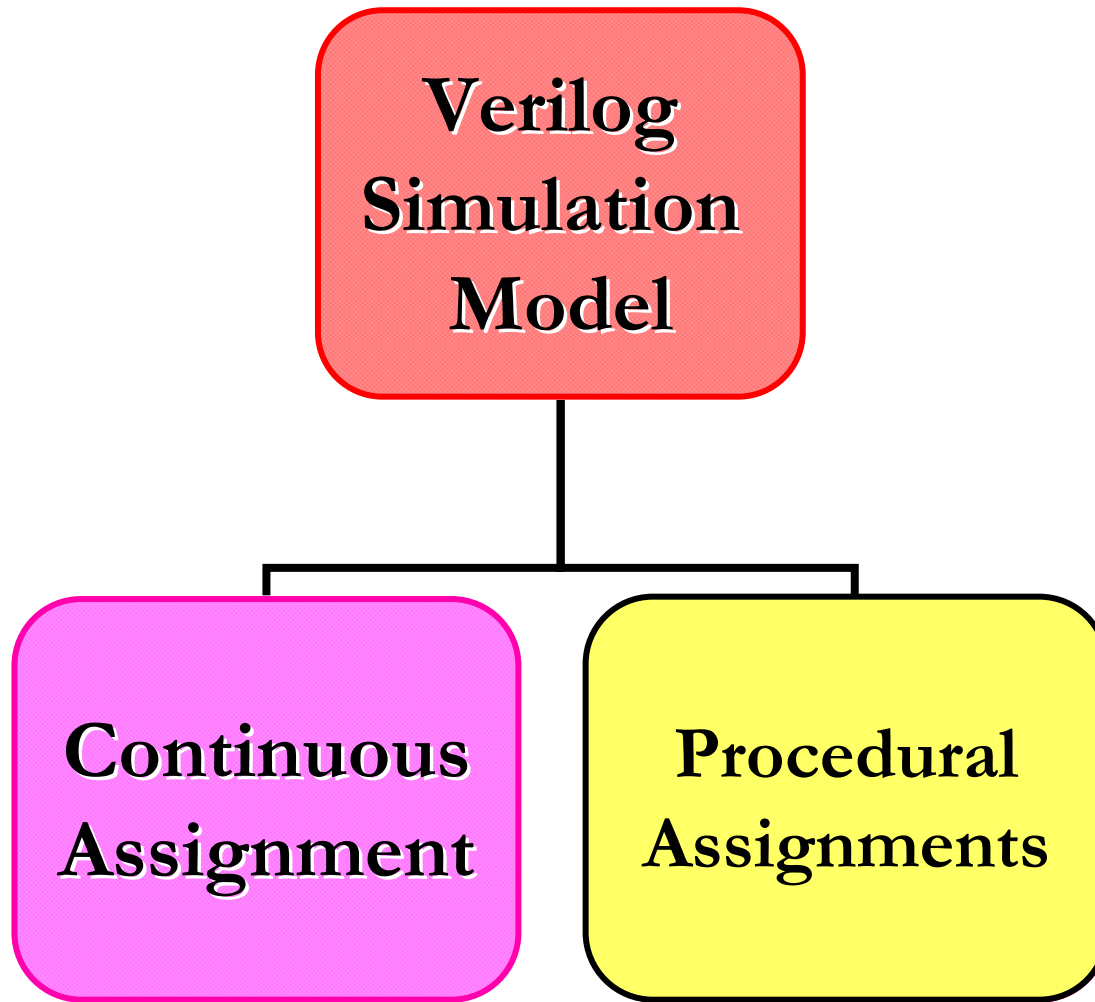



Procedural Assignments

- Procedural assignments in Verilog take place in the **initial** and **always** procedural constructs, which are regarded as procedural bodies.



Initial and Always Blocks

- Basic components for behavioral modeling

initial

begin

... imperative statements ...

end

Runs when simulation starts

Terminates when control reaches the end

Good for providing stimulus

always

begin

... imperative statements ...

end

Runs when simulation starts

Restarts when control reaches the end

Good for modeling/specifying hardware



Procedural Flow Control

- **Statements in a procedural body are executed when program flow reaches them.**
- **Flow control statements are classified as delay control and event control.**
- **An event or delay control statement in a procedural body causes program flow to be put on hold temporarily.**



Procedural Flow Control

<pre>always ▪ ▪ ▪ @ (reset) ▪ ▪ ▪ end</pre>	<pre>always ▪ ▪ ▪ @ (posedge CLK) ▪ ▪ ▪ end</pre>	<pre>always ▪ ▪ ▪ #10 ▪ ▪ ▪ end</pre>
---	---	---------------------------------------

- Procedural Flow Control



Timing Control

- **DelayControl**
- **EventControl**
- **WaitControl**
- **Example**
 - #10
 - #(Period/2)
 - #(1.2:3.5:7.1)
 - @Trigger
 - @(a or b or c)
 - @(posedge clock or negedge reset)
 - wait (!Reset)



Wait : Timing Control

■ Wait — waits for a level on a line

- How is this different from an “@” ?

■ Semantics

- wait (expression) statement;
 - e.g. wait (a == 35) q = q + 4;
- if the expression is FALSE, the process is stopped
 - when a becomes 35, it resumes with q = q + 4
- if the expression is TRUE, the process is not stopped
 - it continues executing

■ Partial comparison to @ and

- @ and # always “block” the process from continuing
- wait blocks only if the condition is FALSE|



Operator: @

- **@ denotes event control:**
meaning that the procedural statements that follow the event-control expression do not execute **until an activating event occurs**
- **When such an event occurs, the statements execute in sequence, top to bottom**
- When the last statement completes execution, the computational activity **returns to the location of the keyword *always***, then the cycle repeats



Initial and Always

- Run until they encounter a delay

initial

begin

```
#10 a = 1; b = 0;
```

```
#10 a = 0; b = 1;
```

end

- Wait for an event

always @(posedge clk) q = d;

always

```
begin wait(i); a = 0; wait(~i); a = 1; end
```




5.7 Cyclic Behavior and Edge Detection

- **delay control(# operator)**
- **event-control (@ operator)**
- **rising edge(*posedge*)**
- **falling edge(*negedge*)**
- A simulator monitors the variables in an event-control expression
- When the expression changes value, the associated procedural statements execute if the enabling change took place



 Example 5.10

```
module asynch_df_behav(q, q_bar, data, set, clk, reset);  
  input    data, set, reset, clk;  
  output   q, q_bar;  
  reg      q;  
  assign   q_bar=~q;  
  always @ (negedge set or negedge reset or posedge clk)  
  begin  
    if (reset==0) q<=0;  
    else if (set==0) q<=1;  
    else q<=data; // synchronized activity  
  end  
endmodule
```





Note

- Verilog language allows a mixture of level-sensitive and edge-qualified variables in an event-control expression
- Synthesis tools do not support such models of behavior
- That description must be entirely edge-sensitive or entirely level-sensitive



Example 5.11

```
module tr_latch (q_out, enable, data);  
    output q_out;  
    input  enable, data;  
    reg q_out;  
    always @ (enable or data)  
        begin  
            if (enable) q_out=data;  
        end  
endmodule
```




5.8 A Comparison of styles for Behavioral Modeling

- Modeling styles based on :
 - 1. Continuous-assignment models
 - 2. Dataflow/RTL models
 - 3. Algorithm-based models



5.8.1 Continuous-Assignment Models

- Continuous assignments
- **Execute concurrently**
 - with each other assignments
 - with gate-level primitives ,and
 - with all of the behaviors in a description



```
compare_2_CA1(A_lt_B,A_gt_B,A_eq_B,A1
               ,A0,B1,B0);
```

endmodule

75



Example 5.13

2-bit comparator

module

 compare_2_CA2(A_lt_B,A_gt_B,A_eq_B,A,B);

input [1:0] A,B;

output A_lt_B, A_gt_B, A_eq_B;

assign A_lt_B=(A<B);

assign A_gt_B=(A>B);

assign A_eq_B=(A==B);


endmodule



 Example 5.14

A 32-bit comparator

```
module compare_32_CA (A_lt_B,A_gt_B,A_eq_B,A,B);  
  parameter          word_size=32;  
  input [wordsize-1:0]  A,B;  
  output               A_lt_B, A_gt_B, A_eq_B;  
  assign               A_lt_B=(A<B);  //note:list of multiple  
                                   // assignment  
  assign               A_gt_B=(A>B);  
  assign               A_eq_B=(A==B);  
endmodule
```





5.8.2

Dataflow/RTL Models

- Describe **concurrent operations on signals**
- Usually **in a synchronous machine**
- Where computations are initiated at the active edges of a clock ,and are completed in time to be stored in a register at the next active edge



Dataflow : Key Points

- Dataflow modeling enables **the designer to focus on where the state is in the design and how the data flows between these state elements** without becoming bogged down in gate-level details
- – Continuous assignments are used to connect combinational logic to nets and ports
- – A wide variety of operators are available
- But: Arithmetic: **- * / % ****
- Avoid these operators since they usually synthesize poorly



Example 5.15

2-bit comparator of RTL model

module

```
compare_2_RTL(A_lt_B,A_gt_B,A_eq_B,A1,A0,B1,B0);
```

```
input      A1,A0,B1,B0;
```

```
output     A_lt_B, A_gt_B, A_eq_B;
```

```
reg        A_lt_B, A_gt_B, A_eq_B;
```

```
always@ (A0 or A1 or B0 or B1) begin
```

```
    A_lt_B=({A1,A0}<{B1,B0});
```

```
    A_gt_B=({A1,A0}>{B1,B0});
```

```
    A_eq_B=({A1,A0}=={B1,B0});
```

```
end
```

```
endmodule
```

the **order** of three procedural assignments which the assignments are listed **does not affect the outcome.** 80



Example 5.16

a 4-bit serial shift register

```
module shiftreg_PA(E ,A, B, C, D, clk, rst);  
  output A;  
  input E;  
  input clk,rst;  
  reg A,B,C,D;  
  always@ (posedge clk or posedge rst) begin  
    if (rst) begin A=0;B=0;C=0;D=0; end  
    else begin  
      A=B;  
      B=C;  
      C=D;  
      D=E;  
    end  
  end  
endmodule
```


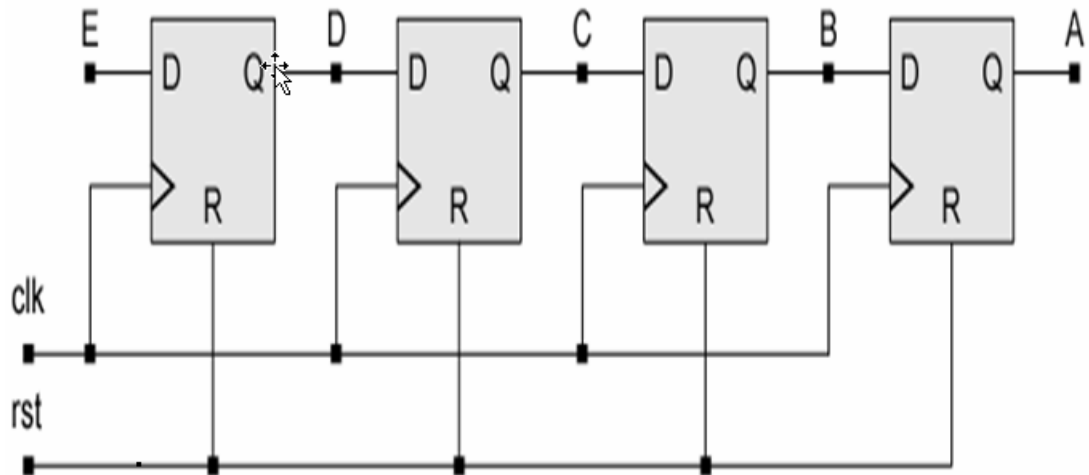


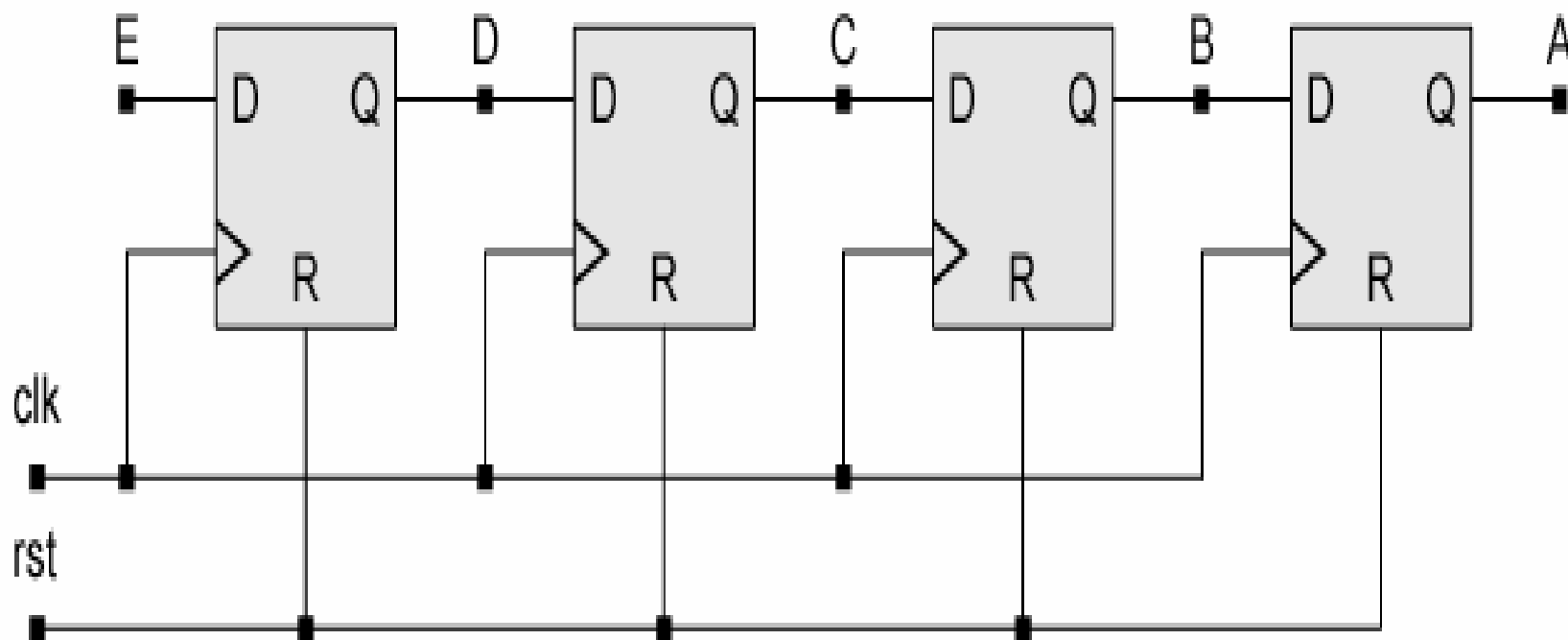

Fig 5-7


The shift register by a synchronous cyclic behavior with a list of procedural assignments





When the order of the procedural assignments in the model is reversed
 
```
module shiftreg_PA_rev(A,E ,clk, rst);  
  output A;  
  input E;  
  input clk,rst;  
  reg A,B,C,D;  
  always@ (posedge clk or posedge rst) begin  
    if (rst) begin A=0;B=0;C=0;D=0; end  
    else begin  
      D=E;  
      C=D;  
      B=C;  
      A=B;  
    end  
  end  
endmodule
```





Two types of Procedural Assignments


- Blocking Assignment (=) : **executed in the order** they are specified in a sequential block
- Nonblocking Assignment (<=) : allow scheduling of assignments without blocking execution of the statements that follow in a sequential block
 - Recommended: **Use Nonblocking assignments for clocked processes when writing synthesizable code.**



Blocking vs. Nonblocking Assignments


Blocking (=)
 
```
initial
begin
    #5    a = b;
    #10   c = d;
end
```



Nonblocking (<=)
 
```
initial
begin
    #5    a <= b;
    #10   c <= d;
end
```







Blocking vs. Nonblocking Assignments

Blocking (=)

```
always @(posedge clk)
begin
    a = in;
    b = a;
    out = b;
end
```



Synthesized Result:

  

Nonblocking (<=)

```
always @ (posedge clk)
begin
    a <= in;
    b <= a;
    out <= b;
end
```

Synthesized Result:

  



Non-blocking Can Behave Oddly

- A sequence of non-blocking assignments don't communicate

a = 1;

b = a;

c = b;

a <= 1;

b <= a;

c <= b;

Blocking assignment:

a = b = c = 1

Non-blocking assignment:

a = 1

b = old value of a

c = old value of b



Non-blocking Looks Like Latches


- RHS of blocking taken from wires
- RHS of non-blocking taken from latches

`a = 1;`

“

`b = a;`

`c = b;`

 


”

`a <= 1;`

`b <= a;`

`c <= b;`

 




Blocking & Non-blocking Assignments


Bad: Circuit from blocking assignment.
 
```
always @(posedge clk)
begin
    b=a;
    a=b;
end
```



Good: Circuit from nonblocking assignment.
 
```
always @(posedge clk)
begin
    b<=a;
    a<=b;
end
```





Ex. A Flawed Shift Register

- This doesn't work as you'd expect:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 = d1;
```

```
always @(posedge clk) d3 = d2;
```

```
always @(posedge clk) d4 = d3;
```

- These run in some order, but you don't know which



Non-blocking Assignments

- This version does work:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 <= d1;
```

```
always @(posedge clk) d3 <= d2;
```

```
always @(posedge clk) d4 <= d3;
```

Non-blocking rule:

RHS evaluated when
assignment runs

LHS updated only after
all events for the current
instant have run



Example 5.17 4-bit serial shift register

```
module shiftreg_nb(A,E ,clk, rst);  
  output A;  
  input E;  
  input clk,rst;  
  reg A,B,C,D;  
  always@ (posedge clk or posedge rst) begin  
    if (rst) begin A=0;B=0;C=0;D=0; end  
    else begin  
      D<=E;          // D<=E;  
      C<=D;          // C<=D;  
      B<=C;          // B<=C;  
      A<=B;          // A<=B;  
    end  
  end  
endmodule
```



Strongly Recommended

- When modeling logic that includes edge-driven register transfers
- **The edge-sensitive operations be described by non-blocking assignments**
- **The combinational logic be described with blocked assignments**
- This practice will **prevent race conditions** between combinational logic and register operations



5.8.3 Algorithm-Based Models

- Algorithm prescribes a sequence of procedural assignments within a cyclic behavior
- The algorithm described by the model **does not have explicit binding to hardware**, and it **does not have an implied architecture of registers, datapaths, and computational resources**.
- **Not all algorithms can be implemented in hardware**
- This descriptive style is abstract, and eliminates the need for an a priori architecture
- Description can be **readable and understandable**




Example 5.18

a 2-bit comparator

```
module compare_2_algo(A_lt_B,A_gt_B,A_eq_B,A,B);  
  input [1:0]    A,B;  
  output        A_lt_B, A_gt_B, A_eq_B;  
  reg           A_lt_B, A_gt_B, A_eq_B;  
  always@ (A or B)    //Level-sensitive behavior  
  begin  
    A_lt_B=0;          // prevent the synthesis of unwanted latches  
    A_gt_B=0;  
    A_eq_B=0;  
    if (A==B)    A_eq_B=1;    // Note: parentheses are required  
    else if (A>B)A_gt_B=1;  
    else A_lt_B=1;  
  end  
endmodule
```



 Synthesis result :the gate-level schematic obtained by synthesizing compare_2_algo





5.8.4 Port Names: A Matter of style

- **Signals ,modules, functions and tasks** should be given names that describe their use the encapsulated functionality
- **The ports will be ordered in the following sequence:**
- (datapath bidirectional signals,
bidirectional control signals,
datapath outputs, control outputs,
datapath inputs, control inputs,
synchronizing signals)



Ports

- **Port List:**

- A listing of the port names
- Example: `module mult_acc (out, ina, inb, clk, clr);`

- **Port Types:**

- `input` --> input port
- `output` --> output port
- `inout` --> bidirectional port

- **Port Declarations:**

- `<port_type> <port_name>;`
- Example:
`input [7:0] ina, inb;`
`input clk, clr;`
`output [15:0] out;`



5.8.5 Simulation with Behavioral Models

- An event at the input of a primitive **causes the simulator to schedule an updating event for its output**
- An event in the RHS expression of a continuous-assignment statement causes the scheduling of an event for the assignment's target variable
- Cyclic behaviors can suspend themselves
prevent endless execution or multiple behaviors at the same time




Procedural Control

- The associated statements execute sequentially, in the same time step, **until the simulator encounters either**
 - (1) a delay control operator (#)
 - (2) an event control operator (@)
 - (3) a wait construct
 - (4) the last statement of the behavior



5.9 Behavioral Models of Multiplexers, Encoders, and Decoders

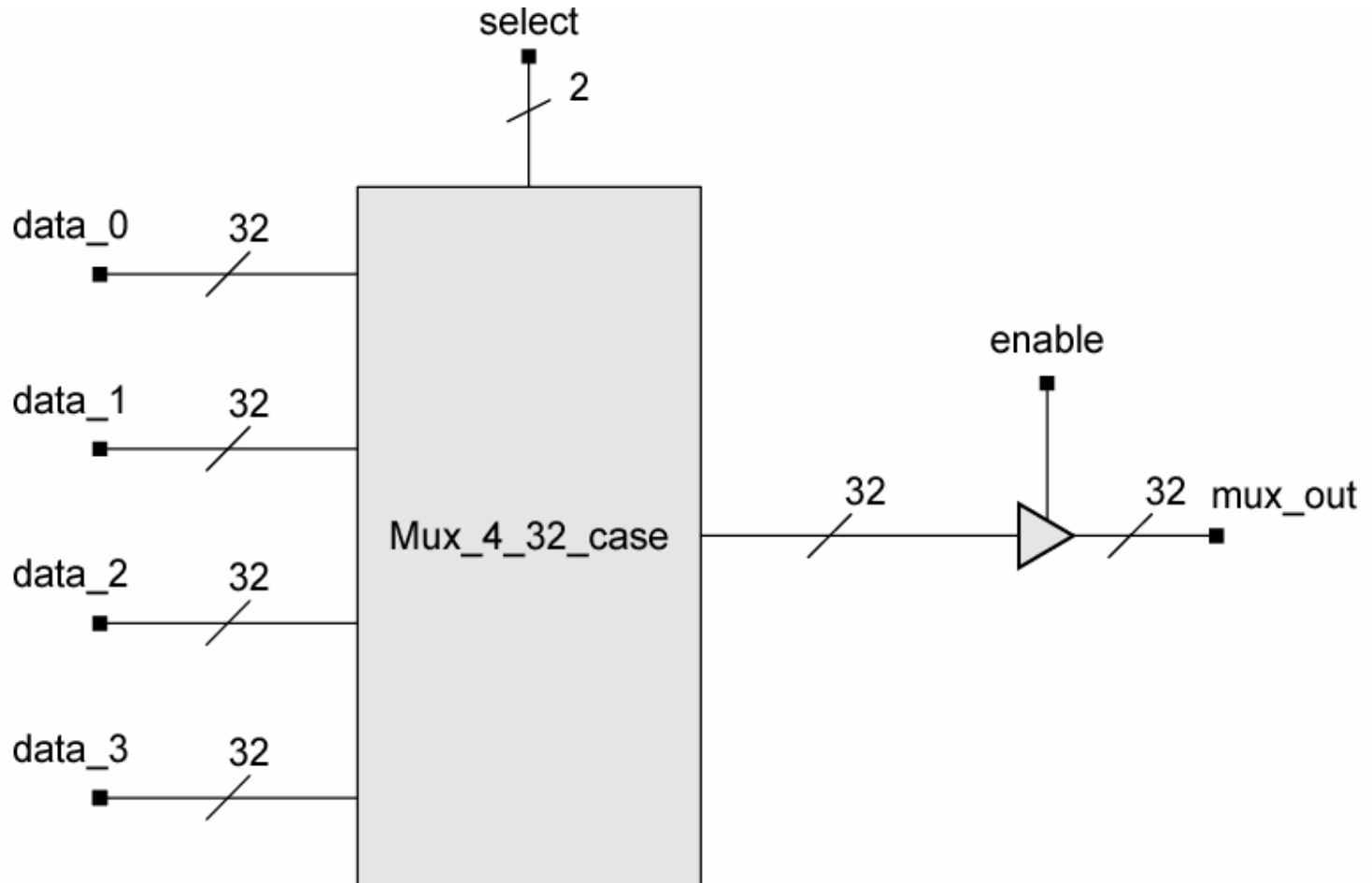



Ex 5.19: a 4-channel,32-bit multiplexer

```
module Mux_4_32_case
    (mux_out,data_3,data_2,data_1,data_0,select,enable);
    output [31:0] mux_out;
    input  [31:0] data_3,data_2,data_1,data_0;
    input  [1:0]  select;
    input          enable;
    reg    [31:0] mux_int;

    assign mux_out=enable ? Mux_int : 32'bz;
    always @ (data_3 or data_2 or data_1 or data_0 or select)
        case (select)
            0:          mux_int=data_0;
            1:          mux_int=data_1;
            2:          mux_int=data_2;
            3:          mux_int=data_3;
            default: mux_int=32'bx; // may execute in simulation
        endcase
    endmodule
```



case statement

- Similar to its counterpart in other languages (eg., the switch statement in C)
- Searches from top to bottom to find a match
- The case statement executes the first match found
- And does not consider any remaining possibilities




Case Statement

■ Format:

```
case (expression)
  <condition1> :
    sequence of statement(s)
  <condition2> :
    sequence of statement(s)
    .
    .
  default :
    sequence of statement(s)
endcase
```

■ Example:
 
```
always @(sel or a or b or c or d)
begin
  case (sel)
    2'b00 :
      q = a;
    2'b01 :
      q = b;
    2'b10 :
      q = c;
    default :
      q = d;
  endcase
end
```





Efficient Case Statement

```
reg [4:0] state;
parameter  s0 = 5'b00000,      s1 = 5'b10001,
            s2 = 5'b10010,      s3 = 5'b10100,
            s4 = 5'b11000;
always @ (posedge clk or negedge reset) begin
    if (reset == 0) state = s0;
    else
        case (state)
            s0:    if (in == 1) state = s1;
                   else state = s0;
            s1:    state = s2;
            s2:    state = s3;
            s3:    state = s4;
            s4:    if (in == 1) state = s1;
                   else state = s0;
            default: state = s0;
        endcase
end
```

- Logic Elements: 10
- All cases covered
- Wherever mutual exclusivity exists, a **case** structure *usually* synthesizes most efficiently
- A **case** structure where **all cases are covered will typically synthesize most efficiently**



Two Other Forms of Case Statements

- **casez**

- Treats all 'z' values in the case conditions as don't cares, instead of logic values
- All 'z' values can also be represented by '?'

- **casex**

- Treats all 'x' and 'z' values in the case conditions as don't cares, instead of logic values

```
casez (encoder)
    4'b1??? : high_lvl = 3;
    4'b01?? : high_lvl = 2;
    4'b001? : high_lvl = 1;
    4'b0001 : high_lvl = 0;
    default : high_lvl = 0;
endcase
```

- if **encoder** = 4'b1zzz, then **high_lvl** = 3

```
casex (encoder)
    4'b1xxx : high_lvl = 3;
    4'b01xx : high_lvl = 2;
    4'b001x : high_lvl = 1;
    4'b0001 : high_lvl = 0;
    default : high_lvl = 0;
endcase
```

- if **encoder** = 4'b1xzx, then **high_lvl** = 3



Example 5.20 use nested conditional statements (if) to model a multiplexer

```
module Mux_4_32_if
  (mux_out,data_3,data_2,data_1,data_0,select,enable);
  output [31:0]    mux_out;
  input  [31:0]    data_3,data_2,data_1,data_0;
  input  [1:0]     select;
  input  enable;
  reg    [31:0]    mux_int;
assign mux_out=enable ? Mux_int : 32'bz;
always @ (data_3 or data_2 or data_1 or data_0 or select)
  if (select==0)  mux_int=data_0; else
    if (select==1) mux_int=data_1; else
      if (select==2) mux_int=data_2; else
        if (select==3) mux_int=data_3; else
          mux_int=32'bx;
endmodule
```




If-Else Statements

Format:

```
if (<condition1>)
    sequence of statement(s)
else
    if (<condition2>)
        sequence of statement(s)
        ▪
        ▪
    else
        sequence of statement(s)
```

Example:

```
always @(sela or selb or a or b or c)
begin
    if (sela)
        q = a;
    else
        if (selb)
            q = b;
        else
            q = c;
end
```

 



Ex 5.21 use ? : operator to model a multiplexer

```
module Mux_4_32_CA
(mux_out,data_3,data_2,data_1,data_0,select,enable);
    output [31:0]    mux_out;
    input  [31:0]    data_3,data_2,data_1,data_0;
    input  [1:0]     select;
    input            enable;
    reg    [31:0]    mux_int;
    assign mux_out=enable ? Mux_int : 32'bz;
    assign mux_int=(select==0) ? data_0 :
                    (select==1) ? data_1 :
                    (select==2) ? data_2 :
                    (select==3) ? data_3 :32'bz;
endmodule
```



Ex 5.22 an 8:3 encoder

```
module encoder (Code, Data);  
    output      [2:0] Code;  
    input       [7:0] Data;  
    reg [2:0] Code;  
    always @ (Data)  
    begin  
        if (Data==8'b00000001) Code=0; else  
        if (Data==8'b00000010) Code=1; else  
        if (Data==8'b00000100) Code=2; else  
        if (Data==8'b00001000) Code=3; else  
        if (Data==8'b00010000) Code=4; else  
        if (Data==8'b00100000) Code=5; else  
        if (Data==8'b01000000) Code=6; else  
        if (Data==8'b10000000) Code=7; else Code=3'bx;  
    end  
endmodule
```





Alternative description of an 8:3 encoder

```
module encoder (Code, Data);  
    output      [2:0] Code;  
    input       [7:0] Data;  
    reg [2:0] Code;  
    always @ (Data)  
        case (Data)  
            8'b00000001 : Code=0;  
            8'b00000010 : Code=1;  
            8'b00000100 : Code=2;  
            8'b00001000 : Code=3;  
            8'b00010000 : Code=4;  
            8'b00100000 : Code=5;  
            8'b01000000 : Code=6;  
            8'b10000000 : Code=7;  
            default      : Code=3'bx;  
        endcase  
    endmodule
```



The 8:3 encoder's the synthesis result

  



Ex 5.23 an 8:3 priority encoder

```
module priority (Code,valid_data,Data);
```

```
    output [2:0]  Code;
```

```
    output valid_data;
```

```
    input  [7:0]  Data;
```

```
    reg  [2:0]  Code;
```

```
    assign valid_data=|Data;
```

```
    // The reduction operators (& ~& | ~| ^ ~^ ^~)
```

```
    // reduce a vector to a scalar value
```

```
    always @ (Data)
```

```
    begin
```

```
        if (Data[7]) Code=7; else
```

```
        if (Data[6]) Code=6; else
```

```
        if (Data[5]) Code=5; else
```

```
        if (Data[4]) Code=4; else
```

```
        if (Data[3]) Code=3; else
```

```
        if (Data[2]) Code=2; else
```


```
        if (Data[1]) Code=1; else
```

```
        if (Data[0]) Code=0; else
```

```
            Code=3'bx;
```

```
    end
```

```
endmodule
```

 



Ex 5.23 an 8:3 priority encoder (Alternative description)


*/**// is give below

```
always @ (Data)
  casex (Data)
```

```
    8'b1xxxxxxx : Code = 7;
    8'b01xxxxxx : Code = 6;
    8'b001xxxxx : Code = 5;
    8'b0001xxxx : Code = 4;
    8'b00001xxx : Code = 3;
    8'b000001xx : Code = 2;
    8'b0000001x : Code = 1;
    8'b00000001 : Code = 0;
    default      : Code = 3'bx;
```



```
endcase
```

**/*

 



synthesis circuit

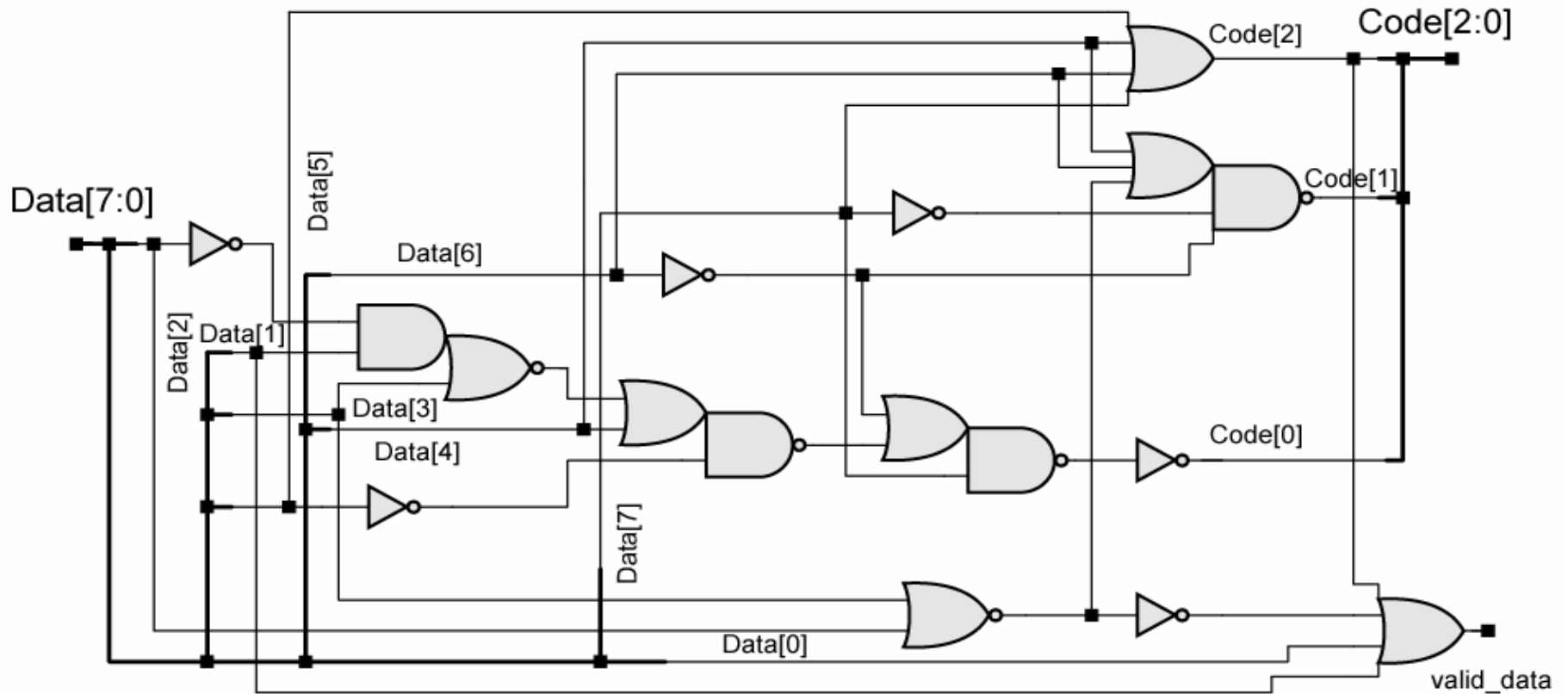 



Ex 5.24 a 3:8 decoder

```
module decoder(Data,Code);  
  output      [7:0] Data;  
  input       [2:0] Code;  
  reg         [7:0] Data;  
  always @ (Code)  
  begin  
    if (Code==0) Data=8'b00000001;  
    else if (Code==1) Data=8'b00000010;  
    else if (Code==2) Data=8'b00000100;  
    else if (Code==3) Data=8'b00001000;  
    else if (Code==4) Data=8'b00010000;  
    else if (Code==5) Data=8'b00100000;  
    else if (Code==6) Data=8'b01000000;  
    else if (Code==7) Data=8'b10000000;  
    else Data=8'bx;  
  end  
endmodule
```




Example 5.24 a 3:8 decoder

```
/* Alternative description is given below
always @ (Code)
  case (Code)
    0: Data=8'b00000001;
    1: Data=8'b00000010;
    2: Data=8'b00000100;
    3: Data=8'b00001000;
    4: Data=8'b00010000;
    5: Data=8'b00100000;
    6: Data=8'b01000000;
    7: Data=8'b10000000;
    default : Data=8'bx;
  endcase
*/
endmodule
```




Synthesis circuit

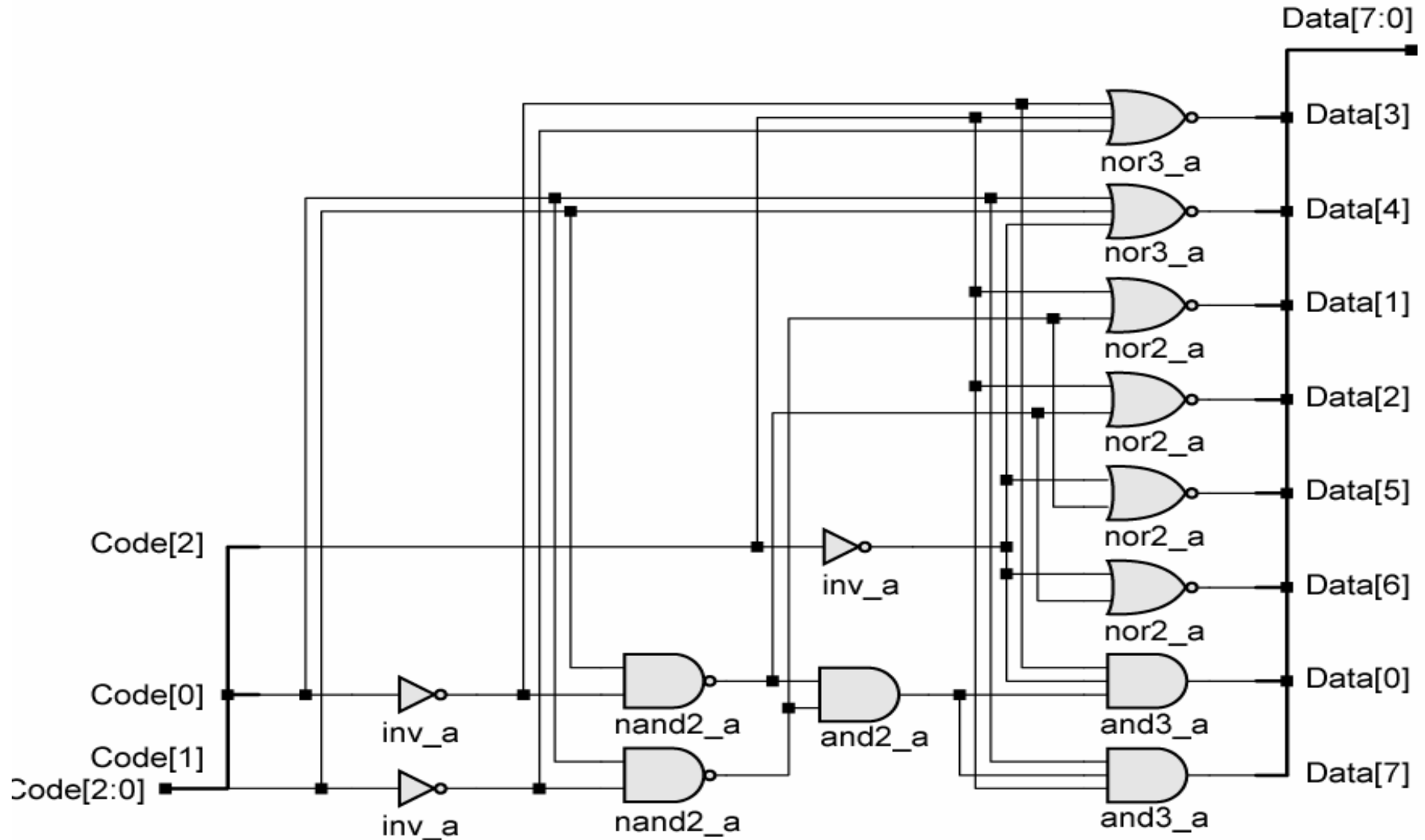



Ex 5.25 The seven-segment light-emitting diode (LED) display

- Module **Seven_Seg_Display** accepts 4-bit words representing BCD digits and displays their decimal value
- Display has active-low illumination outputs
- It can be implemented with combinational logic
- The default assignment blanks the display for all unused codes

 



Example 5.25

The seven-segment light-emitting diode


```
module Seven_Seg_Display (Display, BCD);  
    output      [6:0]    Display;  
    input       [3:0]    BCD;  
    reg         [6:0]    Display;  
    //          abc_defg  
    parameter   BLANK = 7'b111_1111;  
    parameter   ZERO  = 7'b000_0001;           // h01  
    parameter   ONE   = 7'b100_1111;           // h4f  
    parameter   TWO   = 7'b001_0010;           // h12  
    parameter   THREE = 7'b000_0110;           // h06  
    parameter   FOUR  = 7'b100_1100;           // h4c  
    parameter   FIVE  = 7'b010_0100;           // h24  
    parameter   SIX   = 7'b010_0000;           // h20  
    parameter   SEVEN = 7'b000_1111;           // h0f  
    parameter   EIGHT = 7'b000_0000;           // h00  
    parameter   NINE  = 7'b000_0100;           // h04
```



 
Example 5.25 – cont.

The seven-segment light-emitting diode

```
always @ (BCD)
  case (BCD)
    0 :   Display=ZERO;
    1 :   Display=ONE;
    2 :   Display=TWO;
    3 :   Display=THREE;
    4 :   Display=FOUR;
    5 :   Display=FIVE;
    6 :   Display=SIX;
    7 :   Display=SEVEN;
    8 :   Display=EIGHT;
    9 :   Display=NINE;
    default : Display=BLANK;
  endcase
endmodule
```





Parameter

- Parameter - assigning a value to a symbolic name
- Parameters are a means of giving names to constant values
- The values of parameters can be overridden when a design is compiled (but not during simulation), thus enabling parameterization of bus widths etc.

```
parameter size = 8;  
reg [size-1:0] a, b;
```



Parameters

- **Parameter** - assigning a value to a symbolic name
- Parameters are a means of giving names to constant values.
 - Parameters cannot be changed at runtime.
 - Parameters can be declared as signed, real, integer, time or realtime.

Example	Explanation
<code>parameter p1=5, p2=6;</code>	32 bit parameters
<code>parameter [4:0] p1=5, p2=6;</code>	5 bit parameters
<code>parameter integer p1=5;</code>	32 bit parameters
<code>parameter signed [4:0] p1=5;</code>	5 bit signed parameters




5.10 Dataflow Models of a Linear-Feedback Shift Register

- Example 5.26
- **Linear-feedback shift registers (LFSRs)**
- A linear feedback shift register can be formed **by performing exclusive-OR on the outputs of two or more of the flip-flops together and feeding those outputs back into the input of one of the flip-flops**
- LFSRs are frequently **used as pseudorandom pattern generators to generate a random number of 1s and 0s**



Linear-feedback shift registers (LFSRs)

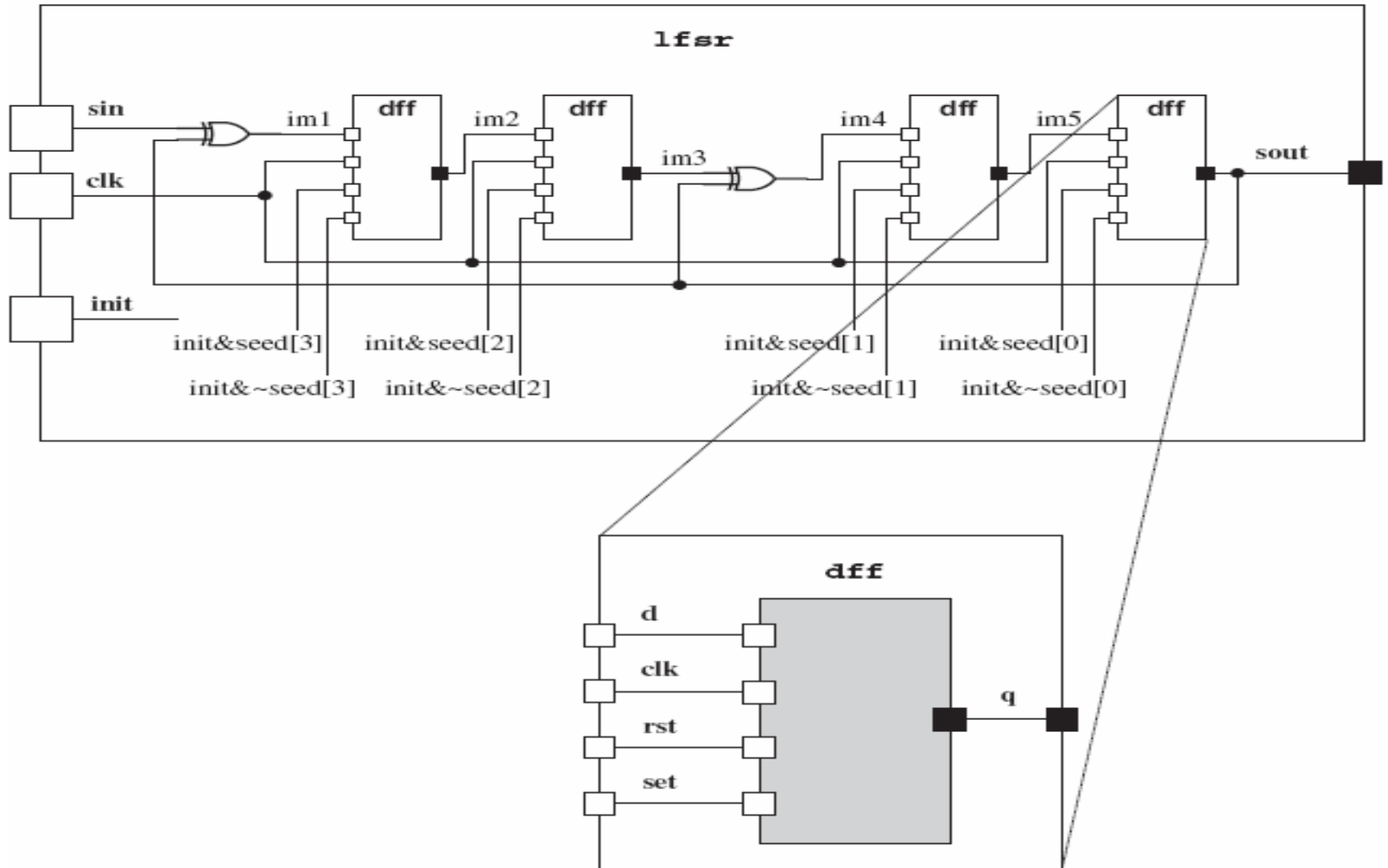



Linear Feedback Shift Registers

- **Properties**

- LFSRs are well-suited to hardware implementation;
- Can produce sequences of large period
- Can produce sequences with good statistical properties
- Because of the structure, can be analyzed using algebra

- **Definition**

- LFSR of length N consists of N stages numbered $0, 1, \dots, N-1$, each capable of storing one bit and having one input and one output, and clock which controls the movement of data
- **content of stage 0 is output** and forms part of the output sequence
- the content of stage i is moved to stage $i-1$ for each i , $1 \leq i \leq N-1$
- new content of stage $N-1$ is feedback bit s_j calculated by adding together modulo 2 previous contents of fixed subset of stages




LFSR Applications

- Pattern Generators
- Counters
- Built-in Self-Test (BIST)
- Encryption
- Compression
- Checksums
- Pseudo-Random Bit Sequences (**PRBS**)




Spread Spectrum

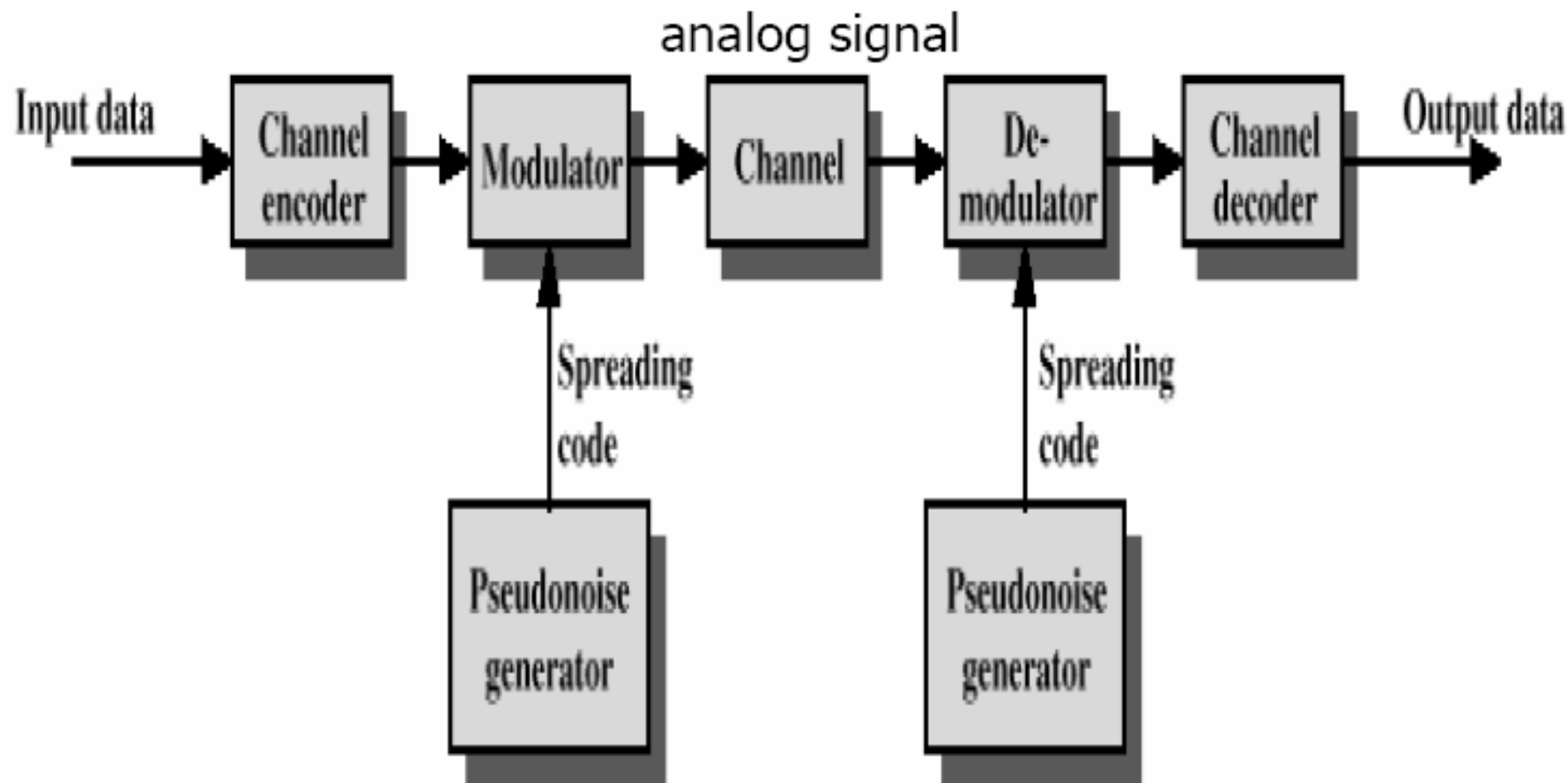




Spread Spectrum

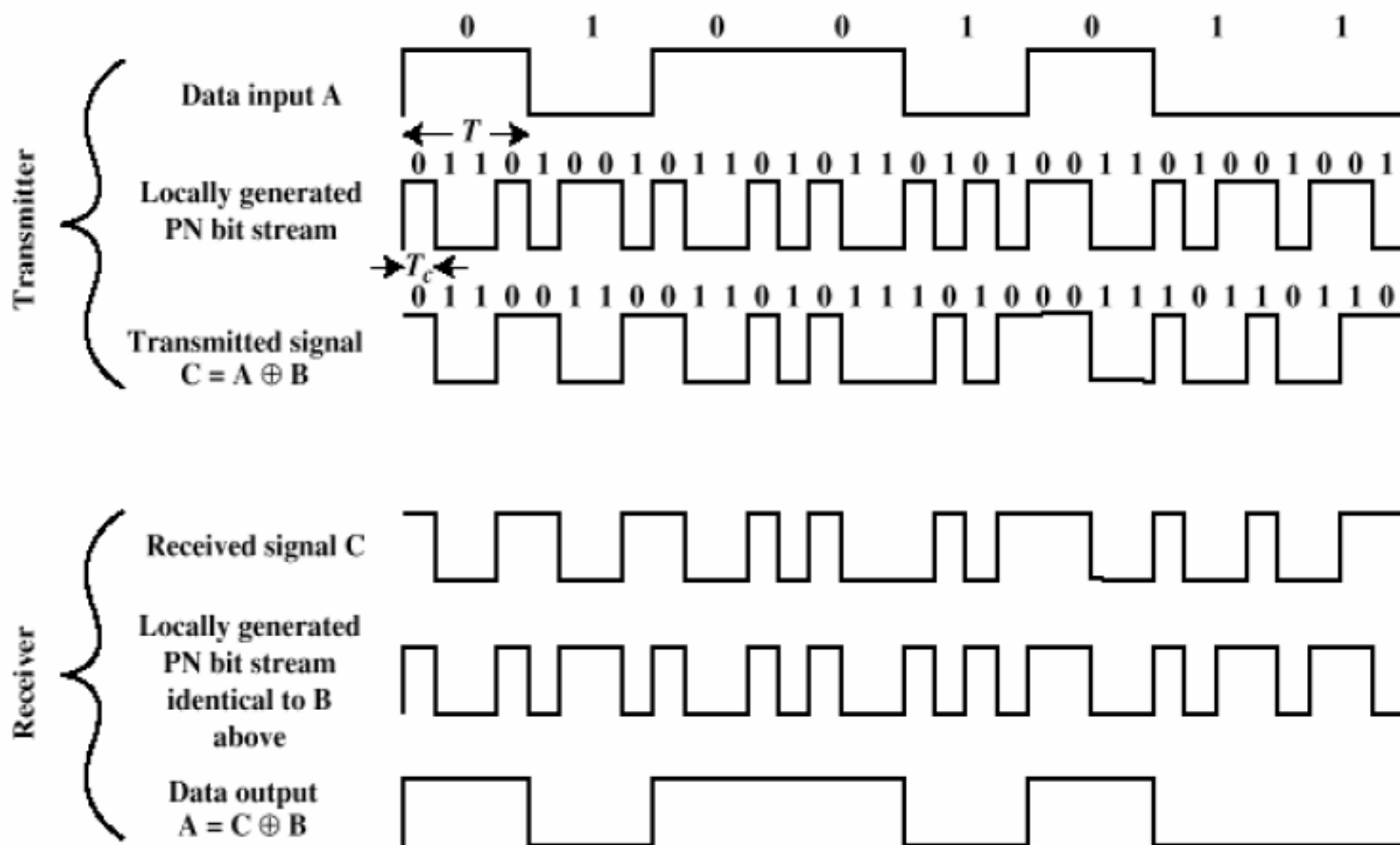



Linear Feedback Shift Register

 



Maximal-Length LFSRs

- A maximal-length LFSR produces the **maximum number of PRPG patterns** possible and has a **pattern count** equal to **$2^n - 1$**
- It produces patterns that have an approximately equal number of 1s and 0s
- **No way to predict mathematically if an LFSR will be maximal length, Peterson and Weldon have compiled tables of maximal-length LFSRs to which designers may refer**



Table . Pattern-Generator Seed Values

CLOCK PULSE	FF1_OUT	FF2_OUT	FF3_OUT	COMMENTS
1	1	1	1	Seed value
2	0	1	1	
3	0	0	1	
4	1	0	0	
5	0	1	0	
6	1	0	1	
7	1	1	0	
8	1	1	1	Starts repeat



In a practical ASIC design

- The user would create an LFSR that is much bigger than three bits to get a large number of pseudorandom patterns before the patterns repeated
- **There are some practical restrictions to the length of the LFSR.**
- A 32-bit maximal-length LFSR would create over 4 billion patterns that, at a 16-MHz clock rate, would **take almost 5 minutes to generate the whole pattern set**




Pseudo Random Pattern Generation (PRPG))

- Linear feedback shift registers **make extremely good pseudorandom pattern generators**
- When the outputs of the flip-flops are loaded with a seed value (**anything except all 0s, which would cause the LFSR to produce all 0 patterns**) and when the LFSR is clocked, it will generate a pseudorandom pattern of 1s and 0s
- Note that **the only signal** necessary to generate the test patterns **is the clock**



LFSR with modulo-2 addition

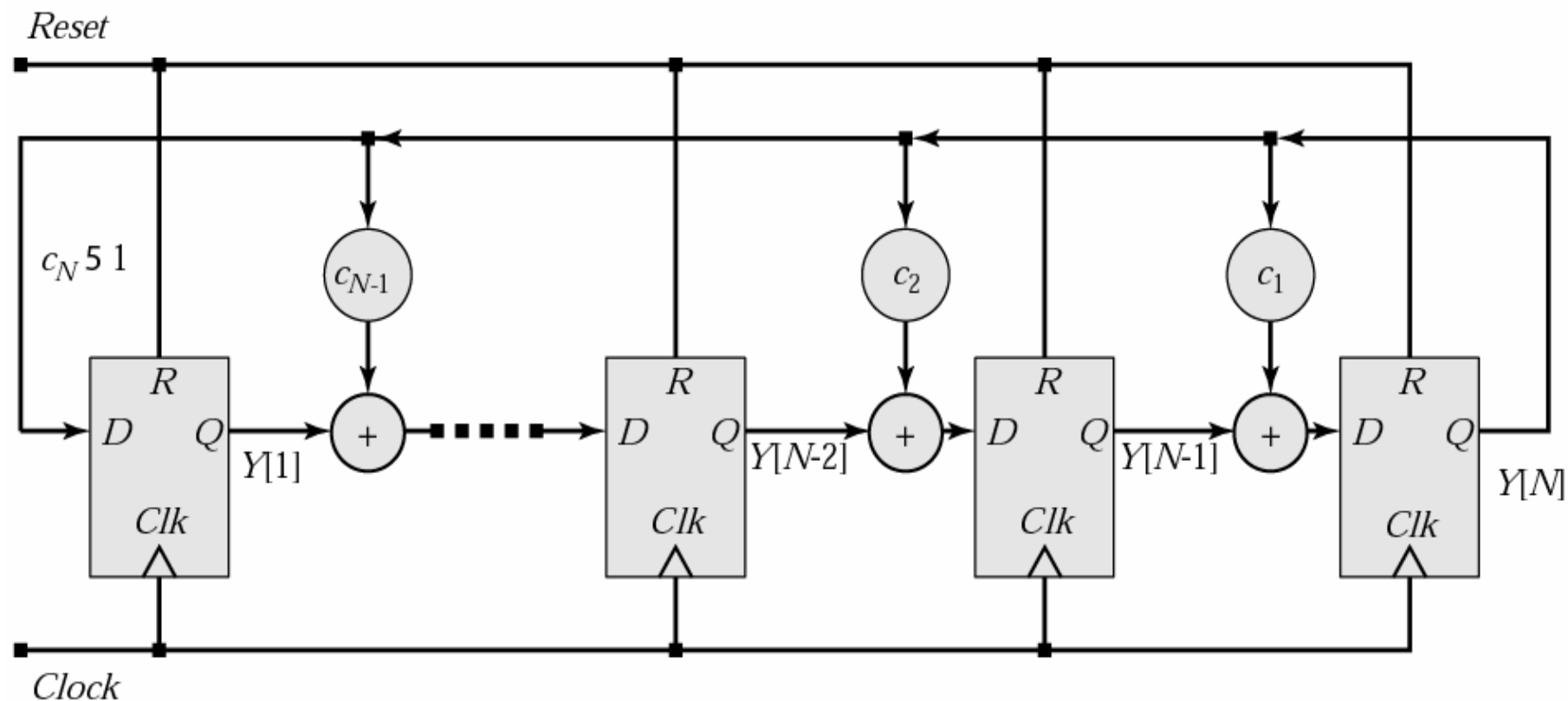



Features of LFSR

- **Binary tap coefficients C_1, \dots, C_N** that determine whether $Y(N)$ is fed back to a given stage of the register
- The vector of tap coefficients determines the coefficients of the characteristic polynomial of the LFSR
- The characteristic polynomial determines the period of the register

$$p(x) = \sum_{i=0}^m f_i x^i = x_m + f_{m-1} x^{m-1} + \dots + f_1 x + 1$$



The characteristic polynomial

- The characteristic polynomial determines the period of the register
- If $p(x) = x^{63} + x + 1$
- $2^{63} - 1 \approx 9.22337 \times 10^{18}$
- If $\text{clk} = 50\text{Mhz}$, $T = 20\text{ns}$
- The period of the register > 5800 years




Example 5.26

- The Verilog code below describes an eight-cell autonomous LFSR with a synchronous (edge-sensitive) cyclic behavior using an RTL style of design.
- The movement of data through the register under simulation is shown in binary and hexadecimal format in Figure 5-16 for the initial state and three cycles of the clock.



LFSR with modulo-2 addition

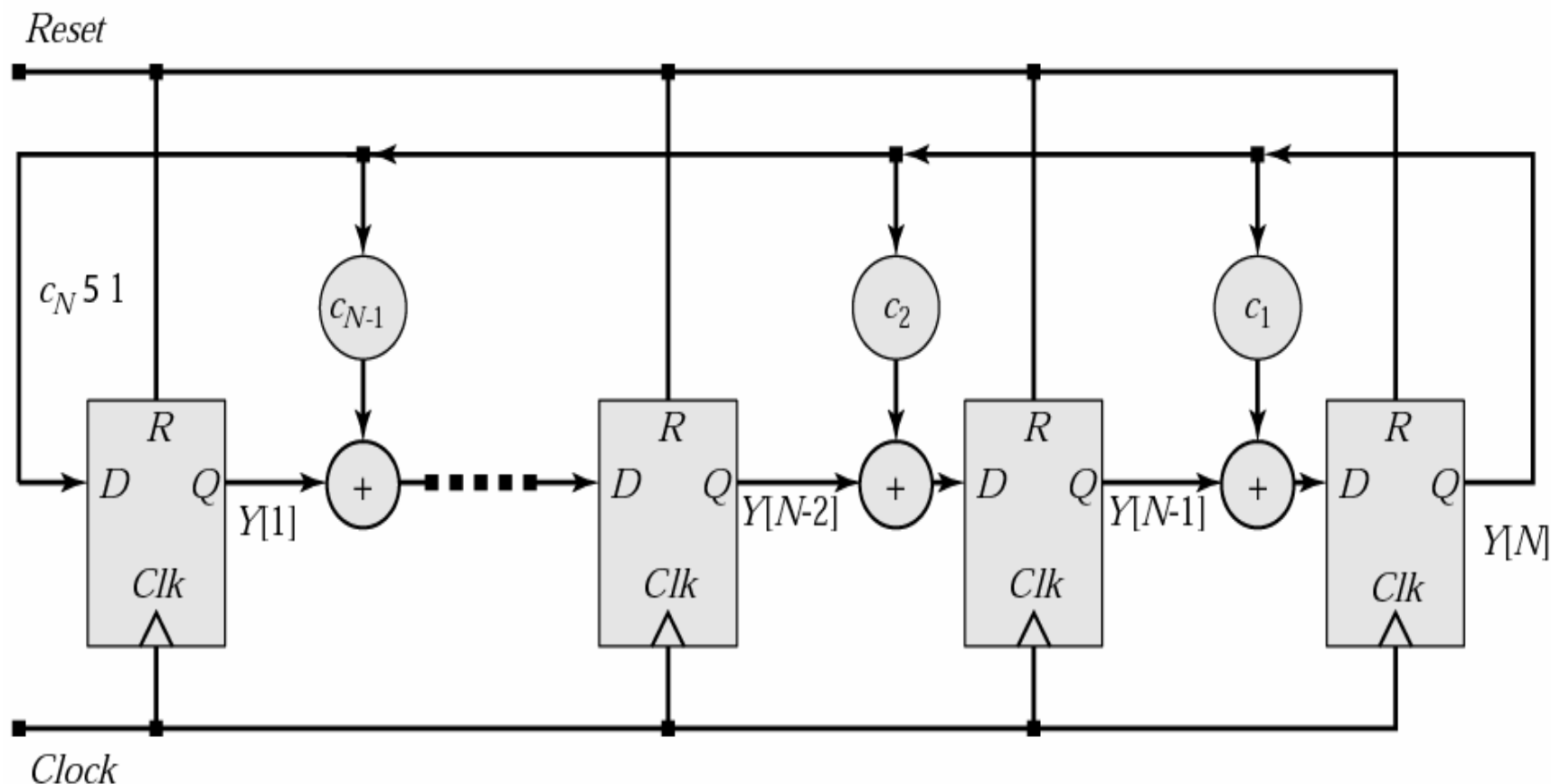




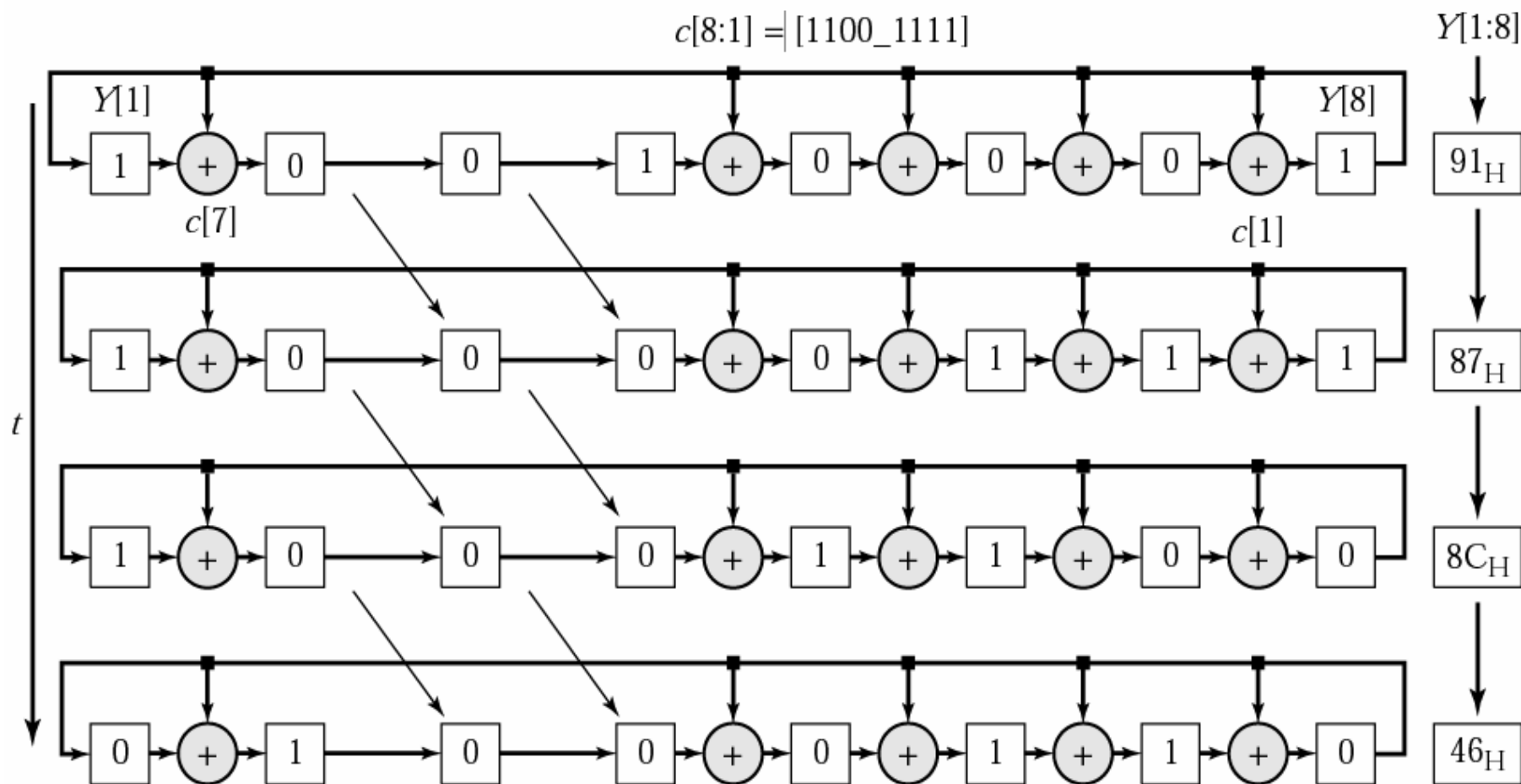Example 5.26

```
module Auto_LFSR_RTL (Y,Clock,Reset);  
parameter          Length=8;  
parameter          initial_state=8'b1001_0001; // 91h  
parameter [1:Length] Tap_Coefficient=8'b1100_1111;  
input  Clock,Reset;  
output [1:Length] Y;  
  reg [1:Length]  Y;  
always @ (posedge Clock)  
  if (Reset==0) Y<= initial_state; // active-low reset to initial state  
  else begin  
    Y[1]<=Y[8];  
    Y[2]<=Tap_Coefficient[7] ? Y[1]^Y[8] : Y[1];  
    Y[3]<=Tap_Coefficient[6] ? Y[2]^Y[8] : Y[2];  
    Y[4]<=Tap_Coefficient[5] ? Y[3]^Y[8] : Y[3];  
    Y[5]<=Tap_Coefficient[4] ? Y[4]^Y[8] : Y[4];  
    Y[6]<=Tap_Coefficient[3] ? Y[5]^Y[8] : Y[5];  
    Y[7]<=Tap_Coefficient[2] ? Y[6]^Y[8] : Y[6];  
    Y[8]<=Tap_Coefficient[1] ? Y[7]^Y[8] : Y[7];  
  end  
endmodule
```



data movement in an LFSR with modulo-2 addition





5.11 Modeling Digital Machines with Repetitive Algorithms

- An algorithm for modeling the behavior of a digital machine may **execute some or all of its steps repeatedly in a given machine cycle**, depending on whether the steps executed unconditionally or not
- For example, an algorithm that sequentially shifts the bits of an LFSR can be described by a **for loop** in Verilog



Example 5.27

```
module Auto_LFSR_ALGO (Y,Clock,Reset);  
parameter      Length=8;  
parameter  initial_state=8'b1001_0001;  
parameter [1:Length] Tap_Coefficient=8'b1100_1111;  
input      Clock,Reset;  
output    [1:Length] Y;  
reg [1:Length]      Y;  
always @ (posedge Clock)  
  begin  
    if (Reset==0) Y<=initial_state; // arbitrary initial state,91h  
    else begin  
      for (Cell_ptr=2;Cell_ptr<=Length;Cell_ptr=Cell_ptr+1)  
        if (Tap_Coefficient[Length-Cell_ptr+1]==1)  
          Y[Cell_ptr]<=Y[Cell_ptr-1]^Y[Length];  
        else  
          Y[Cell_ptr]<=Y[Cell_ptr-1];  
          Y[1]<=Y[Length];  
        end  
    end  
endmodule
```



Loop Statements

- **forever** loop - executes continually
 - **repeat** loop - executes a fixed number of times
 - **while** loop - executes if expression is true
 - **for** loop - executes once at the start of the loop and then executes if expression is true
- ⇒ Loop statements - used for repetitive operations



Loop Statement

A **for loop** has the form:


```
For (initial_statement;  
    control_expression;  
    index_statement )  
statement_for_execution;
```



For Loop

- **for loop** -
executes once
at the start of
the loop and
then executes
if expression is
true

4-bit Left Shifter

 

```
integer i; // declare the index for the FOR LOOP
```

```
always @(inp or cnt)  
begin
```

```
    result[7:4] = 0;  
    result[3:0] = inp;  
    if (cnt == 1)  
        begin
```

```
            for (i = 4; i <= 7; i = i + 1)  
                begin  
                    result[i] = result[i-4];  
                end
```

```
            result[3:0] = 0;
```

```
        end  
    end
```



Forever and Repeat Loops

- **forever loop** - executes continually

```
initial
begin
    clk = 0;
    forever #25 clk = ~clk;
end
```

Clock with period
of 50 time units

- **repeat loop** - executes a fixed number of times

```
if (rotate == 1)
    repeat (8)
        begin
            tmp = data[15];
            data = {data << 1, tmp};
        end
```

Repeats a rotate
operation 8 times



while loop

A Verilog ***while*** loop has the form:

- **while (Expression)**
- **Statement**
- A loop statement that repeats a statement or block of statements **as long as a controlling expression remains true (i.e. non-zero).**



While Loop

- **while** loop - executes if expression is true

```
initial
begin
    count = 0;
    while (count < 101)
        begin
            $display ("Count = %d", count);
            count = count + 1;
        end
    end
end
```

Counts from 0 to 100
Exits loop at count 101



Ex 5.29

The for loop is used to assign values to bits within a register after it has been initialized to x

```
reg [15:0] demo_register;
```

```
integer K ;
```

```
...
```

```
for (K=4;K>0;K=K-1)
```

```
begin
```

```
    demo_register [K+10]=0;
```

```
    demo_register [K+2]=1;
```

```
end
```

```
...
```

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
x	0	0	0	0	x	x	x	x	1	1	1	1	x	x	x



Ex 5.30 A majority circuit

- A majority circuit is a combinational circuit whose **output is equal to 1 if the input variables have more 1's than 0's.**

The output is 0 otherwise.

- Ex. Design **a 3-input majority circuit.**

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

	00	01	11	10
0			1	
1		1	1	1

$$F = xy + xz + yz$$



Example 5.30

```
module Majority_4b (Y,A,B,C,D);  
    input      A,B,C,D;  
    output     Y;  
    reg        Y;  
    always @ (A or B or C or D) begin  
        case ({A,B,C,D})  
            7,11,13,14,15: Y=1;  
            default      Y=0;  
        endcase  
    end  
endmodule
```





Ex 5.30- Majority

```
module Majority (Y,Data);  
    parameter    size=8;  
    parameter    max=3;  
    parameter    majority=5;  
    input         [size-1:0]  Data;  
    output        Y;  
    reg           Y;  
    reg           [max-1:0]   count;  
    integer       k;  
    always @ (Data) begin  
        count=0;  
        for (k=0; k<=size; k=k+1) begin  
            if (Data[k]==1) count=count+1;  
        end  
        Y=(count>=majority);  
    end  
endmodule
```



Simulation result

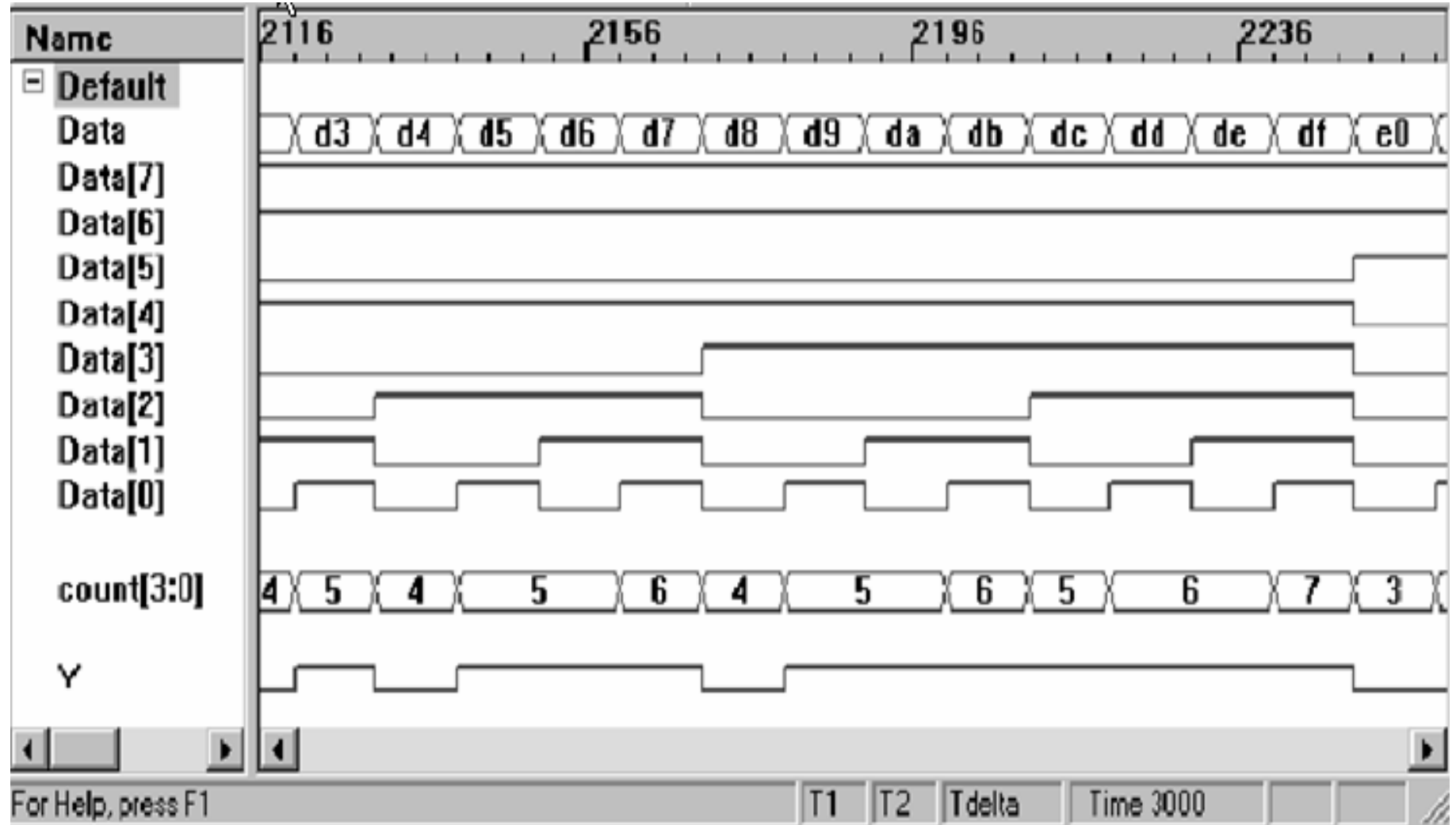



5.11.1

Intellectual Property Reuse and Parameterized Models

- Models have increased value **if they are written to be extendable to more than one application**
- Use parameters to specify:
**bus widths, word length,
and other details that customize a model
to an application**



Ex 5.31 an eight-cell autonomous LFSR

```
module Auto_LFSR_Param (Y, Clock, Reset);  
  parameter          Length=8;  
  parameter          initial_state=8'b1001_0001;  
  parameter [1:Length] Tap_Coefficient=8'b1100_1111;  
  input              Clock, Reset;  
  output [1:Length] Y;  
  reg [1:Length]      Y;  
  integer            k;  
  always @ (posedge Clock)  
    if (Reset==0) Y<= initial_state;  
    else begin  
      for (k=2;k<=Length;k=k+1)  
        Y[k]<=Tap_Coefficient[Length-k+1] ? Y[k-1]^Y[Length] : Y[k-1];  
      Y[1]<=Y[Length];  
    end  
endmodule
```



Example 5.32

```
begin: count_of_1s // count_of_1s declares a named
                // block of statements

reg [7:0] temp_reg;
    count=0;
    temp_reg=reg_a; // load a data word
while (temp_reg)
    begin
        if (temp_reg[0]) count = count + 1;
        temp_reg = temp_reg >>1;
    end
end
```



An alternative description of Ex 5.32

```
begin: count_of_1s // count_of_1s declares a named  
                // block of statements
```

```
reg [7:0] temp_reg;
```

```
count=0;
```

```
temp_reg=reg_a; // load a data word
```

```
while (temp_reg)
```

```
  begin
```

```
    count=count+temp_reg[0];
```

```
    temp_reg = temp_reg>>1;
```

```
  end
```

```
end
```



5.11.2 Clock Generators

- **In testbenches to provide a clock signal** for testing the model of a synchronous circuit
- A flexible clock generator will be parameterized for a variety of applications
- The **forever** loop causes **unconditional repetitive** execution of statements, **subject to the *disable* statement**
- The ***disable*** statement is used to prematurely terminate a named block of procedural statement
- **Some EDA synthesis tools will synthesize only the **for** loop**



Example 5.33

```
parameter half_ccle = 50;
```

```
parameter stop_time = 350;
```

```
initial
```

```
begin: clock_loop // Note: clock_loop is a named block  
      // of statements
```

```
clock=0;
```

```
forever
```

```
begin
```

```
# half_cycle clock=1;
```


```
# half_cycle clock=0;
```

```
end
```

```
end
```

```
initial
```

```
# 350 disable clock_loop;
```

 



Distinction of *always* and *forever*

- ***always*** and ***forever*** are not the same construct
- **1. *always*** construct declares a concurrent behavior;
forever loop is a **computational activity** flow and is used only within a behavior
- **2. *forever*** loops can be nested; **cyclic and single-pass behaviors may not be nested**
- **3. *forever*** loop executes only when it is reached within a sequential activity flow
always behavior becomes active and can execute at the beginning of simulation



Example 5.34 finds the location of the first 1 in a 16-bit

```
module find_first_one (index_value, A_word, trigger)
  output [3:0] index_value;
  input [15:0] A_word;
  input      trigger;
  reg [3:0]   index_value;
  always @ (trigger)
    begin: search_for_1
      index_value=0;
      for (index_value=0; index_value<=15;
          index_value=index_value+1)
        if (A_word[index_value]==1) disable search_for_1;
      end
    endmodule
```



5.12 Machines with Multicycle Operations

- Some digital machines have repetitive operations distributed over multiple clock cycles
- This activity can be modeled in Verilog by a synchronous cyclic behavior that has nested edge-sensitive event-control expressions



Ex 5.35 4-cycle adder


```
module add_4cycle (sum, data, clk, reset);  
    output [5:0] sum;  
    input  [3:0] data;  
    input      clk, reset;  
    reg        sum;  
    always @ (posedge clk)  
    begin: add_loop  
        if (reset) disable add_loop;           else sum<=data;  
        @ (posedge clk) if (reset) disable add_loop; else sum<=sum+data;  
        @ (posedge clk) if (reset) disable add_loop; else sum<=sum+data;  
        @ (posedge clk) if (reset) disable add_loop; else sum<=sum+data;  
    end  
endmodule
```

Disable:

Causes the execution of an active task or named block to terminate before all its statements have been executed.



synthesis circuit

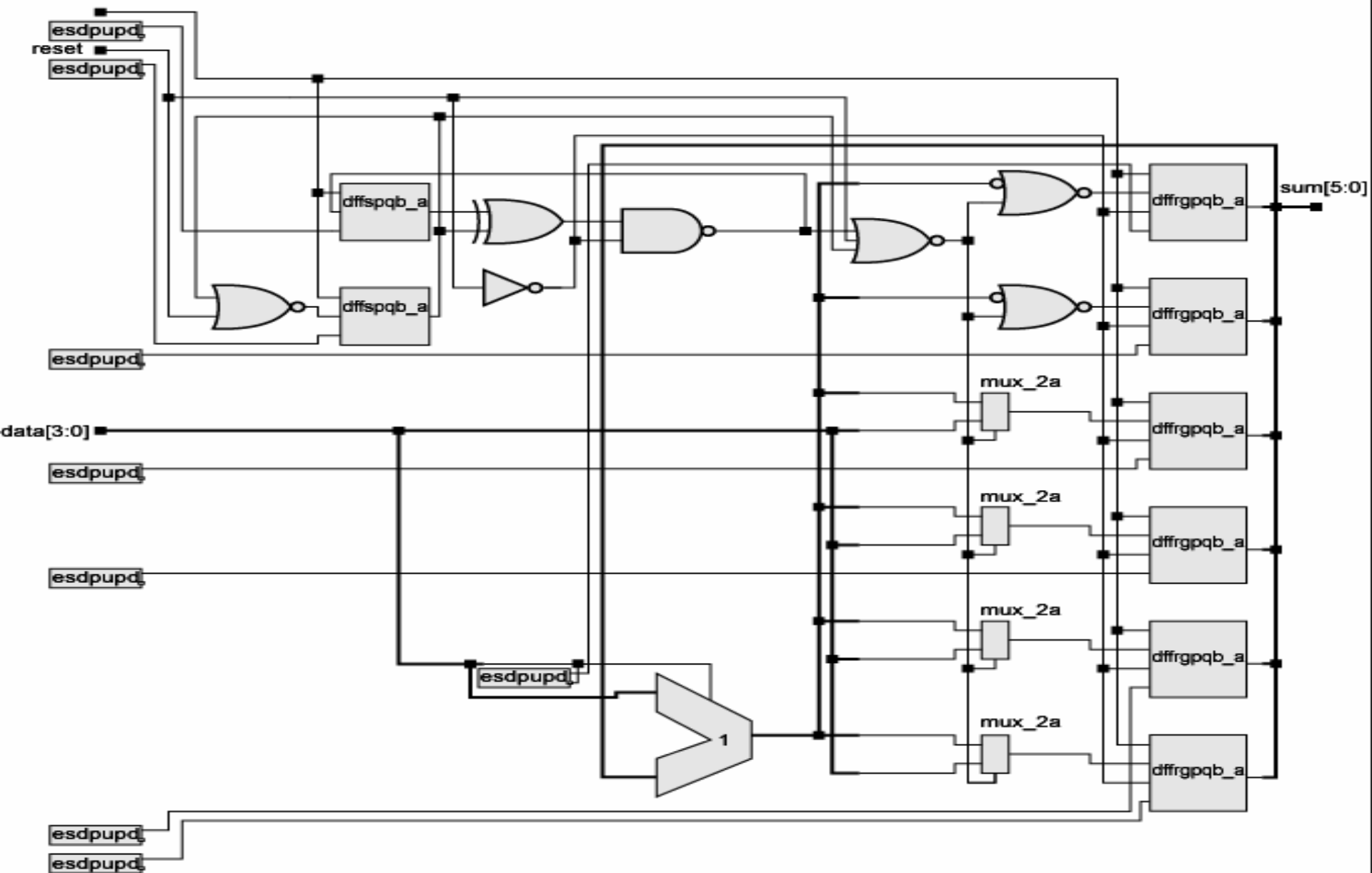



5.13 Design documentation with Functions and Tasks

- Two types of subprograms can improve the clarity of a description: **task, function**
- **Tasks create a hierarchical organization** of the procedural statements within a Verilog behavior
- **Functions substitute for an expression**
- Tasks and functions let designers manage a smaller segment of code and hide the details of an implementation from the outside world
- Function and task **improve the readability, portability and maintainability of a model**



5.13.1 Tasks

- Two kinds of type: **User Defined Task** , **System Task**
- Tasks are declared within a module, and they may be **referenced only from within a cyclic or single-pass behavior**.
- A task can have **parameters passed to it**, and the results of executing the task can be passed back to the environment
- **A task can call itself**
- Original standard(1995) does not support **recursion**
- **More general than functions and may contain timing controls**
- **Tasks to be synthesized may contain event-control operators** but not delay-control operators



Tasks

- **Syntax:**
- ***task TaskName;***
[Declarations...]
Statement
endtask
- Declarations of any number or combination of the following:
- ***parameter, input, output, inout, reg, integer, event, (real, time, realtime)***
- **All declarations of variables are local to the task**
- When a task is invoked, **its formal and actual arguments are associated in the order** in which the task's ports have been declared



Task Enable (or 'call')

- When a task is enabled, values are passed into the task using the input and inout arguments
- When the task completes, values are passed out from the task using the task's output and inout arguments.
- Syntax
- **TaskName[(Expression,...)];**
- For synthesis, a task may not contain timing controls.
- Task enables are synthesized as combinational logic.




Ex 5.36 a user-defined task that adds two 4-bit words and a carry bit

```
module adder_task (c_out,sum,c_in,data_a,data_b,clk,reset)
  output [3:0] sum;
  output      c_out;
  input  [3:0] data_a,data_b;
  input      clk, reset;
  input      c_in;
  reg       sum;
  reg       c_out;
  always @ (posedge clk or posedge reset)
    if (reset) {c_out,sum}<=0; else add_value (c_out,sum,data_a,data_b,c_in);
  task add_value;
  output [3:0] sum;
  output      c_out;
  input  [3:0] data_a,data_b;
  input      c_in;
  begin
    {c_out,sum}<=data_a+(data_b+c_in);
  end
endtask
endmodule
```



synthesis circuit

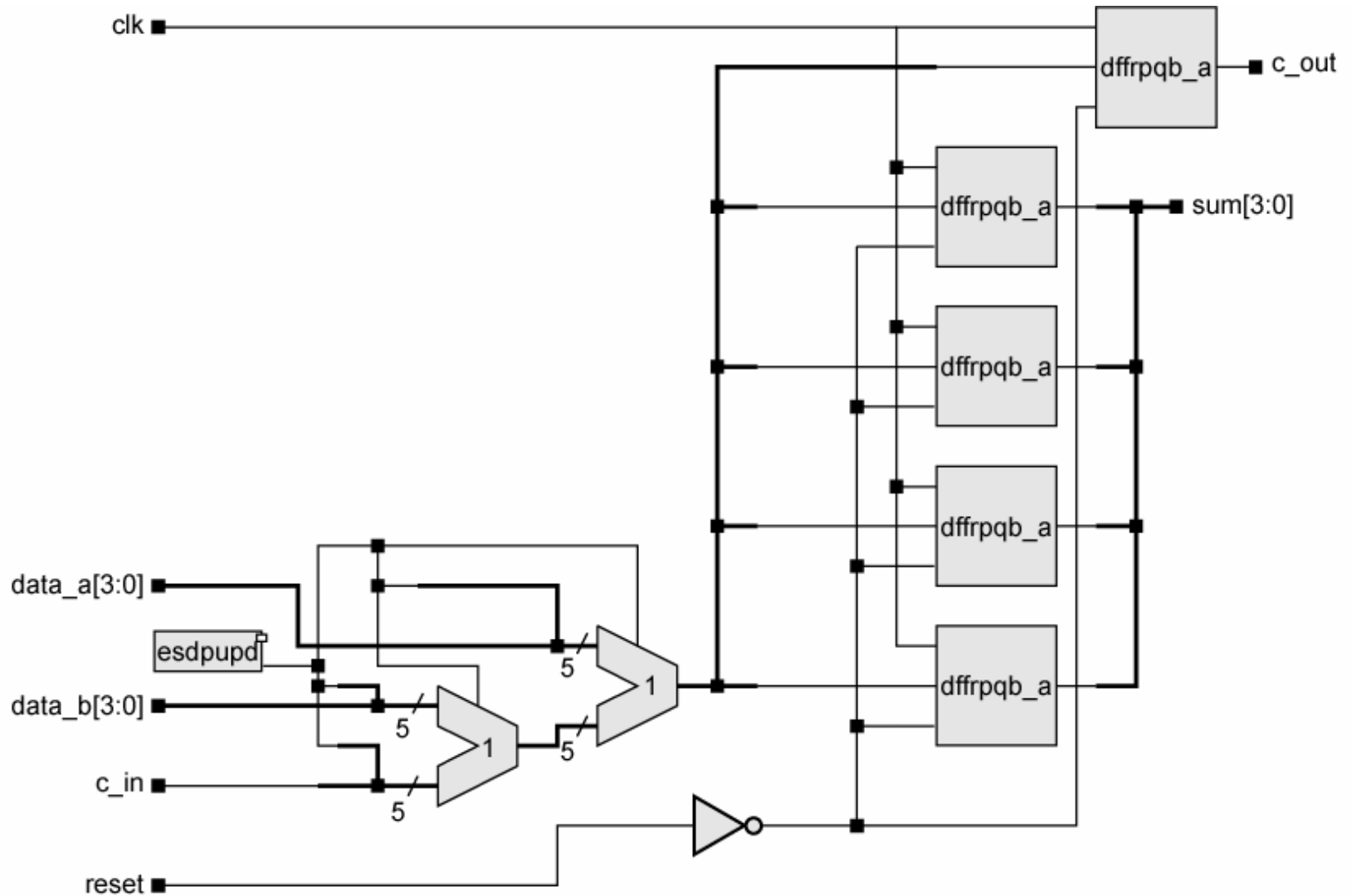



5.13.2 Functions

- A function is also implemented by an expression and **returns a value at the location of the function's identifier**
- **Functions may implement only combinational behavior**, not contain timing controls(no #, @)
- The definition of a function implicitly defines **an internal register variable with the same name, range, and type as the function itself**



Function

- **function [Range Or Type] FunctionName;
Declarations...
Statement
endfunction**
- Calls a function, which returns a value for use in an expression.
- **FunctionName (Expression,...);**
- Each call to a function is synthesized as a separate block of combinational logic



Rules

- A function **must have at least one input argument.**
- **It may not have any outputs or inouts.**
- Functions may **not contain timing controls** (delays, event controls or waits).
- A function returns a value by assigning the function name, as if it were a register.
- **Functions may not enable tasks.**
- **Functions may not be disabled.**



Ex 5.37 shift a word to the left until the most significant bit is '1'

```
module word_aligner (word_out, word_in);  
    output [7:0] word_out;  
    input  [7:0] word_in;  
    assign word_out = aligned_word (word_in);  
    function [7:0] aligned_word;  
        input  [7:0] word;  
        begin  
            aligned_word=word_in;  
            if (aligned_word!=0)  
                while (aligned_word[7]==0)  
                    aligned_word=aligned_word <<1;  
        end  
    endfunction  
endmodule
```




Example 5.38

```
module arithmetic_unit (result_1,result_2,operand_1,operand_2);  
    output      [4:0] result_1;  
    output      [3:0] result_2;  
    input        [3:0] operand_1,operand_2;  
    assign result_1=sum_of_operands (operand_1,operand_2);  
    assign result_2=largest_operand (operand_1, operand_2);  
    function [4:0] sum_of_operands;  
                                //implicitly defines an internal register variable  
    input [3:0] operand_1,operand_2;  
    sum_of_operands=operand_1+operand_2;  
    endfunction  
    function [3:0] largest_operand;  
    input [3:0] operand_1,operand_2;  
    largest_operand=(operand_1>=operand_2)? operand_1:operand_2;  
    endfunction  
endmodule
```




Figure 5-22 synthesis circuit

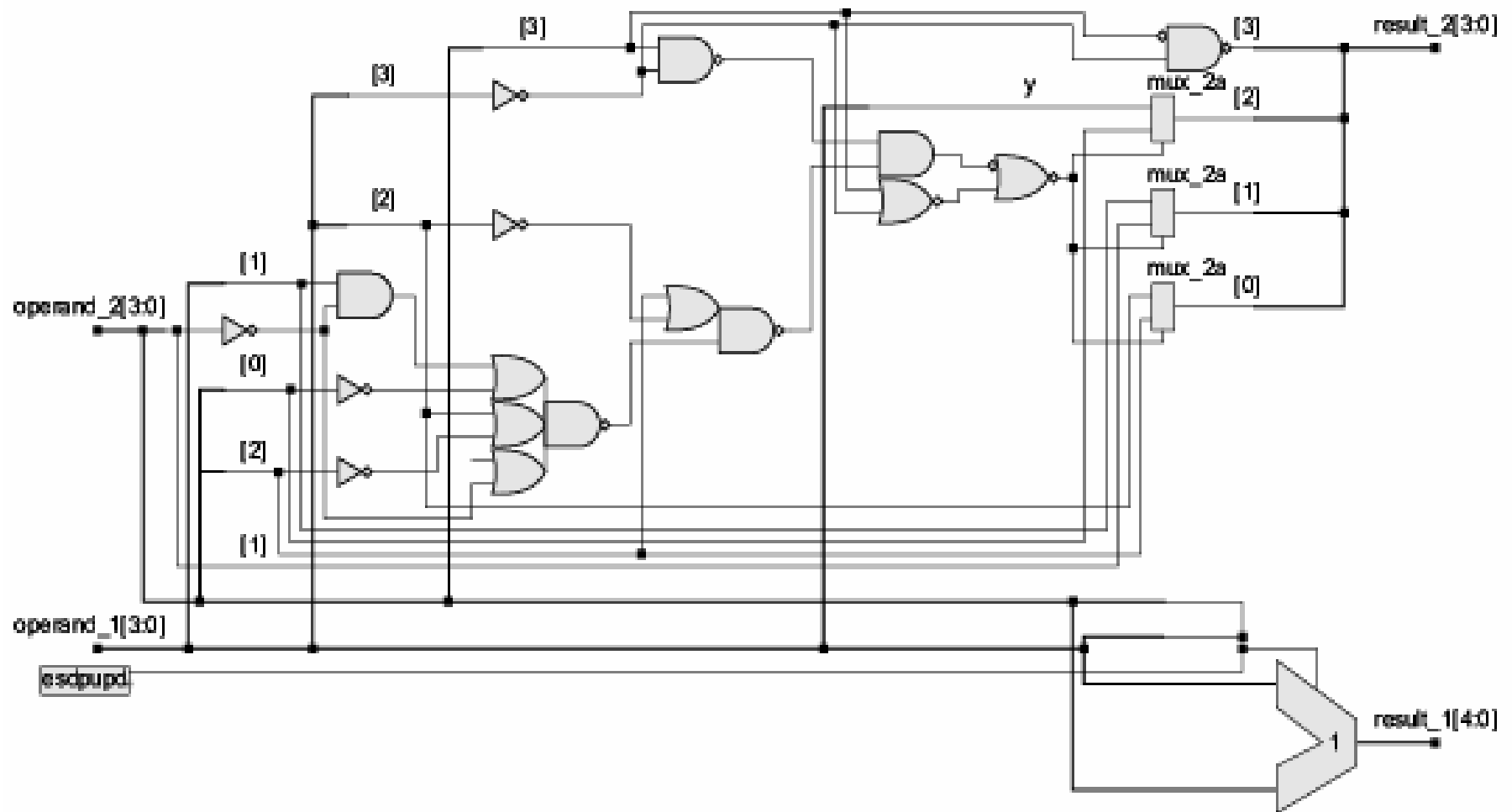



Compare of Task ,Function

- **Input,Output**(Function:a input,no inout)
- **Enabel(call):**always(task),assign
- **F:**no Timing & Event Control
- **T:**no Timing Control
- **Call another Task or Function :**
 Func. Not call Task
- **Return value:** Func. Return Value



5.14 Algorithmic State Machine Charts for Behavioral Modeling

- A machine's activity **consists of a synchronous sequence of operations** on the registers of its datapaths, usually **under the direction of a controlling state machine**
- State-transition Graphs (STGs) indicate the transitions that result from inputs when the state machine is in a particular
- An ASM chart **focuses on the activity of the machine, rather than on the contents** of all the storage elements.





Algorithmic State Machine charts

- **ASM are an abstraction of the functionality of a sequential machine**
- Similar to software flowcharts ,display **the time sequence of computational activity as well as the sequential steps that occur** under the influence of the machine's inputs
- **Focus on the activity of the machine**
- Helpful in describing the behavior of sequential machines and in designing a state machine to control a datapath




Construct

  - An ASM chart has three basic elements:
- **state box**
- **conditional box**
- **decision box**





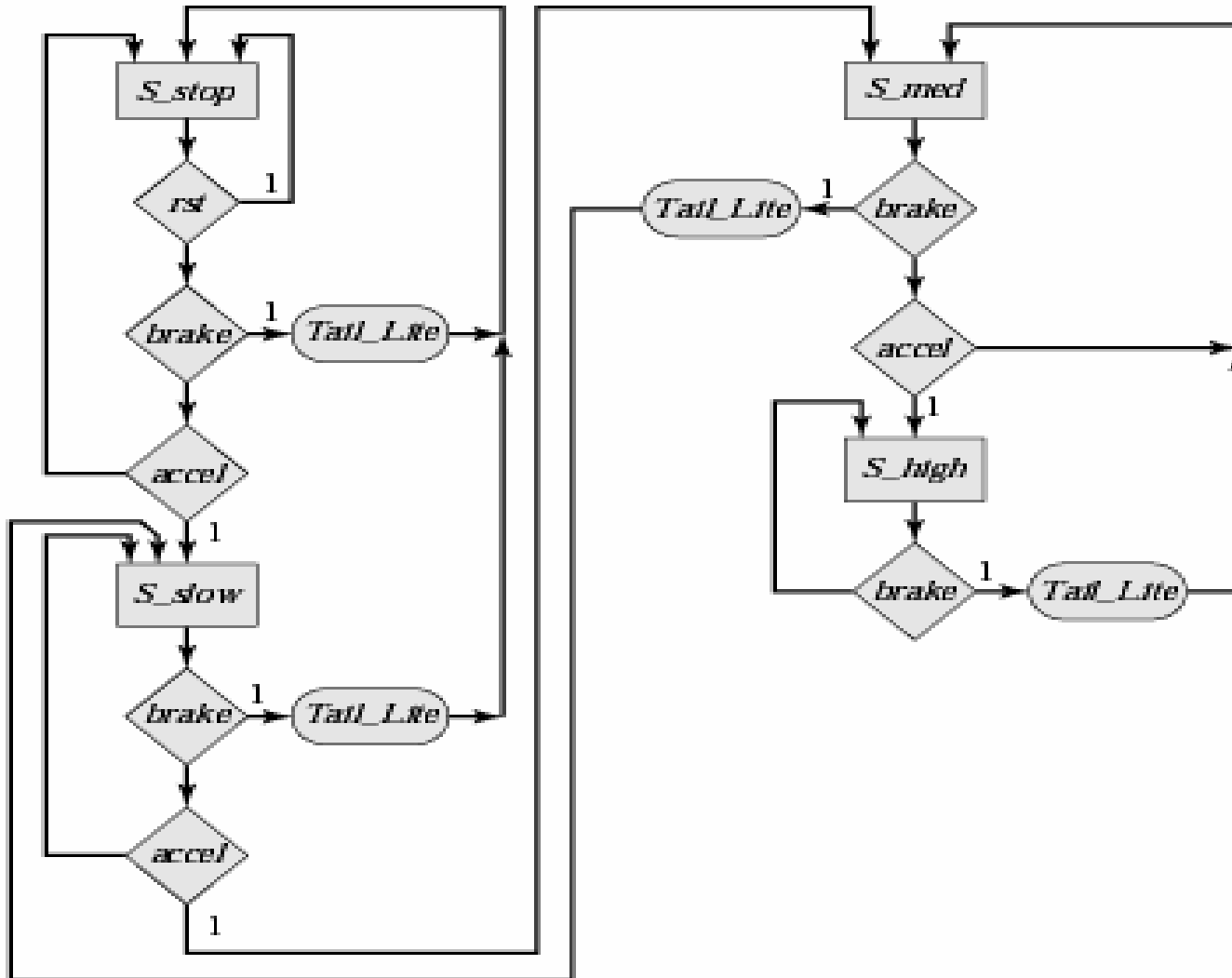an ASM chart for a vehicle speed controller






5.15 ASMD Charts

- A state machine will **control register operations on a datapath** in a sequential machine which has been partitioned into a controller and a datapath
- ASM charts that have been linked to a datapath in this manner are called **Algorithmic State Machine and Datapath (ASMD)** charts.
- The controller is described by an ASM chart modify the chart to link it to the datapath that is controlled by the machine



Datapath & Controller:

State-machine controller for a datapath

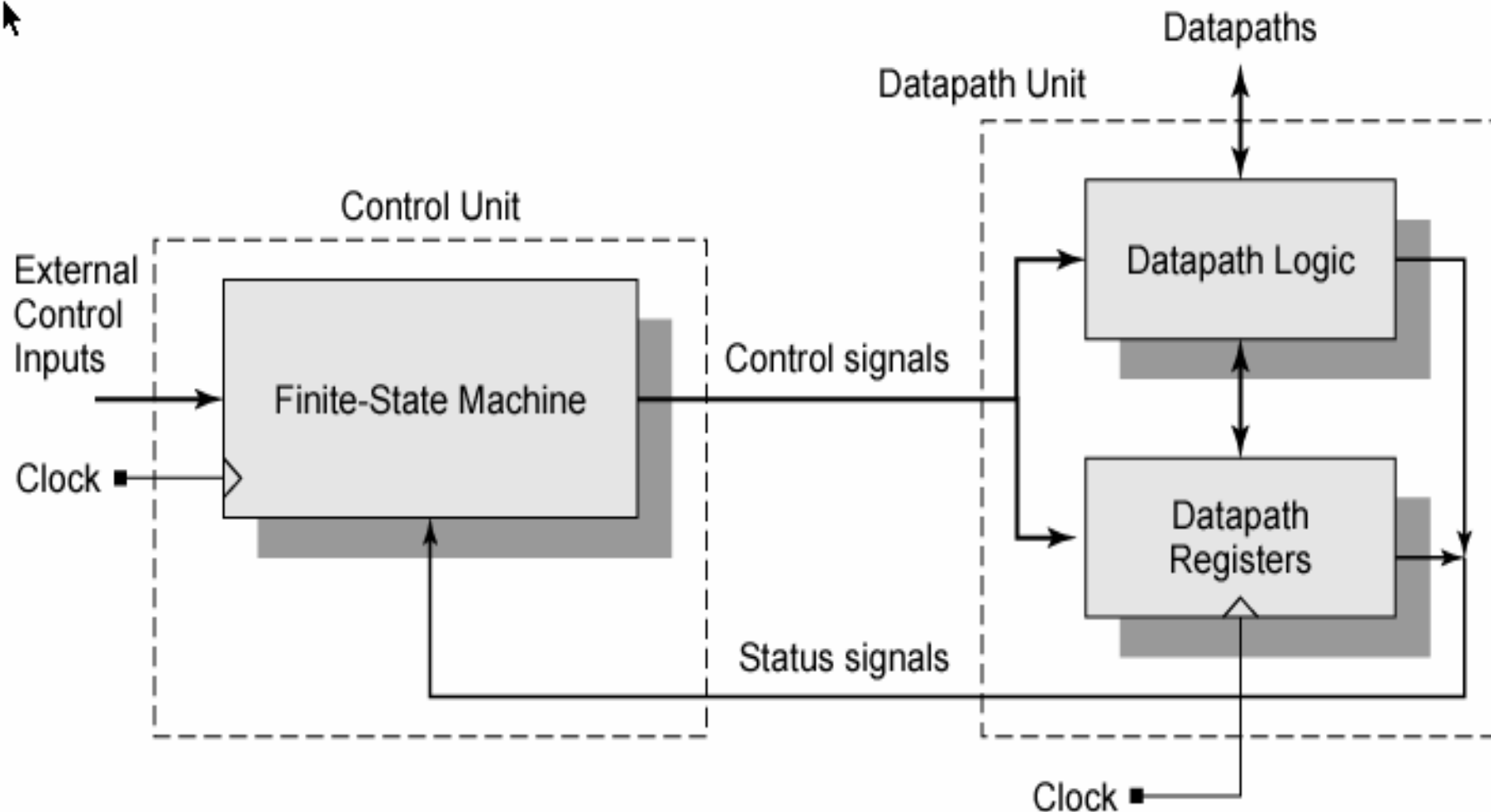



Datapath & Controller

- The datapath portion of the circuit is the portion that transforms the input signals into the corresponding output signals.
- The controller is the portion that governs the flow of the input signals through the various components comprising the datapath.




Example 5.39

- The architecture and ASMD chart describe the behavior of pipe_2stage, **a two-stage pipeline that acts as a 2:1 decimator** with a parallel input and output
- Decimators are used in digital signal processors to **move data from a high-clock-rate datapath to a lower-clock-rate datapath**
- They are also used **to convert data from a parallel format to a serial format**




A two-stage pipeline architecture

 



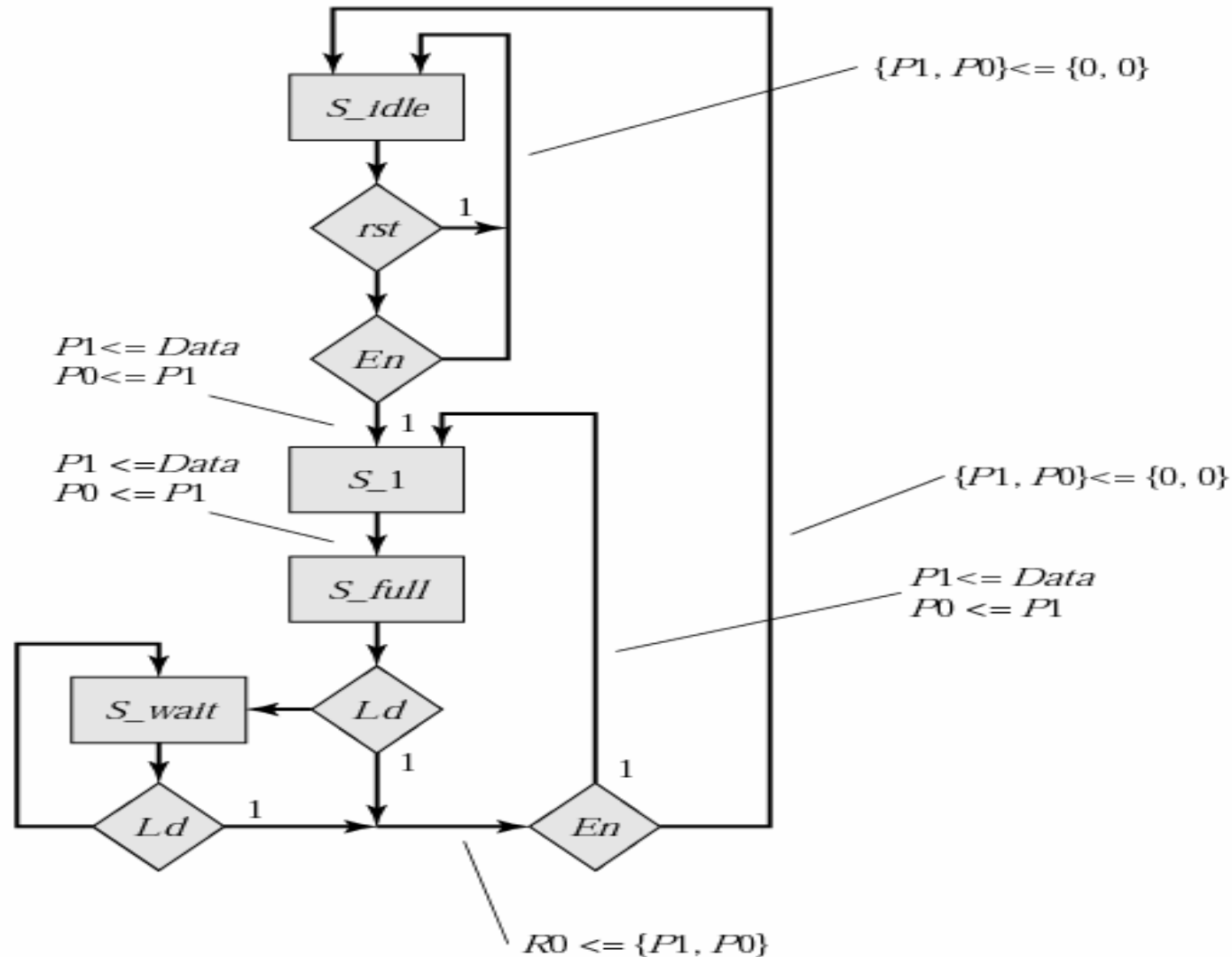Ex 5.39 ASMD chart of a two-stage pipeline architecture





ASMD chart

- synchronous **reset to S_idle**
- With **En asserted**, the machine transitions **from S_idle to S_1**, accompanied by concurrent register operations that **load the MSByte of the pipe with Data and move the content of P1 to the LSByte (P0)**
- At the next clock the state goes to **S_full**, and now the pipe is full
- **The data rate at R0 is one-half the rate at which data is supplied to the unit from an external datapath**




Pipelining

- Purposefully **Inserting Register(s) into Middle of Combinatorial Data (Critical) Path**
- Increases Clocking Speed
- Adds Levels of Latency
 - More Clock Cycles Needed to Obtain Output
- Some Tools Perform Automatic Pipelining
 - Same Advantages/Disadvantages As Automatic Fan-Out




Adding Single Pipeline Stage

25 MHz System

 


50 MHz System

 




Registered Datapath

 

DFFs are rising
edge triggered


$$\text{Clk Freq} = 1 / (T_{\text{clk}2q} + T_{\text{pd}} + T_{\text{su}})$$

$$\text{Latency} = 1 \text{ clk}$$

 




Add a pipeline stage

 

$$\text{Clk Freq} = 1 / (\text{Tclk2q} + \text{Tpd}/2 + \text{Tsu})$$

Latency = 2 clks

 



The design of a datapath controller

1. Begins with an understanding of the sequential register operations that must execute on a given datapath architecture
2. Defines an ASM chart describing a state machine that is controlled by primary input signals and/or status signals from the datapath
3. Forms an ASMD chart by annotation the arcs of the ASM chart with the datapath operations associated with the state transition of the controller the design of a datapath controller
4. Annotates the state of the controller with unconditional output signals
5. Includes conditional boxes for the signals that are generated by the controller to control the datapath



5.16 Behavioral Models of Counters, Shift Registers, and Register Files


- The storage elements of counters and registers usually have the same synchronizing and control signals
- A **counter** generates a sequence of related binary words
- A **register** stores data that can be retrieved and/or overwritten
- **Register files are a collection of registers** that share the same synchronizing and control signals
- **Behavioral descriptions of many counters, shift registers and register files are routinely synthesized by modern synthesis tools**



5.16.1 Counters


- Example 5.40

```
module Up_Down_Implicit1(count, up_dwn, clock, reset_);  
  output [2:0] count;  
  input  [1:0] up_dwn;  
  input  clock,reset_  
  reg    [2:0] count;  
  always @ (negedge clock or negedge reset_)  
    if (reset_==0)    count<=3'b0;  
    else if (up_dwn==2'b00||up_dwn==2'b11) count<=count;  
    else if (up_dwn==2'b01) count<=count+1;  
    else if (up_dwn==2'b10)  
      count<=count-1;  
endmodule
```

 




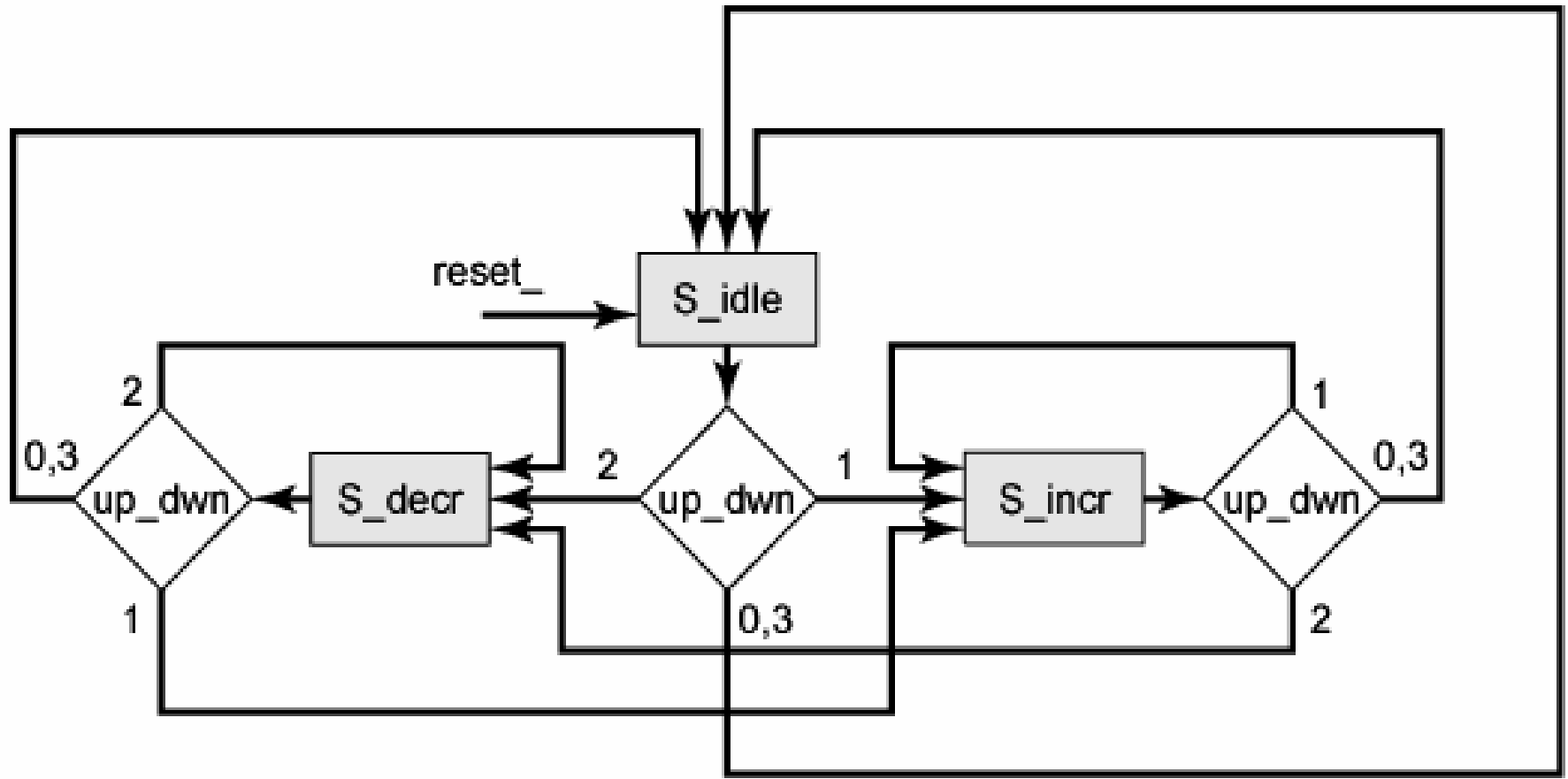ASM chart without conditional output boxes






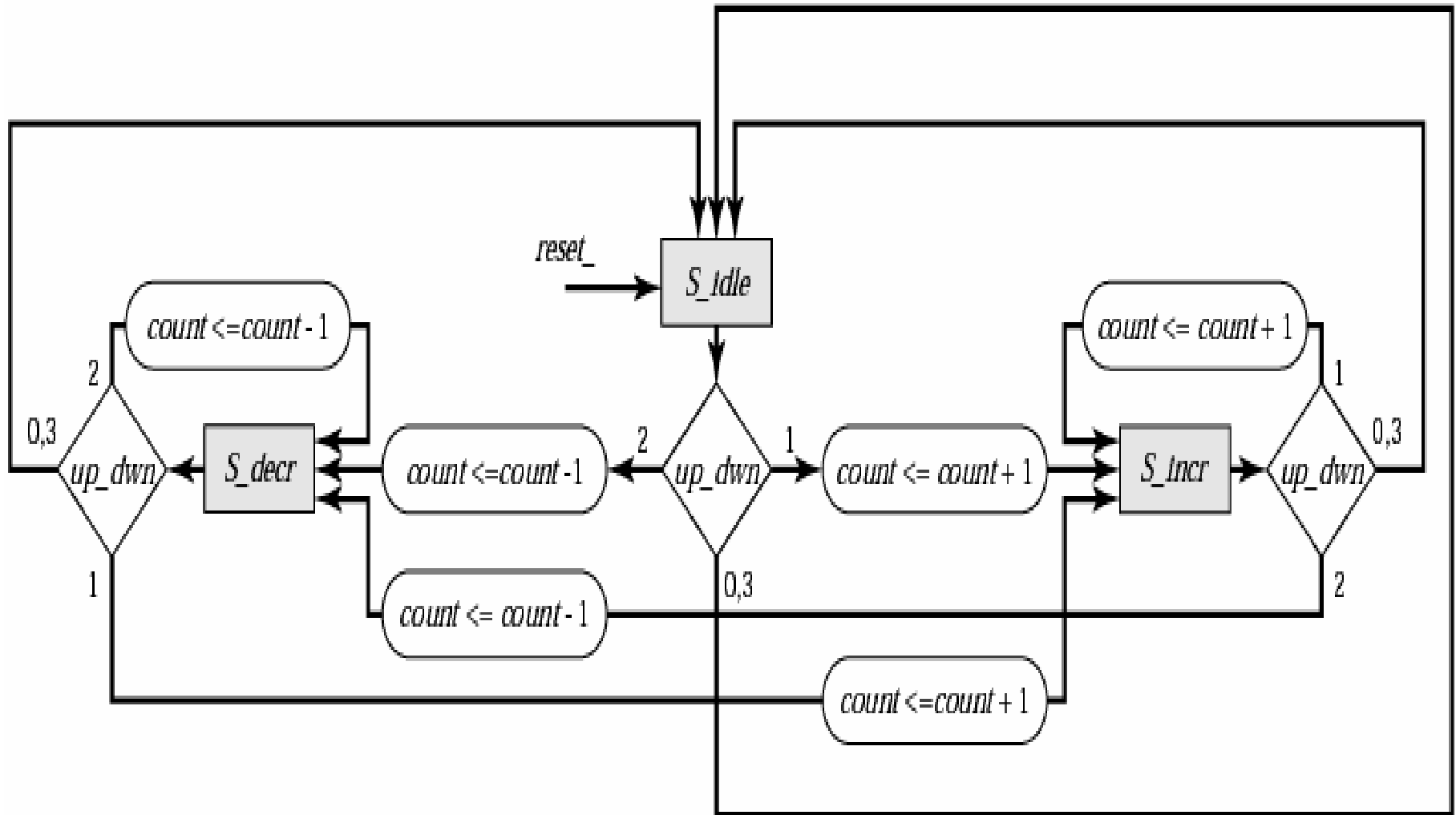ASM chart with conditional output boxes for register operations






 a simplified ASMD chart for a 4-bit binary counter with **asynchronous active-low reset**





a simplified ASMD chart for a 4-bit binary counter with **synchronous active-low reset**

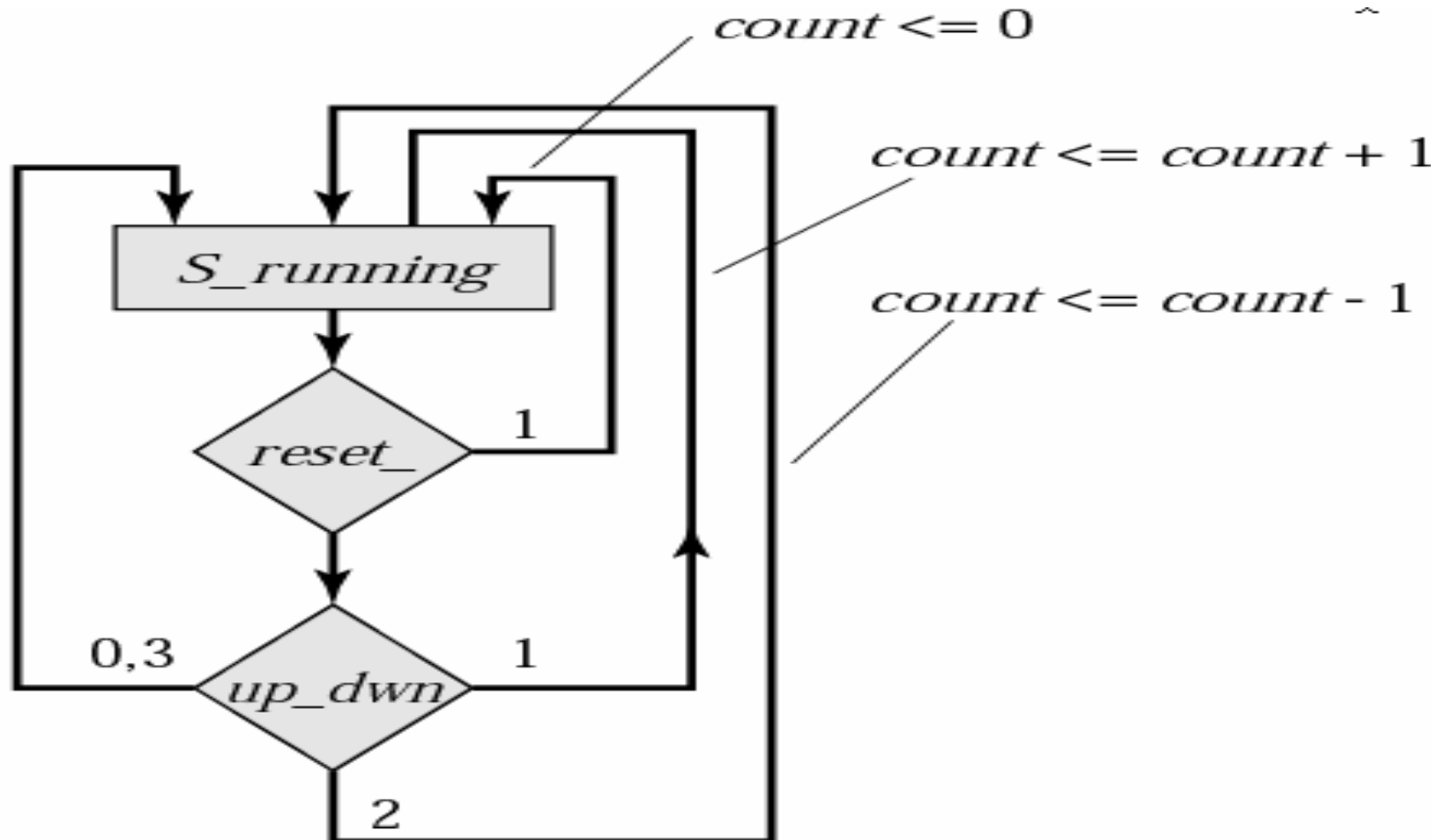




Example 5.41 a ring counter

```
module ring_counter (count, enable, clock, reset);  
  output    [7:0] count;  
  input      enable, reset, clock;  
  reg        [7:0] count;  
  always @ (posedge reset or posedge clock)  
    if (reset==1'b1) count<= 8'b0000_0001; else  
      if (enable==1'b1) count<={count[6:0],count[7]};  
      // concatenation operator  
endmodule
```




Data movement in a 8-bit ring counter

 



ring counter

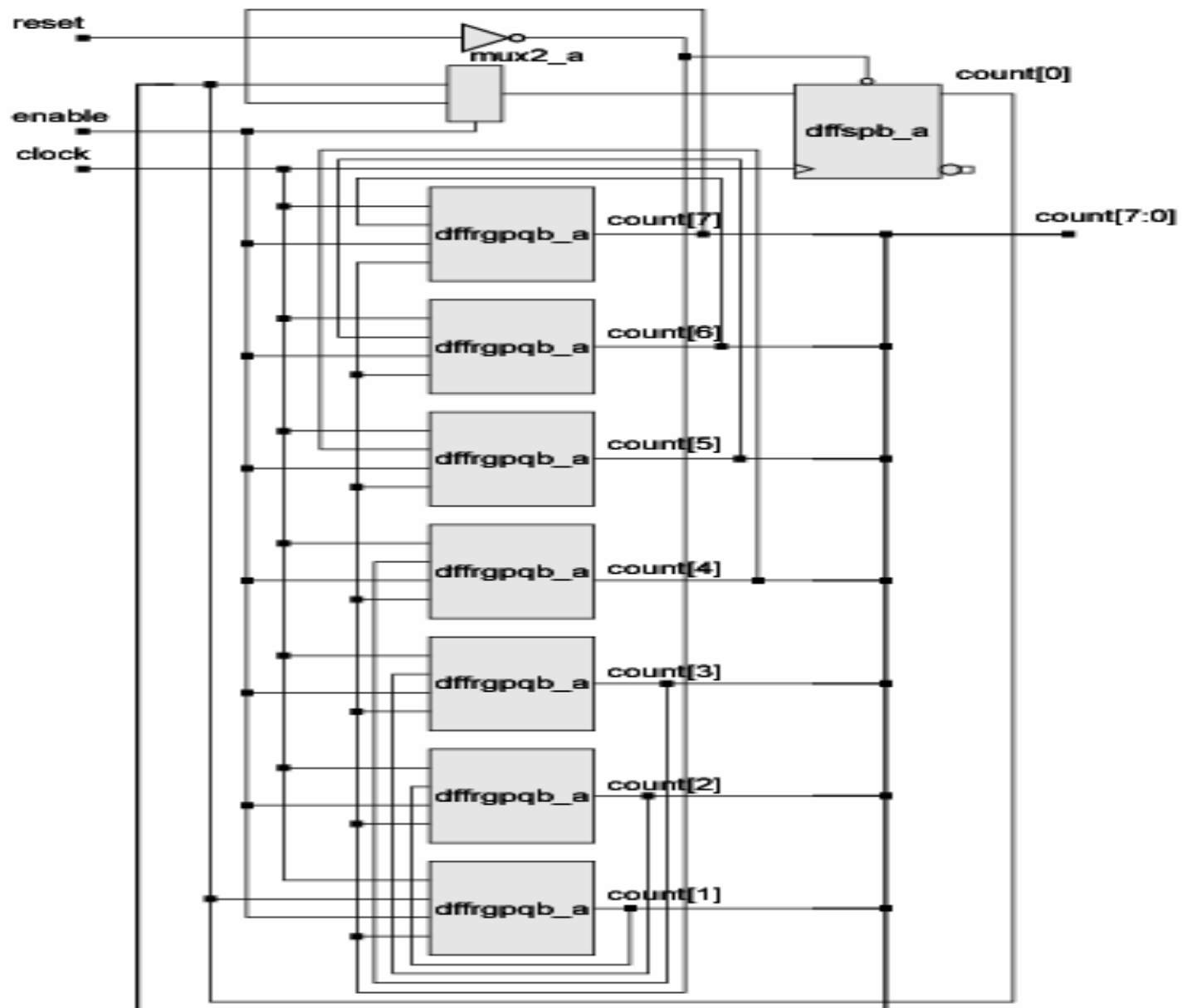



Example 5.42 3-bit up-down counter

```
module up_down_counter
  (Count,Data_in,load,count_up,counter_on,clk,reset);
  output [2:0] Count;
  input      load, count_up, count_on, clk, reset;
  input  [2:0] Data_in;
  reg    [2:0] Count;
  always @ (posedge reset or posedge clk)
    if (reset==1'b1) Count=3'b0;
    else if (load==1'b1) Count=Data_in;
    else if (counter_on==1'b1)
      begin
        if (counter_up==1'b1) Count=Count+1;
        else Count=Count-1;
      end
  endmodule
```



Features

- Two additional features:
- a signal, **counter_on**, which enables the counter
- a signal, **load**, which loads an initial count from an external datapath




3-bit up-down counter

```

module up_down_counter (Count, Data_in, load, count_up, counter_on, clk, reset);
    output [2: 0] Count;
    input load, count_up, counter_on, clk, reset;
    input [2: 0] Data_in;
    reg [2: 0] Count;


    always @ (posedge reset or posedge clk)
        if (reset == 1'b1) Count = 3'b0; else
            if (load == 1'b1) Count = Data_in; else
                if (counter_on == 1'b1) begin
                    if (count_up == 1'b1) Count = Count + 1;
                    else Count = Count - 1;
                end
    end
endmodule

```

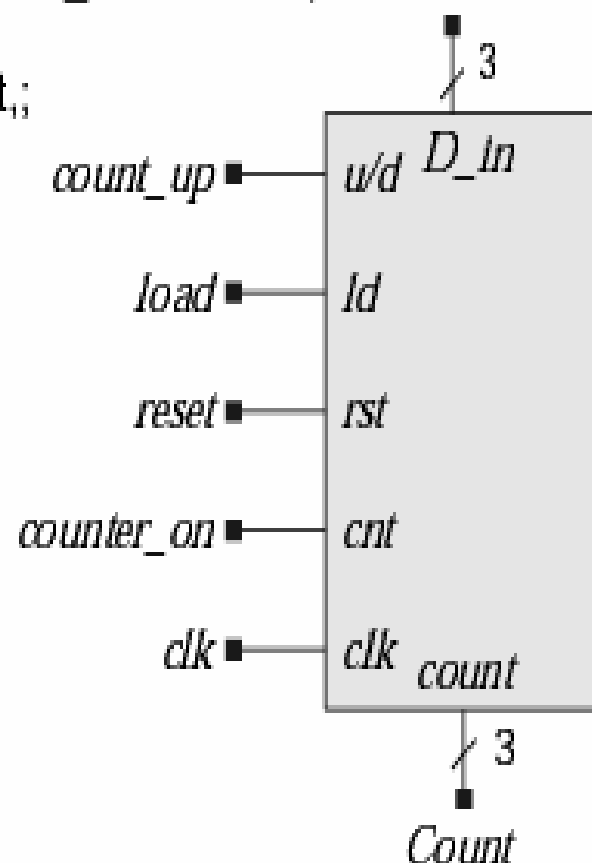



Synthesis circuit

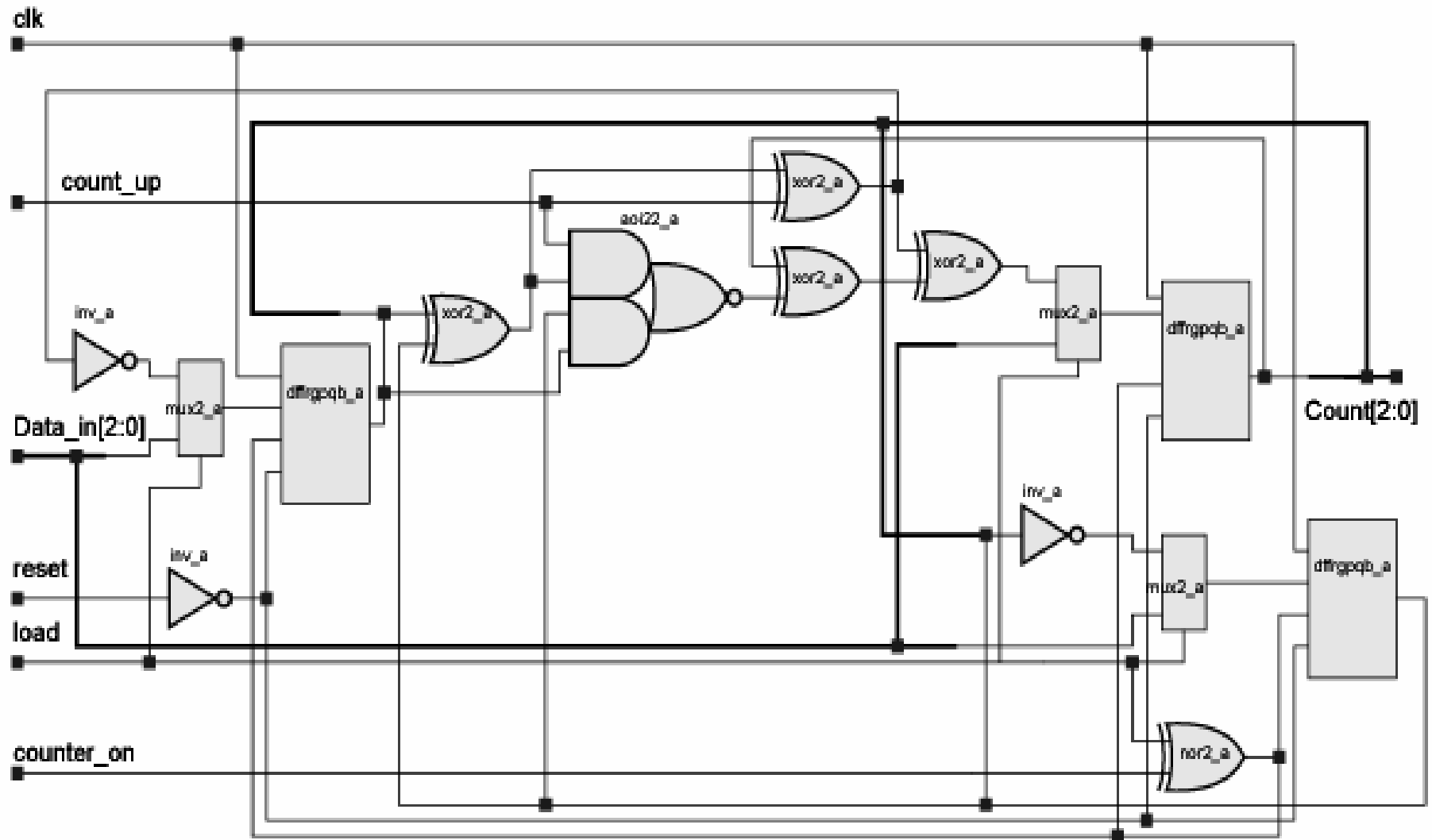




5.16.2 Shift Registers

- Example 5.43 an internal 4-bit register

```
module Shift_reg4 (Data_out,Data_in,clock,reset);  
  output    Data_out;  
  input     Data_in,clock,reset;  
  reg [3:0]  Data_reg;  
  assign    Data_out=Data_reg[0];  
  always @ (negedge reset or posedge clock)  
  begin  
    if (reset==1'b0)    Data_reg<=4'b0;  
    else  Data_reg <= {Data_in, Data_reg[3:1]};  
  end  
endmodule
```




synthesis circuit

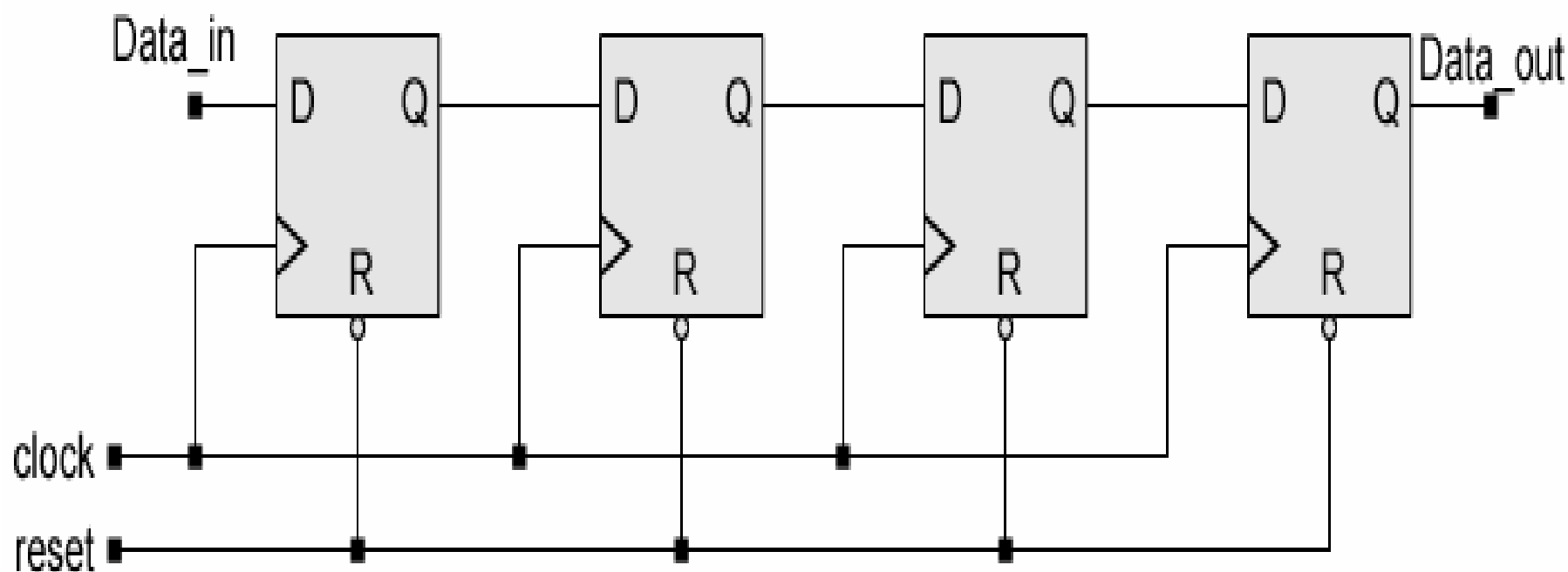




Example 5.44 a register with reset and parallel load

```
module Par_load_reg4 (Data_out,Data_in,load,clock,reset);  
  input [3:0] Data_in;  
  input      load, clock, reset;  
  output [3:0] Data_out;  // Port size  
  reg      Data_out;  // Data type  
  always @ (posedge reset or posedge clock)  
  begin  
    if (reset==1'b1) Data_out<=4'b0;  
    else if (load==1'b1) Data_out<=Data_in;  
  end  
endmodule
```



synthesis circuit

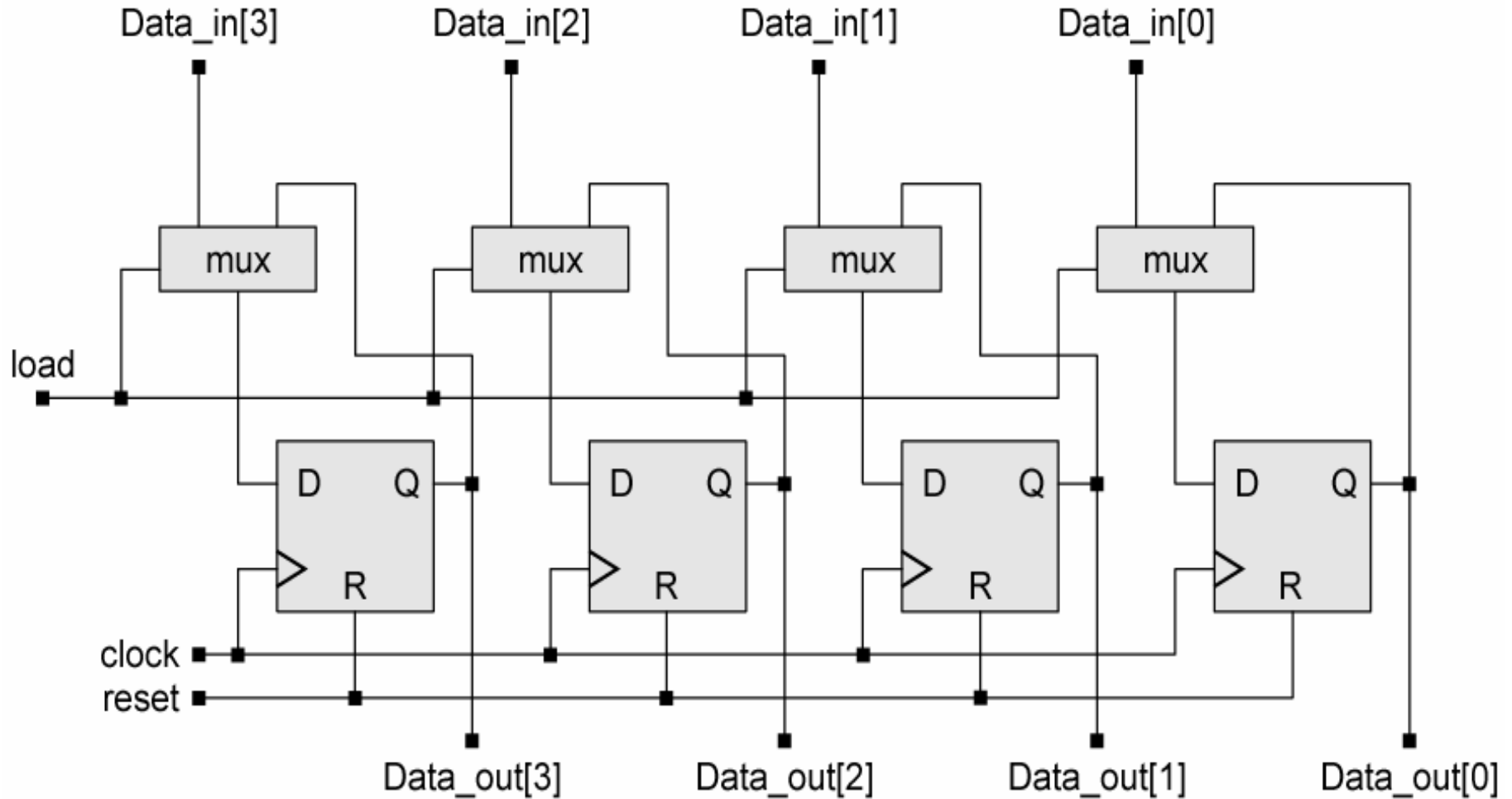




Example 5.45 barrel shifter

- Shifting a word to the right divides the word by 2; shifting a word to the left multiplies the word by 2

```
module barrel_shifter (Data_out,Data_in,load,clock,reset);  
  output [7:0] Data_out;  
  input   [7:0] Data_in;  
  input    load,clock,reset;  
  reg     [7:0] Data_out;  
  always @ (posedge reset or posedge clock)  
  begin  
    if (reset==1'b1) Data_out<=8'b0;  
    else if (load==1'b1) Data_out<=Data_in;  
    else Data_out<={Data_out[6:0],Data_out[7]};  
  end  
endmodule
```




Data movement

 




synthesis circuit

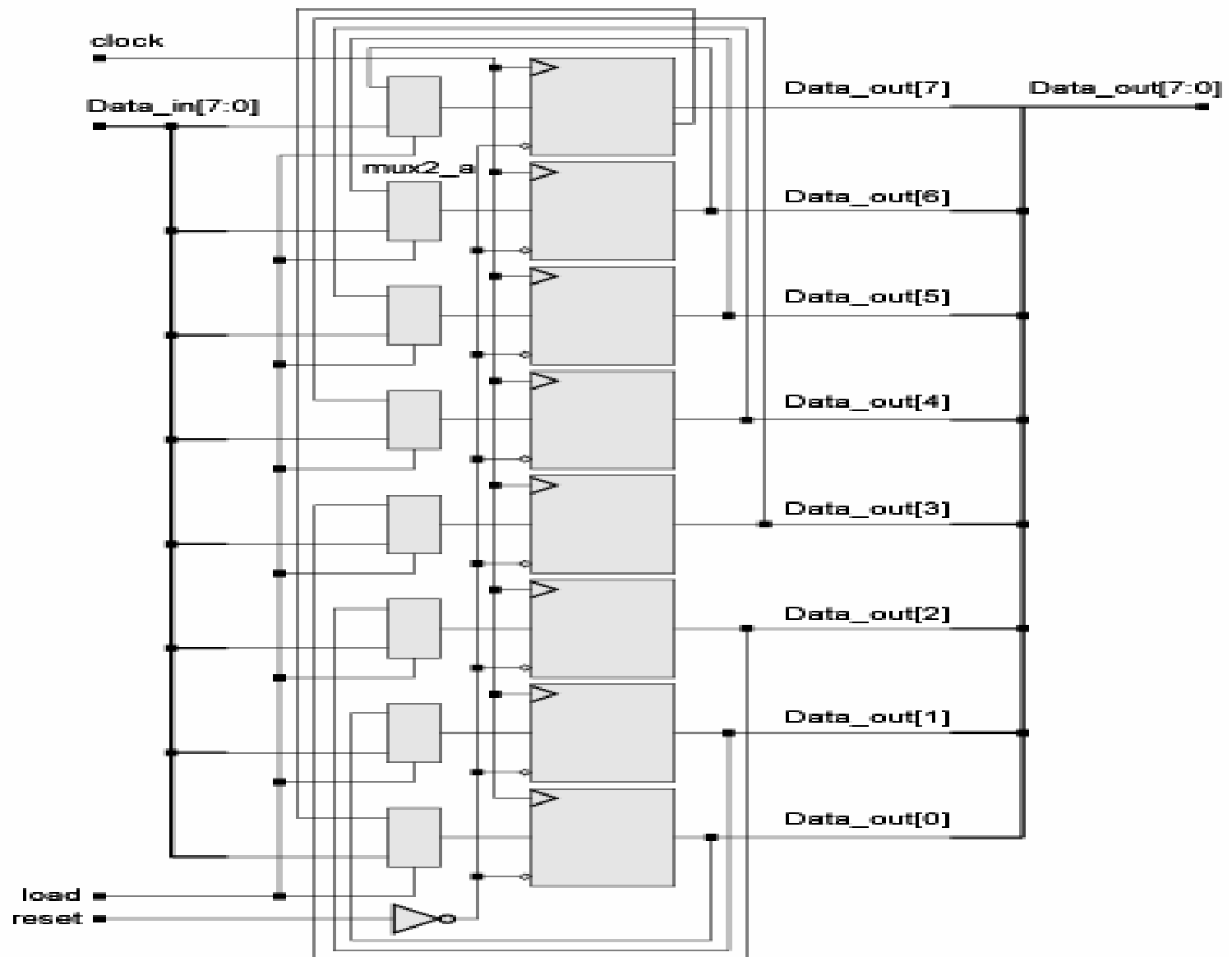



Example 5.46

a 4-bit universal shift register

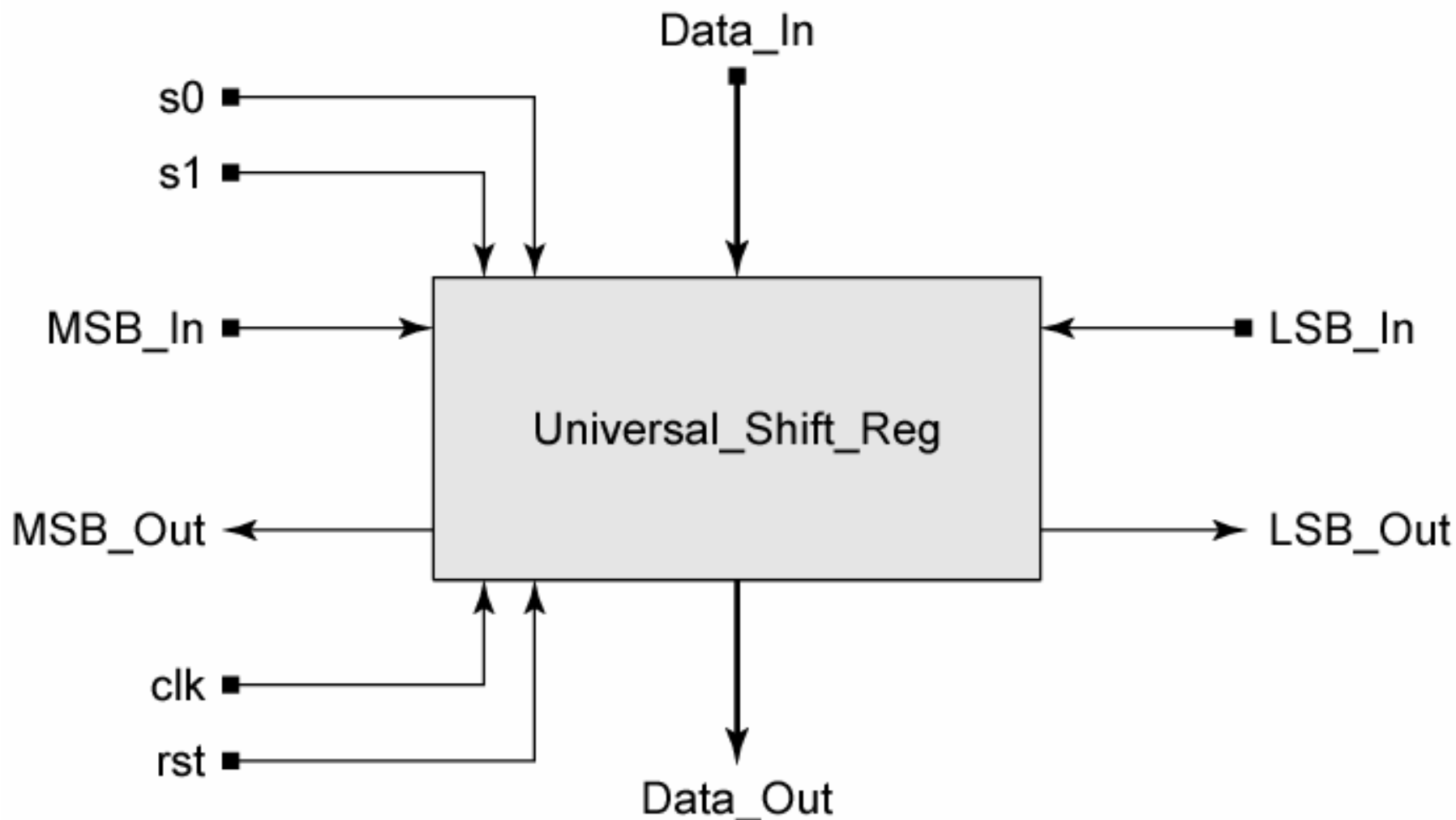




Ex 5.46 a 4-bit universal shift register

```
module Universal_Shift_Reg
    (Data_Out, MSB_Out, LSB_Out, Data_In, MSB_In, LSB_In, s1, s0, clk, rst);
    output [3:0] Data_Out;
    output      MSB_Out, LSB_Out;
    input      [3:0] Data_In;
    input      MSB_In, LSB_In;
    input      s1, s0, clk, rst;
    reg       Data_Out;
    assign MSB_Out=Data_Out[3];
    assign LSB_Out=Data_Out[0];
    always @ (posedge clk) begin
        if (rst) Data_Out<=0;
        else case ({s1,s0})
            0: Data_Out<=Data_Out;      // Hold
            1: Data_Out<={MSB_In,Data_Out[3:1]};
                // Serial shift from MSB
            2: Data_Out<={Data_Out[2:1],LSB_In};
                // Serial shift from LSB
            3: Data_Out<=Data_In; // Parallel Load
        endcase
    end
endmodule
```




Simulation result

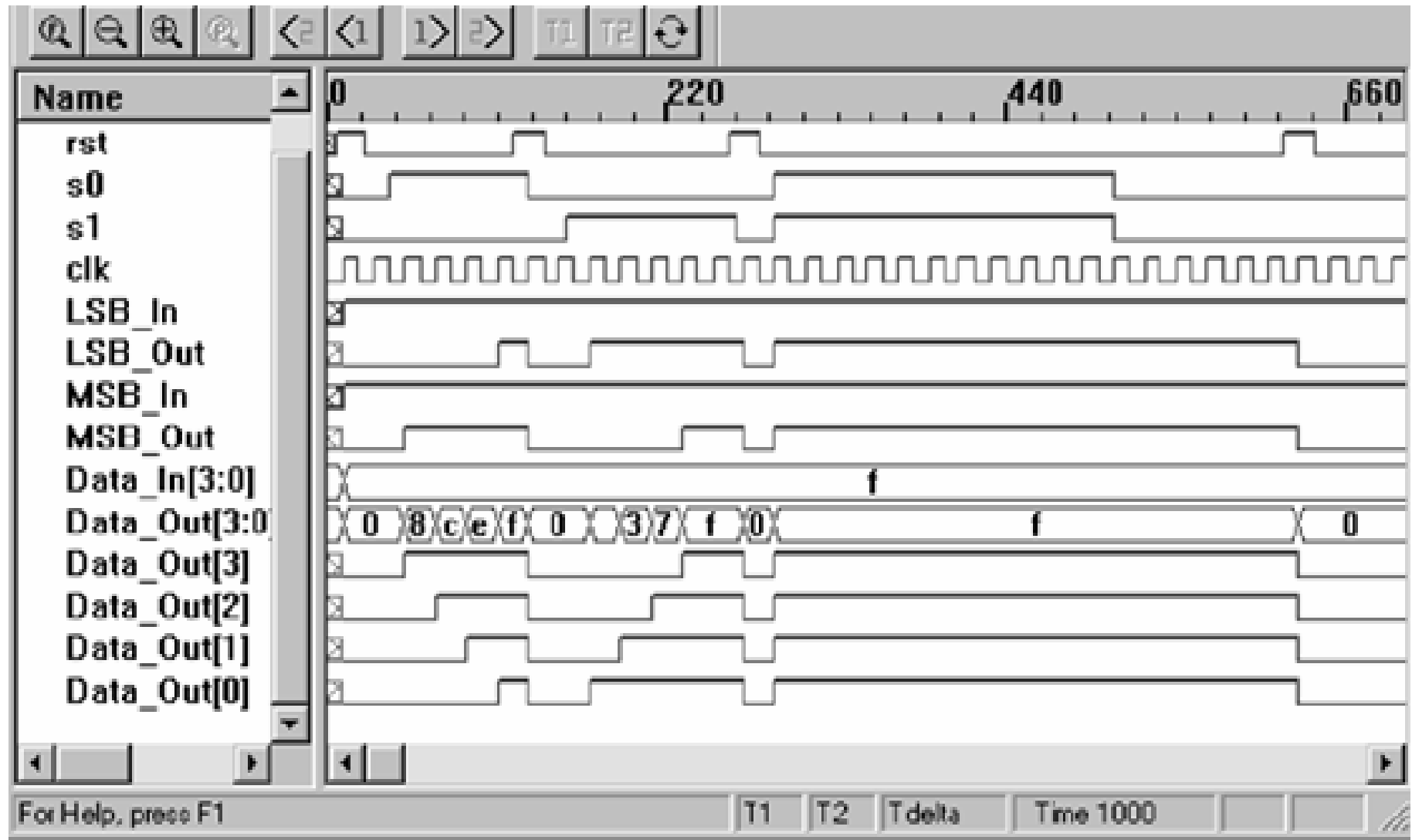




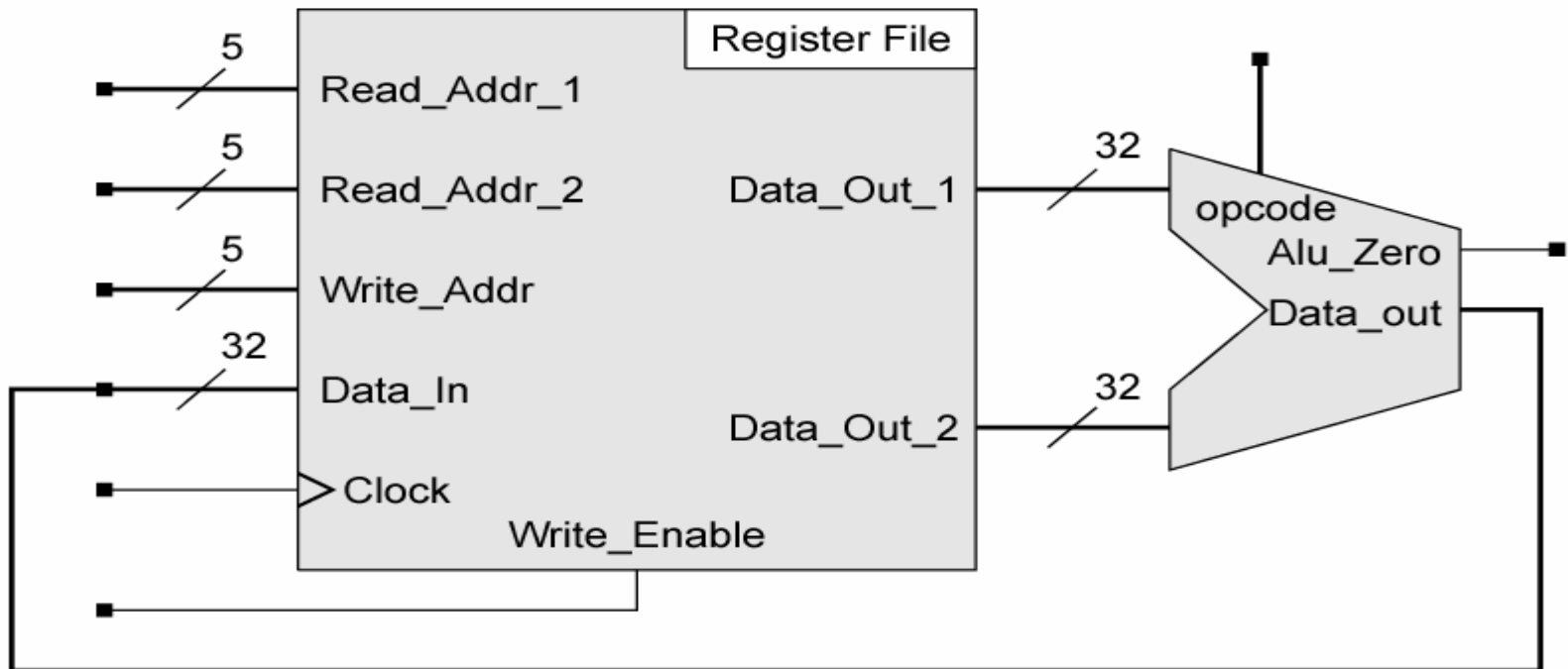5.16.3 Register Files and Arrays of Registers (Memories)

- A register file **consists of a small number of registers** and is integrated with additional logic
- Usually **implemented by D-type flip-flops**, register files are **not used for mass storage** because they occupy significantly more silicon area than compiled memory
- A common application combines a register file **in tandem with an arithmetic and logic unit (ALU)**, as shown in Figure 5-34



A register file in tandem with an Arithmetic and Logic Unit (ALU)





A register file in tandem with an ALU

- The dual-channel outputs of the register file form the datapaths to the ALU, and the output of the ALU is stored in the register file at a designated location
- A host processor provides the addresses for the operations and controls the sequence of reading and writing to prevent a simultaneous read and write affecting the same location



Ex 5.47 single-input, dual-output register file

```
module Register_File (Data_Out_1, Data_Out_2, Data_in,  
    Read_Addr_1, Read_Addr_2, Write_Addr, Write_Enable, Clock);  
    output [31:0] Data_Out_1, Data_Out_2;  
    input  [31:0] Data_in;  
    input  [4:0] Read_Addr_1, Read_Addr_2, Write_Addr;  
    input    Write_Enable, Clock;  
    reg [31:0] Reg_File [31:0]; // 32bit×32 word memory declaration  
    assign Data_Out_1=Reg_File[Read_Addr_1];  
    assign Data_Out_2=Reg_File[Read_Addr_2];  
    always @ (posedge Clock)  
    begin  
        if (Write_Enable) Reg_File [Write_Addr]<=Data_in;  
    end  
endmodule
```



5.17 Switch Debounce, Metastability, and Synchronizers for Asynchronous Signals

- A hardware latch may enter the metastable
 1. if a pulse at one of its inputs is too short
 2. if both inputs are asserted either simultaneously or within a sufficiently small interval of each other
 3. If the data are unstable around the edge of the enable input



A D-type Flip-Flop may enter metastable

A DFF is metastable:


- if the data are unstable in the setup interval preceding **the clock edge**
- if the clock pulse is **too narrow**

A signal is asynchronous:

- If it is **not controlled by a clock**
- If it is synchronized by **a clock in a different domain**
- In both cases, a signal transition can occur in a random manner with respect to the active edge of the clock that is controlling sequential devices



 An illustration of how metastability can happen in a physical system






Switch bounce

- If a mechanical switch generates an input that drives a DFF, **the input signal could oscillate during the setup interval and enter a metastable state**
- **The mechanical contact will vibrate momentarily, for a few milliseconds, creating an unstable signal on the line**
- There are various ways to deal with switch bounce, **depending on the application**
- For example, the push button switches have a **resistor-capacitor (RC) lowpass filter** and a **buffer** placed between the switch and the chip




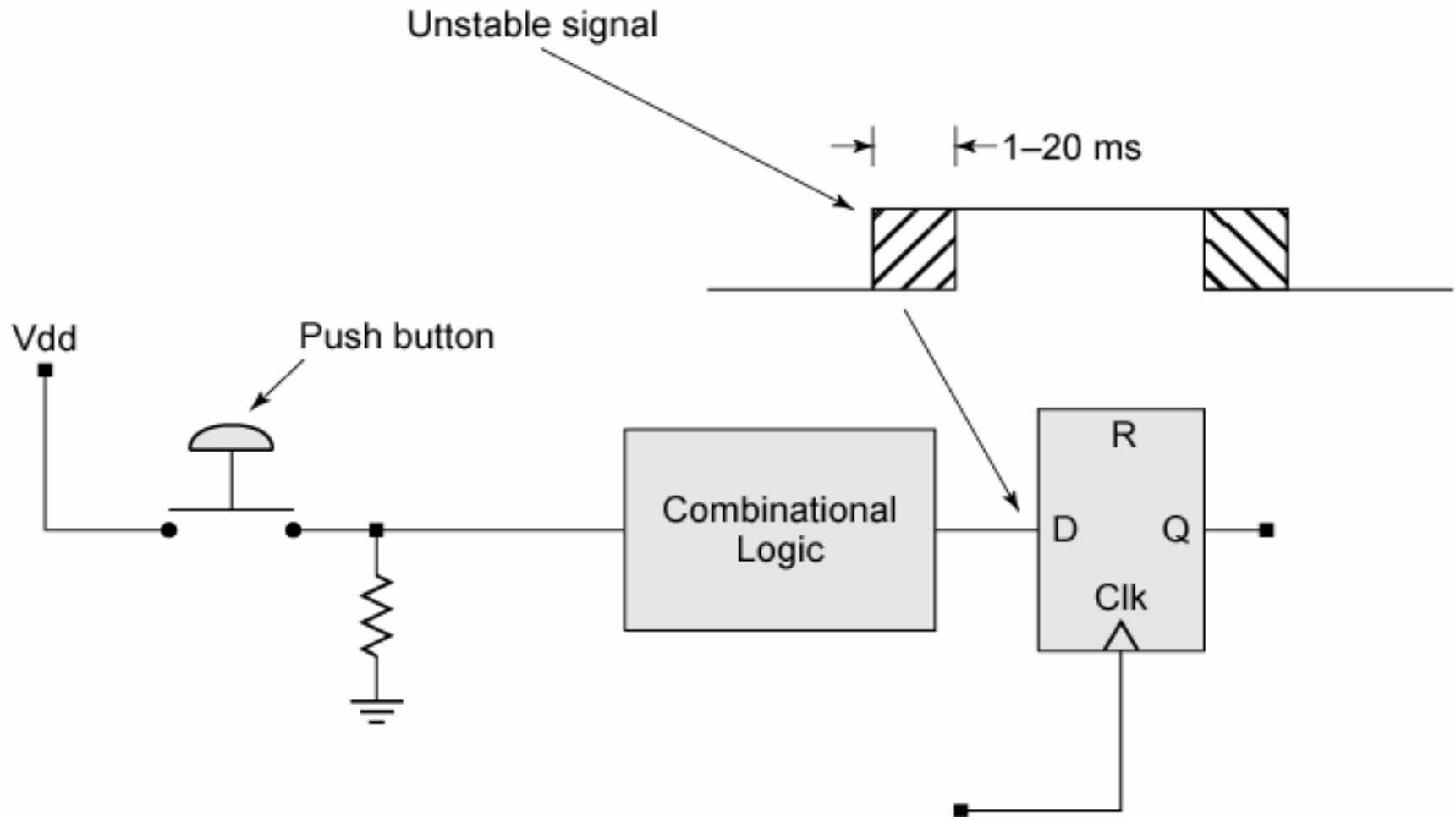a push-button input device with closure bounce





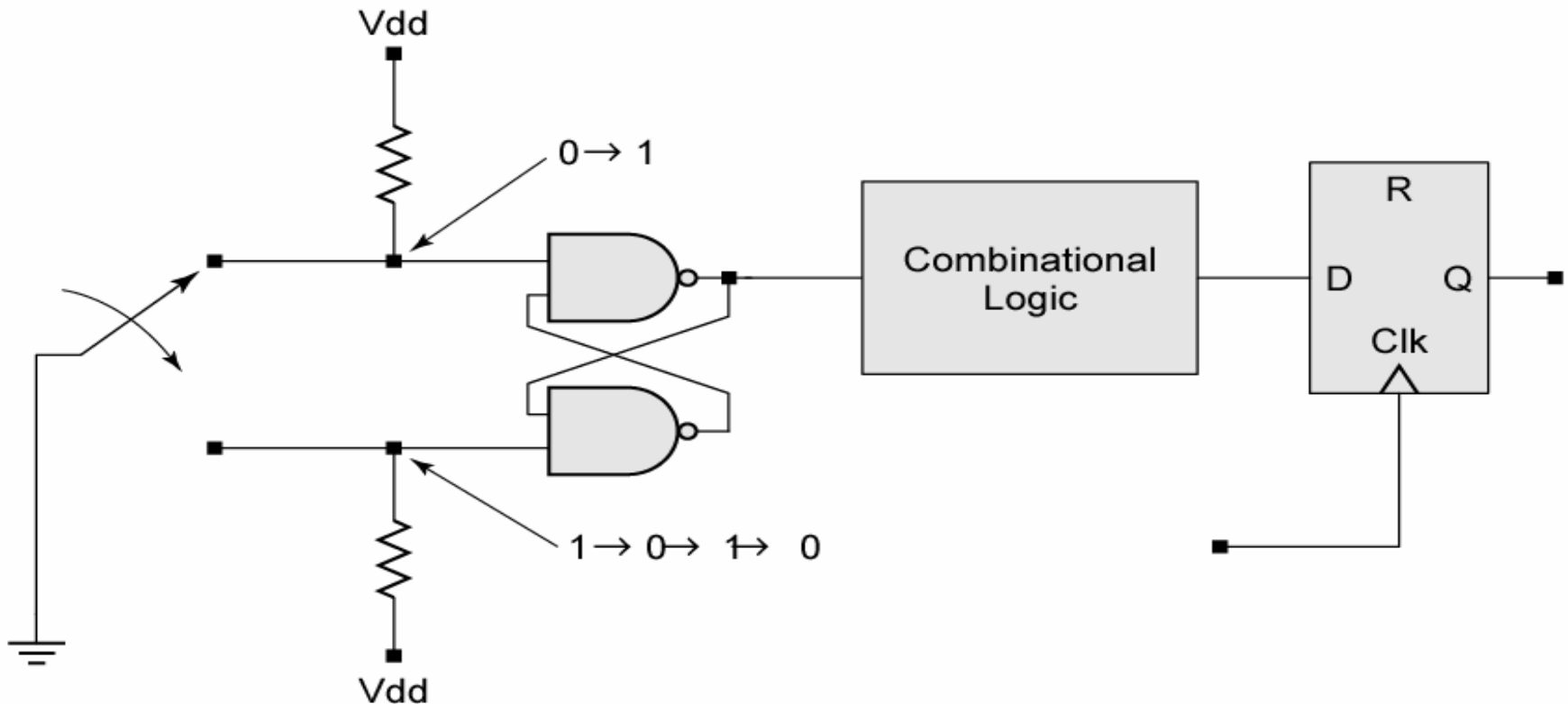A NAND latch configuration for eliminating the effects of switch closure bounce (a single pole-double throw switch)






Metastability

- **It cannot be prevented** ,Its effect can be reduced
- The mean time between failures with an asynchronous input is exponentially related to the length of time available for recovery from the metastable condition
- High-speed digital circuits **rely on synchronizers to create a time buffer** for recovering from a metastable event
- **First rule is that an asynchronous signal should never be synchronized by more than one synchronizer**




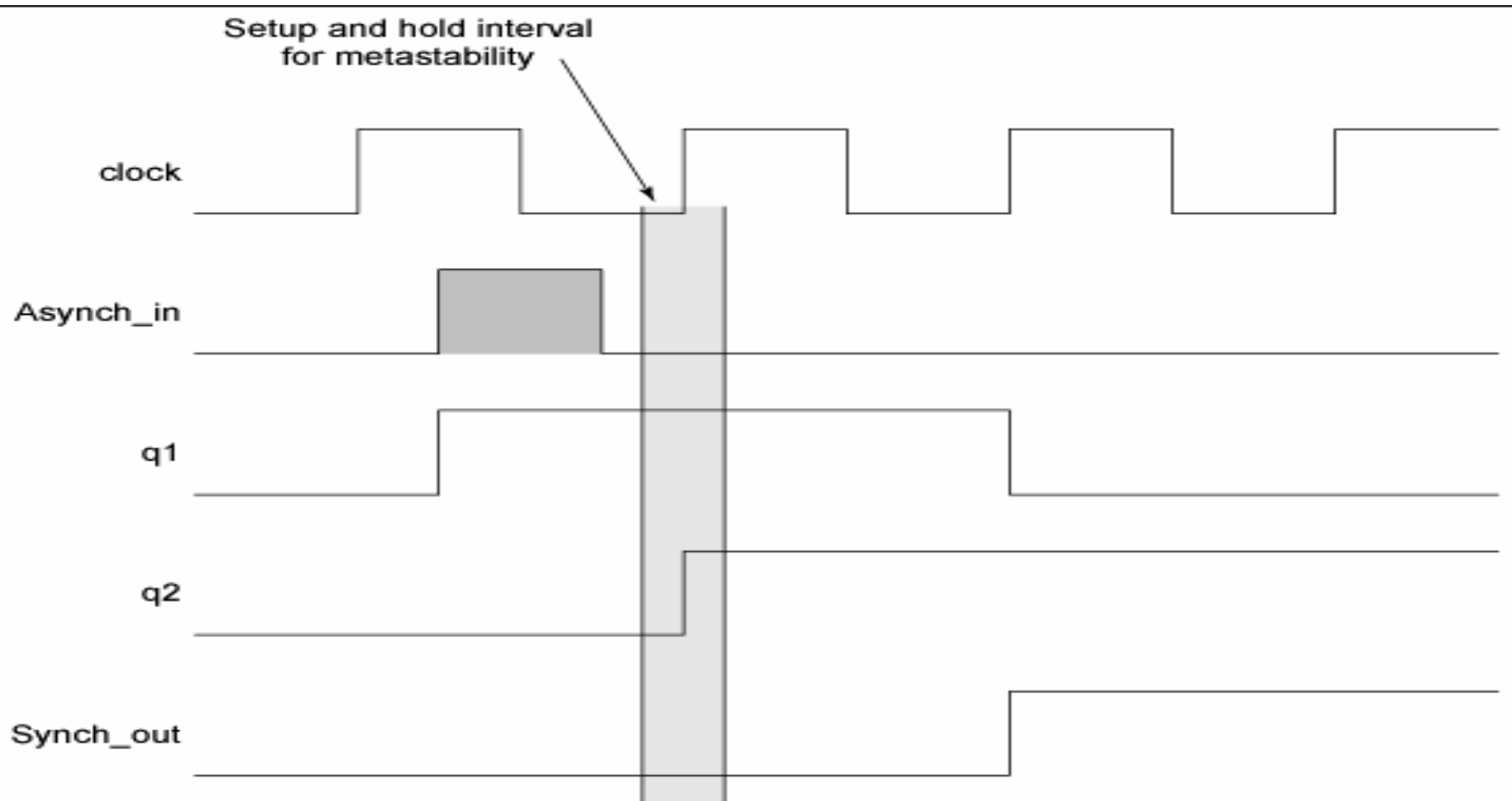waveforms in the circuit of the asynchronous pulse does not cause a metastable condition





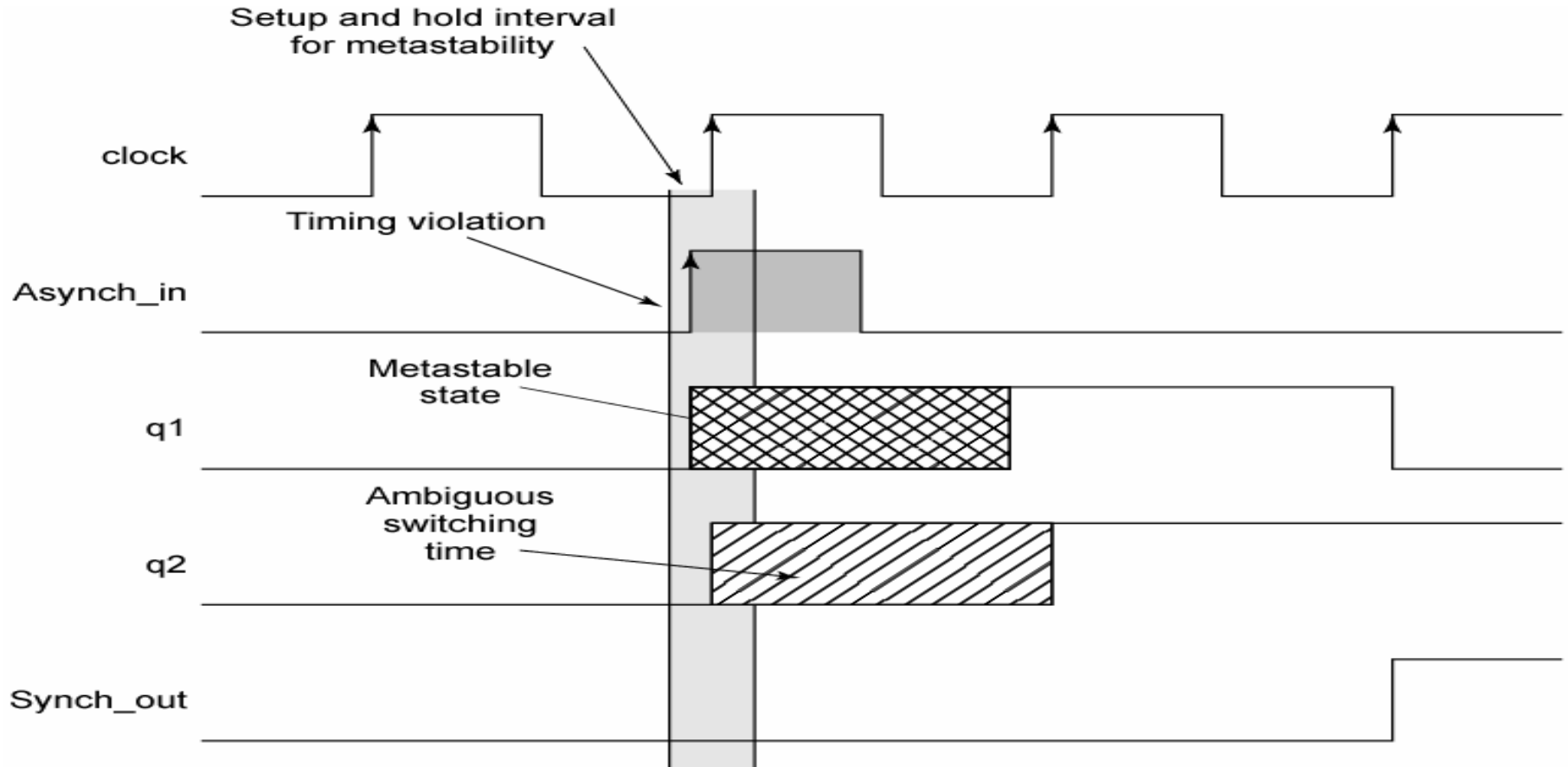waveforms of the circuit in when the asynchronous input signal causes a metastable condition






Two basic types of synchronizers

- There are two basic types of synchronizer circuits
- Depending on whether the asynchronous input pulse has a width that is larger or smaller than the period of the clock



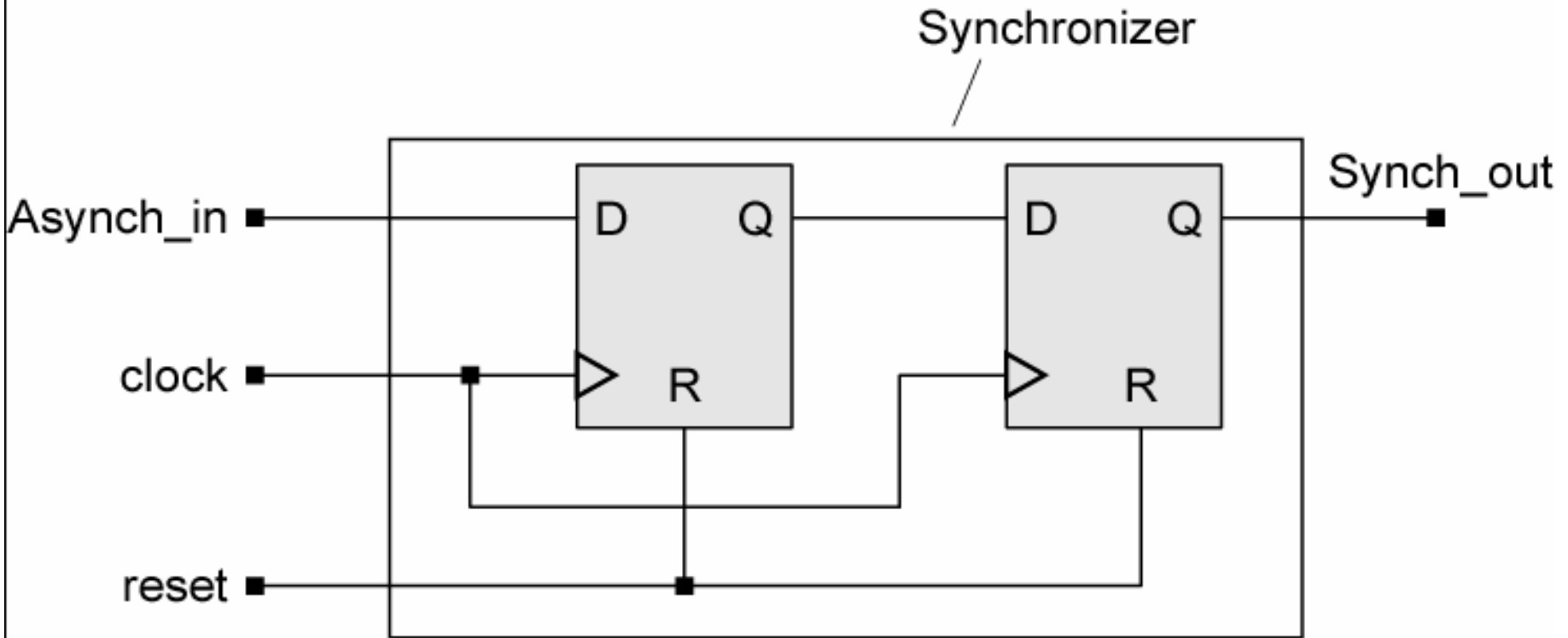The width of the asynchronous input pulse is greater than the period of the clock






The width of the asynchronous input pulse is greater than the period of the clock

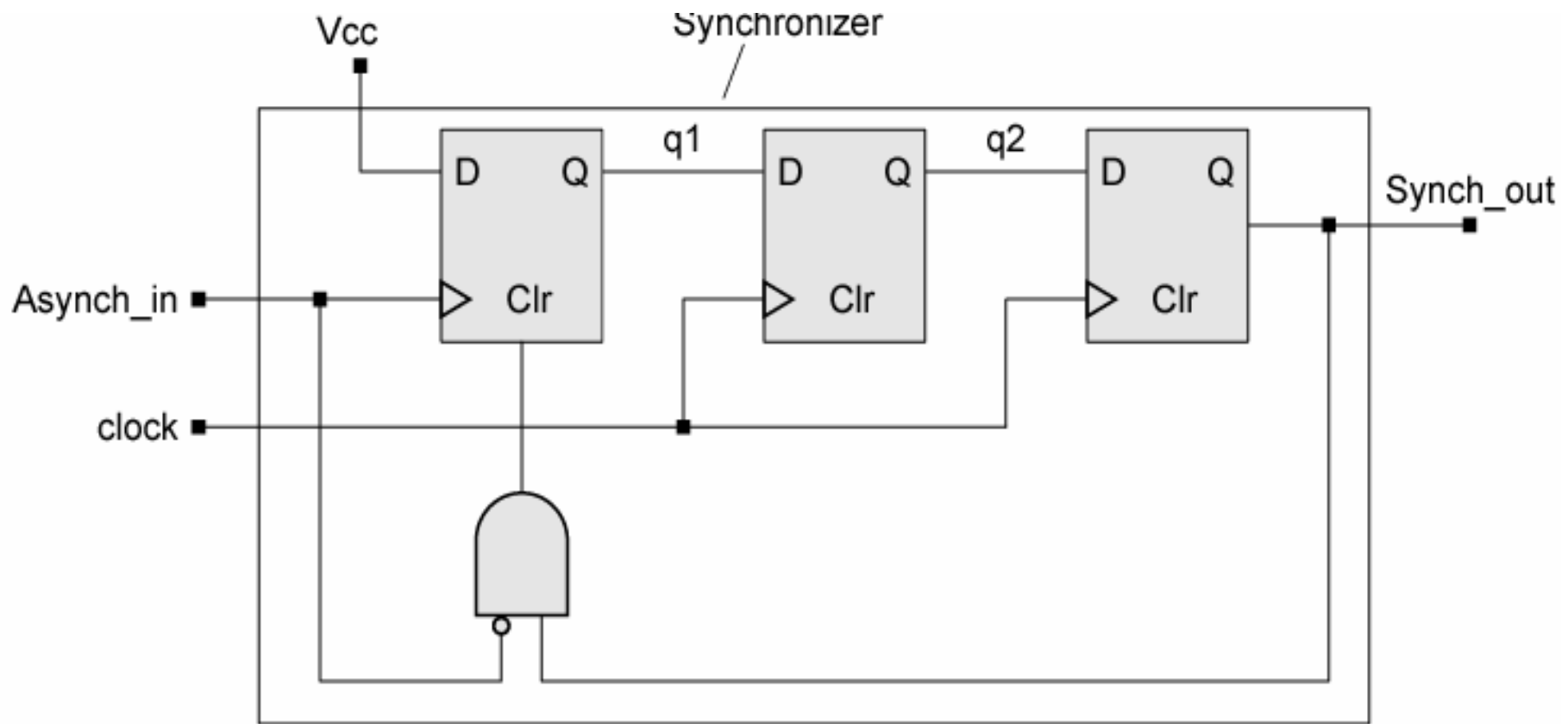- 1、 if the asynchronous input signal reaches a **stable condition** outside the setup interval, it will be clocked through with a latency of two cycles
- 2、 if Asynch_in **is unstable during the setup interval** (due to bounce or to a late-arriving input) there are **two possibilities**
- If the **unstable input is sampled as a 0**, but ultimately **settles to a 1**, the 1 will appear at the output with a latency of three cycles
- If the signal **settles to 0**, it will have arrived with a latency of two cycles



The width of the asynchronous input pulse is less than the period of the clock






The width of the asynchronous input pulse is less than the period of the clock

- The first flip-flop has V_{cc} connected to its data input and has $Asynch_in$ connected to its clock input
- A short pulse at $Asynch_in$ will drive $q1$ to 1; this value will propagate to $Synch_out$ after the next two clock edges
- When $Synch_out$ becomes 1, the signal at Clr is asserted, assuming that $Asynch_in$ returns to 0 before $Synch_out$ becomes 1
- The flip-flop driving $q2$ guards against metastability in the first stage of the chain




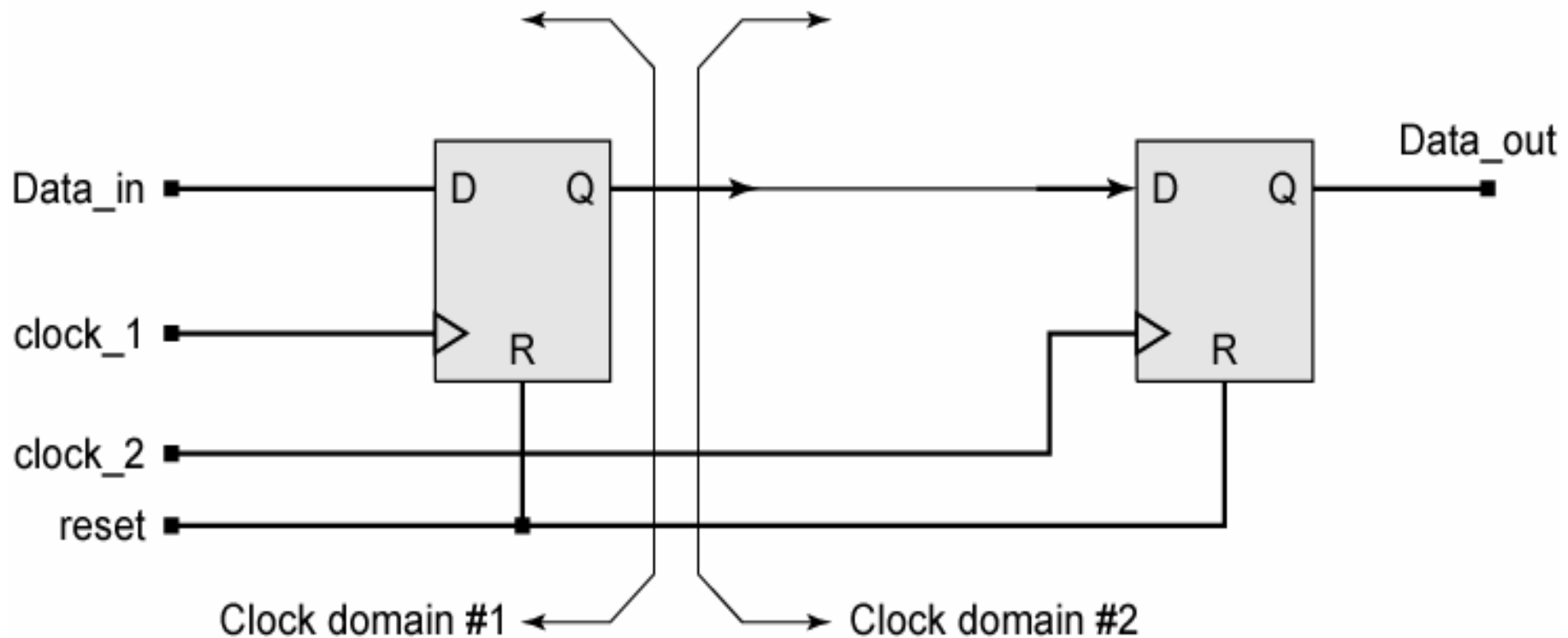Synchronizers are also used when a signal must cross a boundary between two clock domains





Clock domain interface

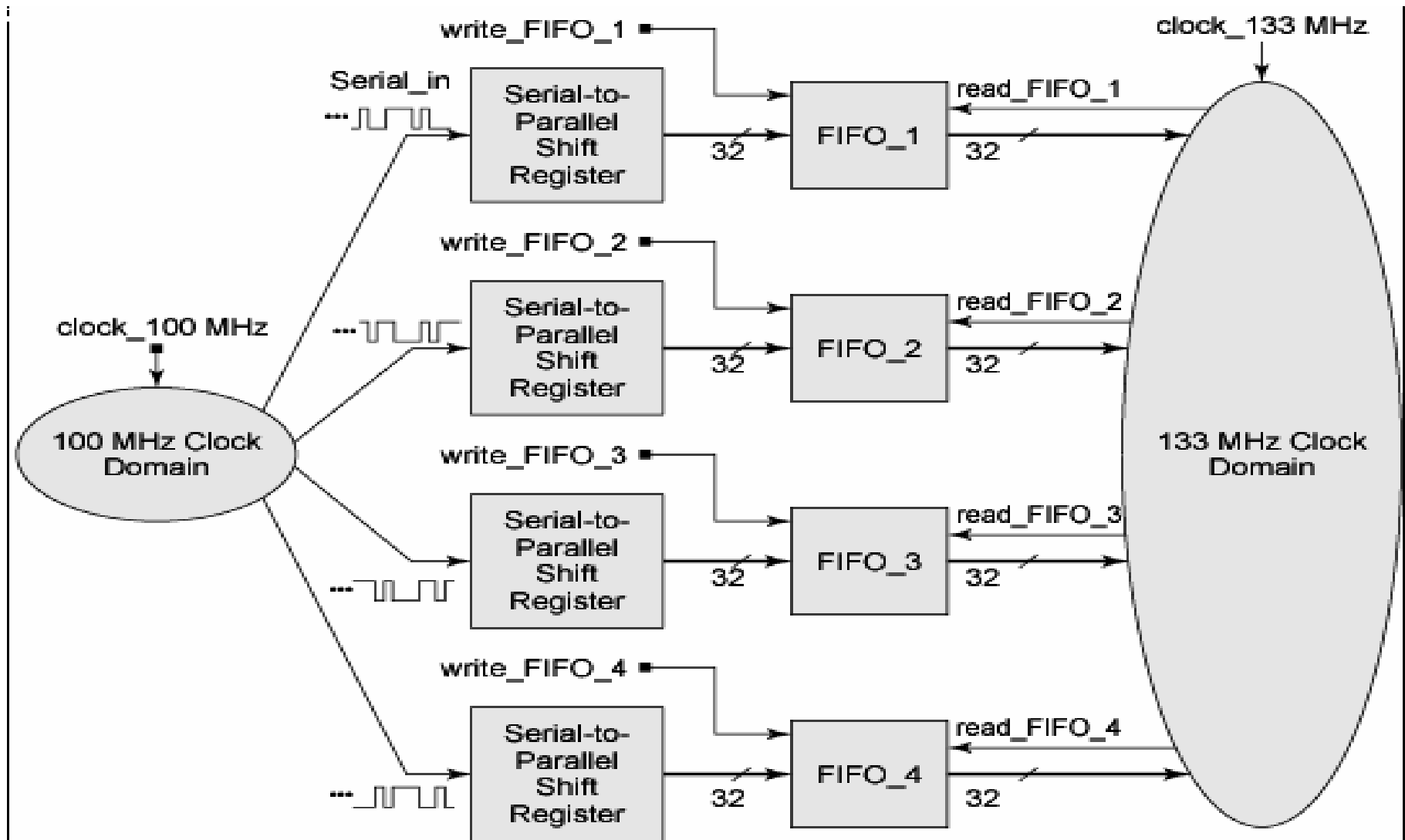




5.18 design Example: keypad Scanner and Encoder

- Keypad scanners are used to enter data manually in digital telephones, computer keyboards and other digital systems
- **A keypad scanner responds to a pressed key and forms a code that uniquely identifies the key that is pressed**
- Must take into account the asynchronous nature of the inputs and deal with switch debounce



Scanner/encoder for a hexadecimal keypad

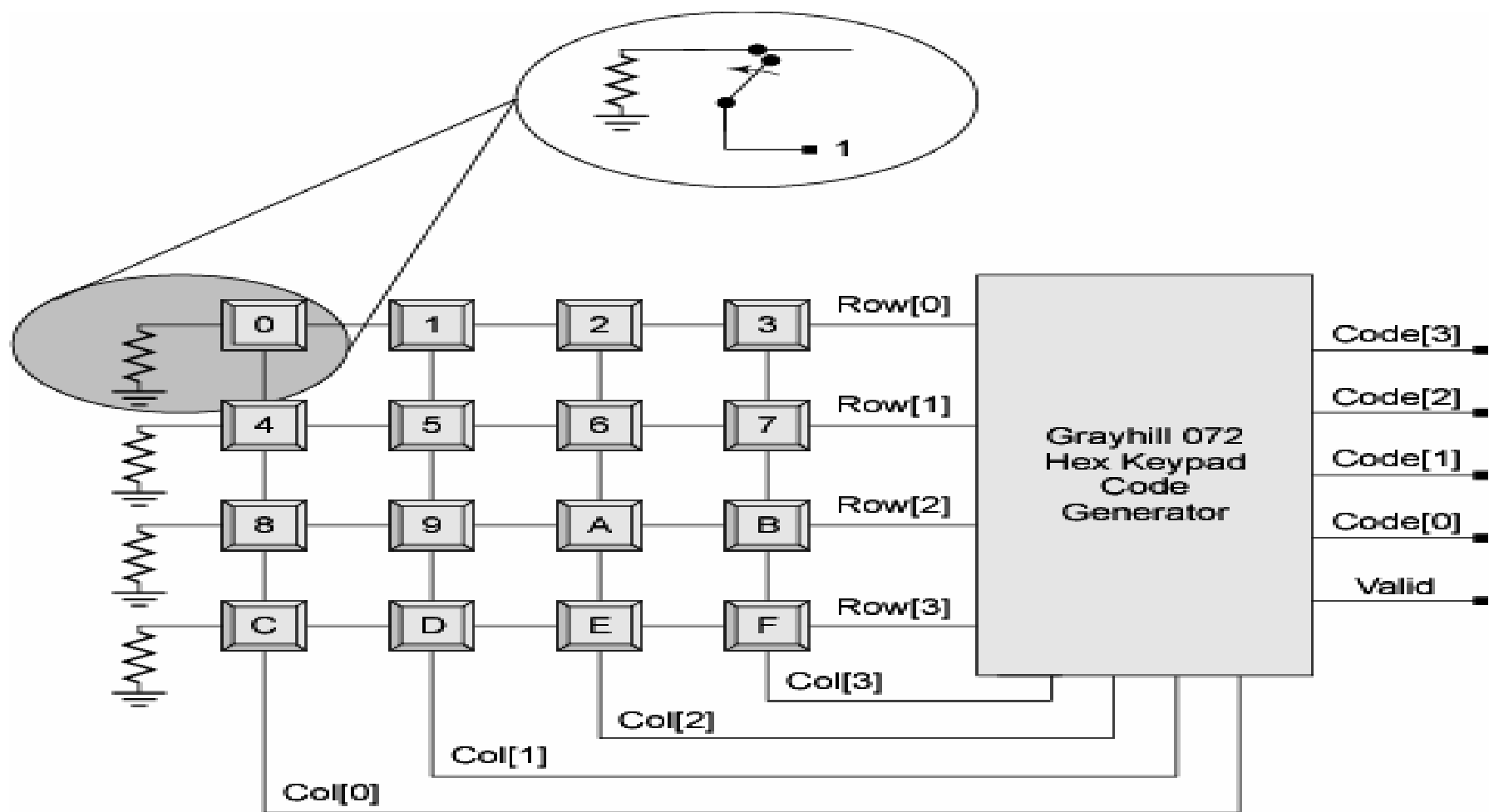



A keypad code generator

- A keypad code generator must implement a decoding scheme
- Detects whether a button is pressed
- Identifies the button that is pressed
- Generates an output consisting of the unique code of the button






Keypad codes for a hexadecimal scanner

Key	Row[3:0]	Col[3:0]	Code
0	0001	0001	0000
1	0001	0010	0001
2	0001	0100	0010
3	0001	1000	0011
4	0010	0001	0100
5	0010	0010	0101
6	0010	0100	0110
7	0010	1000	0111
8	0100	0001	1000
9	0100	0010	1001
A	0100	0100	1010
B	0100	1000	1011
C	1000	0001	1100
D	1000	0010	1101
E	1000	0100	1110
F	1000	1000	1111



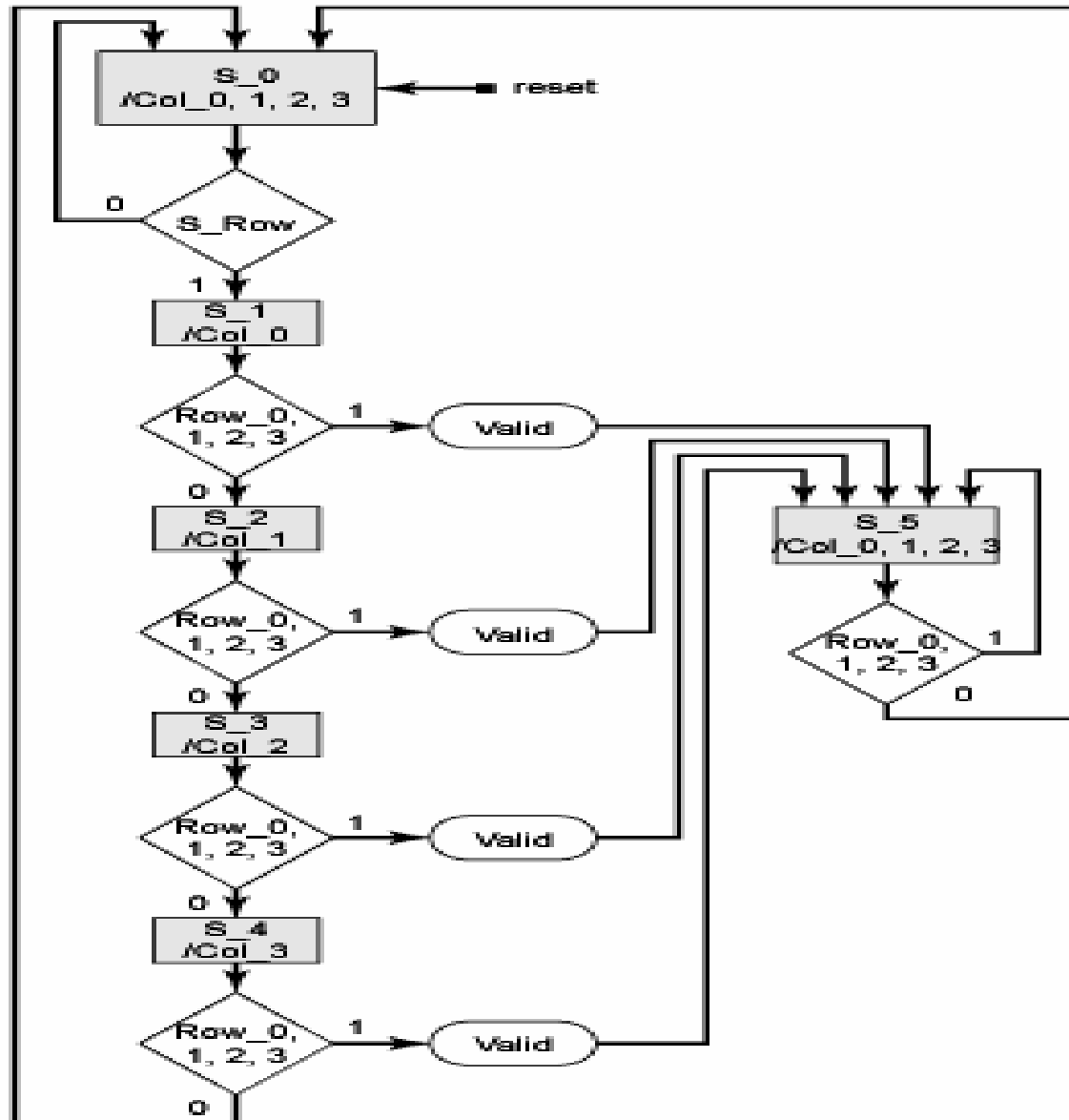The behavior of the keypad scanner/encoder



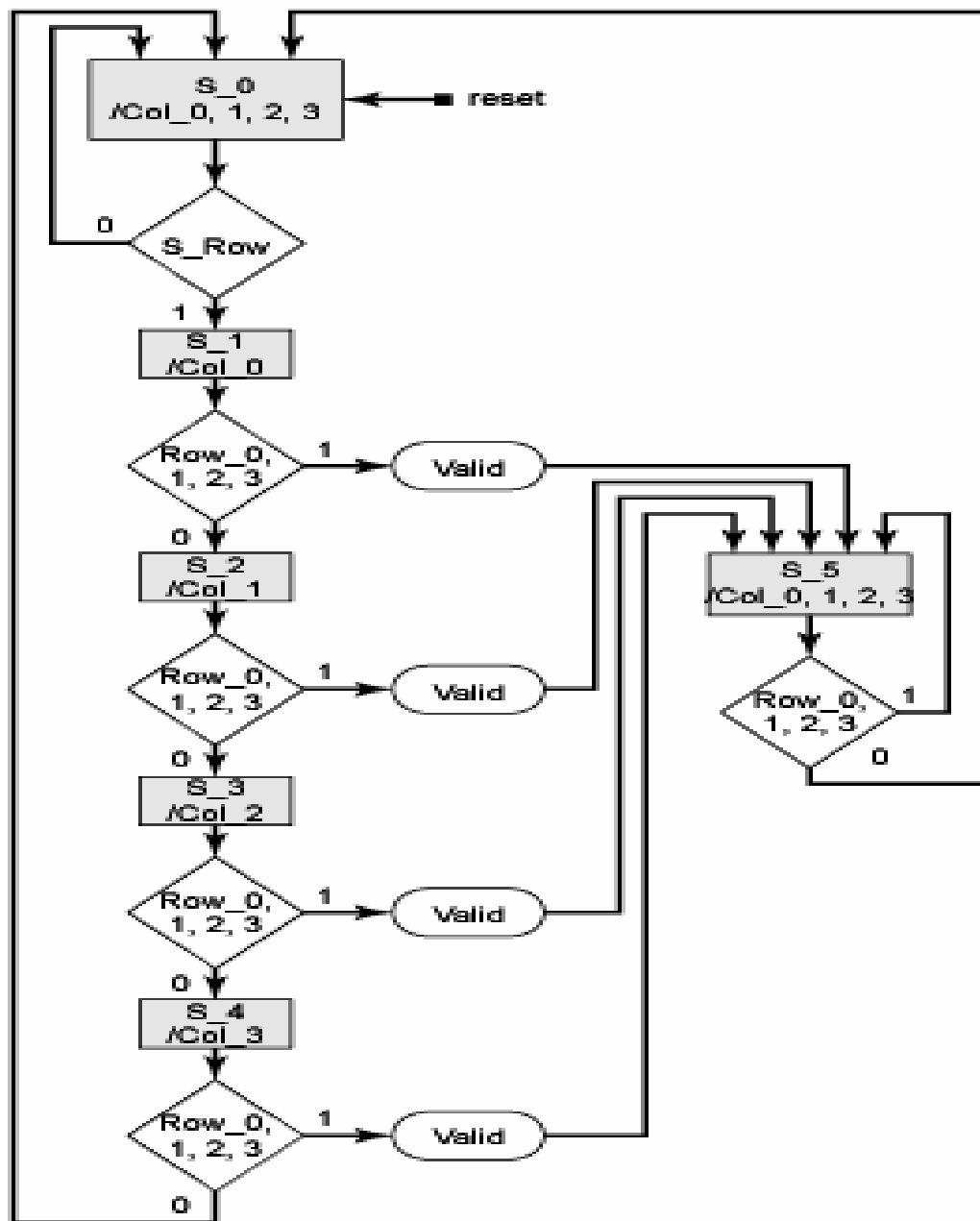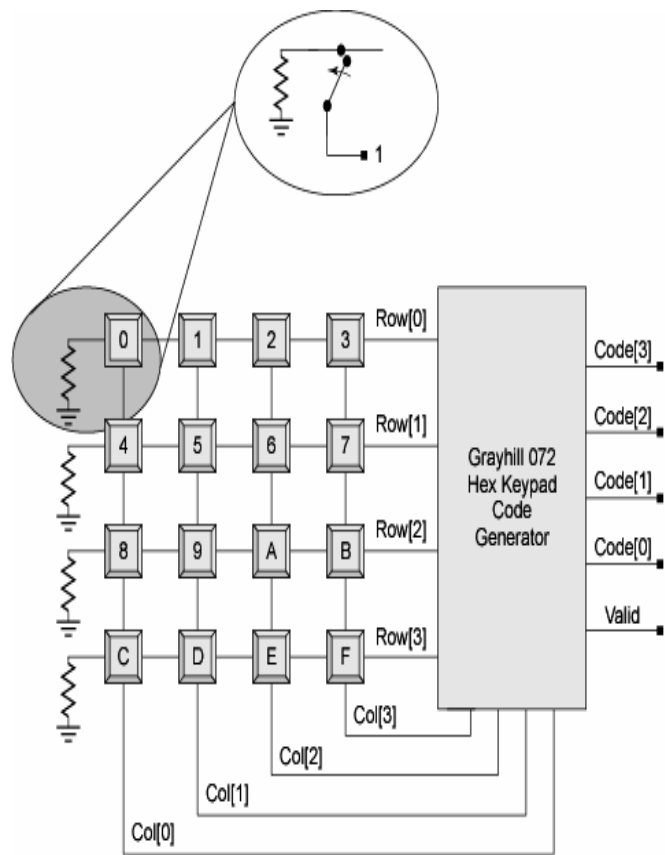




The behavior of the keypad scanner/encoder

- state **S_0**, with all column lines asserted, until one row line or more is asserted
- In **S_1** only column 0 is asserted
- If a row is also asserted the output Valid is asserted for one clock and the machine moves to **S_5**, where it remains with all of the column lines asserted until the row is de-asserted
- Then the machine returns to **S_0** for one cycle
- Note that all of the columns are asserted in **S_5**
- This eliminates the need to add two more states to the machine as it moves from **S_2**, **S_3** and **S_4** and awaits de-assertion of the row



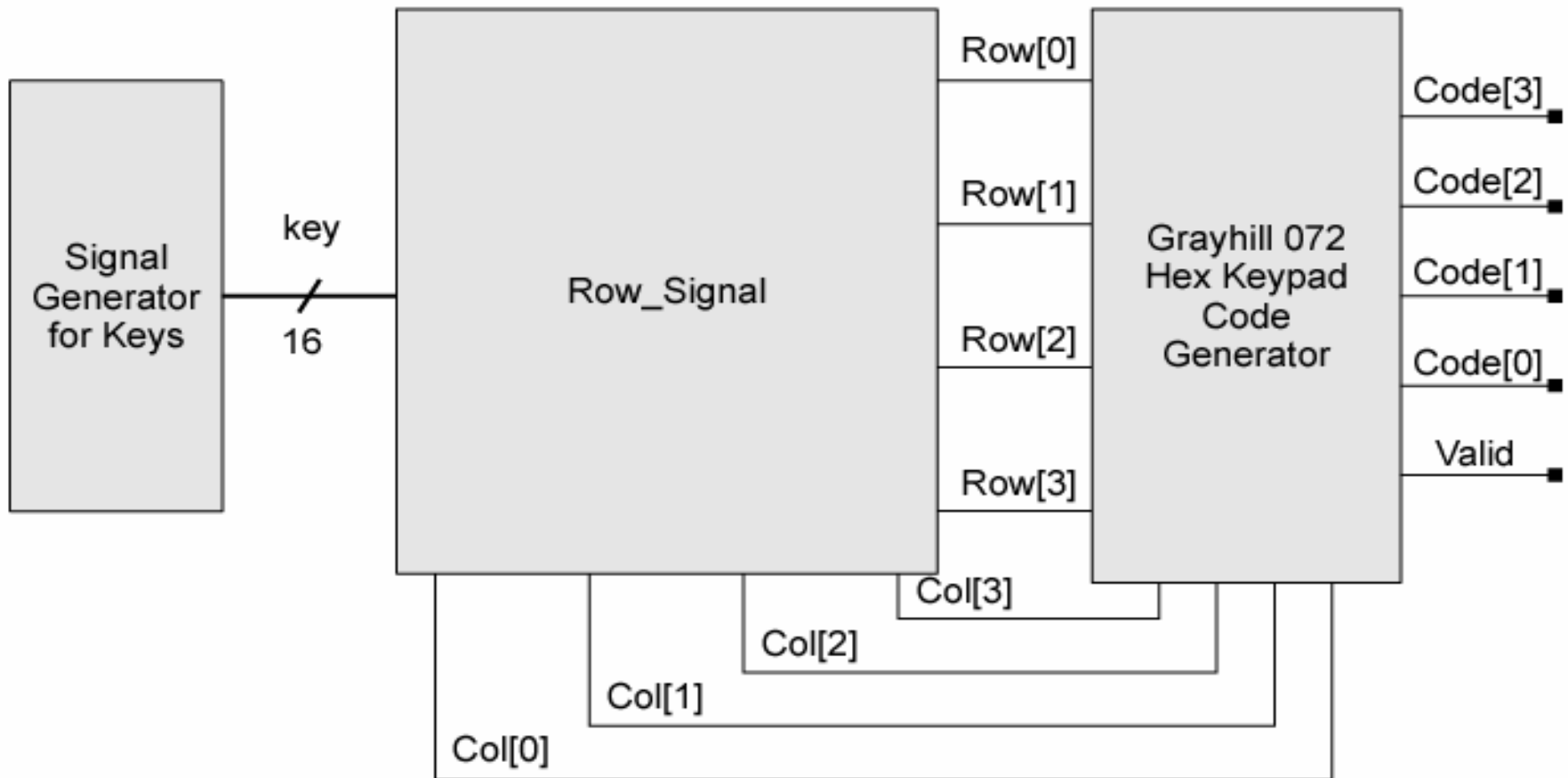Testbench organization for the Grayhill 072 hexadecimal keypad scanner/encoder





```
// Decode the asserted Row and Col
// Grayhill 072 hex Keypad
//          Col[0]  Col[1]  Col[2]  Col[3]
// Row[0]    0      1      2      3
// Row[1]    4      5      6      7
// Row[2]    8      9      A      B
// Row[3]    C      D      E      F
```

```
module Hex_Keypad_Grayhill_072
  (Code,Col,Valid,Row,S_Row,clock,reset);
  output      [3:0] Code;
  output      Valid;
  output      [3:0] Col;
  input       [3:0] Row;
  input       S_Row;
  input       clock,reset
  reg        Col,Code;
  reg        [5:0] state,next_state;
```



// One-hot

parameter

S_0=6'b000001,S_1=6'b000010,S_2=6'b000100;

parameter

S_3=6'b001000,S_4=6'b010000,S_5=6'b100000;

assign

Valid=((state==S_1)|| (state==S_2)|| (state==S_3)||
(state== S_4))&&Row;

// Does not matter if the row signal is not the

// debounced version.

// Assumed to settle before it is used at the clock edge

always @ (Row or Col)

case ({Row,Col})

8'b0001_0001: Code=0;

8'b0001_0010: Code=1;

8'b0001_0100: Code=2;

8'b0001_1000: Code=3;



8'b0010_0001: Code=4;

8'b0010_0010: Code=5;

8'b0010_0100: Code=6;

8'b0010_1000: Code=7;

8'b0100_0001: Code=8;

8'b0100_0010: Code=9;

8'b0100_0100: Code=10; // A

8'b0100_1000: Code=11; // B

8'b1000_0001: Code=12; // C

8'b1000_0010: Code=13; // D

8'b1000_0100: Code=14; // E

8'b1000_1000: Code=15; // F

default: Code=0; // Arbitrary choice

endcase



```
always @ (posedge clock or posedge reset)  
  if (reset) state<=S_0;  
  else state<=next_state;  
always @ (state or S_Row or Row) // Next-state logic  
  begin next_state=state; Col=0;  
    case (state)  
      // Assert all rows  
      S_0: begin Col=15; if (S_Row) next_state=S_1; end  
      // Assert col 0  
      S_1: begin Col=1; if (Row) next_state=S_5; else next_state=S_2; end  
      // Assert col 1  
      S_2: begin Col=2; if (Row) next_state=S_5; else next_state=S_3; end  
      // Assert col 2  
      S_3: begin Col=4; if (Row) next_state=S_5; else next_state=S_4; end  
      // Assert col 3  
      S_4: begin Col=8; if (Row) next_state=S_5; else next_state=S_0; end  
      // Assert all rows  
      S_5: begin Col=15; if (Row==0) next_state=S_0; end  
    endcase  
  end  
endmodule
```



```
module Synchronizer (S_Row,Row,clk,reset);
```

```
    output      S_Row;
```

```
    input [3:0]  Row;
```

```
    input      clk, reset;
```

```
    reg        A_Row,S_Row;
```

```
// Two stage pipeline synchronizer
```

```
always @ (negedge clk or posedge reset)
```

```
begin
```

```
    if (reset) begin      A_Row<=0;
```

```
                        S_Row<=0;
```

```
    end
```

```
    else begin  A_Row<=(Row[0] || Row[1] || Row[2] ||Row[3]);
```

```
              S_Row<=A_Row;
```

```
    end
```

```
    end
```

```
end
```

```
endmodule
```




```

module Row_Signal (Row,Key,Col);
  // Scans for row of the asserted key
  output [3:0] Row;
  input [15:0] Key;
  input [3:0] Col;
  reg Row;
  always @ (Key or Col) begin // Combinational logic for key
  assertion
    Row[0]=Key[0]&&Col[0]||Key[1]&&Col[1]||Key[2]&&Col[2]||
      Key[3]&&Col[3];
    Row[1]=Key[4]&&Col[0]||Key[5]&&Col[1]||Key[6]&&Col[2]||
      Key[7]&&Col[3];
    Row[2]=Key[8]&&Col[0]||Key[9]&&Col[1]||Key[10]&&Col[2]||
      Key[13] &&Col[3];
    Row[3]=Key[12]&&Col[0]||Key[13]&&Col[1]||Key[14]&&Col[2]||
      Key[15]&Col[3];

  end
endmodule

```

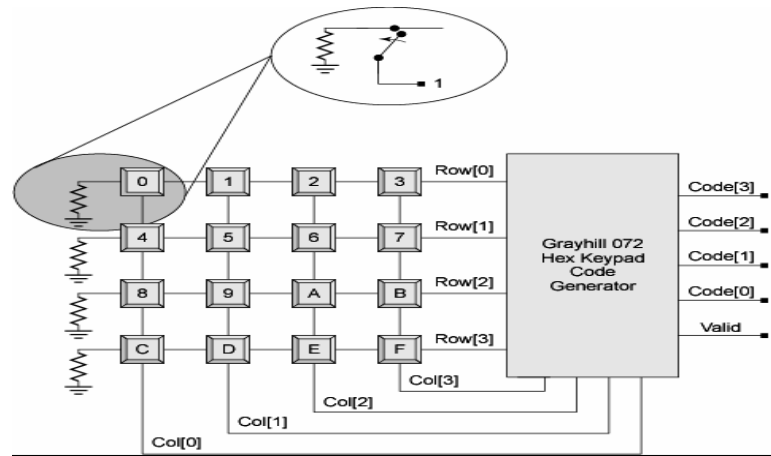



//////////////// Test Bench //////////////////

```
module test_Hex_Keypad_Grayhill_072 ();  
  wire [3:0]    Code;  
  wire          Valid;  
  wire [3:0]    Col;  
  wire [3:0]    Row;  
  reg           clock,reset;  
  reg [15:0]    Key;  
  integer       j,k;  
  reg [39:0]    Pressed;  
  parameter [39:0] Key_0="Key_0";  
  parameter [39:0] Key_1="Key_1";  
  parameter [39:0] Key_2="Key_2";  
  parameter [39:0] Key_3="Key_3";  
  parameter [39:0] Key_4="Key_4";  
  parameter [39:0] Key_5="Key_5";  
  parameter [39:0] Key_6="Key_6";
```



```
parameter [39:0] Key_7="Key_7";  
parameter [39:0] Key_8="Key_8";  
parameter [39:0] Key_9="Key_9";  
parameter [39:0] Key_A="Key_A";  
parameter [39:0] Key_B="Key_B";  
parameter [39:0] Key_C="Key_C";  
parameter [39:0] Key_D="Key_D";  
parameter [39:0] Key_E="Key_E";  
parameter [39:0] Key_F="Key_F";  
parameter [39:0] None="None";  
always @ (Key) begin  
  case (Key)  
    16'h0000: Pressed=None;  
    16'h0001: Pressed=Key_0;  
    16'h0002: Pressed=Key_1;  
    16'h0004: Pressed=Key_2;  
    16'h0008: Pressed=Key_3;  
    16'h0010: Pressed=Key_4;  
    16'h0020: Pressed=Key_5;
```



```
16'h0040: Pressed=Key_6;
16'h0080: Pressed=Key_7;
16'h0100: Pressed=Key_8;
16'h0200: Pressed=Key_9;
16'h0400: Pressed=Key_A;
16'h0800: Pressed=Key_B;
16'h1000: Pressed=Key_C;
16'h2000: Pressed=Key_D;
16'h4000: Pressed=Key_E;
16'h8000: Pressed=Key_F;
default: Pressed=None;
endcase
end

Hex_Keypad_Grayhill_072 M1
  (Code,Col,Valid,Row,S_Row,clock,reset);
Row_Signal M2 (Row,Key,Col);
Synchronizer M3 (S_Row,Row,clock,reset);
```



initial #2000 \$finish;

initial

begin clock=0; forever #5 clock=~clock; **end**

initial begin reset=1; #10 reset=0; **end**

initial

begin for (k=0;k<=1;k=k+1)

begin Key=0;#25 **for** (j=0;j<=16;j=j+1)

begin

#20 Key[j]=1; #60 Key=0;

end

end


end

endmodule






Simulation result

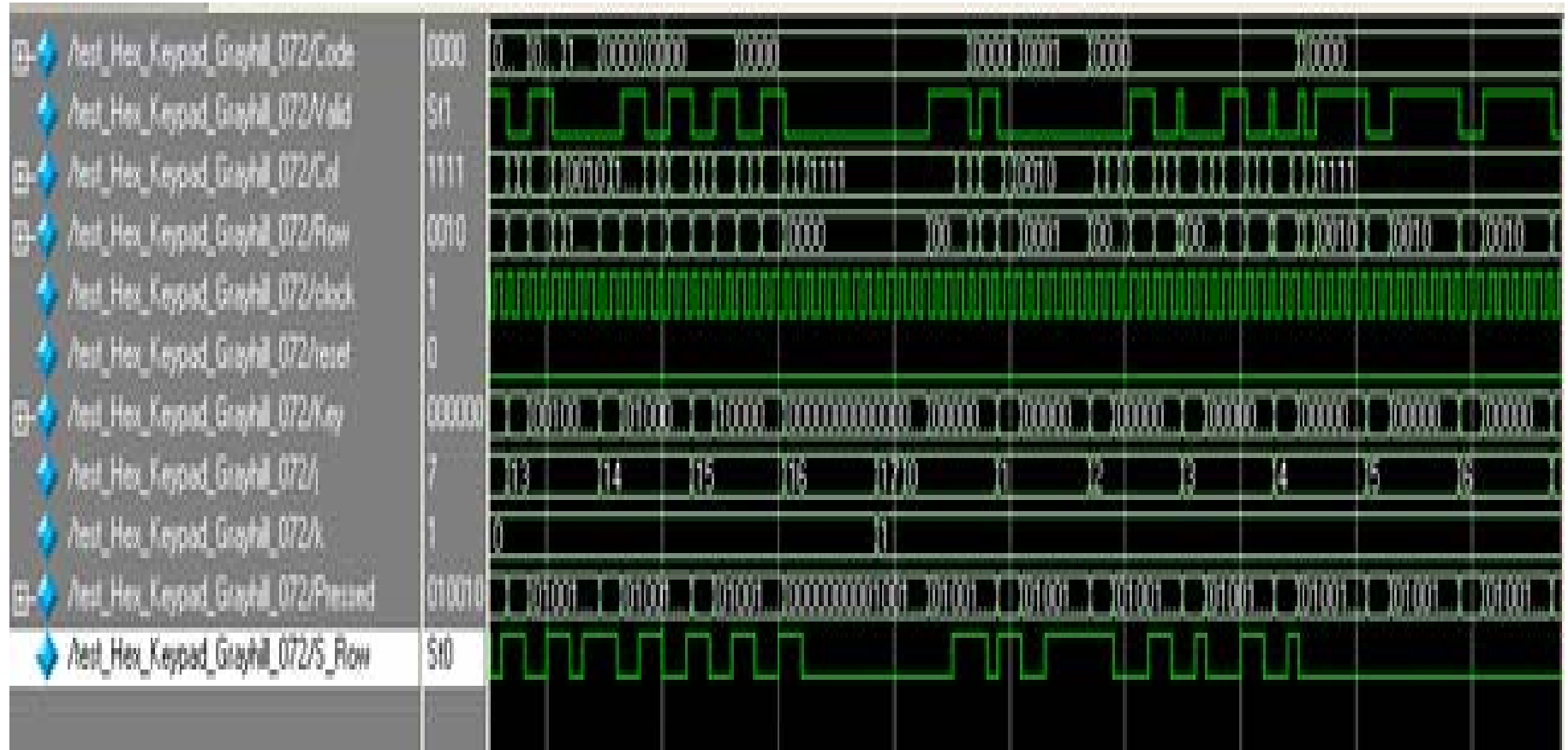



Problem 5-15

- Write a Verilog description of the circuit shown in Figure P5-15 and verify that the circuit- output, P_odd, is asserted if successive samples of D_in have an odd number of 1s.

 



Problem 5-16

Develop and verify a Verilog model of a 4-bit binary synchronous counter with the following specifications:

- negative edge-triggered synchronization
- synchronous load
- reset
- parallel load of data
- active-low enabled counting.



- **Problem 5-20**
- Develop and verify a Verilog model of a modulo-6 counter
- **Problem 5-23**
- Write a parameterized and portable Verilog model of an 8-bit ring counter whose movement is from its MSB to its LSB.