



# Chapter 6

## Synthesis of Combinational and Sequential Logic



# Synthesis tools' task

- Detect and eliminate redundant logic
- Detect combinational feedback loops
- Exploit don't-care conditions
- Detect unused states
- Detect and collapse equivalent states
- Make state assignments
- Synthesize optimal, multilevel realizations of logic **subject to constraints on area and/or speed in a physical technology**




# 6.1 Introduction to synthesis

- Circuit design **begins with specification** of the circuit's functionality and **ends with physical hardware**
- An HDL can facilitate the design process by providing different views of the circuit
- **Three common views:**
  - behavioral, structural , physical


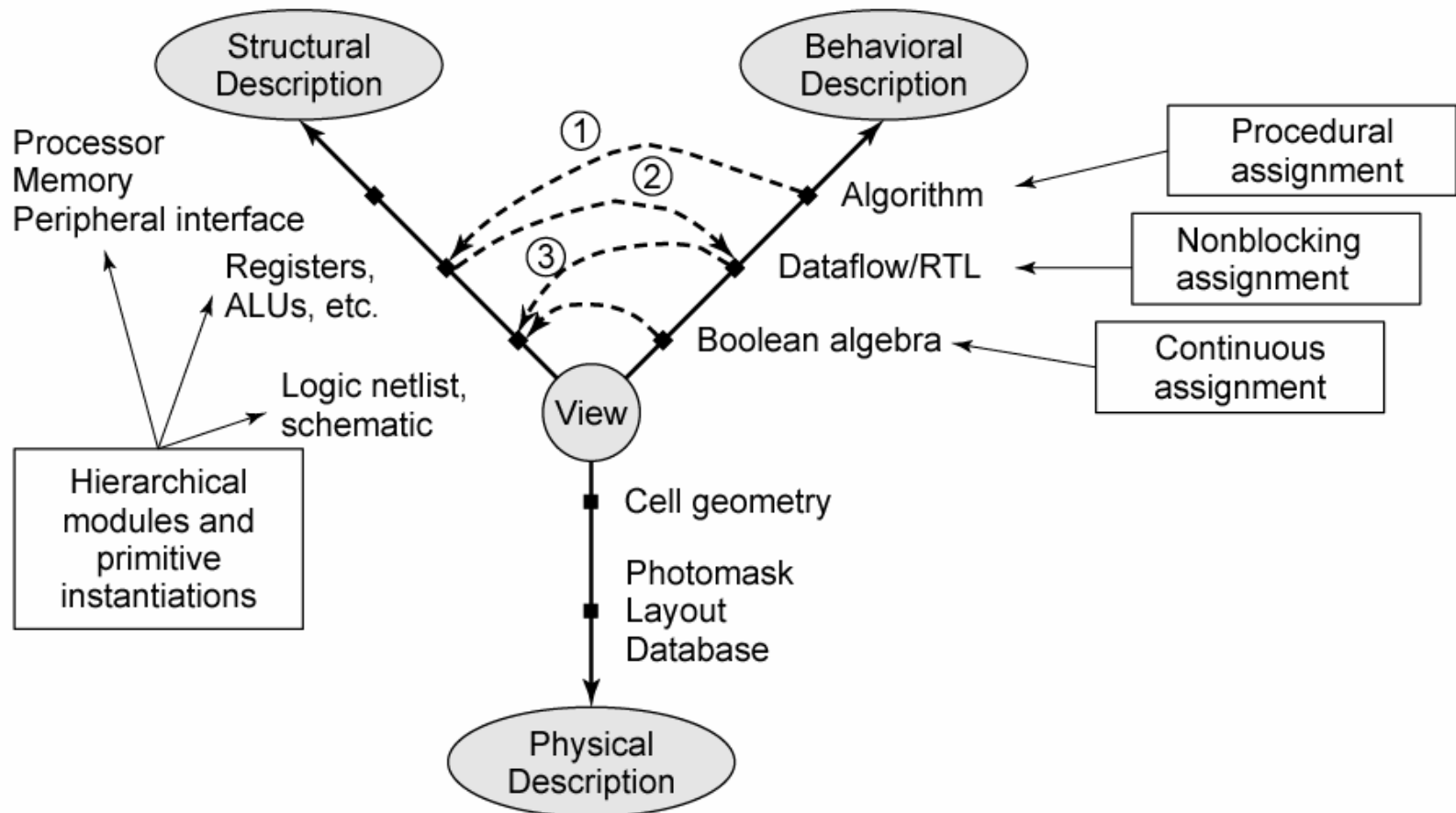
# Y-chart

- representation of Verilog constructs supporting synthesis activity in three views of a circuit






# The chart shows a sequence of transformations

- (1) **behavioral synthesis** transforms an algorithm (behavioral view) **to an architecture of registers**
- (2) a Verilog **model of this architecture** is formed as a **data flow/register transfer level (RTL) description**
- (3) logic synthesis translates the **data flow/RTL description** into a Boolean representation and synthesizes it into **a netlist**




# Design Abstraction Levels

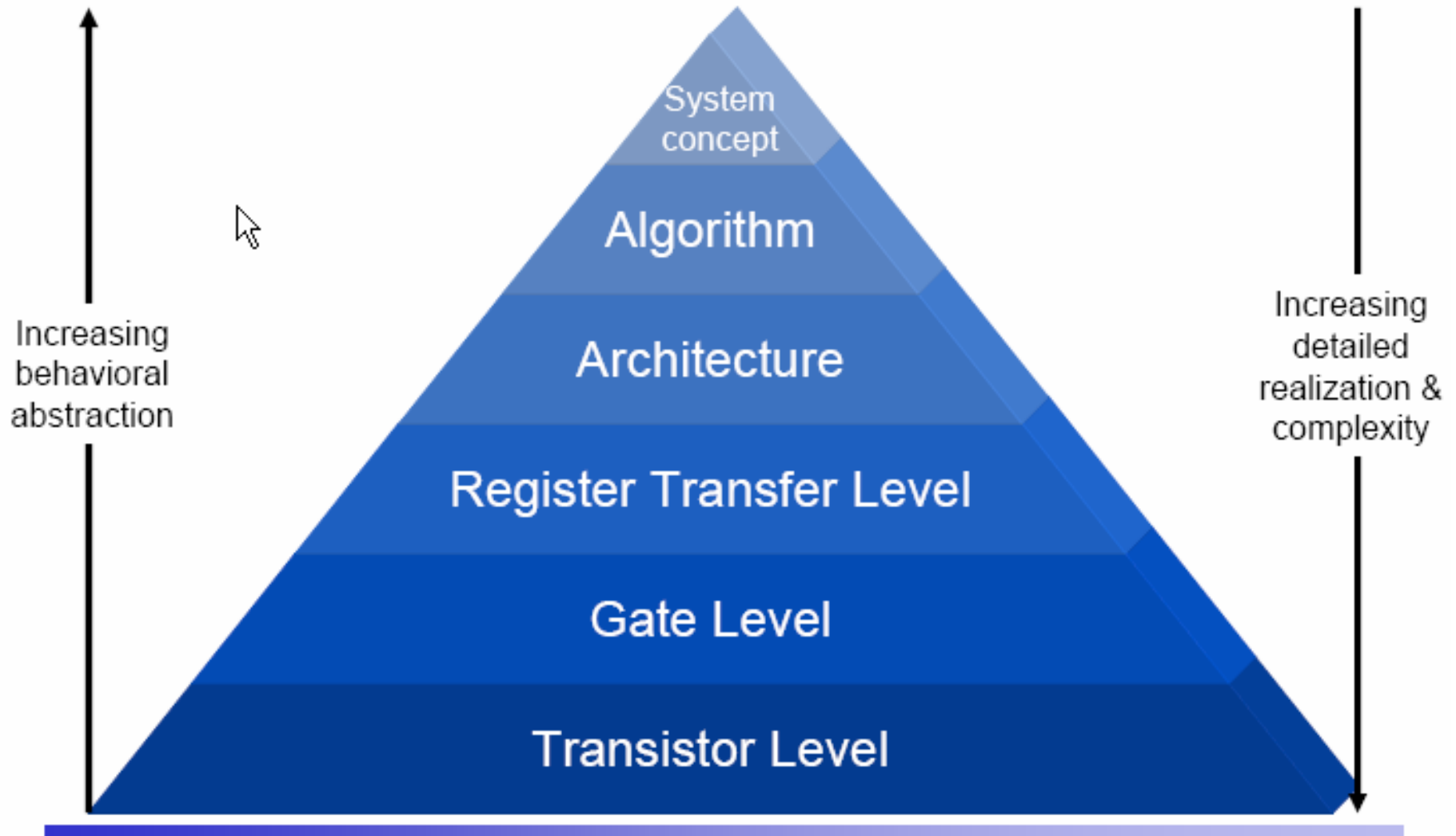



# Design Abstraction Levels

 



# Architectural level

- The operations that must be executed by the circuit **to transform a sequence of inputs into a specified sequence of outputs**
- **Design challenge** is to extract from the **architectural description** ,a structure of **computational resources** that implements the functionality of the machine








# Logical level

- Describes a set of variables and a set of Boolean functions
- The design task here is **to translate the Boolean descriptions into an optimized netlist** of combinational gates and storage registers that will implement the circuit at a satisfactory level of performance




# Gate and Circuit Level Design

   



 
# Geometrical model

- Describes the shapes that **define the doping regions of semiconductor materials** used to fabricate transistors
- HDLs do not treat geometric models





# Verilog HDL in Design Domain

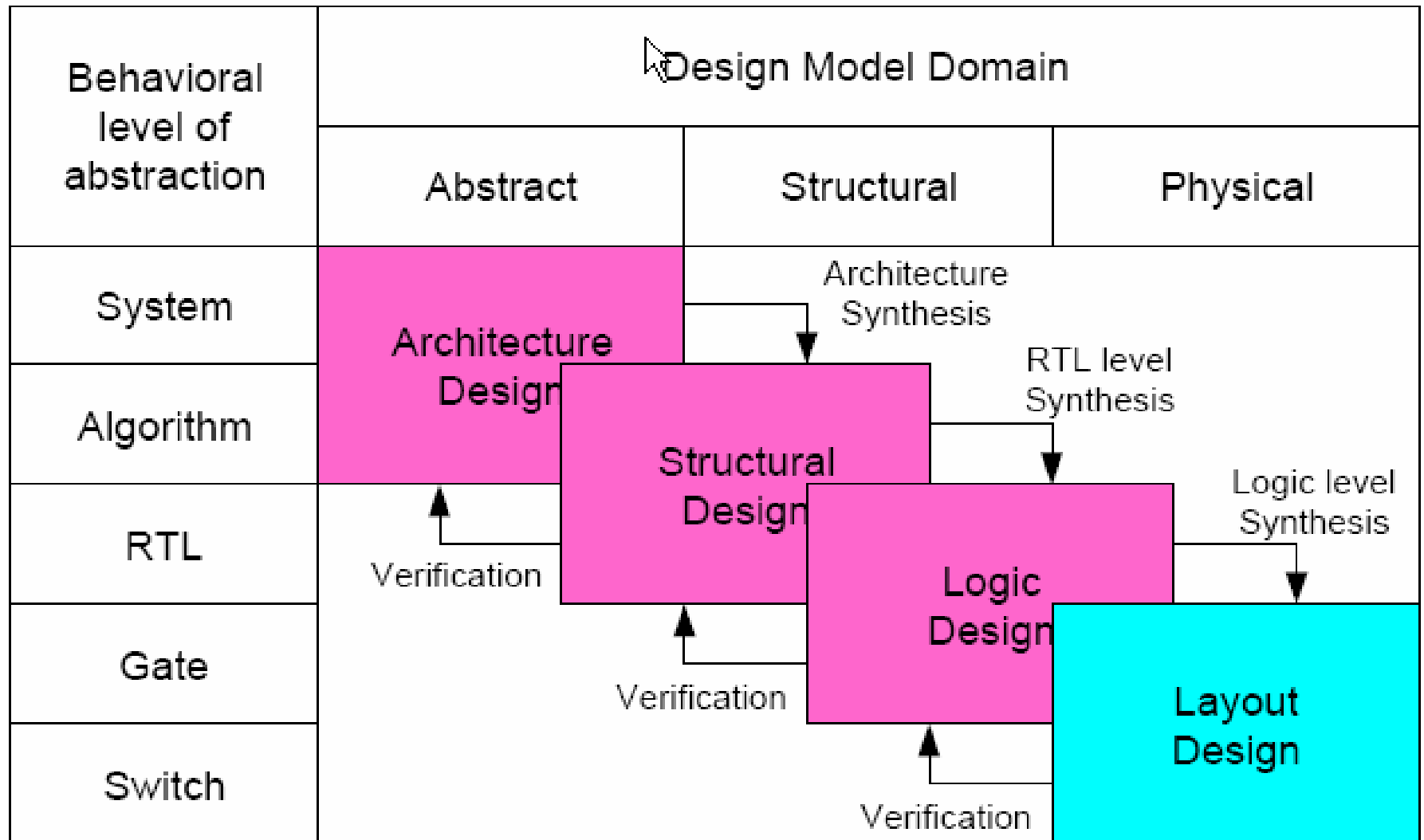



# Three common views

- **A behavioral view** of an architectural model could be **an algorithm that specifies a sequence of data transformations**
- **A structural view** of the same model might consist of **a structure of datapath elements** (registers, memory, adders, and a controller) that implement the algorithm
- **Physical descriptions**, the **actual geometric patterns** of the physical devices that implement the circuit, will not be considered here




## 6.1.1 Logic synthesis

- Logic synthesis includes:
- **Transforming** a given netlist of primitives into an **optimized netlist of Verilog primitives**
- **Mapping** a generic optimal netlist into an equivalent circuit composed of physical resources in a target technology



# Abstraction levels and synthesis

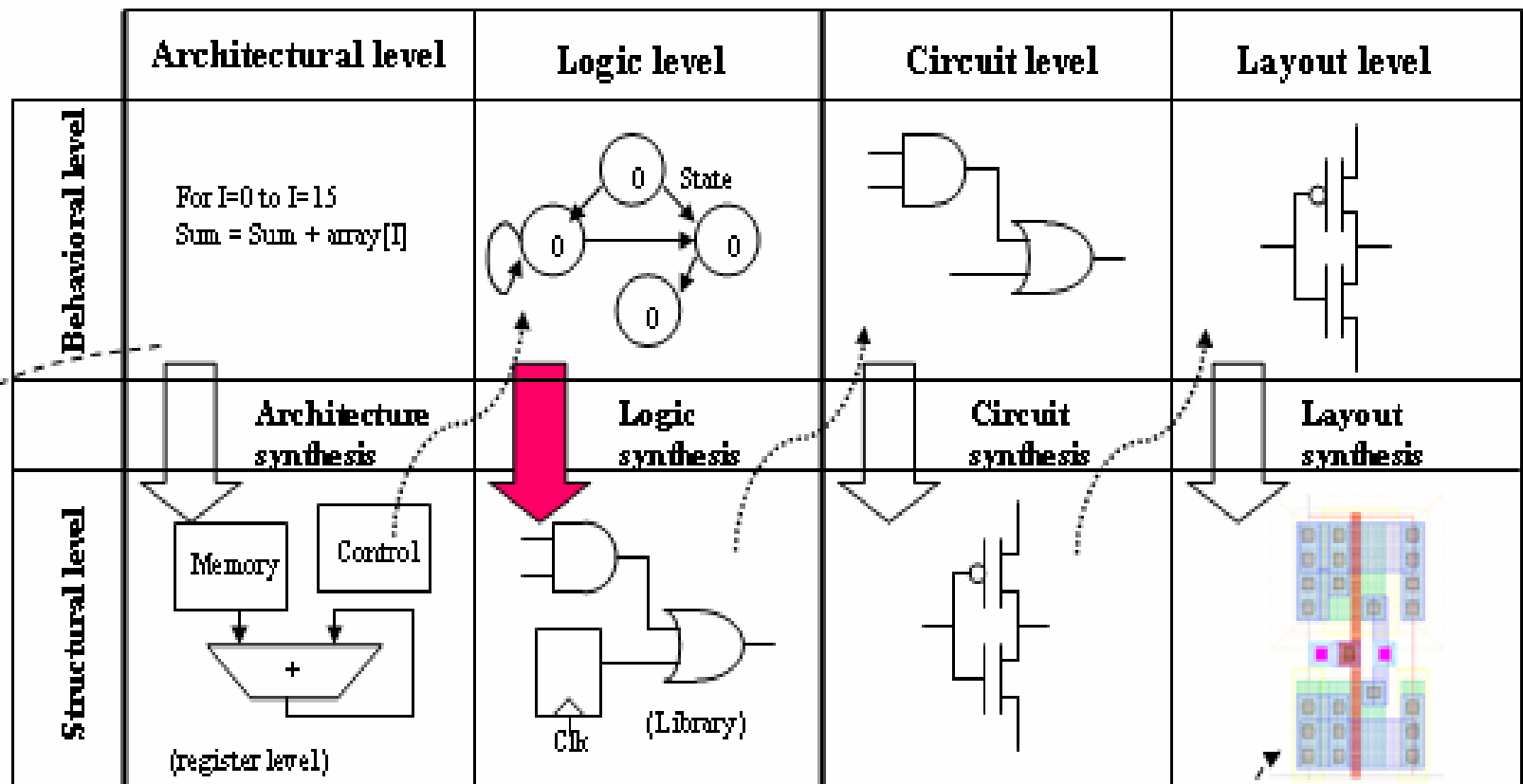

Silicon compilation (not a big success)






# Synthesis and Technology Mapping

Simulation and Synthesis are components of a design methodology

always  
mumble  
mumble  
blah  
blah

Synthesis


Synthesizable Verilog

 

Technology Mapping



Place and Route

 




# Logic synthesis

- Three steps:
- **Synthesis =**  
**Translation**  
**+ Logic optimization**  
**+ mapping**


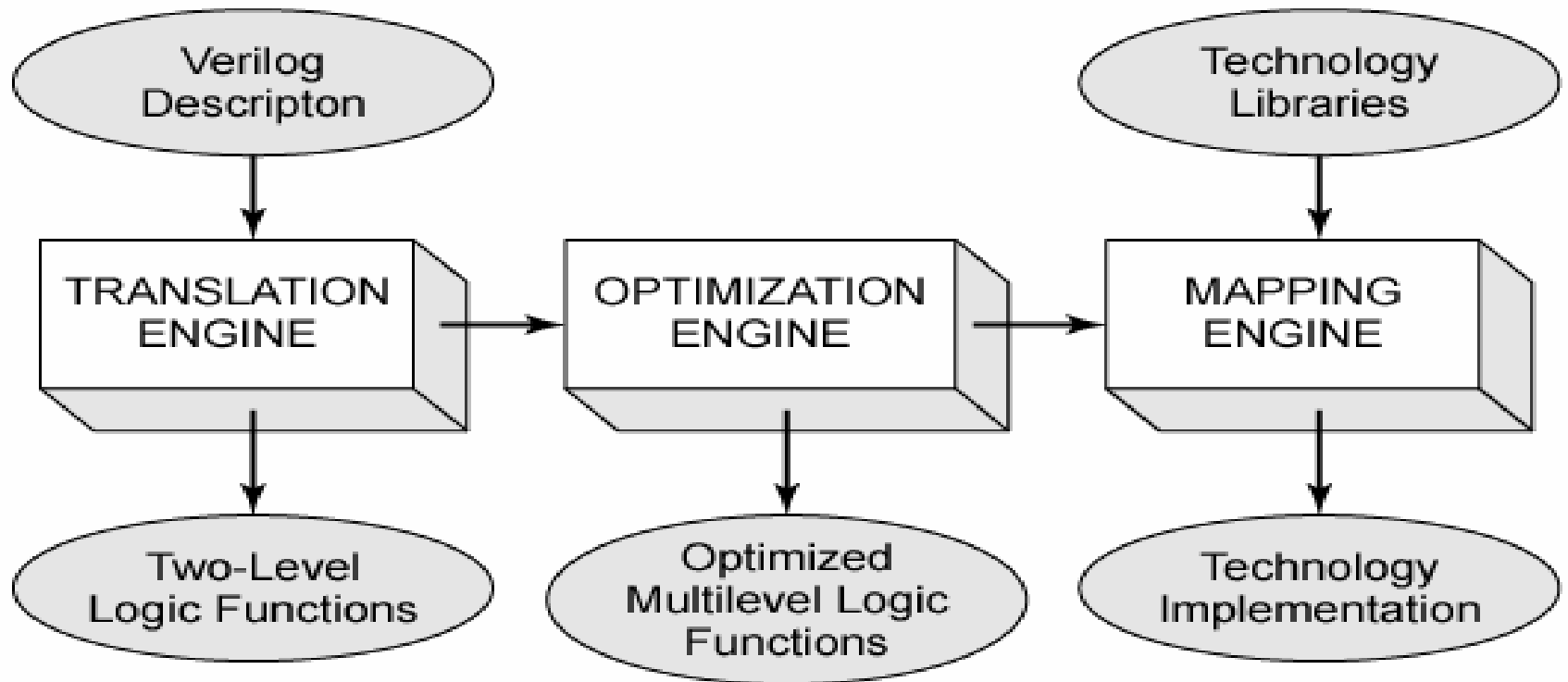
# The organization of a logic synthesis tool

The tool forms a hardware realization (technology implementation) from a Verilog RTL model or primitive netlist.





# Synthesis

- **Synthesis creates a sequence of transformations**
- **From a higher level of abstraction to a lower one**
- There may be multiple realizations of a multi-input, multi-output combinational logic circuit
- But the transformations made in synthesis are guaranteed to maintain the input-output equivalence of the circuit and produce a testable circuit



# Optimization

- The optimization process is **based on an iterative search**
- **Logic optimization is followed by performance optimization**, which seeks a circuit that has optimal performance in the physical technology
- By **removing redundant logic, sharing internal logic, and exploiting** input and output don't-care conditions



# Structure & Flattening optimization

- ① Decomposition
- ② Extraction
- ③ Factoring
- ④ Substitution
- ⑤ Elimination

■ **The reason :**

**Types of component ,  
Cost,  
Delay ,  
Fan in/out**




# Decomposition

- The operation of decomposition transforms the circuit  
**by expressing a single Boolean function in terms of new nodes.**


 
## Ex 6.1 decomposition

- $F = abc + abd + a'b'c' + b'c'd'$  (before decomposition)








$F=XY+X'Y'$  (after decomposition)

$X=ab$  ,  $Y=c+d$ ,

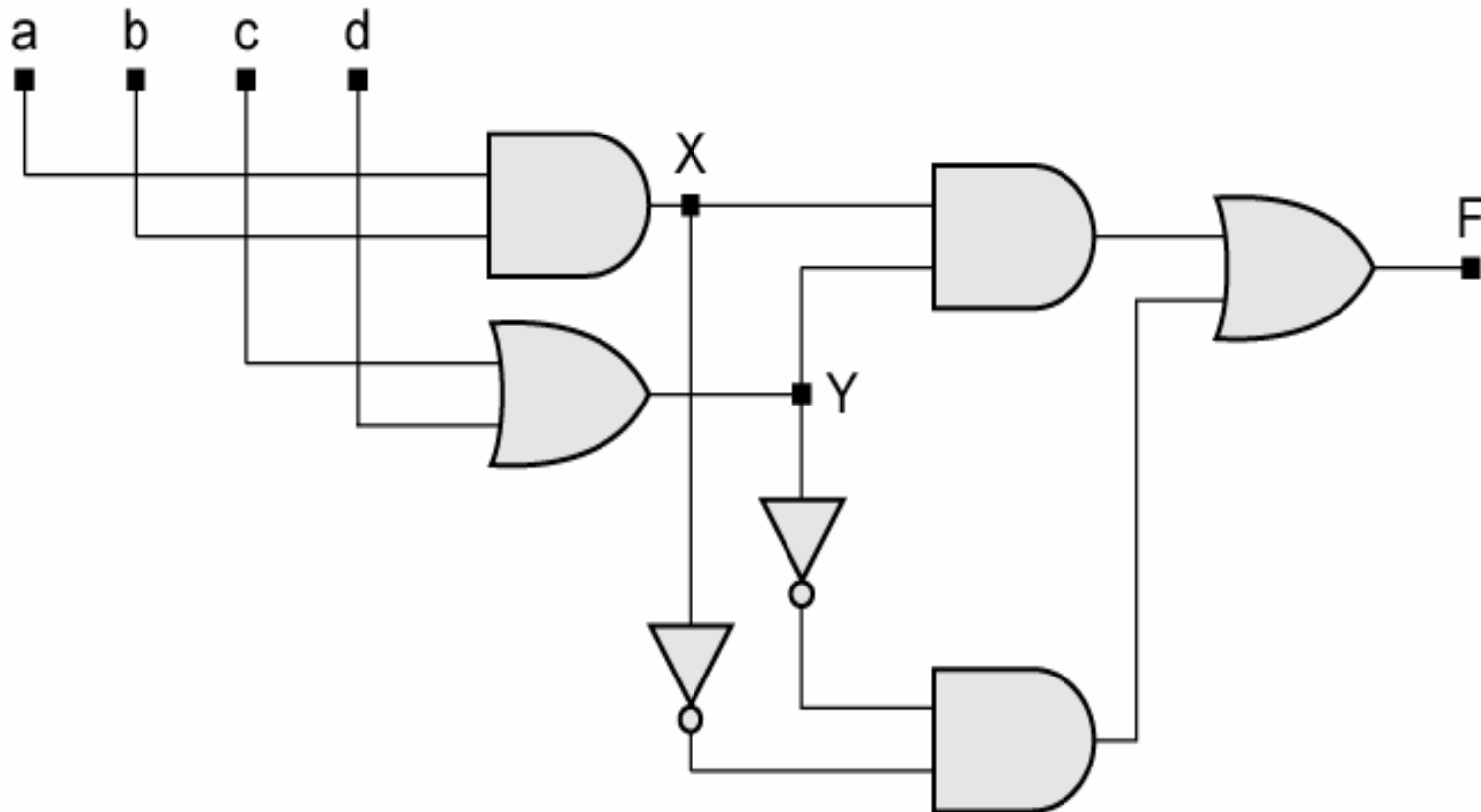**Result:** reduce Gates,wires , Chip area





# Extraction

- The operation of extraction **expresses a set of functions in terms of intermediate nodes** by expressing each function in terms of its factors and then detecting which **factors are shared among functions**




# Directed Acyclic Graph (DAG)

- **DAG** – directed graph with no directed cycles
 
## Application

- Describe a process of a system
- *Design and Analysis of Algorithms*
- *Shortest Paths*






## Ex 6.2 Extraction

- $F = (a+b)cd + e$

$$G = (a+b)e'$$

$$H = cde$$

 ( DAG of a set of functions before extraction)





# By the new internal nodes $X$ and $Y$ to produce the new DAG

$$X = a + b$$


$$Y = cd$$

$$F = XY + e$$

$$G = Xe'$$

$$H = Ye$$

 ( DAG of a set  
of functions  
after  
extraction)





# The optimization process

- The optimization process seeks a set of intermediate nodes
- to **eliminate replicated logic**
- to **optimize the circuit's delay and area**
- Because the intermediate nodes correspond to factors that are common to more than one Boolean function, and therefore can be shared




# Factoring

- The task of **finding the common factors among a set of functions** is called factoring
- Factoring **produces a set of functions in a products of sum form**
- It creates a structural transformation of the circuit from a two-level realization to an equivalent multilevel realization that **uses less area, but is possibly slower**


 
# Ex 6.3 Factoring

- $F = ac + ad + bc + bd + e$  (before factoring)







 
# After Factoring

- $F = (a+b)(c+d)+e$ ;
- Before:(w:14,G:5 );Now:(w:9,G:4)






# Factoring

- The substitution process expresses a Boolean function **in terms of its inputs and another function**
- Since both functions need to be implemented, this step **provides a potential reduction of replicated logic**


 
## Ex 6.4 Substitution


- $G = a + b$   
 $F = a + b + c$   
(before)





# After substitution

- $F=G+c$

 



# Elimination


- Elimination **removes a node in a function and reduces the structure of the circuit**
- This step is also referred to as **flattening the circuit**
- The transformation would ultimately **eliminate the area-efficient internal multilevel structure** and **create a faster two-level structure**



# Ex. 6.5 Elimination

- $F = Ga + G'b$   
 $G = c + d$   
(before  
elimination)


Figure 6-11(a)

 



$$F = ac + ad + bc'd$$

(after elimination)

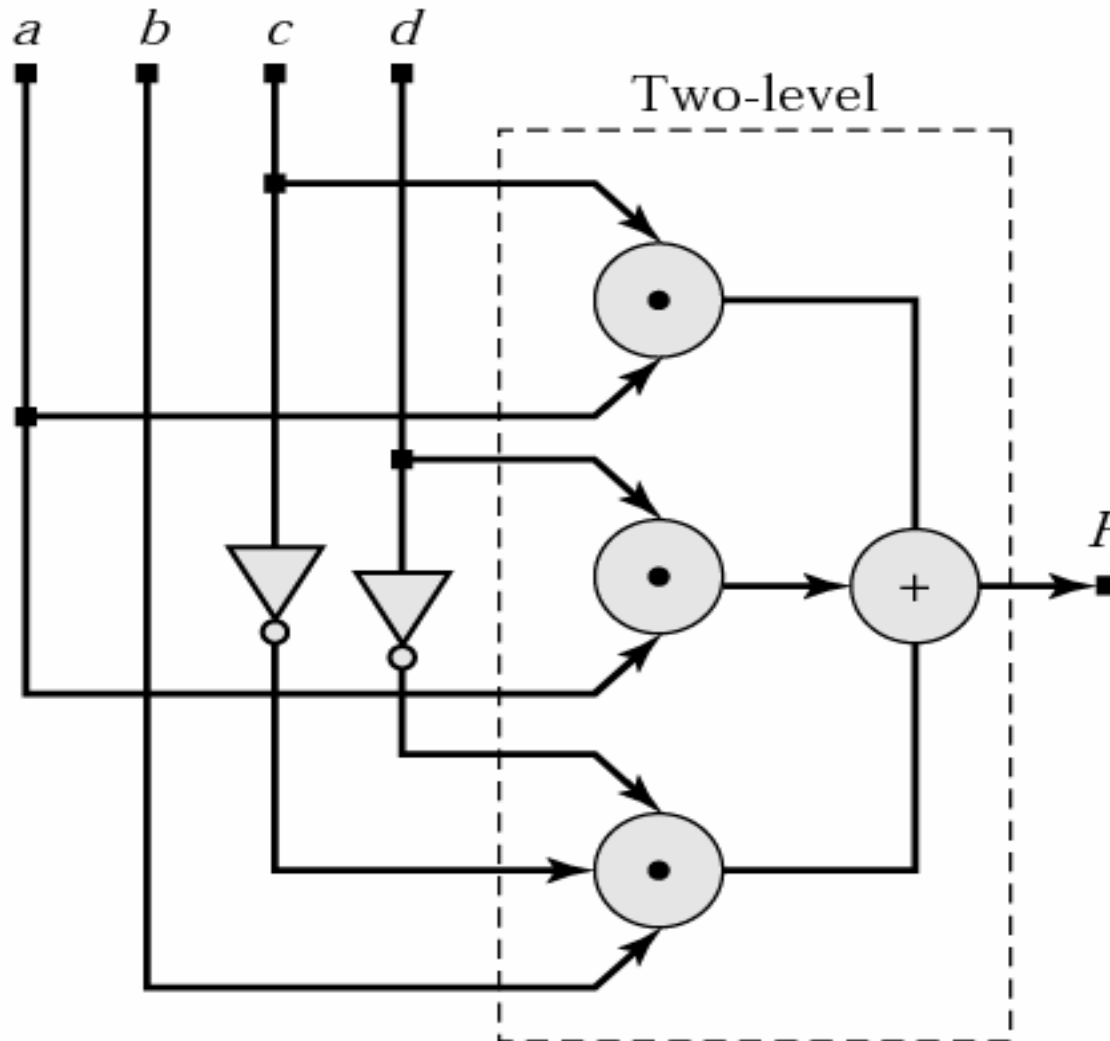



# Multilevel networks

- Multilevel networks may be used because two-level networks might require **higher fan-in than is practical**
- **Multilevel circuits present an opportunity to share logic, but can be slower than a two-level counterpart**






# Balancing Operators

- Use Parenthesis to Define Logic Groupings
  - Increases Performance & Utilization
  - Balances Delay from All Inputs to Output
  - Circuit Functionality Unchanged


## Unbalanced

$$\text{out} = a * b * c * d;$$

 

## Balanced

$$\text{out} = (a * b) * (c * d);$$

 




# Balancing Operators: Example

- a, b, c, d: 4-bit vectors


Unbalanced

$$\text{out} = a * b * c * d$$

 

Balanced

$$\text{out} = (a * b) * (c * d)$$

 



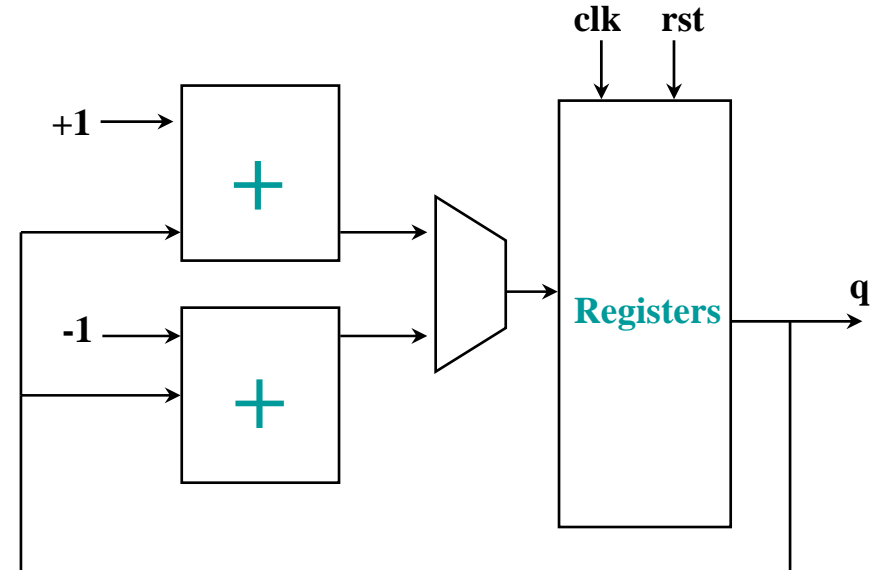
# Mutually Exclusive Operators

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
  
always@(posedge clk or negedge rst)  
begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        q<=q+1;  
    else  
        q<=q-1;  
    end  
endmodule
```

- *Up/Down Counter*
- *Quartus recognizes this code as a counter and will implement it efficiently, but not all tools will recognize it.*





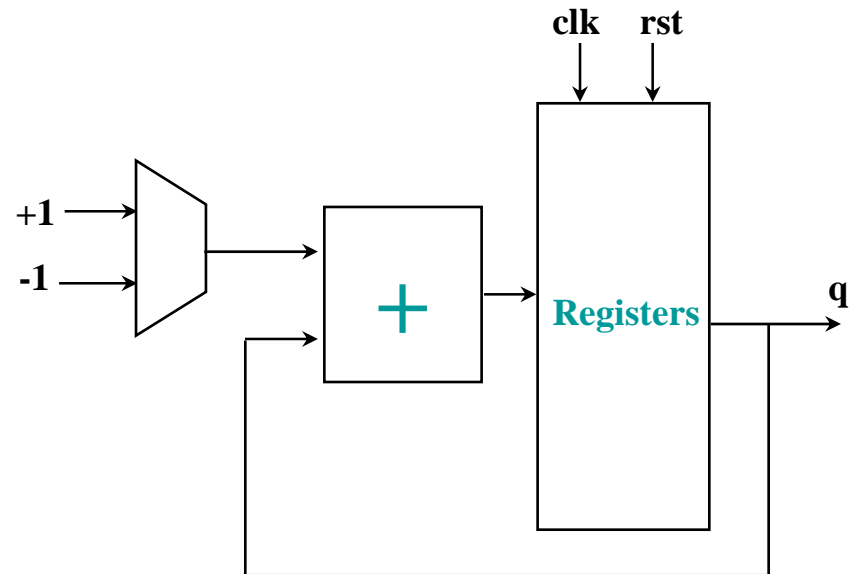
# Sharing Mutually Exclusive Operators

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
integer dir;  
  
always@(posedge clk or negedge  
rst)begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        dir<=1;  
    else  
        dir<=-1;  
    q<=q+dir;  
end  
endmodule
```


- Up/Down Counter
- Only One Adder Required




 
## 6.1.2 RTL synthesis

- RTL synthesis begins with an architecture and **converts language-based RTL statements into a set of Boolean equations** that can be optimized by a logic synthesis tool





# RTL description

- RTL codes define:
  - ① The register **structure** and register **amount** of the circuit
  - ② The **topology** of the circuits
  - ③ The **logic function** of the combination circuits between in/out to register or register to register



## 6.1.3 High-level synthesis

- Goal is to find an architecture whose resources **can be scheduled and allocated to implement an algorithm**
- The algorithm describes only the functionality, **not explicitly declare a structure of registers and datapaths**
- Many different architectures may implement the same functional specification



# A behavioral synthesis

- **resource allocation and resource scheduling**
- two main steps to create an architecture of datapath elements, control units, and memory:
- **The allocation step** identifies the operators and infers the need for memory resources
- The operations are assigned to specific clock cycles **to implement the ordered sequential activity flow of the algorithm**
- **Resource scheduling** determines the number of computational units





 
# Representation of a behavioral model

parse trees


$A = B + C;$   
 $D = A * E;$   
 $M = D - A$





# Representation of a behavioral model

## Data Flow Graph

 



## 6.2 Synthesis of combinational logic

- There are many ways to describe combinational logic, but some are not supported by synthesis tools

**Synthesizable combinational logic** can be described by:

1. a netlist of structural primitives
2. a set of continuous-assignment statement
3. a level-sensitive cyclic behavior




# 1. Synthesizes a netlist

- A netlist of primitives should be synthesized **to remove any redundant logic before mapping the design into a technology**
- To ensure that the logic has been minimized correctly



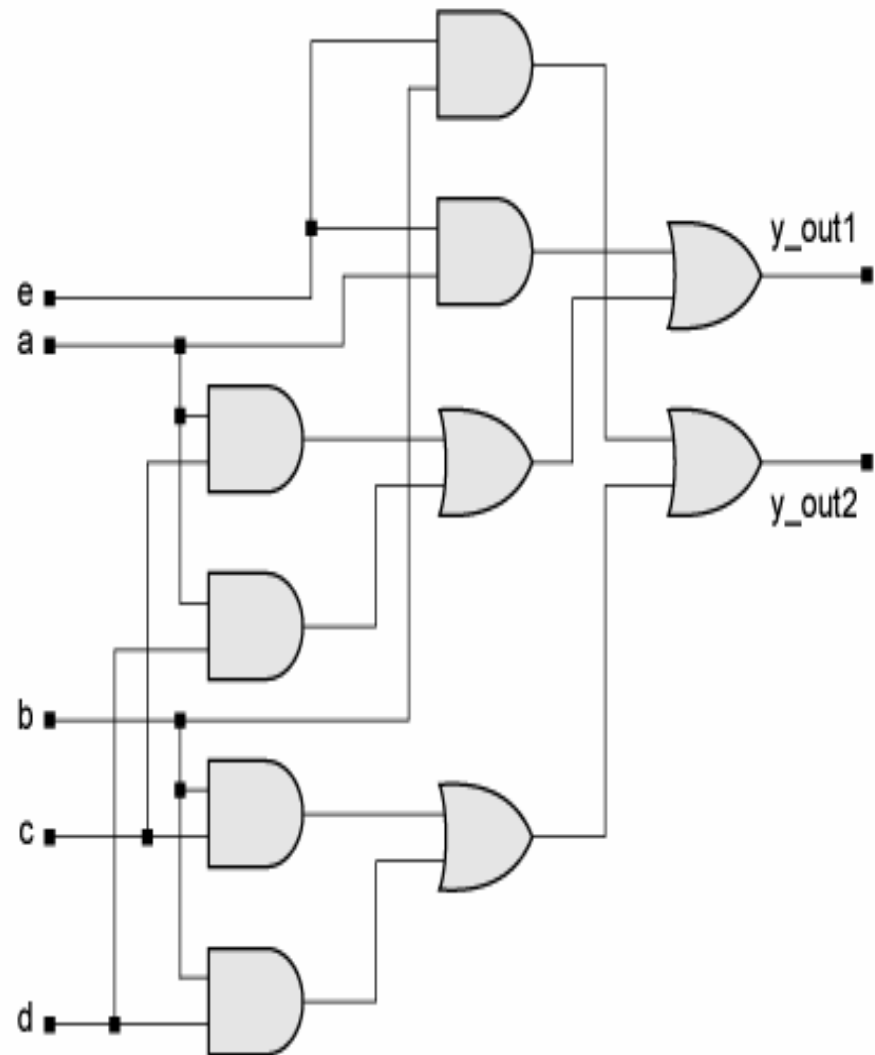
## Ex 6.6 Synthesizes a netlist : the pre-optimized circuit

```
module boole_opt(y_out1,  
  y_out2, a, b, c, d, e);  
output    y_out1, y_out2;  
input     a, b, c, d, e;  
and       (y1,a,c);  
and       (y2,a,d);  
and       (y3,a,e);  
or        (y4,y1,y2);  
or        (y_out1,y3,y4);  
and       (y5,b,c);  
and       (y6,b,d);  
and       (y7,b,e);  
or        (y8,y5,y6);  
or        (y_out2,y7,y8);  
endmodule
```





# The synthesized circuit

 




## 2. Continuous-assignment statements are synthesizable

- The expression in a continuous assignment statement will **be translated by the synthesis tool to an equivalent Boolean equation**
- The designer must **verify** that the continuous assignment correctly describes the logic, and that the synthesized multilevel logic circuit has the **correct functionality**



## Example 6.7 The continuous assignment in or\_nand

```
module or_nand (y, enable, x1,x2,x3,x4)  
  output y;  
  input enable, x1,x2,x3,x4;  
  assign y=~(enable&(x1|x2)&(x3|x4));  
endmodule
```

 





### 3. Level-sensitive cyclic behavior

- A level-sensitive cyclic behavior will synthesize to combinational logic **if it assigns a value to each output for every possible value of its inputs**
- The event control expression of the behavior **must be sensitive to every input**
- The every path of the activity flow **must assign value to every output**




## Ex 6.8 2-bit comparator

```
module comparator (a_gt_b,a_lt_b,a_eq_b,a,b); // Alternative algorithm
  parameter    size=2;
  output       a_gt_b,a_lt_b,a_eq_b;
  input        [size:1] a,b;
  reg          a_gt_b,a_lt_b,a_eq_b;
  integer      k;
  always @ (a or b) begin: compare_loop
    for (k=size; k>0;k=k-1)
      begin
        if (a[k] != b[k]) begin
          a_gt_b=a[k]; a_lt_b=~a[k]; a_eq_b=0;
          disable compare_loop;
        end
      end
    a_gt_b=0; a_lt_b=0;a_eq_b=1;
  end
endmodule
```


 
# Combinational logic synthesis of 2-bit comparator






# Timing

- Timing imposes a constraint on the speed of a circuit, but not on its functionality
- The speed of ASIC is proportional to the physical geometry
- **Faster parts require more area**
- Technology-dependent timing constructs are not to be included in the model



# Example 6.9

```
module mux_logic (y,select,sig_G,sig_max,sig_a,sig_b);  
  output y;  
  input select,sig_G,sig_max,sig_a,sig_b;  
  assign  
    y=(select==1)||(sig_G==1)||(sig_max==0)?sig_a:sig_b;  
endmodule
```

 



## 6.2.1 Synthesis of priority structures

- A **case** statement **implicitly attaches higher priority** to the first item that it decodes than to the last one
- An **if** statement implies higher priority to the first branch than to the remaining branches.



# Ex 6.10 Mux with priority

**module**

```
    mux_4pri(y,a,b,c,d,sel_a,s  
    el_b,sel_c);
```

```
    output y;
```

```
    input
```

```
    a,b,c,d,sel_a,sel_b,sel_c;
```

```
    reg y;
```

```
    always @ (sel_a or sel_b  
    or sel_c or a or b or c or d)
```

```
    begin
```

```
        if (sel_a==1) y=a; else
```

```
        if (sel_b==0) y=b; else
```

```
        if (sel_c==1) y=c; else
```

```
    end
```

```
endmodule
```



## Ex 6.10 Mux with priority

**module**

```
  mux_4pri(y,a,b,c,d,sel_a,s  
    el_b,sel_c);
```

```
output y;
```

```
input
```

```
  a,b,c,d,sel_a,sel_b,sel_c;
```

```
reg y;
```

```
always @ (sel_a or sel_b  
  or sel_c or a or b or c or d)
```

```
begin
```


```
  if (sel_a==1) y=a; else
```

```
  if (sel_b==0) y=b; else
```

```
  if (sel_c==1) y=c; else
```

```
end
```

```
endmodule
```

 





## 6.2.2 Exploiting logical don't-care conditions

- When **case, if, ?... :** are used, synthesized netlist should produce the same simulation results if **default** assignments are **purely 0 or 1**
- Simulation results may differ if the default or branch statement makes an explicit assignment of an **x** or a **z**
- **An assignment to x in a case or an if statement is treated as a don't-care condition in synthesis**
- This may lead to a mismatch between the results of simulation and synthesis



# Example 6.11

```
module Latched_Seven_Seg_Display
    (Display_L, Display_R, Blanking, Enable, clock, reset);
output    [6:0]  Display_L, Display_R;
input      Blanking, Enable, clock, reset;
reg       [6:0]  Display_L, Display_R;
reg       [3:0]  count; // abc_defg

parameter BLANK = 7'b111_1111;
parameter ZERO  = 7'b000_0001; // h01
parameter ONE   = 7'b100_1111; // h4f
parameter TWO   = 7'b001_0010; // h12
parameter THREE = 7'b000_0110; // h06
parameter FOUR  = 7'b100_1100; // h4c
parameter FIVE  = 7'b010_0100; // h24
```



```
parameter SIX = 7'b010_0000; // h20
parameter SEVEN = 7'b000_1111; // h0f
parameter EIGHT = 7'b000_0000; // h00
parameter NINE = 7'b000_0100; // h04
```

```
always @ (posedge clock)
```

```
    if (reset) count<=0;
```

```
    else if (Enable) count<=count+1;
```

```
always @ (count or Blanking)
```

```
    if (Blanking) begin Display_L=BLANK; Display_R=BLANK; end
    else
```

```
        case (count)
```

```
            0 : Display_L=ZERO; Display_R=ZERO; end
```

```
            2 : Display_L=ZERO; Display_R=TWO; end
```

```
            4 : Display_L=ZERO; Display_R=FOUR; end
```

```
            6 : Display_L=ZERO; Display_R=SIX; end
```

```
            8 : Display_L=ZERO; Display_R=EIGHT; end
```

```
           10 : Display_L=ONE; Display_R=ZERO; end
```

```
           12 : Display_L=ONE; Display_R=TWO; end
```

```
           14 : Display_L=ONE; Display_R=FOUR; end
```


```
        //default : Display_L=BLANK; Display_R=BLANK; end
```

```
    endcase
```

```
endmodule
```




# Seven-segment LED display

 

(a)



# Simulation result

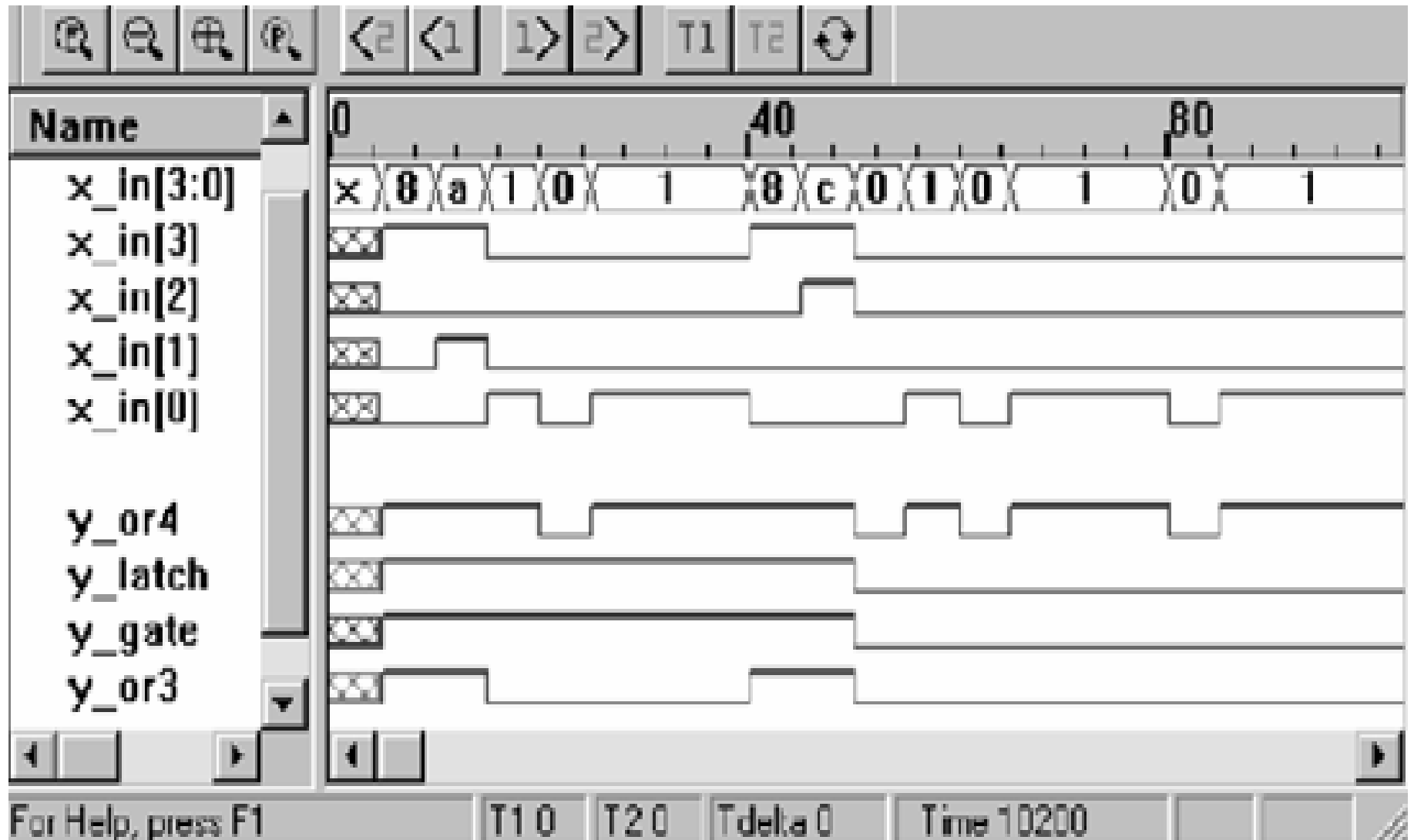




# Example 6.12

```
module alu_with_z1 (alu_out,data_a,data_b,enable,opcode);  
    input [2:0] opcode;  
    input [3:0] data_a,data_b;  
    input      enable;  
    output alu_out; //scalar for illustration  
    reg [3:0] alu_reg;  
    assign alu_out=(enable==1) ? alu_reg : 4'z;  
    always @ (opcode or data_a or data_b)  
        case (opcode)  
            3'b001: alu_reg=data_a | data_b;  
            3'b010: alu_reg=data_a ^ data_b;  
            3'b110: alu_reg=~data_b;  
            default: alu_reg=4'b0;  
        endcase  
endmodule
```


 
# Circuits synthesized from alu\_with\_z1





```
module alu_with_z2
```

```
(alu_out,data_a,data_b,enable,opcode);
```

```
input [2:0] opcode;
```

```
input [3:0] data_a,data_b;
```

```
input      enable;
```

```
output alu_out; //scalar for illustration
```

```
reg [3:0] alu_reg;
```

```
assign alu_out=(enable==1)?alu_reg:4'z;
```

```
always @ (opcode or data_a or data_b)
```

```
  case (opcode)
```

```
    3'b001: alu_reg=data_a | data_b;
```

```
    3'b010: alu_reg=data_a ^ data_b;
```

```
    3'b110: alu_reg=~data_b;
```

```
    default: alu_reg=4'bx;
```


```
  endcase
```

```
endmodule
```




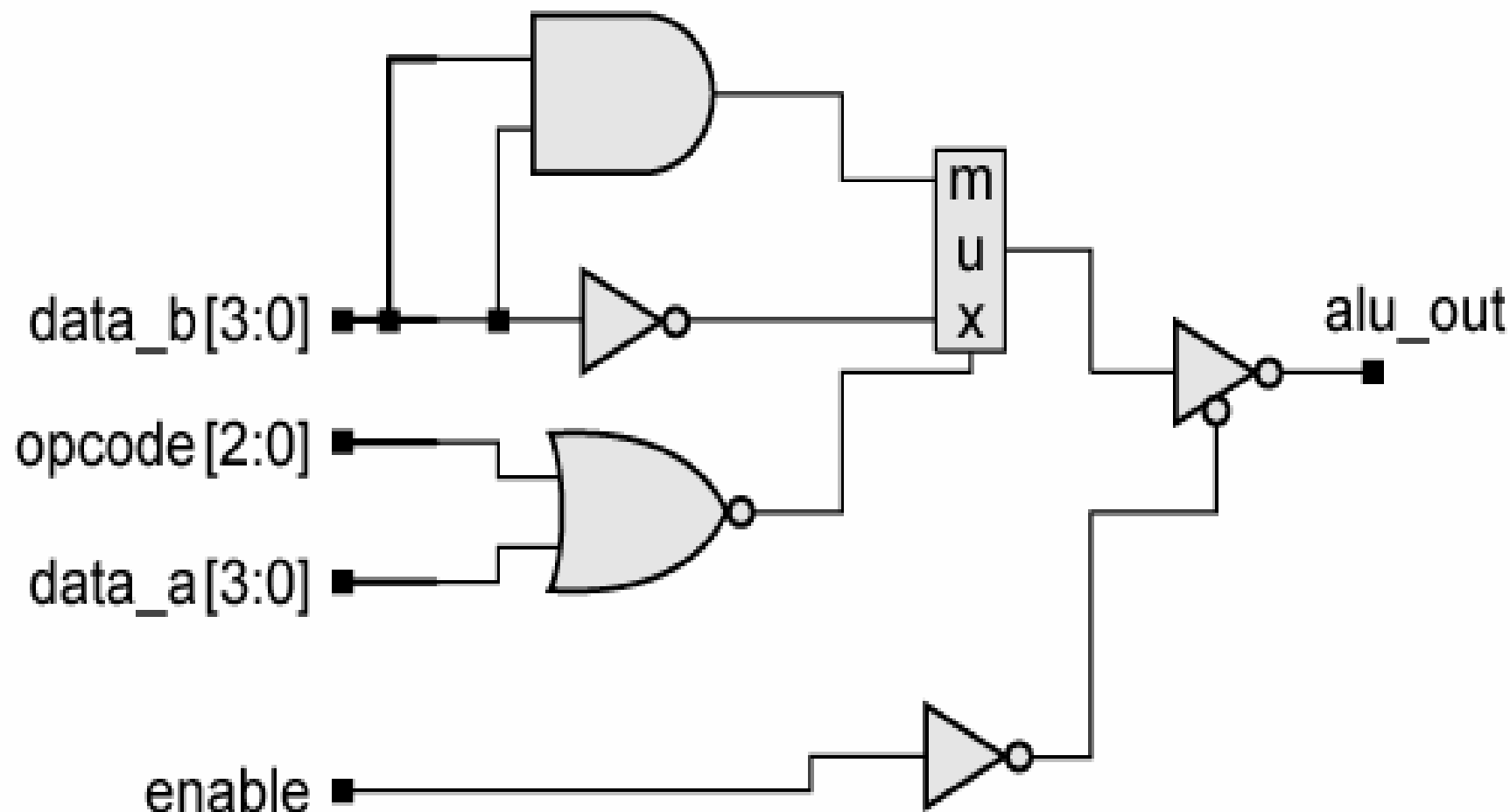
# Circuits synthesized from alu\_with\_z2





## 6.2.3 ASIC cells and resource sharing

- An ASIC cell library contains cells that are more complex than combinational primitive gates
- The tool must share resources to minimize needless duplication of circuitry
- Use parentheses to control operator grouping for reducing the size of a circuit




# Example: Balancing Operators

- $a, b, c, d$ : 4-bit vectors


Unbalanced

$$\text{out} = a * b * c * d$$

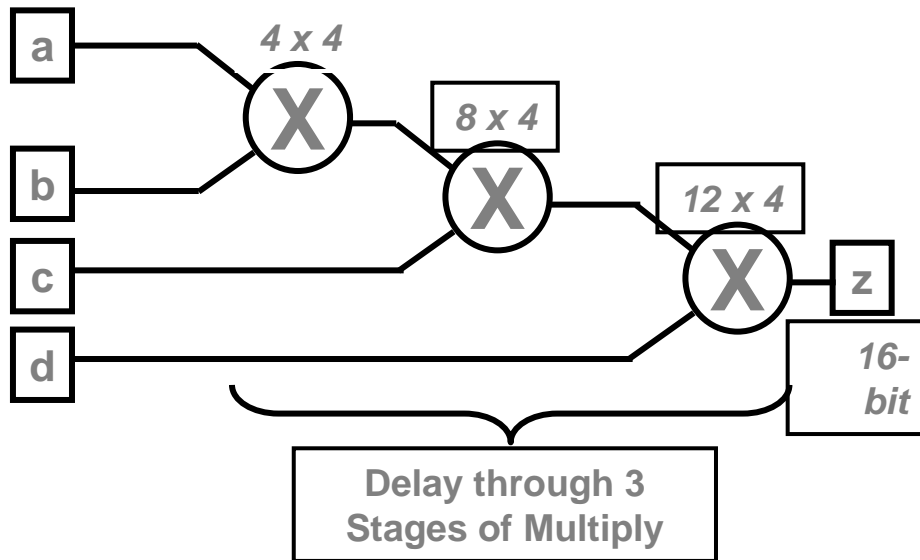

Balanced

$$\text{out} = (a * b) * (c * d)$$

 




# Example 6.13

```
module badd_4 (Sum,C_out,A,B,C_in);  
    output [3:0] Sum;  
    output    C_out;  
    input [3:0] A,B  
    input    C_in;  
    assign {C_out,Sum}=A+B+C_in;  
endmodule
```





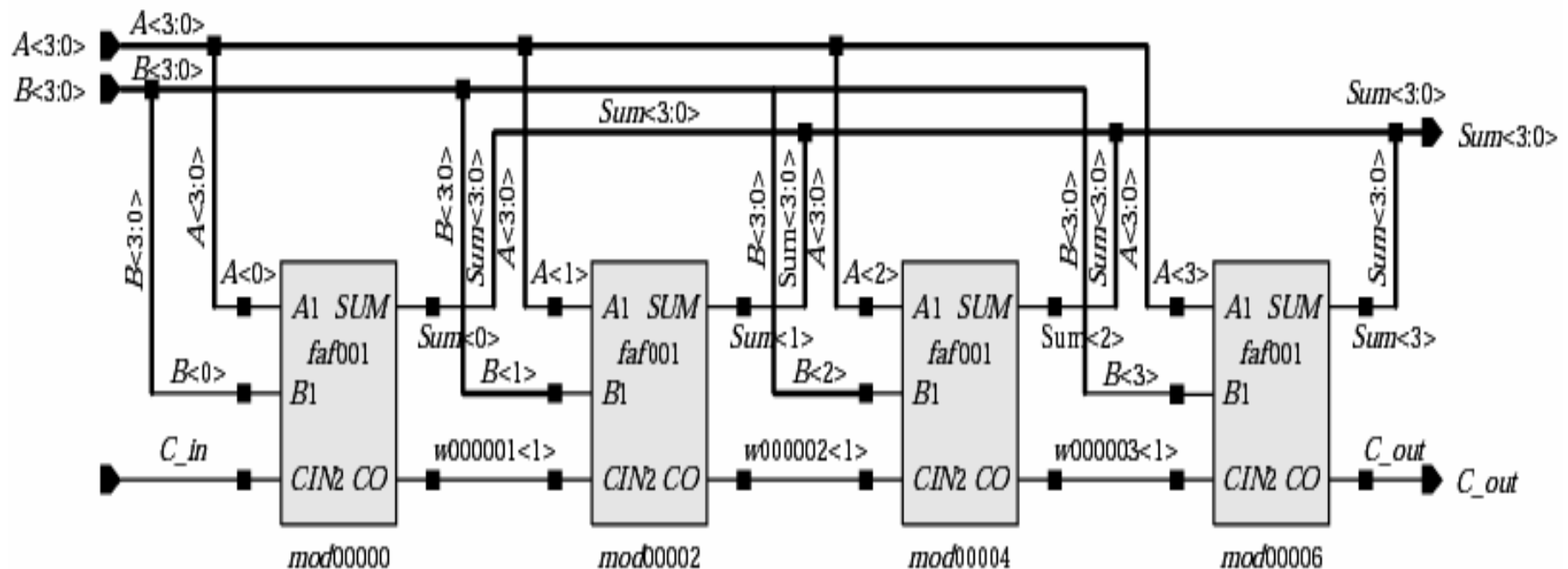
# The synthesis result of the addition operator in a full-adder ASIC library cell




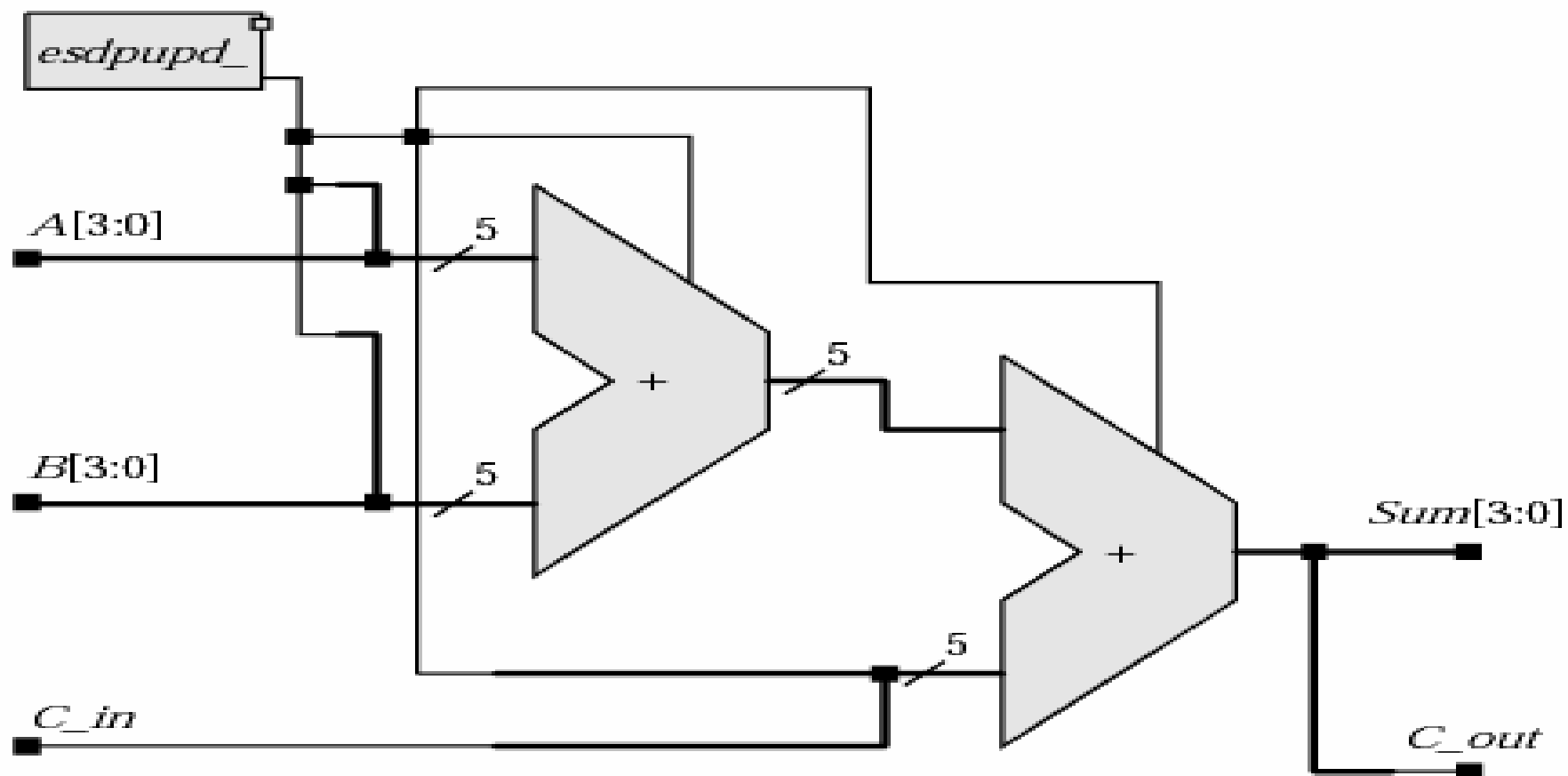
# The synthesis result of the addition operator in 5-bit adder blocks



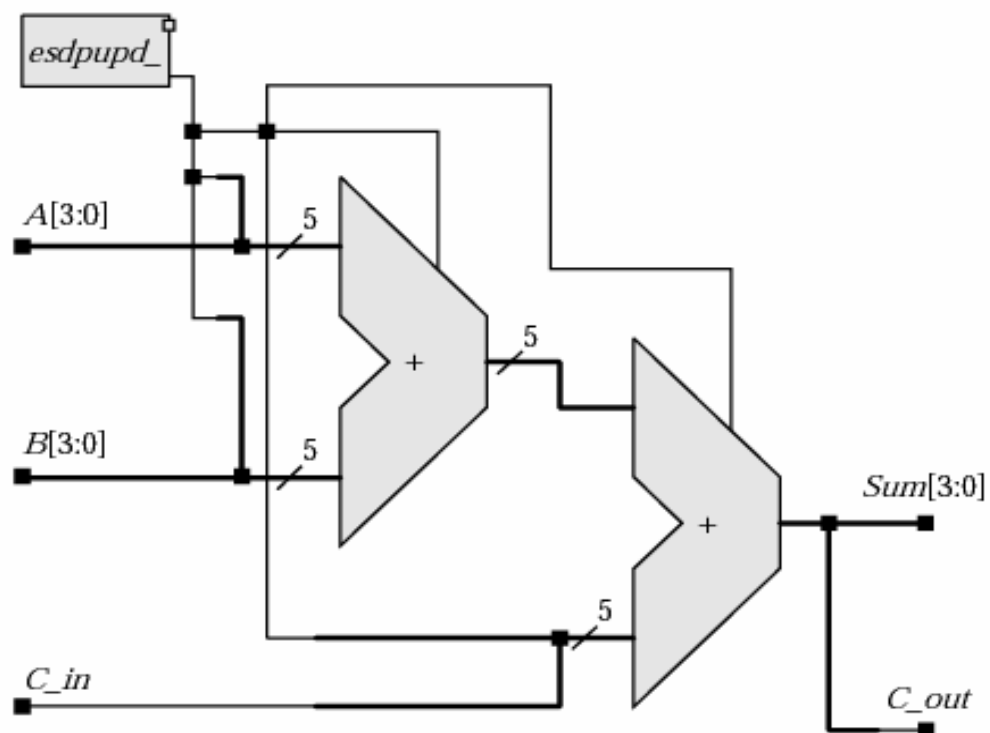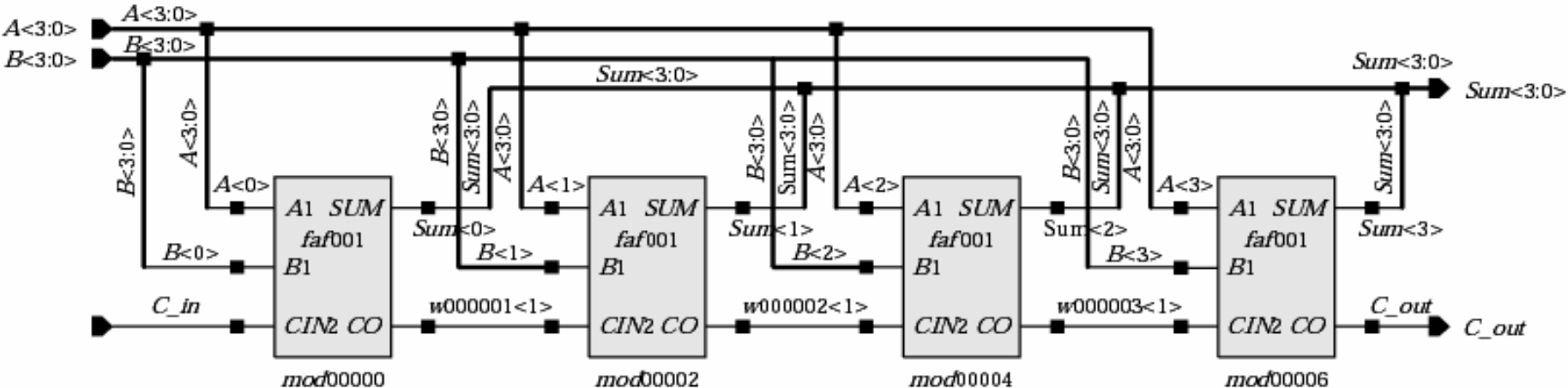



# Share resources

- For example:
- **assign y\_out =**  
    **sel ? data\_a + accum : data\_a + data\_b;**
- The operators can be implemented by a shared adder whose input datapaths are multiplexed.
- **This feature is vendor-dependent**





 
# Example: Share resources

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
  
always@(posedge clk or negedge rst)  
begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        q<=q+1;  
    else  
        q<=q-1;  
    end  
endmodule
```

- *Up/Down Counter*
- *Quartus recognizes this code as a counter and will implement it efficiently, but not all tools will recognize it.*





 
# Share resources

```
module test(rst, clk, updn, q);  
input rst, clk, updn;  
output [7:0] q;  
reg [7:0] q;  
integer dir;  
  
always@(posedge clk or negedge  
rst)begin  
    if (!rst)  
        q<=0;  
    else if (updn)  
        dir<=1;  
    else  
        dir<=-1;  
    q<=q+dir;  
end  
endmodule
```

- Up/Down Counter
- Only One Adder Required






## Ex 6.14 The use of parentheses in the description in res\_share forces the synthesis tool to multiplex the datapaths

```
module res_share (y_out,sel,data_a,data_b,accum);  
    output [4:0] y_out;  
    input [3:0] data_a,data_b,accum;  
    input  sel;  
    assign y_out=data_a+(sel?accum:data_b);  
endmodule
```


 
# Implementation of a datapath with shared resources





## 6.3 Synthesis of sequential logic with latches

- Latches are synthesized in two ways: **intentionally and accidentally**
- A **feedback-free netlist** of combinational primitives, **a set of feedback-free continuous assignments** will synthesize into latch-free combinational logic
- A continuous assignment using **a conditional operator with feedback** will synthesize into a latch



# Example 6.15

- **A cell of an SRAM memory** can be modeled by the following continuous assignment statement having feedback:

**Assign**

```
data_out=(CS_b==0)?(WE==0)?data_in:1'bz;
```



## 6.3.1 Accidental Synthesis of Latches


- **Example 6.16**

```
module or4_behav (y, x_in);  
    parameter word_length=4;  
    output y;  
    input [word_length-1:0] x_in;  
    reg y;  
    integer k;  
    always @ x_in  
        begin: check_for_1  
            y=0;  
            for (k=0;k<=word_length-1;k=k+1)  
                if (x_in[k]==1)  
                    begin y=1;  
                        disable check_for_1;  
                    end  
            end  
        end  
end  
endmodule
```


 
## Example 6.16

```
module or4_behav (y, x_in);  
    parameter word_length=4;  
    output y;  
    input [word_length-1:0] x_in;  
    reg y;  
    integer k;  
    always @ x_in  
    begin: check_for_1  
        y=0;  
        for (k=0;k<=word_length-1;k=k+1)  
            if (x_in[k]==1)  
                begin y=1;  
                    disable check_for_1;  
                end  
        end  
    end  
endmodule
```








# Example 6.16

```
module or4_behav_latch (y, x_in);  
    parameter word_length=4;  
    output y;  
    input [word_length-1:0] x_in;  
    reg y;  
    integer k;  
    always @ (x_in[3:1])  
        begin: check_for_1  
            y=0;  
            for (k=0;k<=word_length-1;k=k+1)  
                if (x_in[k]==1)  
                    begin y=1;  
                        disable check_for_1;  
                    end  
            end  
        end  
endmodule
```



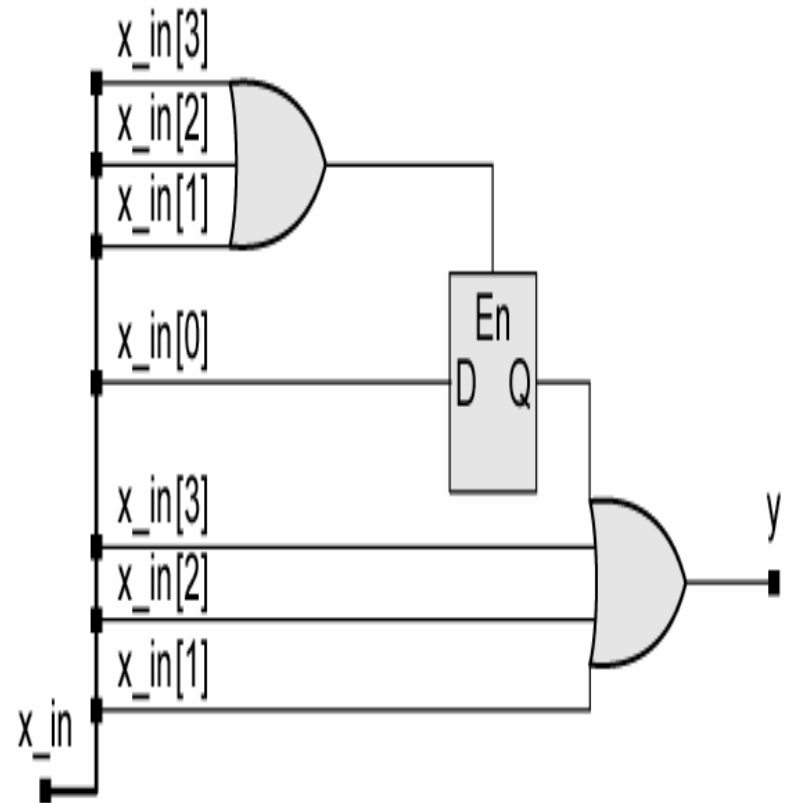
# Example 6.16

```
module or4_behav_latch (y, x_in);  
  parameter word_length=4;  
  output y;  
  input [word_length-1:0] x_in;  
  reg y;  
  integer k;  
  always @ (x_in[3:1])  
    begin: check_for_1  
      y=0;  
      for (k=0;k<=word_length-1;k=k+1)  
        if (x_in[k]==1)  
          begin y=1;  
          disable check_for_1;  
        end  
      end  
    endmodule
```





# Simulation result

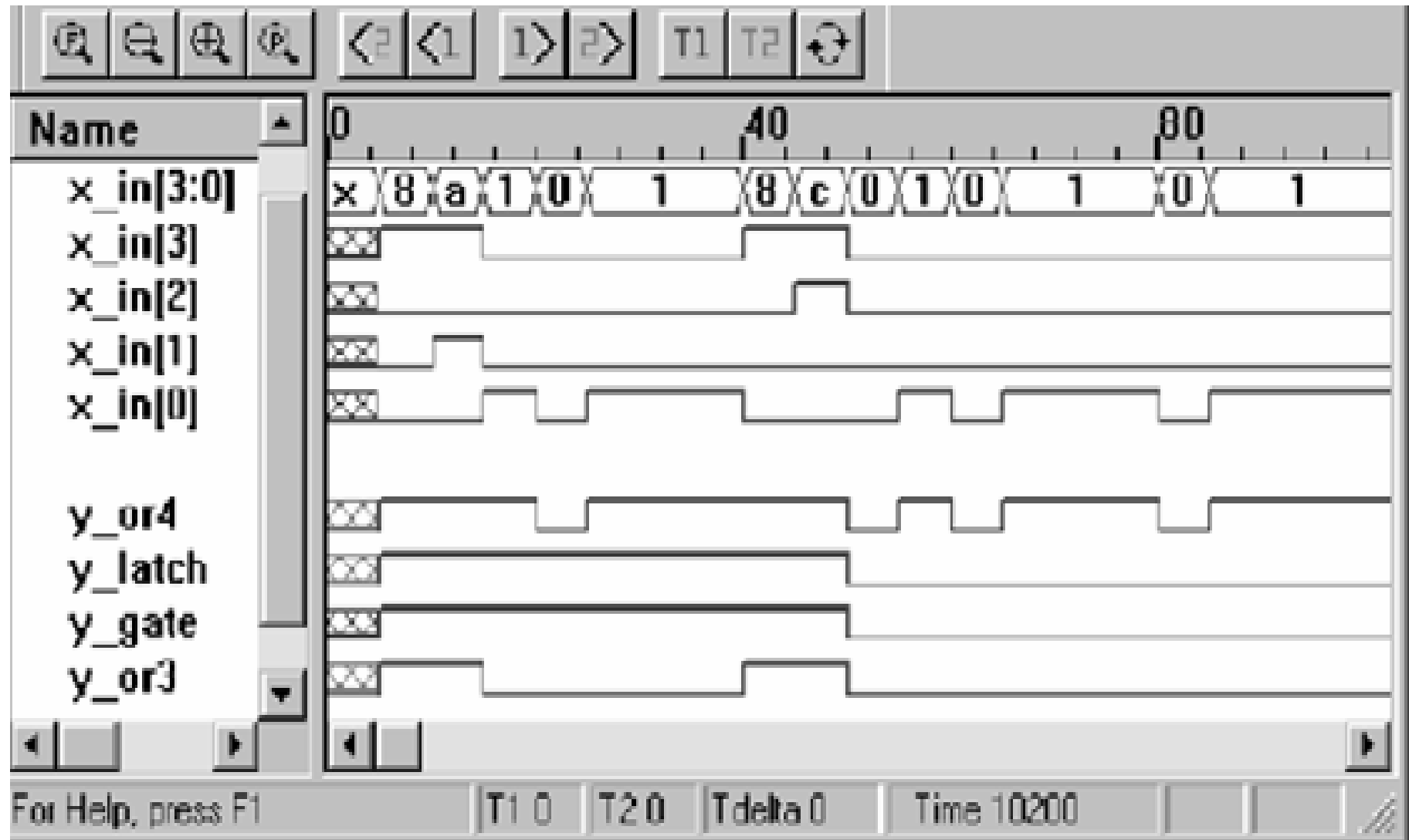



# To avoid latches

- All of the variables that are assigned value by the behavior must be assigned value under all events that affect the right-hand side expressions of the assignments that implement the logic
- **Failure to do so will produce a design with unwanted latches**



# Remember

- If the output of **combinational logic** is not completely specified for all cases of the inputs, then a latch will be inferred, **a same signal will not appear on both sides of a level-sensitive cyclic behavior**



# Synthesis tips

- A Verilog description of **combinational logic** must assign value to the outputs for all possible values of the inputs
- **When *case* or *if* statements are incompletely specified ,it may lead to synthesis of unwanted latches in the design**




## Example 6.17

```
module mux_latch
    (y_out,sel_a,sel_b,data_a,data_b);
output y_out;
input sel_a,sel_b,data_a,data_b;
reg y_out;
always @ (sel_a or sel_b or data_a or data_b)
    case ({sel_a,sel_b})
        2'b10: y_out=data_a;
        2'b01: y_out=data_b;
    endcase
endmodule
```



 
# Synthesized circuit using generic parts






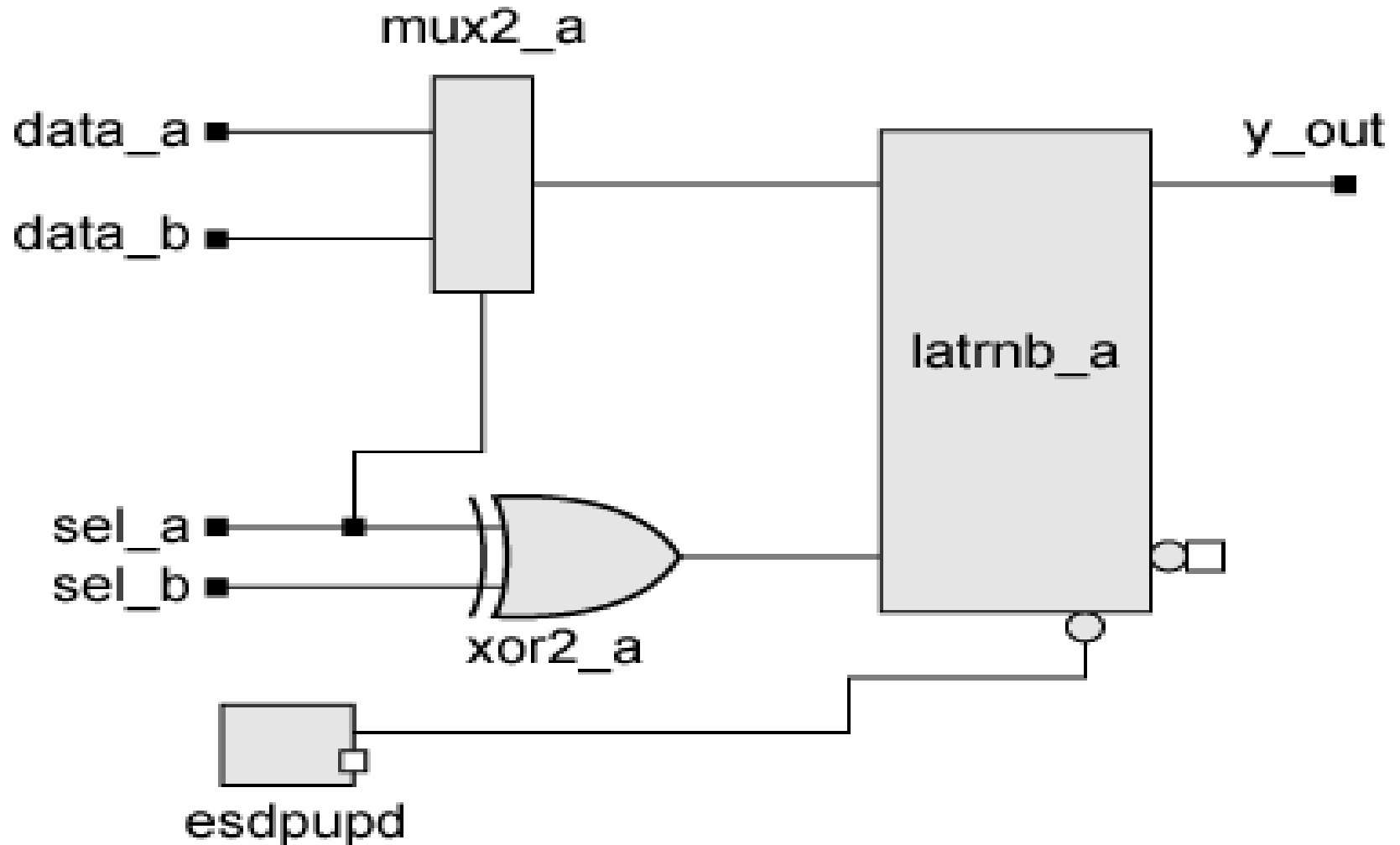
# Synthesized circuit using parts from a cell library





## 6.3.2 Intentional synthesis of latches

- A synthesis tool infers the need for a latch **when a register variable in a level-sensitive behavior is assigned value in some threads of activity, but not in others**
- (e.g., an incomplete **if statement** in a behavior)



# if & case statement

- **If a case statement has a default assignment with feedback**, the synthesis tool will form a mux structure with feedback
- **If an if statement in a level-sensitive behavior assigns a variable to itself**, the result will be a mux structure with feedback
- **If the behavior is edge-sensitive, incomplete case and conditional statements** synthesize register variables to flip-flops
- **If the statements are completed with feedback**, the result is a register whose output is fed back through a mux at its datapath



# Implemented of ( $? \dots : \dots$ )

- when the conditional operator ( $? \dots : \dots$ ) is implemented with feedback, but the actual implementation chosen by a synthesis tool **depends on the context**
- 1. If the conditional operator is used **in a continuous assignment**, the result will be a mux with feedback
- 2. If the conditional operator is used **in an edge-sensitive cyclic behavior**, the result will be a register with a gated data path in a feedback configuration with the output of the register
- 3. If it is used **in a level-sensitive cyclic behavior**, the results will be a hardware latch




## Example 6.18

```
module latch_if (data_out,data_in,latch_enable);  
    output [3:0] data_out;  
    input [3:0] data_in;  
    input latch_enable;  
    reg [3:0] data_out;  
    always @ (latch_enable or data_in)  
        if (latch_enable) data_out=data_in;  
        else data_out=data_out;  
endmodule
```

**If an *if statement* in a level-sensitive behavior assigns a variable to itself, the result will be a mux structure with feedback**



# Synthesized circuit

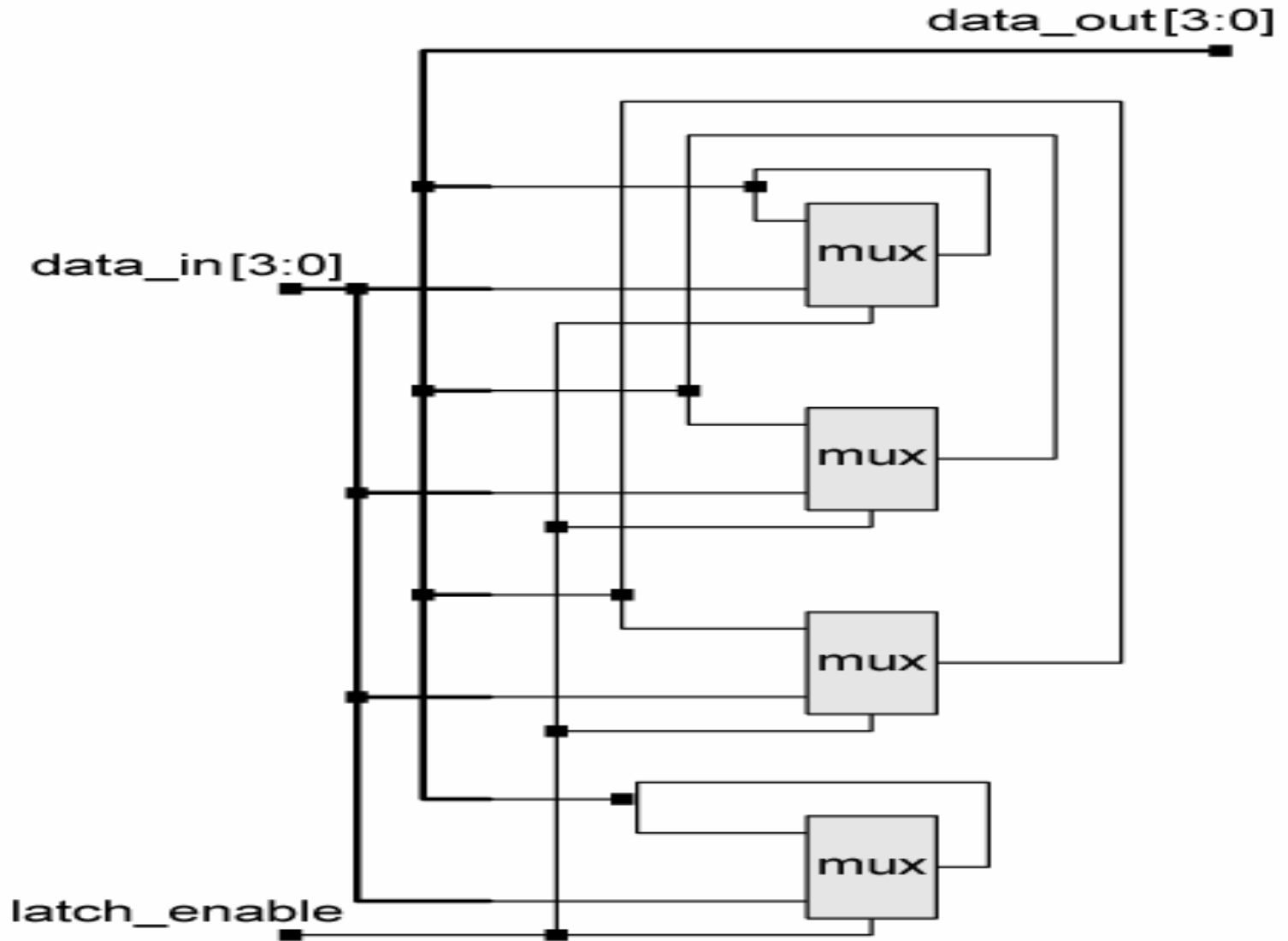



# Synthesis tips

- An ***if statement*** in a level-sensitive behavior will synthesize to a latch,  
**if the statement assigns value to a register variable in some, but not all, branches**



# Example 6.19


```
module latch_if (data_out,data_in,latch_enable);  
    output [3:0] data_out;  
    input [3:0] data_in;  
    input latch_enable;  
    reg [3:0] data_out;  
    always @ (latch_enable or data_in)  
        if (latch_enable) data_out=data_in;  
endmodule
```

If *an if statement* is used **in a level-sensitive cyclic behavior** (if the statement assigns value to a register variable **in some, but not all**), the results will be **a hardware latch**





# Synthesized circuit

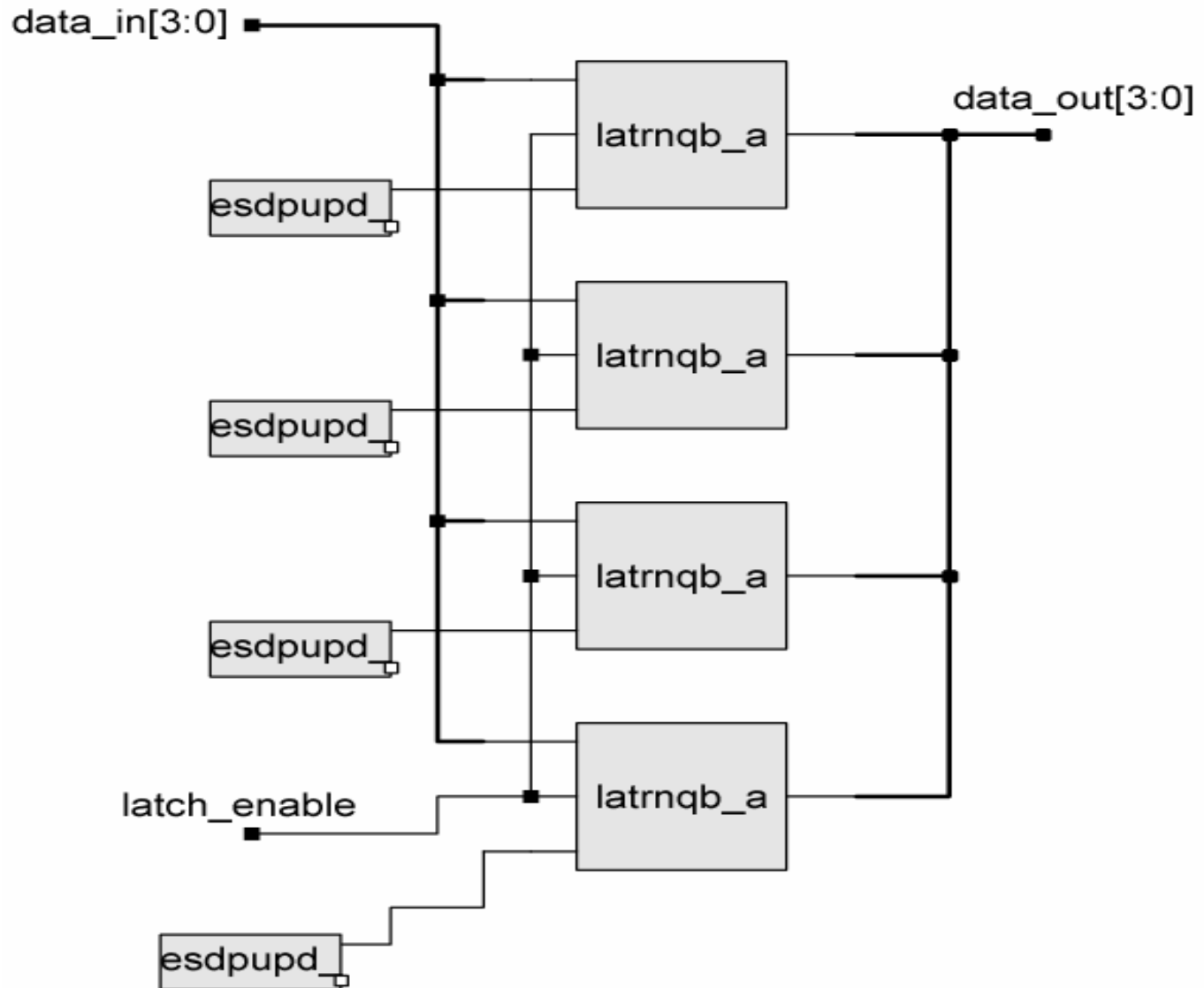




## Example 6.20
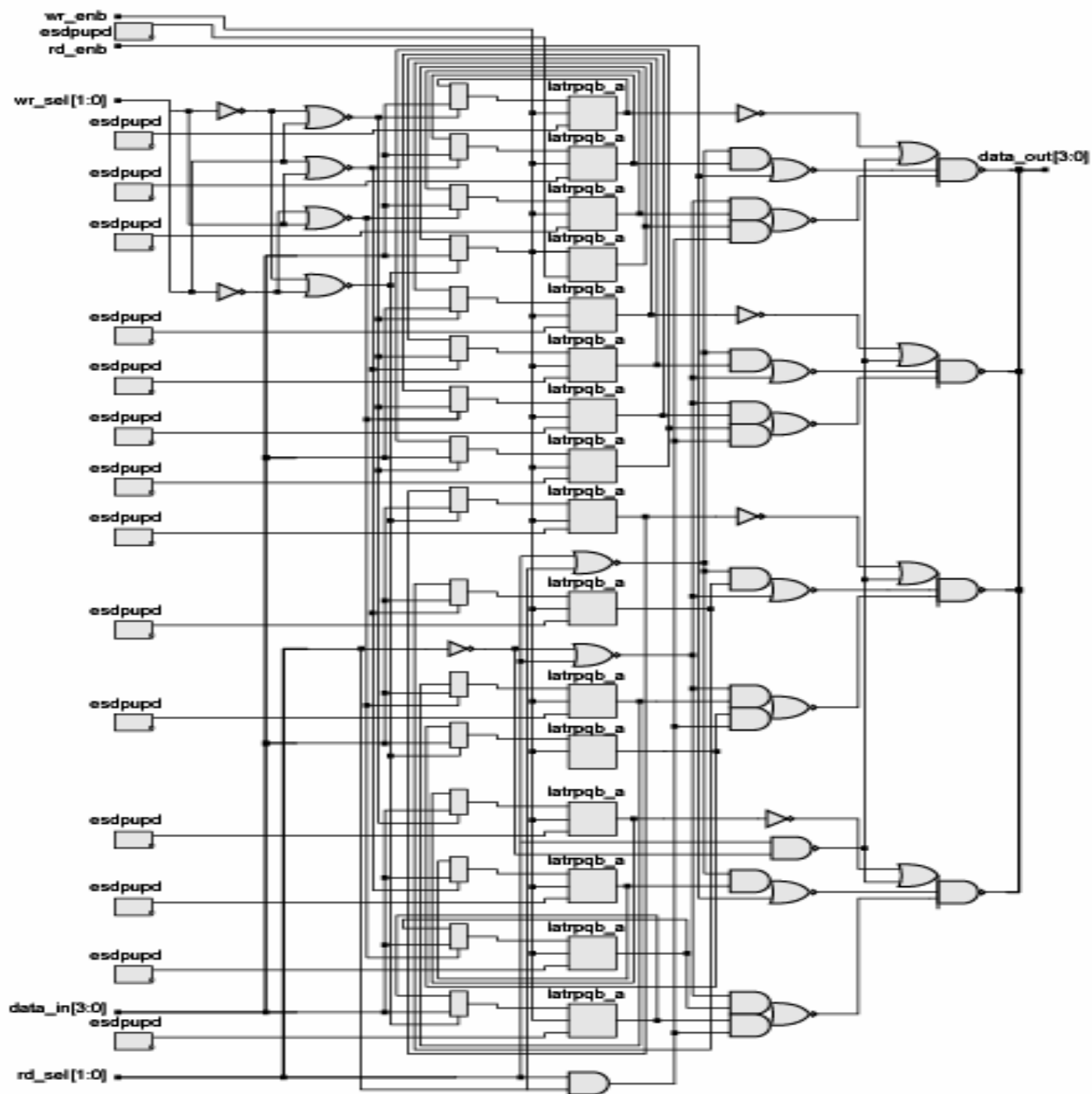
### an array of four 4-bit words

```
module sn54170
  (data_out,data_in,wr_sel,rd_sel,wr_enb,rd_enb);
  output [3:0] data_out;
  input wr_enb,rd_enb;
  input [1:0] wr_sel,rd_sel;
  input [3:0] data_in;
  reg [3:0] latched_data;
  always @ (wr_enb or wr_sel or data_in)
    begin
      if (!wr_enb) latched_data[wr_sel]=data_in;
    end
  assign data_out = (rd_enb) ? 4'b1111 : latched_data[rd_sel];
endmodule
```





## 6.4 Synthesis of three-state devices and bus interfaces

- Three-state device allow buses to be shared among multiple devices
- The preferred style for inferring a three-state bus driver **uses a continuous assignment statement** that has one branch set to a three-state logic value (**z**)




## Ex 6.21 a three-state unidirectional interface to a bus

```
module Uni_dir_bus (data_to_bus,bus_unable);  
    input bus_enable;  
    output [31:0] data_to_bus;  
    reg [31:0] ckt_to_bus;  
    assign  
        data_to_bus=(bus_enabled) ?ckt_to_bus:32'bz;  
    // Description of core circuit goes here to drive ckt_to_bus  
endmodule
```

- a continuous assignment statement that has one branch set to a three-state logic value (**z**)


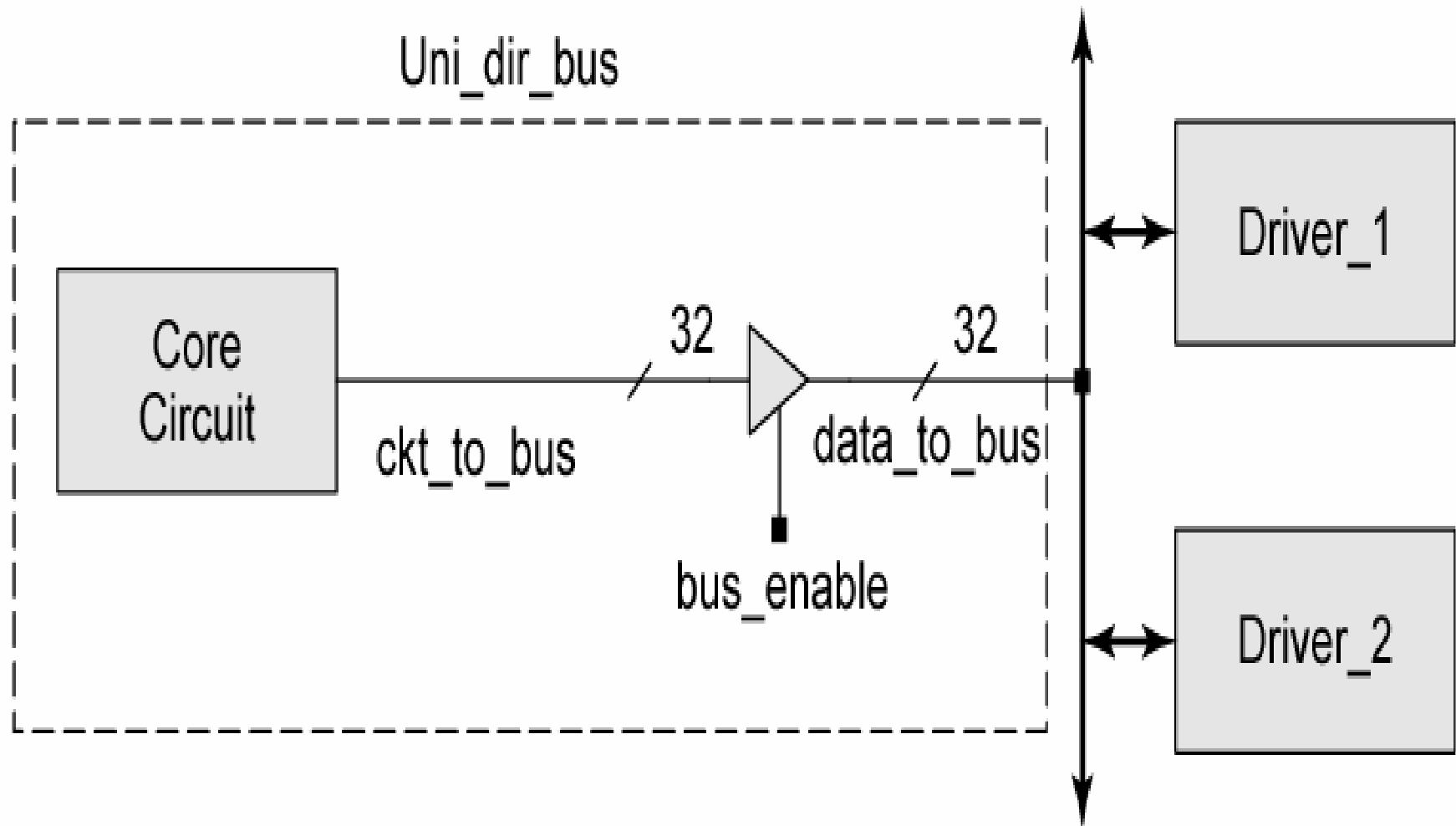
# A three-state unidirectional interface to a bus






## Ex 6.22 bidirectional interface to a bidirectional bus

```
module Bi_dir_bus (data_to_from_bus,send_data,rcv_data);  
    inout [31:0] data_to_from_bus;  
    input  send_data,rcv_data;  
    wire [31:0] ckt_to_bus;  
    wire [31:0] data_to_from_bus,data_from_bus;  
    assign data_from_bus=(rcv_data)?data_to_from_bus:32'bz;  
    assign data_to_from_bus=  
        (send_data)?ckt_to_bus:data_to_from_bus;  
    // Behavior using data_from_bus and generating  
    // ckt_to_bus goes here  
endmodule
```


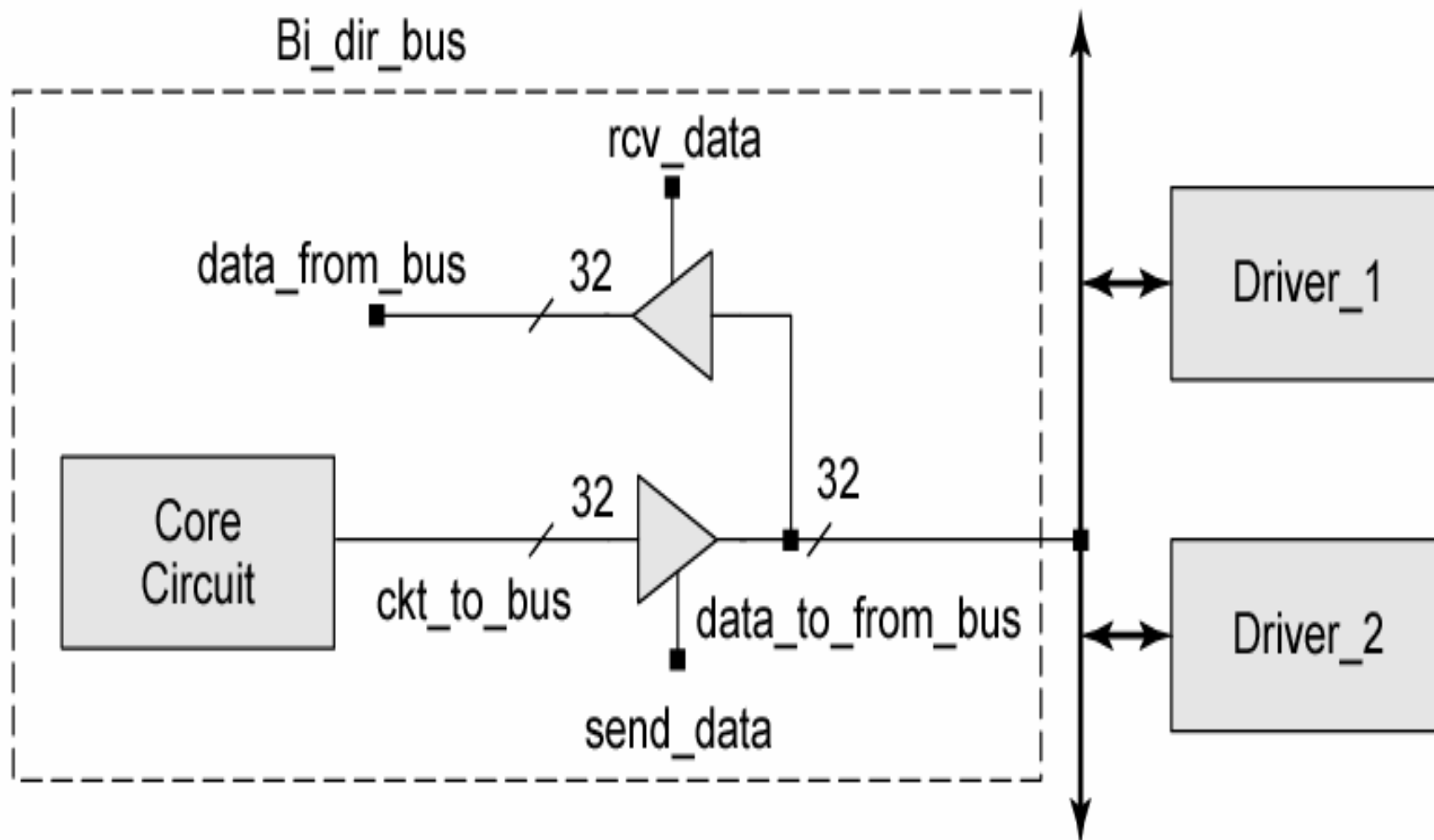
# bidirectional interface to a bidirectional bus







## 6.5 Synthesis of sequential logic with flip-flops

- Flip-flops are synthesized only from edge-sensitive cyclic behaviors
- Not every register variable that is assigned value in an edge-sensitive behavior synthesizes to a flip-flop



# A register variable in an edge-sensitive behavior

- **Synthesized as a flip-flop:**
  - ① If it is referenced outside the scope of the behavior
  - ② If it is referenced within the behavior before it is assigned value
  - ③ If it is assigned value in only some of the **branches** of the activity within the behavior
- **All of these situations imply the need for memory, or residual value**




## Ex 6.23 A synchronous data swapping mechanism

```
module swap_synch (data_a,data_b,set1,set2,clk);  
    output data_a,data_b;  
    input clk,set1,set2,swap;  
    reg data_a,data_b;  
    always @ (posedge clk)  
        begin  
            if (set1) begin data_a<=1;data_b<=0; end  
            else if (set2) begin data_a<=0;data_b<=1; end  
            else begin  
                data_b<=data_a; data_a<=data_b;  
            end  
        end  
endmodule
```



# Fig 6-29 synthesis circuit

 




## Ex 6.24 A 4-bit parallel-load data register

```
module D_reg4_a (Data_out, clock, reset, Data_in);  
    output          [3: 0] Data_out;  
    input           [3: 0] Data_in;  
    input           clock, reset;  
    reg             [3: 0] Data_out;  
    always @ (posedge clock or posedge reset)  
    begin  
        if (reset == 1'b1) Data_out <= 4'b0;  
        else Data_out <= Data_in;  
    end  
endmodule
```


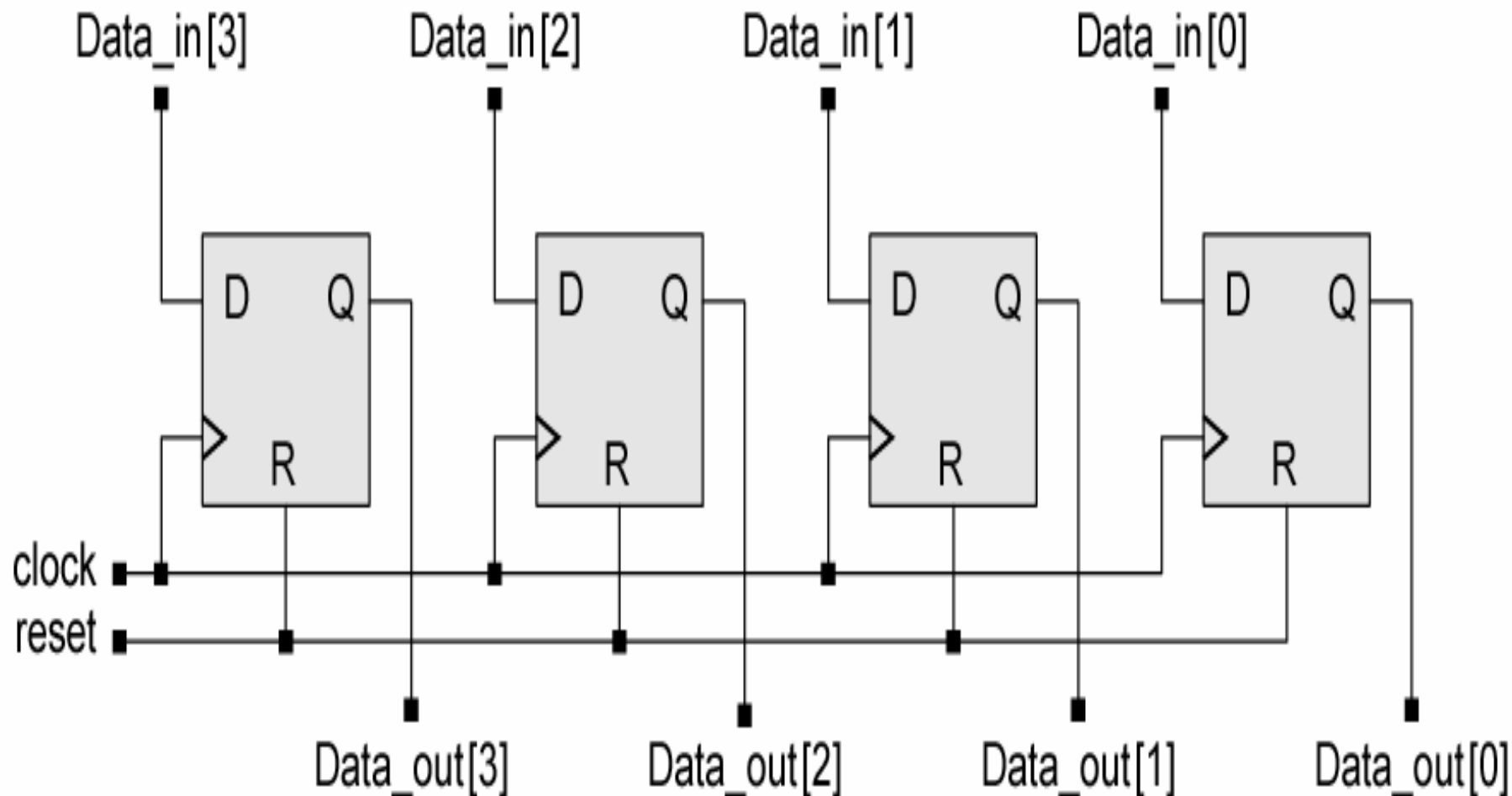
# Synthesis circuit of a 4-bit parallel-load data register





## Example 6.25

```
module empty_circuit (D_in,clk);  
    input D_in;  
    input clk;  
    reg D_out;  
    always @ (posedge clk) begin  
        D_out<=D_in;  
    end  
endmodule
```



## Example 6.25

```
module empty_circuit (D_in,clk);  
    input D_in;  
    input clk;  
    reg D_out;  
    always @ (posedge clk) begin  
        D_out<=D_in;  
    end  
endmodule
```

The synthesis tool will **eliminate D\_out**.

**D\_out** is not referenced outside the scope  
of the behavior





# Synthesis tips

- A variable that is assigned value by a cyclic behavior **before it is referenced within the behavior, but is not referenced outside the behavior, will be eliminated by the synthesis process**
- A variable that **is assigned value by an edge-sensitive behavior and is referenced outside the behavior** will be synthesized as the output of a flip-flop




## 6.6 Synthesis of explicit state machines

- Explicit machine have **an explicitly declared state register and explicit logic** that governs the evolution of the state under the influence of the inputs
- Be described by two behaviors:
  1. **an edge-sensitive behavior that synchronizes the evolution of the state**
  2. **a level sensitive behavior that describe the next state and output logic**



# State Machines

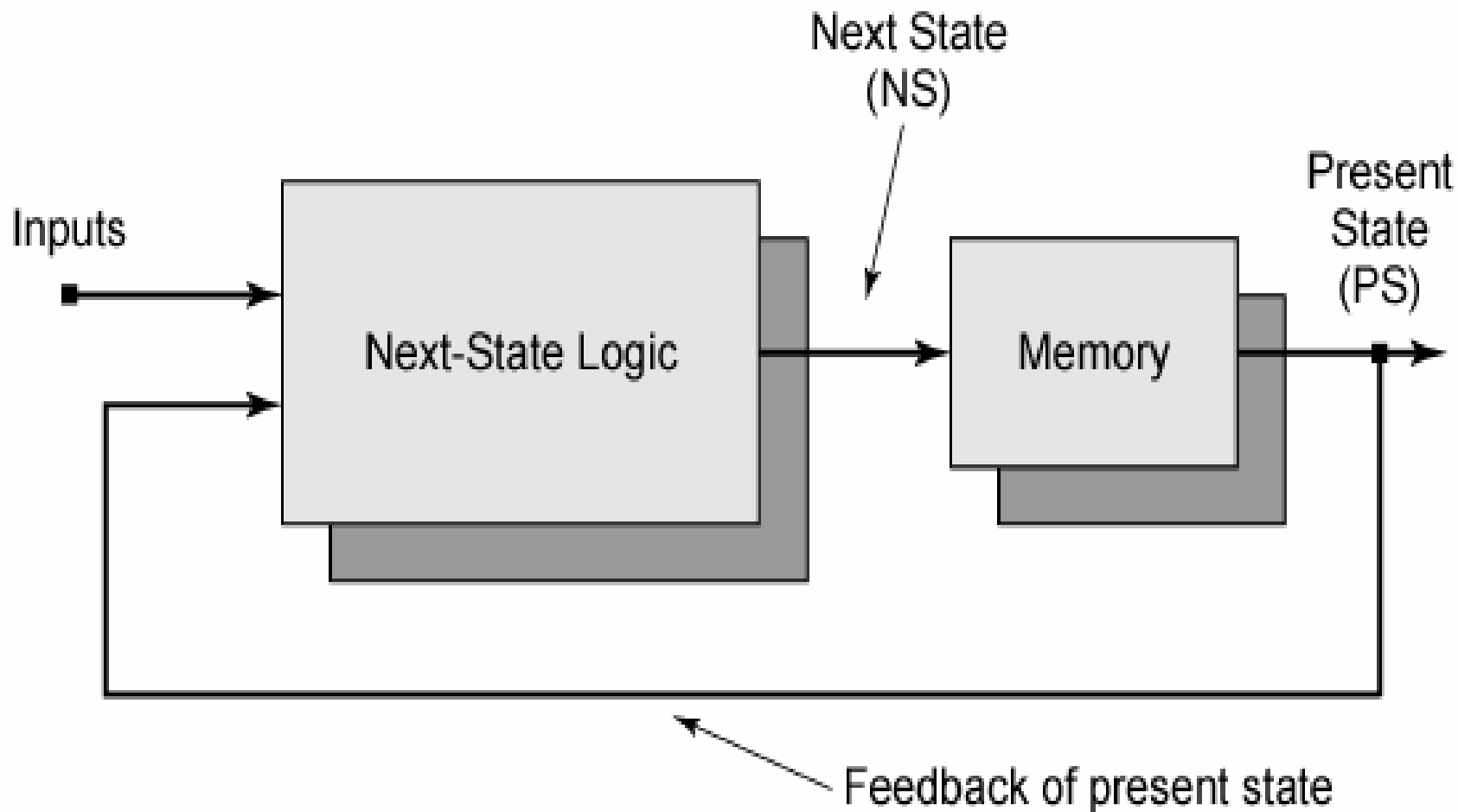



# Finite State Machines

- **Moore State Machines:**

**Outputs Are a Function of the States Only**



Isolates the Outputs from the Inputs

- **Mealy State Machines:**

**Outputs are a Function of the Inputs as well as the States.**



# Mealy & Moore State Machine

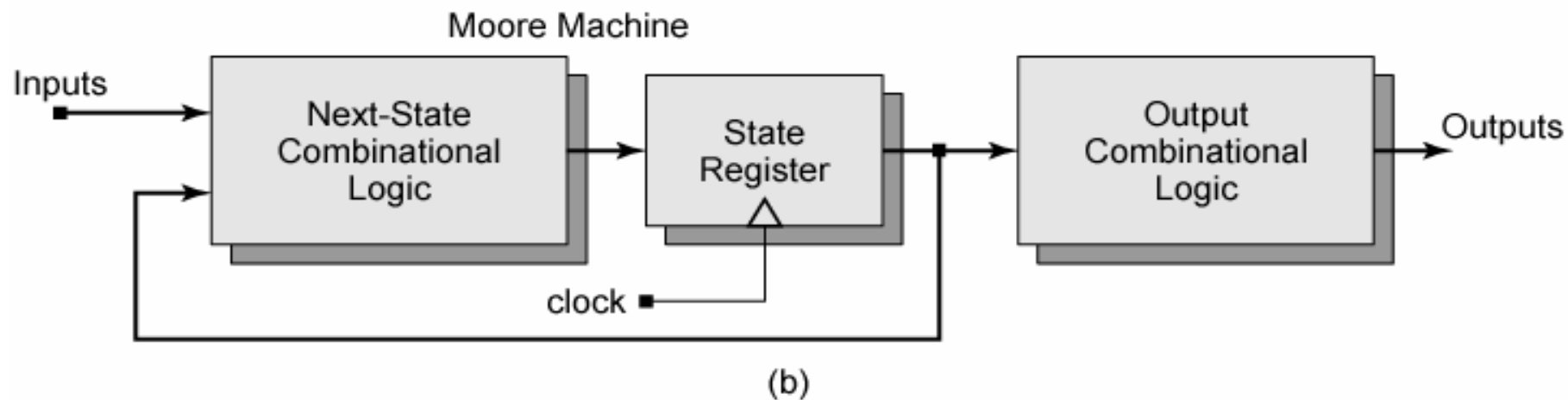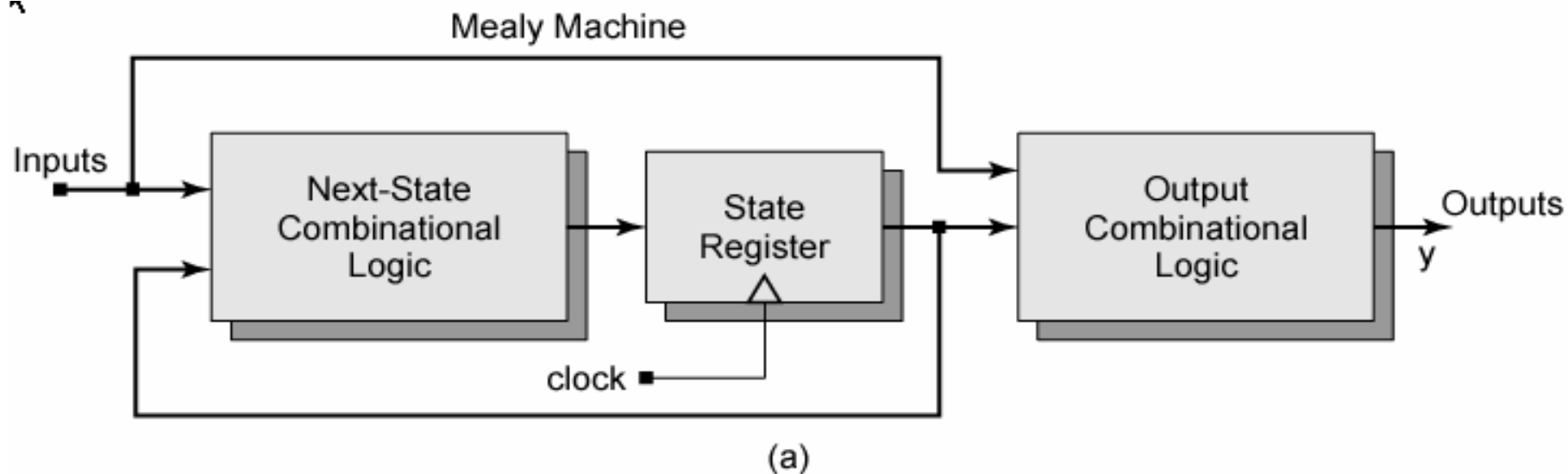



# Synthesis Tip

- **Use two cyclic behaviors to describe an explicit state machine:**
- **a level-sensitive behavior to describe the combinational logic for the next state and outputs:**  
Use the procedural assignment operator(=)
- **an edge-sensitive behavior to synchronize the state transitions:**  
Use the nonblocking assignment operator (<=)



## 6.6.1 Synthesis of a BCD-to-excess-3 code converter

- ✓ An Excess-3 code word is obtained by adding 3 to the decimal value of the BCD word and taking the binary equivalent of the result

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1



# Formulation: BCD to Excess 3

**Conversion of 4-bit codes can be most easily formulated by a truth table**


- Variables  
- BCD:  
A,B,C,D
- Variables  
- Excess-3  
W,X,Y,Z
- Don't Cares  
- BCD  
1010 to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1





# A BCD-to-Excess-3 Code Converter

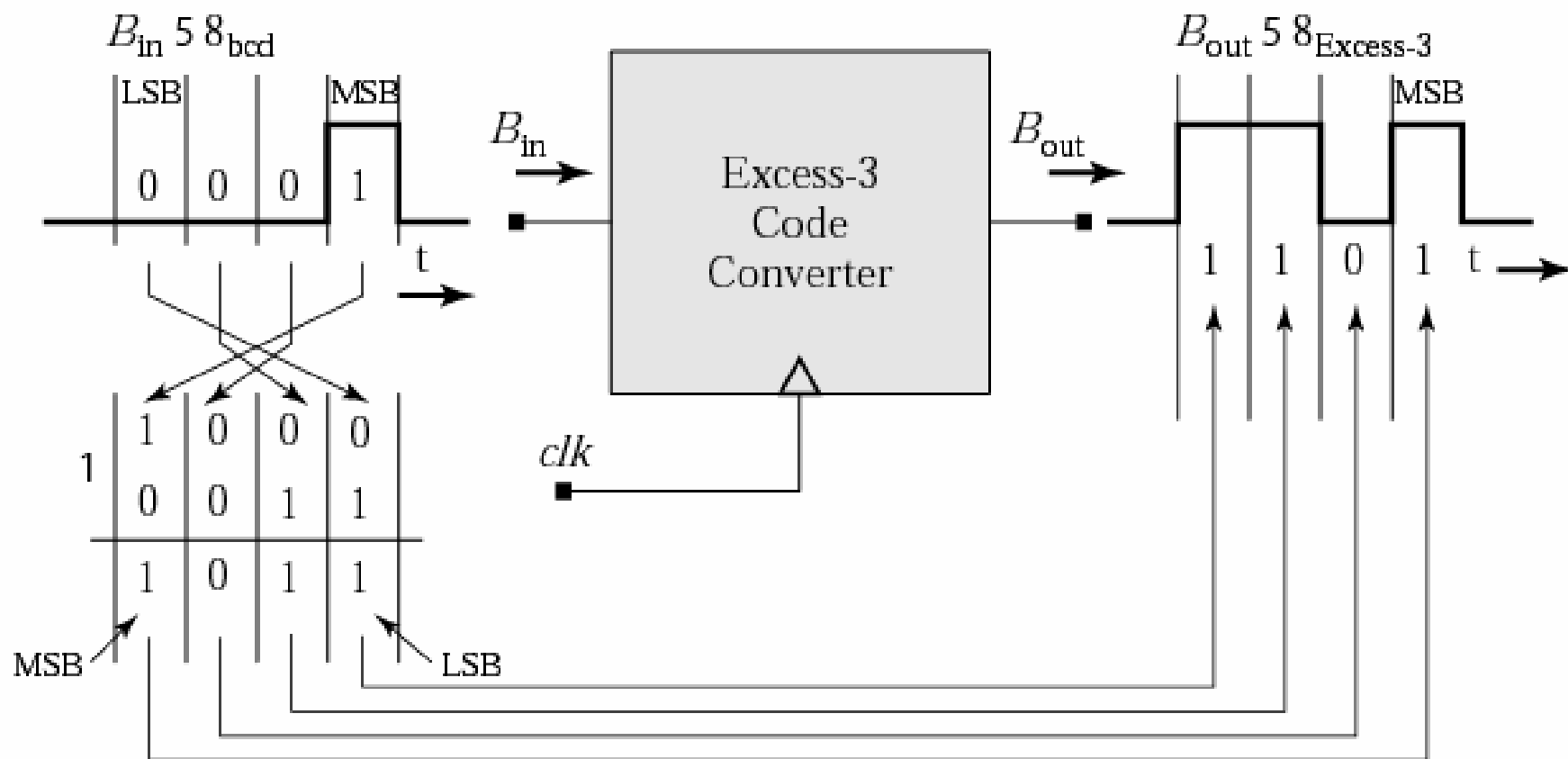



# Basic steps

- (1) forming a state-transition graph
- (2) defining a state table
- (3) choosing a state assignment
- (4) encoding the next state and output table
- (5) developing and minimizing the Karnaugh maps for the encoded state bits and output
- (6) creating the circuit's implementation (schematic).




# Mealy type FSM:

(a) state transition

(b) the machine's state table

Input BCD A B C D	Output Excess-3 WXYZ
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1

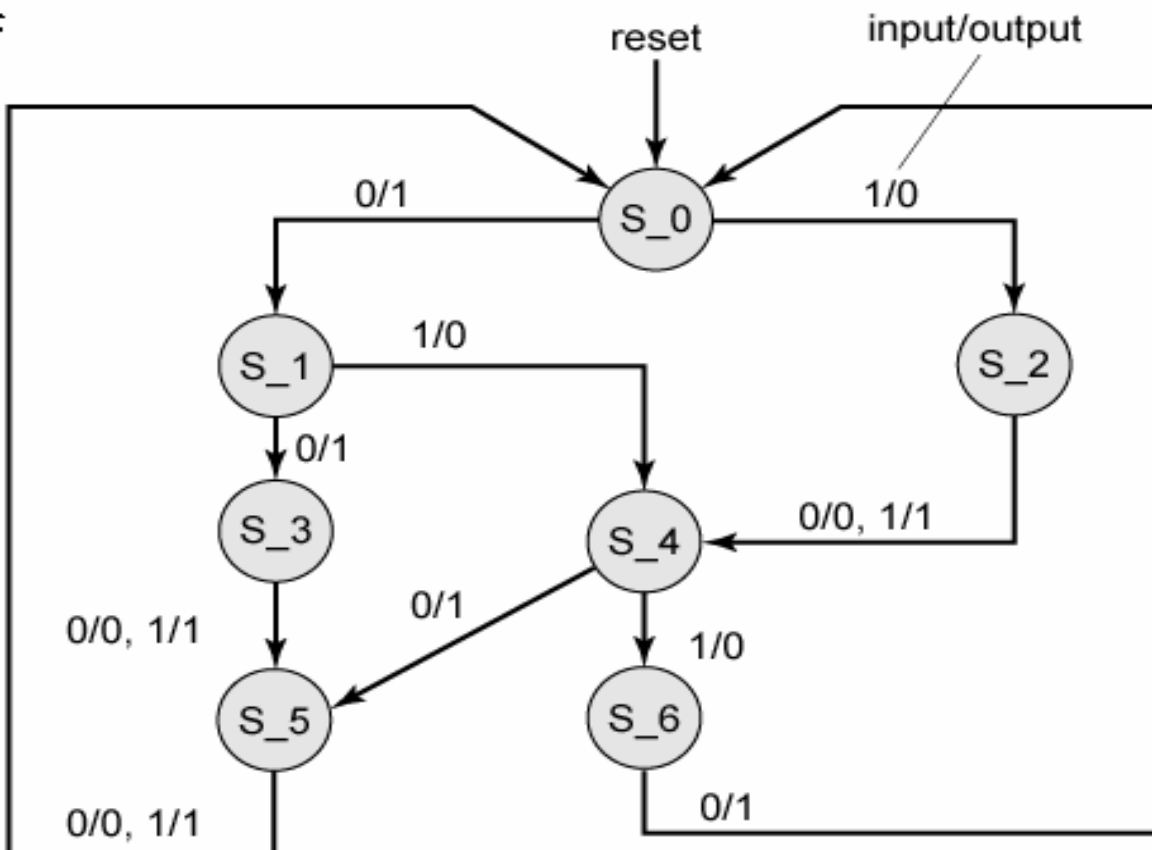

(a)

Next State/Output Table		
state	next state/output	
	input	
	0	1
S_0	S_1/1	S_2/0
S_1	S_3/1	S_4/0
S_2	S_4/0	S_4/1
S_3	S_5/0	S_5/1
S_4	S_5/1	S_6/0
S_5	S_0/0	S_0/1
S_6	S_0/1	- / -

(b)



# BCD-to-Excess-3 Code Converter

## (a) state assignment

## (b) encoded next state & out table

State Assignment	
$q_2 q_1 q_0$	State
000	S_0
001	S_1
010	S_6
011	S_4
100	
101	S_2
110	S_5
111	S_3

(a)

Encoded Next State / Output Table					
	State	Next State		Output	
	$q_2\ q_1\ q_0$	$q_2^1\ q_1^1\ q_0^1$			
		Input		Input	
		0	1	0	1
S_0	000	001	101	1	0
S_1	001	111	011	1	0
S_2	101	011	011	0	1
S_3	111	110	110	0	1
S_4	011	110	010	1	0
S_5	110	000	000	0	1
S_6	010	000	—	1	—
	100	—	—	—	—

(b)



# A BCD-to-Excess-3 Code Converter


```
module BCD_to_Excess_3b (B_out, B_in,clk,reset_b);  
  output B_out;  
  input B_in,clk,reset_b;  
  parameter    S_0=3'b000,      // state assignment  
                S_1=3'b001,  
                S_2=3'b101,  
                S_3=3'b111,  
                S_4=3'b011,  
                S_5=3'b110,  
                S_6=3'b010,  
                dont_care_state=3'bx,  
                dont_care_out=1'bx;  
  reg [2:0]    state,next_state;  
  reg          B_out;  
  always @ (posedge clk or negedge reset_b)  
    if (reset_b==0) stae<=S_0; else state<=next_state;
```



```
always @ (state or B_in) begin // determine next state  
    B_out=0;  
    case (state)  
        S_0: if (B_in==0) begin next_state=S_1;B_out=1; end  
             else if (B_in==1) begin next_state=S_2; end  
        S_1: if (B_in==0) begin next_state=S_3;B_out=1; end  
             else if (B_in==1) begin next_state=S_4; end  
        S_2: begin next_state=S_4; B_out=B_in; end  
        S_3: begin next_state=S_5; B_out=B_in; end  
        S_4: if (B_in==0) begin next_state=S_5;B_out=1; end  
             else if (B_in==1) begin next_state=S_6; end  
        S_5: begin next_state=S_0; B_out=B_in; end  
        S_6: begin next_state=S_0; B_out=1; end  
    endcase  
end  
endmodule
```




# Simulation of BCD\_to\_Excess\_3b

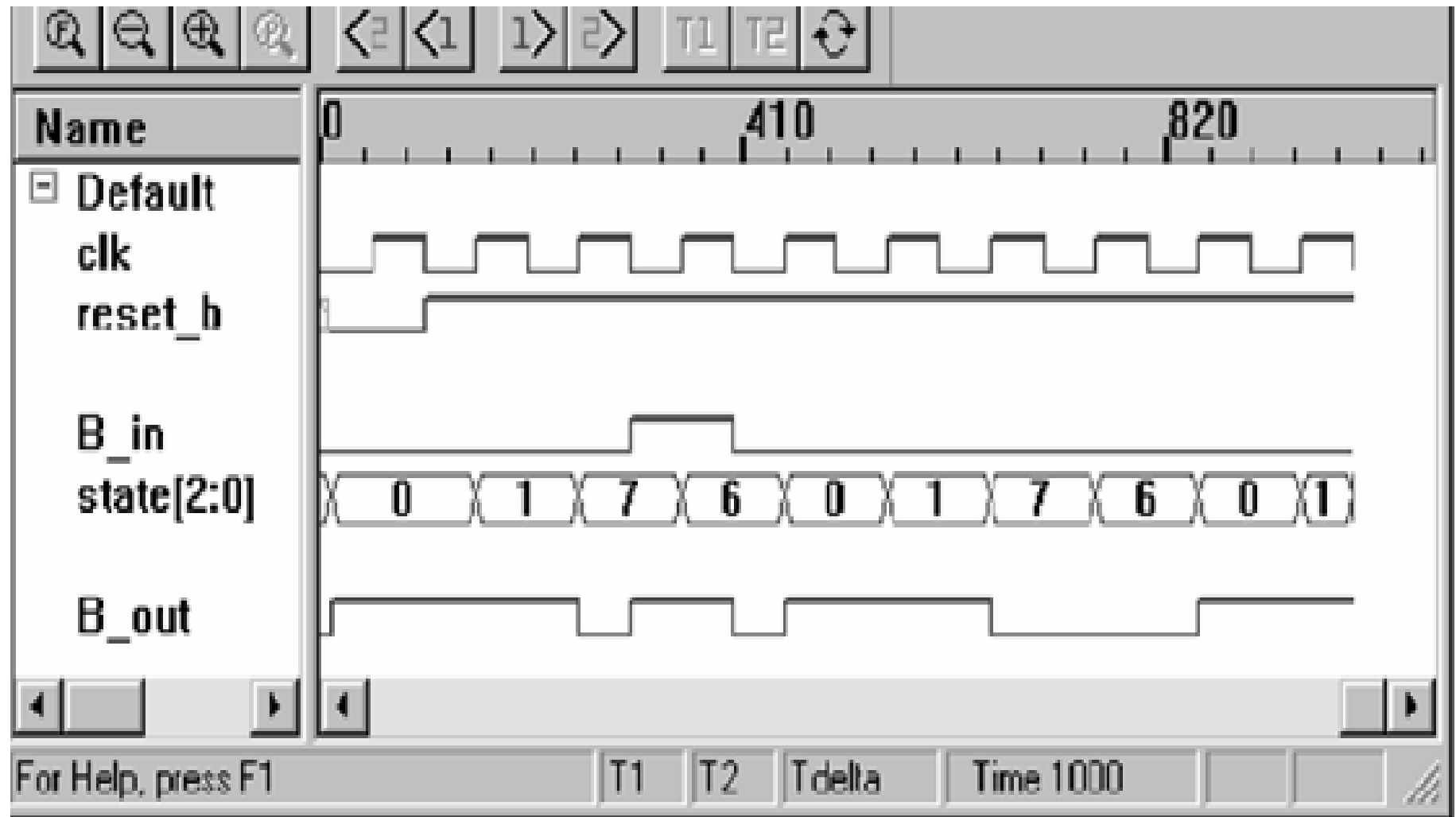


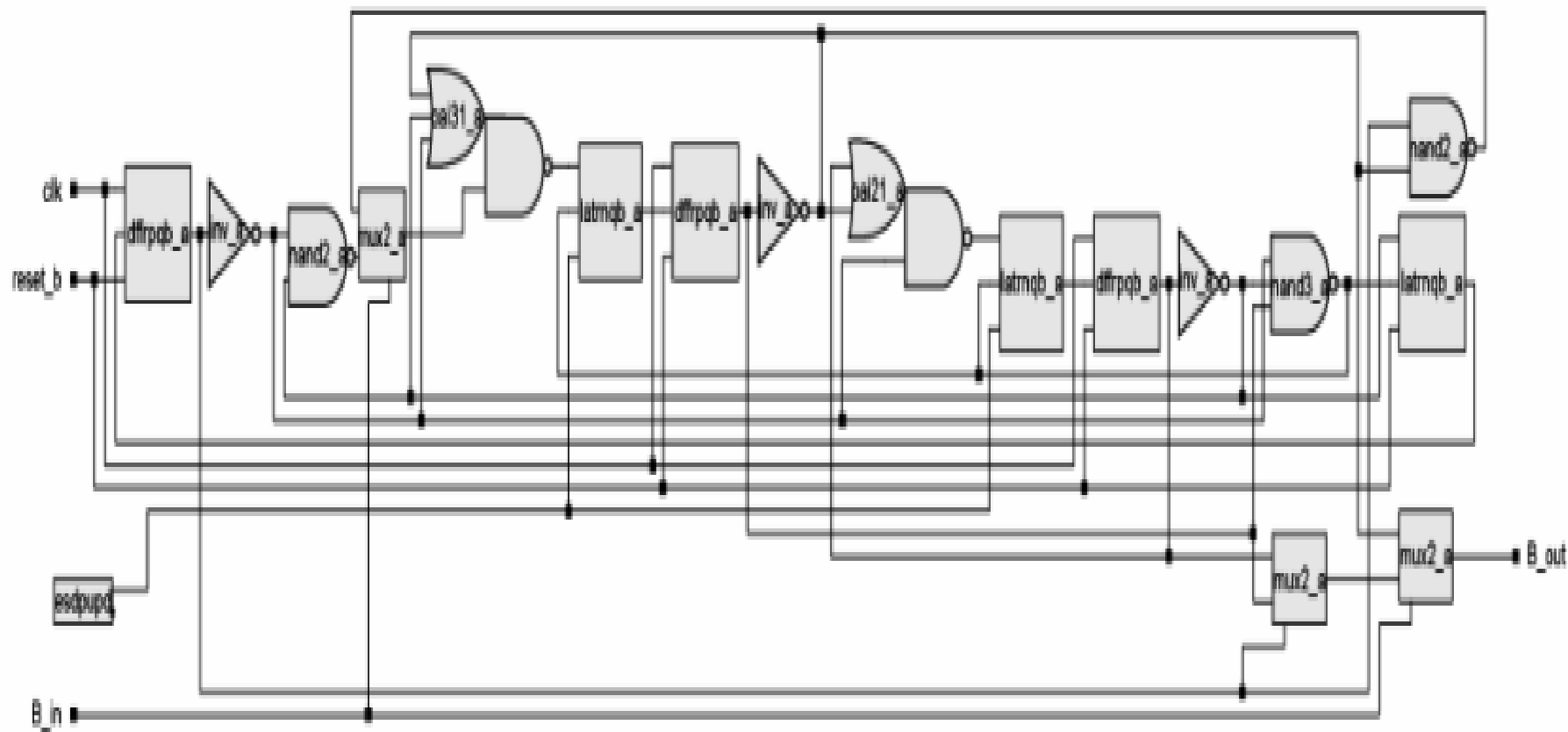
# Circuit synthesized from BCD\_to\_Excess\_3b



(a)






```
module BCD_to_Excess_3c (B_out, B_in,clk,reset_b);  
    output B_out;  
    input B_in,clk,reset_b;  
    parameter    S_0=3'b000,    // state assignment  
                S_1=3'b001,  
                S_2=3'b101,  
                S_3=3'b111,  
                S_4=3'b011,  
                S_5=3'b110,  
                S_6=3'b010,  
                dont_care_state=3'bx,  
                dont_care_out=1'bx;  
    reg [2:0]    state,next_state;  
    reg          B_out;  
    always @ (posedge clk or negedge reset_b)  
        if (reset_b==0) stae<=S_0; else state<=next_state;
```




```
always @ (state or B_in) begin  
    B_out=0;  
    case (state)  
        S_0: if (B_in==0) begin next_state=S_1;B_out=1; end  
             else if (B_in==1) begin next_state=S_2; end  
        S_1: if (B_in==0) begin next_state=S_3;B_out=1; end  
             else if (B_in==1) begin next_state=S_4; end  
        S_2: begin next_state=S_4; B_out=B_in; end  
        S_3: begin next_state=S_5; B_out=B_in; end  
        S_4: if (B_in==0) begin next_state=S_5;B_out=1; end  
             else if (B_in==1) begin next_state=S_6; end  
        S_5: begin next_state=S_0; B_out=B_in; end  
        S_6: begin next_state=S_0; B_out=1; end  
            default: beign next_state=dont_care_state;  
            B_out=dont_care_out;  
    end  
    endcase  
end  
endmodule
```



# Simulation of BCD\_to\_Excess\_3c

 

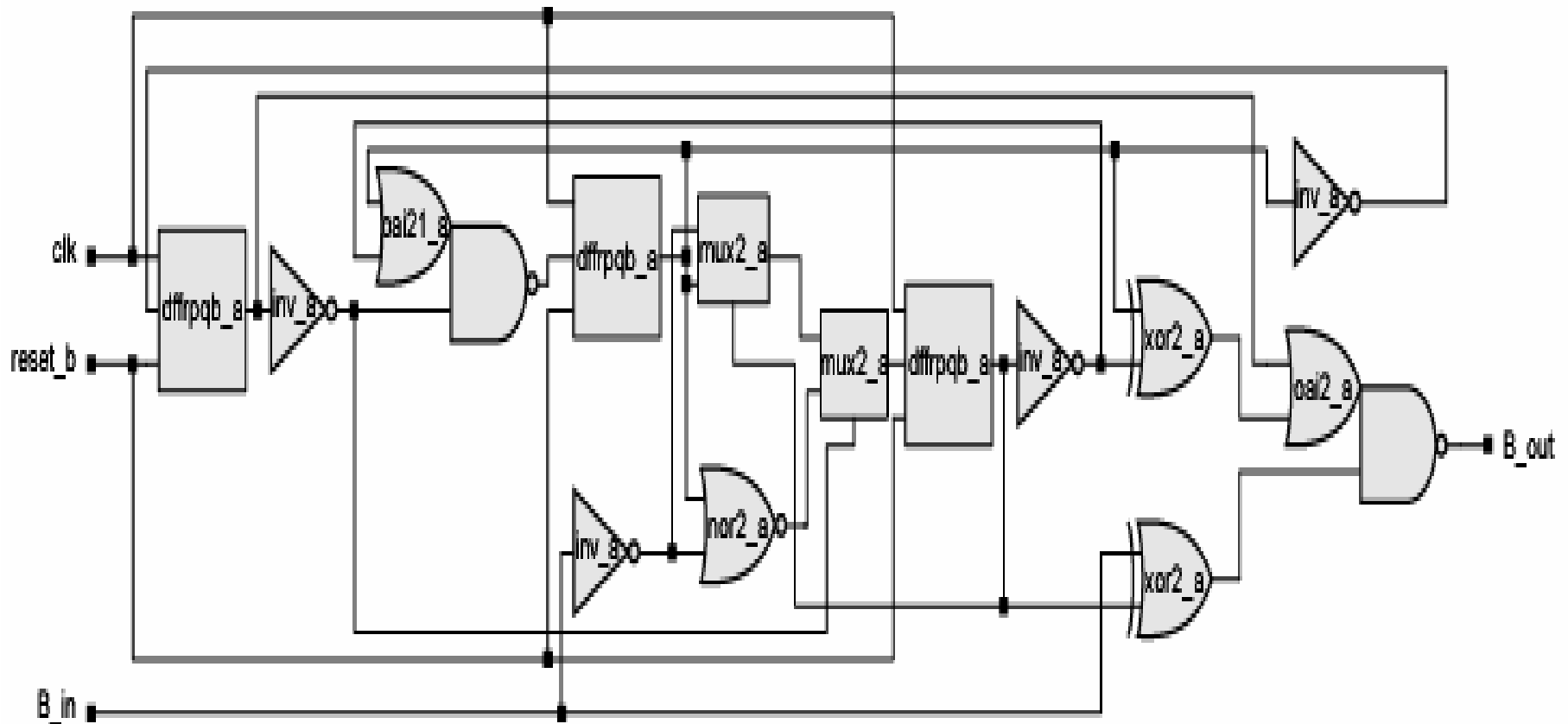



# Synthesis Tip

- **Decode all possible states in a level-sensitive behavior**  
describing the combinational next state and output logic of an explicit state machine



## 6.6.2 Synthesis of a mealy-type NRZ-to-Manchester line code converter

- **A serial line code converter** converts a non-return-to-zero (NRZ) bit stream into a Manchester encoded bit stream
- Line codes are used in data transmission or storage systems **to reduce the effects of noise** in serial communications channels and/or **to reduce the width of channel datapaths**



# Manchester encoding

## (Self Synchronizing code)

- There is **always** a mid-bit transition {which is used as a clocking mechanism}.
- **The direction of the mid-bit transition represents the digital data.**


0  $\Leftrightarrow$  low-to-high transition

1  $\Leftrightarrow$  high-to-low transition

There may be a second transition at the beginning of the bit interval.



 
# The signal waveform of the NRZ-to-Manchester line code







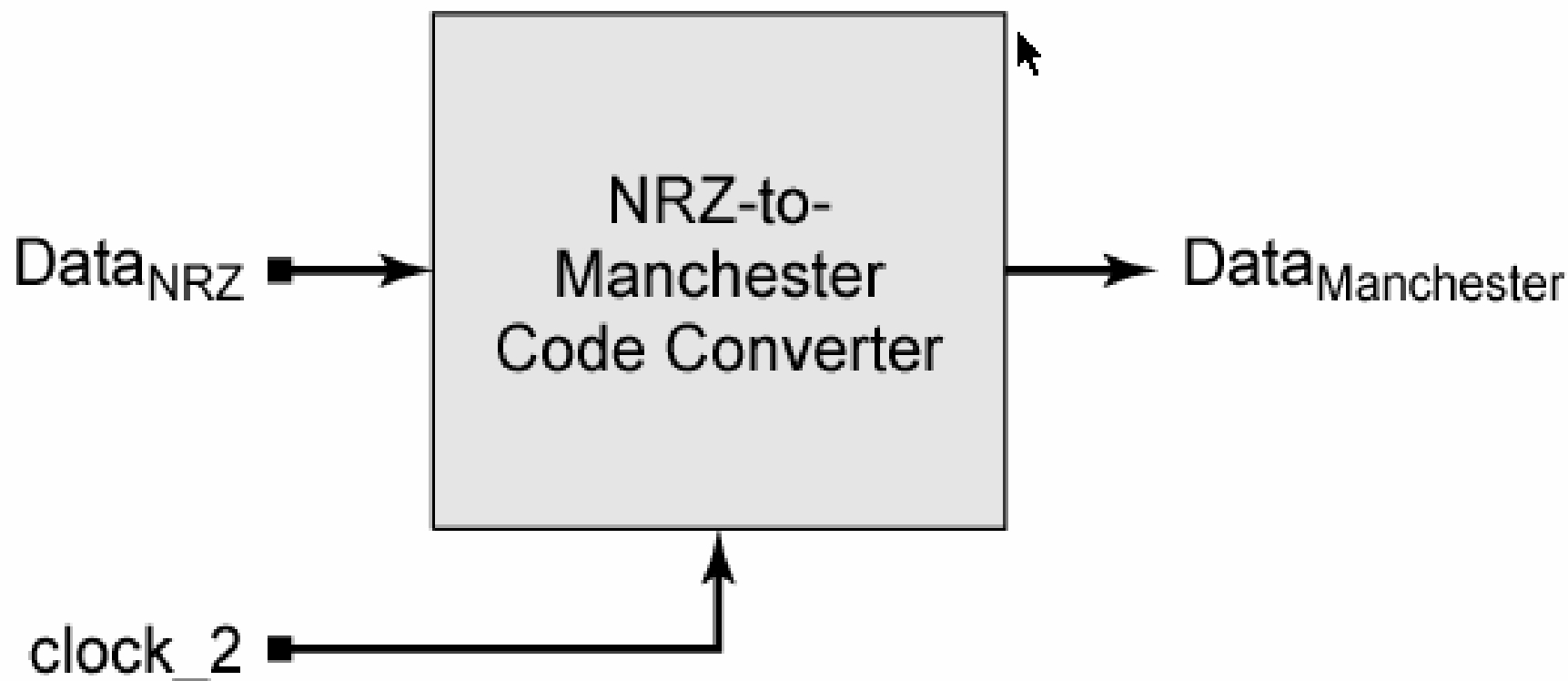
# A Mealy-type NRZ-to-Manchester line code converter




 
# A Mealy-type NRZ-to-Manchester line code converter




State	Next State/Output	
	Input	
	0	1
S_0	S_1/0	S_2/1
S_1	S_0/1	—
S_2	—	S_0/0

(b)



 (a) state assignment  
(b) encoded next state & out table




		$q_0$	
$q_1$		0	1
		$S_0$	$S_1$
0		$S_0$	$S_1$
1		$S_2$	

State		Next State		Output	
$q_1 q_0$		$q_1^1 q_0^1$			
		Input		Input	
		0	1	0	1
$S_0$	00	01	10	0	1
$S_1$	01	00	00	1	—
$S_2$	10	00	00	—	0





```
module NRZ_2_Manchester_Mealy
    (B_out,B_in,clock,reset_b);
    output B_out;
    input B_in;
    input clock,reset_b;
    reg [1:0] state,next_state;
    reg B_out;
    parameter S_0=0, S_1=1, S_2=2, dont_care_state=2'bx,
        dont_care_out=1'bx;
    always @ (negedge clock or negedge reset_b)
        if (reset_b==0) state<=S_0; else state<=next_state;
    always @ (state or B_in) begin
        B_out=0;
        case (state)
            S_0: if (B_in==0) next_state=S_1;
                  else if (B_in==1) begin next_state=S_2; B_out=1; end
            S_1: begin next_state=S_0; B_out=1; end
            S_2: begin next_state=S_0; end
            default: begin next_state=dont_care_state; B_out=dont_care_out; end
        endcase
    end
endmodule
```

 




# Simulation

  




# Schematic

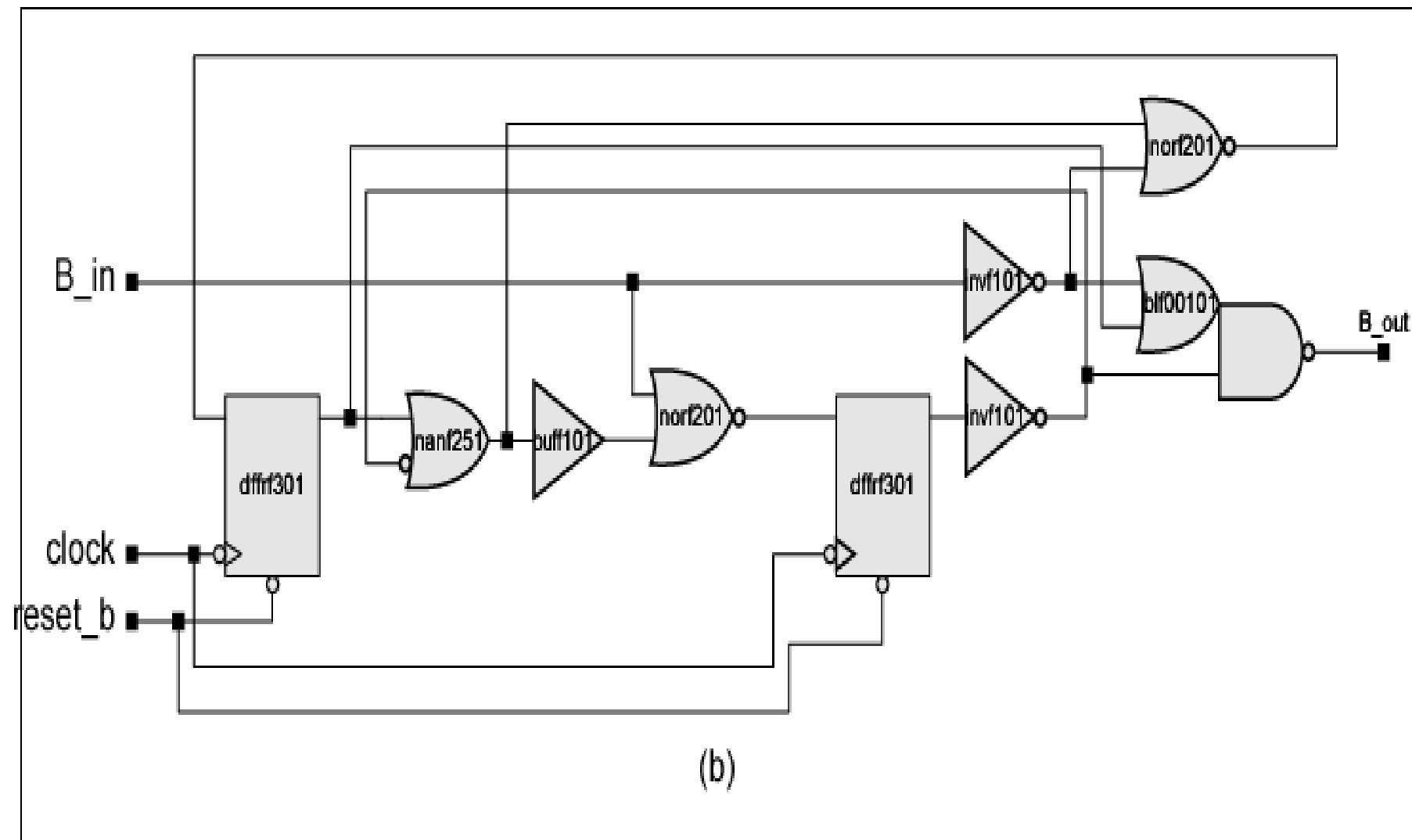


 
## 6.6.3 Synthesis of a Moore-type NRZ-to-Manchester line code converter



State	Next State/Output	
	Input	
	0	1
$S_0$	$S_1/0$	$S_3/1$
$S_1$	$S_2/1$	—
$S_3$	—	$S_0/1$
$S_2$	$S_1/0$	$S_3/0$


(b)



```

module NRZ_2_Manchester_Moore (B_out,B_in,clock,reset_b);
  output B_out;
  input B_in, input clock,reset_b;
  reg [1:0] state,next_state;
  reg B_out;
  parameter S_0=0, S_1=1, S_2=2, S_3=3;
  always @ (negedge clock or negedge reset_b)
    if (reset_b==0) state<=S_0; else state<=next_state;
  always @ (state or B_in) begin
    case (state)
      S_0: begin if (B_in==0) next_state=S_1;
              else next_state=S_3;
            end
      S_1: begin next_state=S_2; end
      S_2: begin B_out=1;
              if (B_in==0) next_state=S_1;
              else next_state=S_3;
            end
      S_3: begin B_out=1; next_state=S_0; end
    endcase
  end
endmodule



```

 






# Simulation

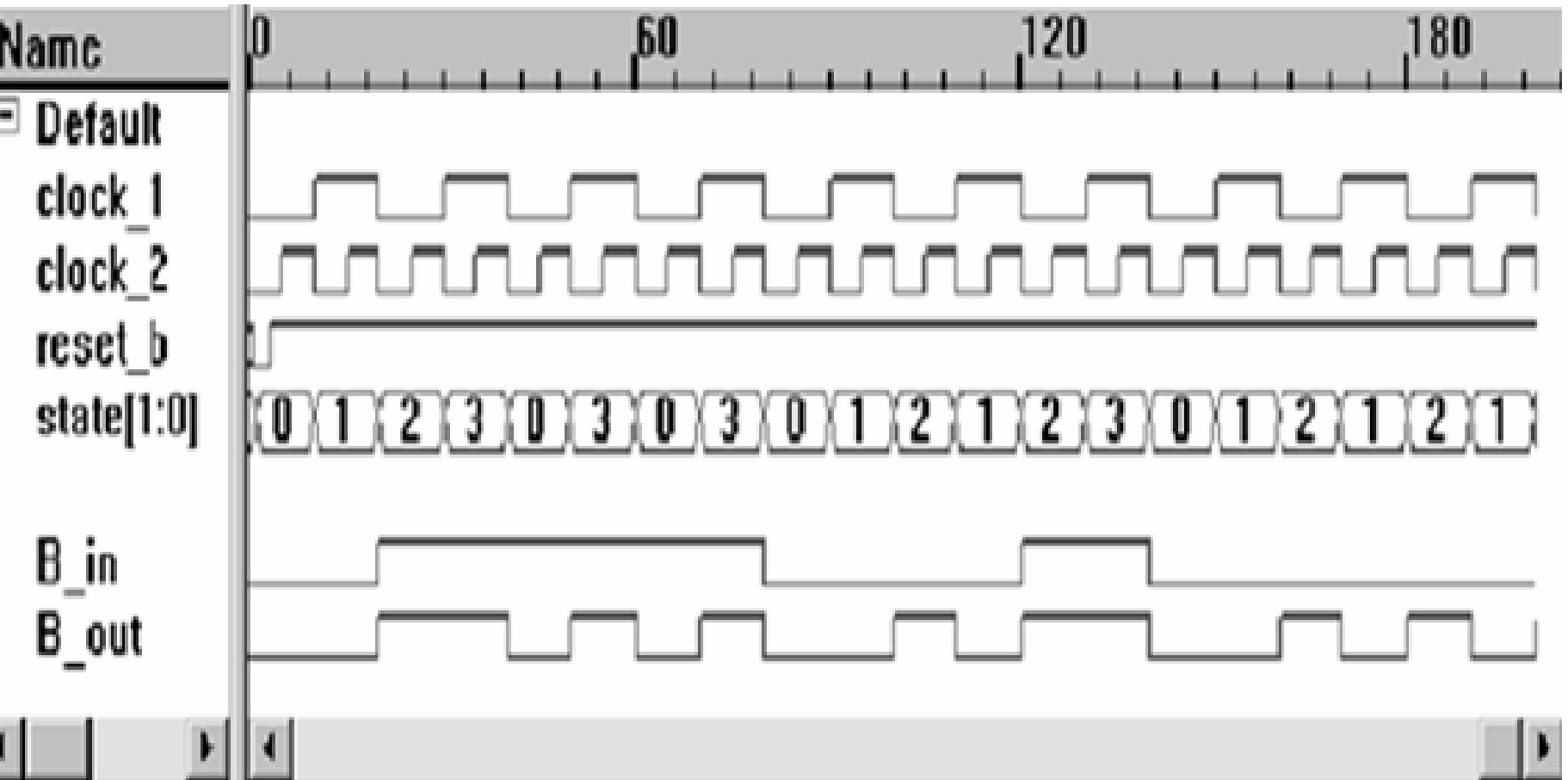 



# ASIC synthesis circuit

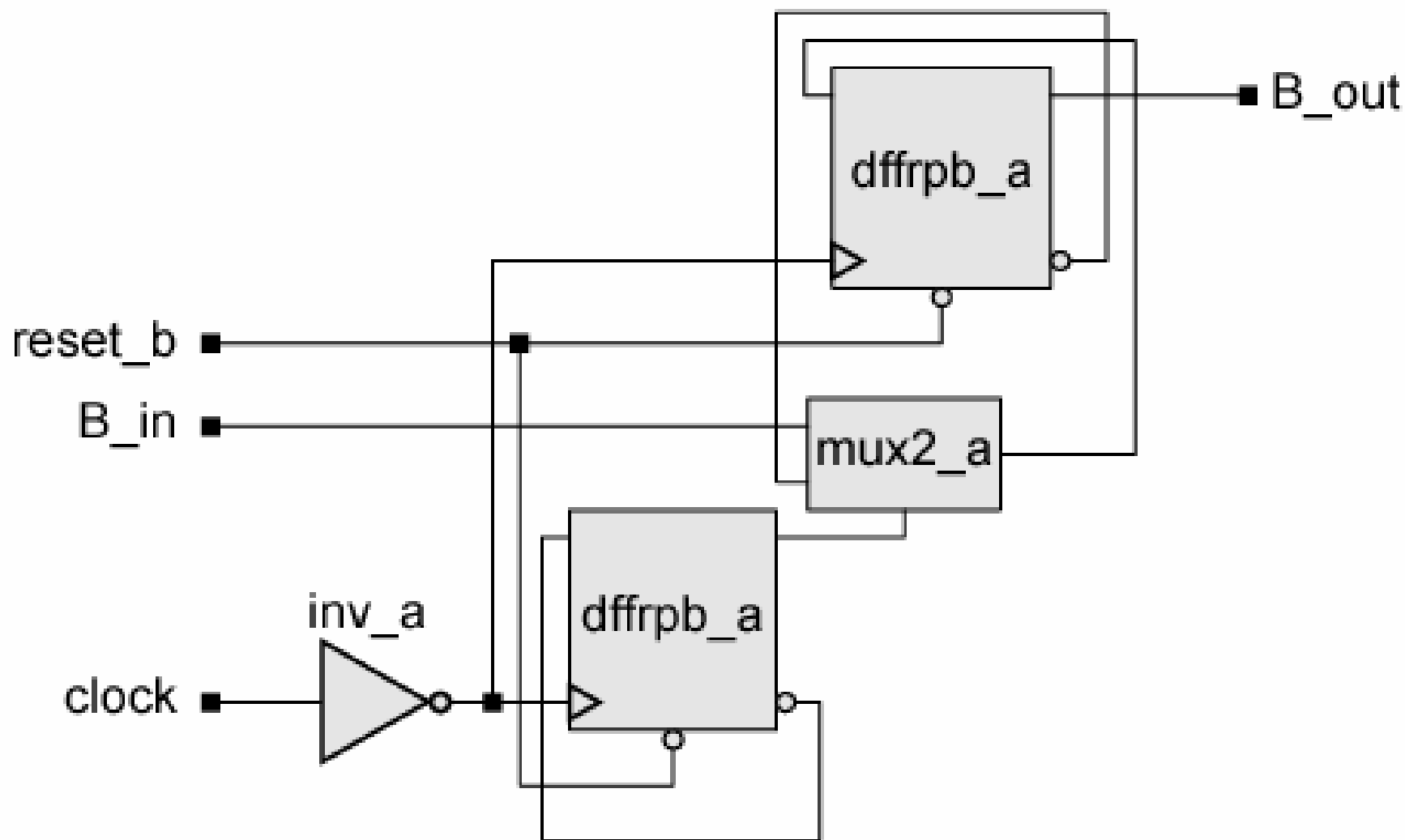



## 6.6.4 Synthesis of a sequence recognizer


- To describe sequence recognizers:
- 1. To clarify the semantics of how the machine receives input bits
- 2. To distinguish between resetting and non-resetting machines

A non-resetting machine continues to assert its output if the input bit pattern is overlapping



 
## Example 6.26

- The sequence recognizer is to sample the serial input, D\_in, **on the falling edge of the clock and assert D\_out if three successive samples are 1**





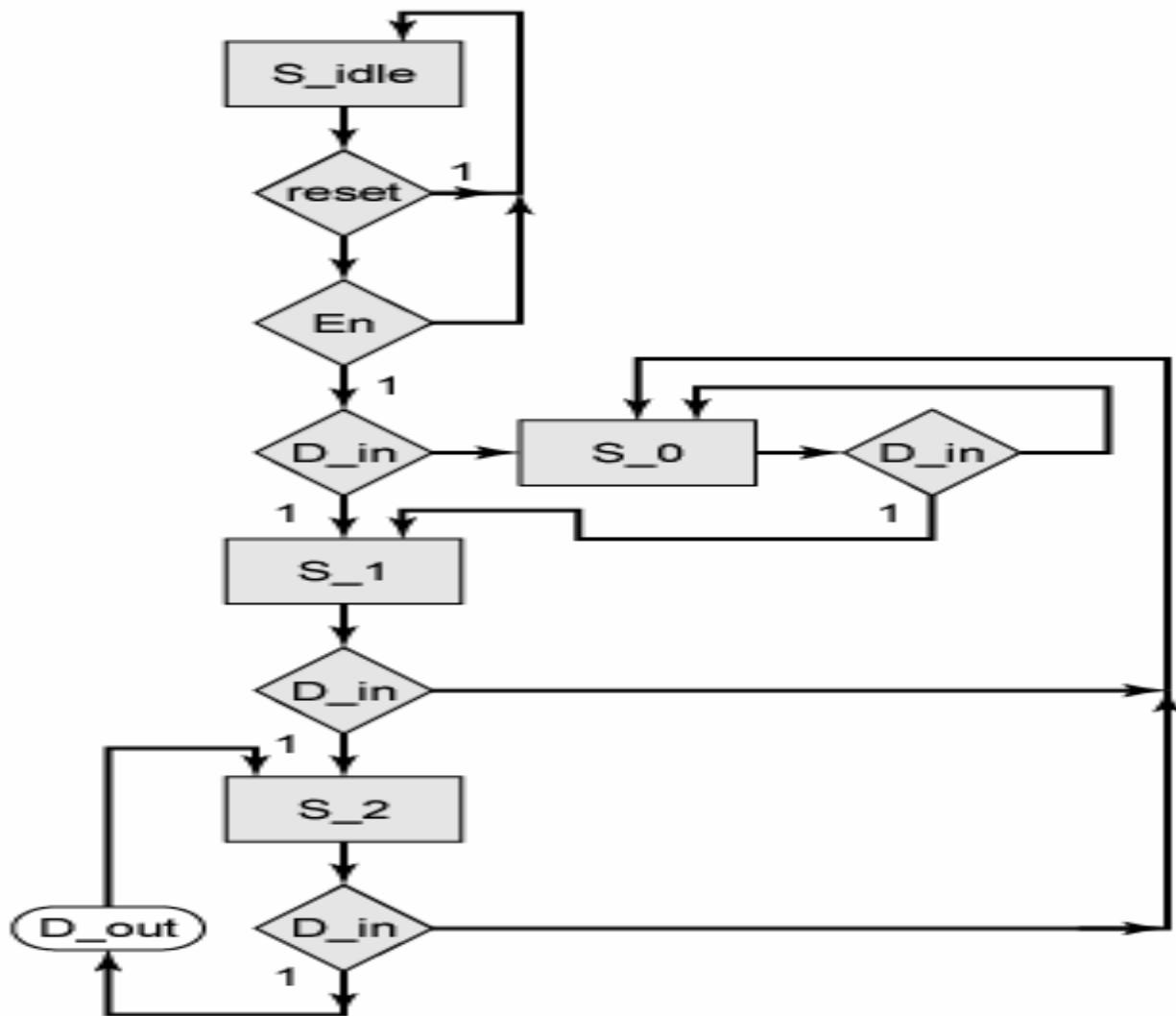
# ASM chart for a Mealy-type explicit FSM implementation




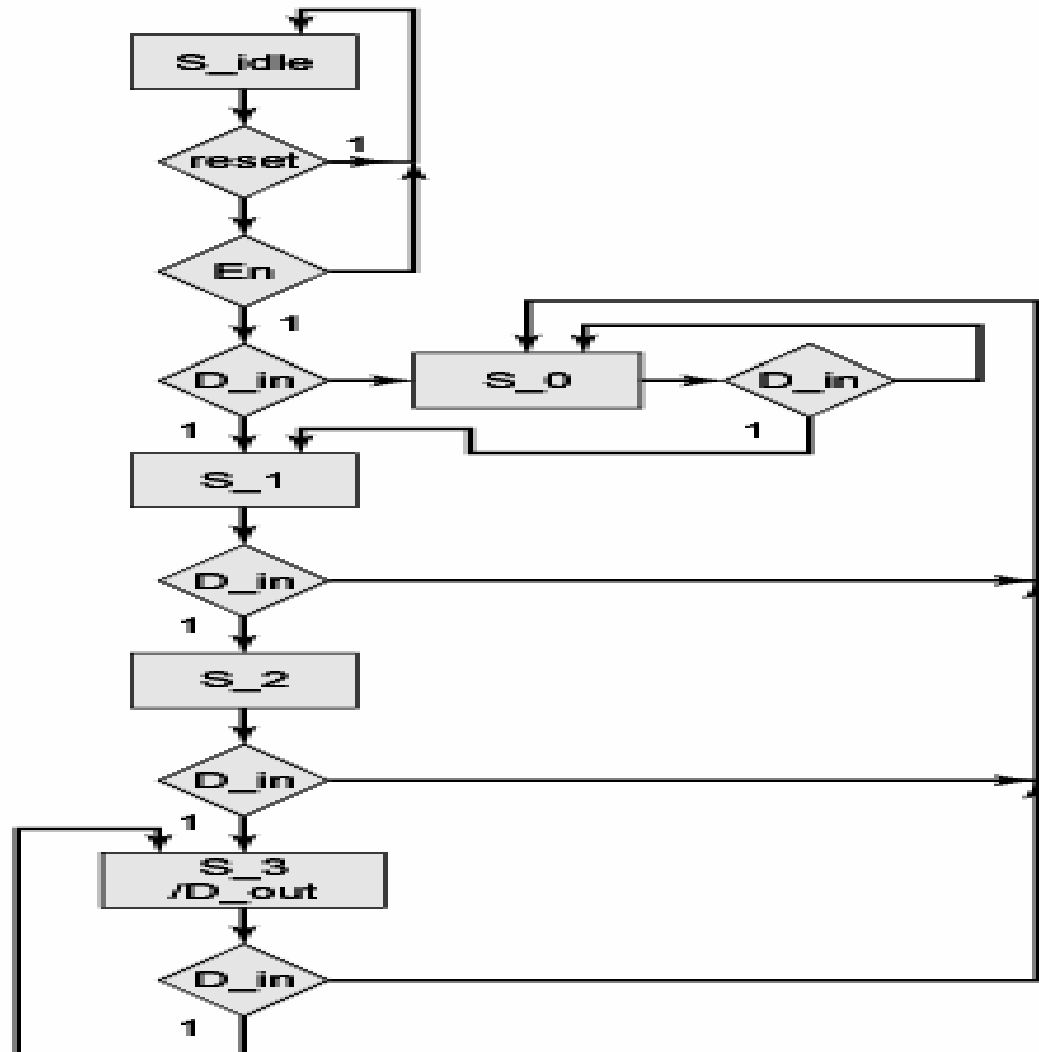
# ASM chart for a Moore-type explicit FSM implementation





# Mealy-type sequence recognizer

```
module Seq_Rec_3_1s_Mealy (D_out, D_in, En, clk, reset);  
    output D_out;  
    input D_in, En;  
    input clk, reset;  
    parameter S_idle=0; // Binary code  
    parameter S_0=1;  
    parameter S_1=2;  
    parameter S_2=3;  
    reg [1:0] state, next_state;  
    always @ (negedge clk)  
    if (reset==1) state<=S_idle; else state<=next_state;
```




```
always @ (state or D_in) begin
    case (state)
        S_idle: if ((En==1)&&(D_in==1)) next_state=S_1; else
                if ((En==1)&&(D_in==0)) next_state=S_0;
                else      next_state=S_idle;
        S_0:    if (D_in==0) next_state=S_0;
                else if (D_in==1) next_state=S_1;
                else  next_state=S_idle;
        S_1:    if (D_in==0) next_state=S_0;
                else if (D_in==1) next_state=S_2;
                else      next_state=S_idle;
        S_2:    if (D_in==0) next_state=S_0;
                else if (D_in==1) next_state=S_2;
                else      next_state=S_idle;
        default:      next_state=S_idle;
    endcase
end
assign D_out=((state=S_2) && (D_in==1)); // Mealy output
endmodule
```





# ASIC synthesis circuit

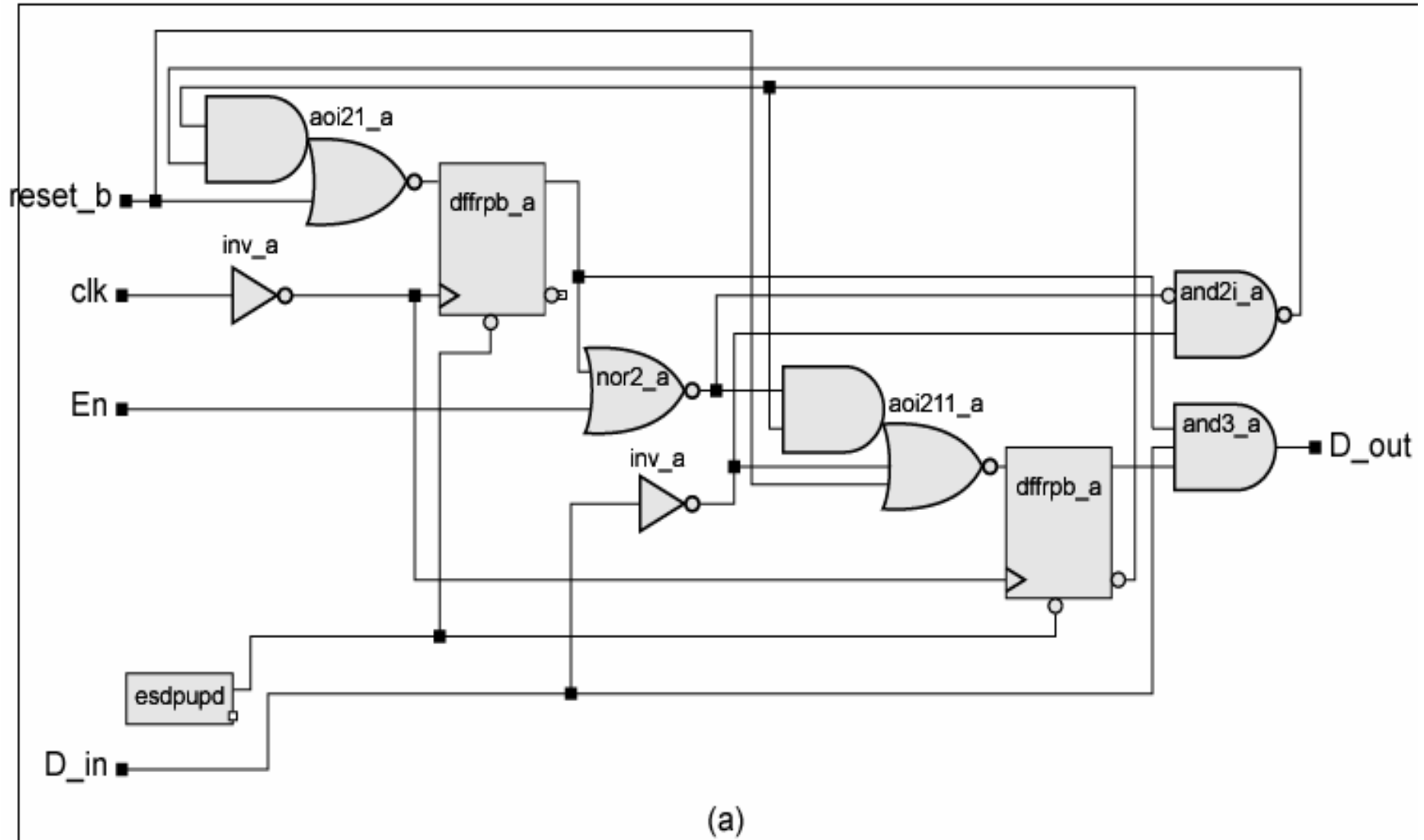



# Moore-type sequence recognizer

```
module Seq_Rec_3_1s_Moore (D_out, D_in, En, clk, reset);  
  output D_out;  
  input D_in, En;  
  input clk, reset;  
  parameter S_idle=0;  // One-hot  
  parameter S_0=1;  
  parameter S_1=2;  
  parameter S_2=3;  
  parameter S_3=4;  
  reg [2:0] state, next_state;  
  always @ (negedge clk)  
  if (reset==1) state<=S_idle; else state<=next_state;
```



```
always @ (state or D_in) begin
```

```
  case (state)
```

```
    S_idle:  if ((En==1)&&(D_in==1) next_state=S_1; else  
              if ((En==1)&&(D_in==0) next_state=S_0;  
              else                                next_state=S_idle;
```

```
    S_0:     if (D_in==0) next_state=S_0; else  
              if (D_in==1) next_state=S_1;  
              else          next_state=S_idle;
```

```
    S_1:     if (D_in==0) next_state=S_0; else  
              if (D_in==1) next_state=S_2;  
              else          next_state=S_idle;
```

```
    S_2,S_3: if (D_in==0) next_state=S_0; else  
              if (D_in==1) next_state=S_3;  
              else          next_state=S_idle;
```

```
    default:          next_state=S_idle;
```

```
  endcase
```


```
  end
```

```
  assign D_out=(state=S_3);    // Moore output
```

```
endmodule
```



# ASIC synthesis circuit

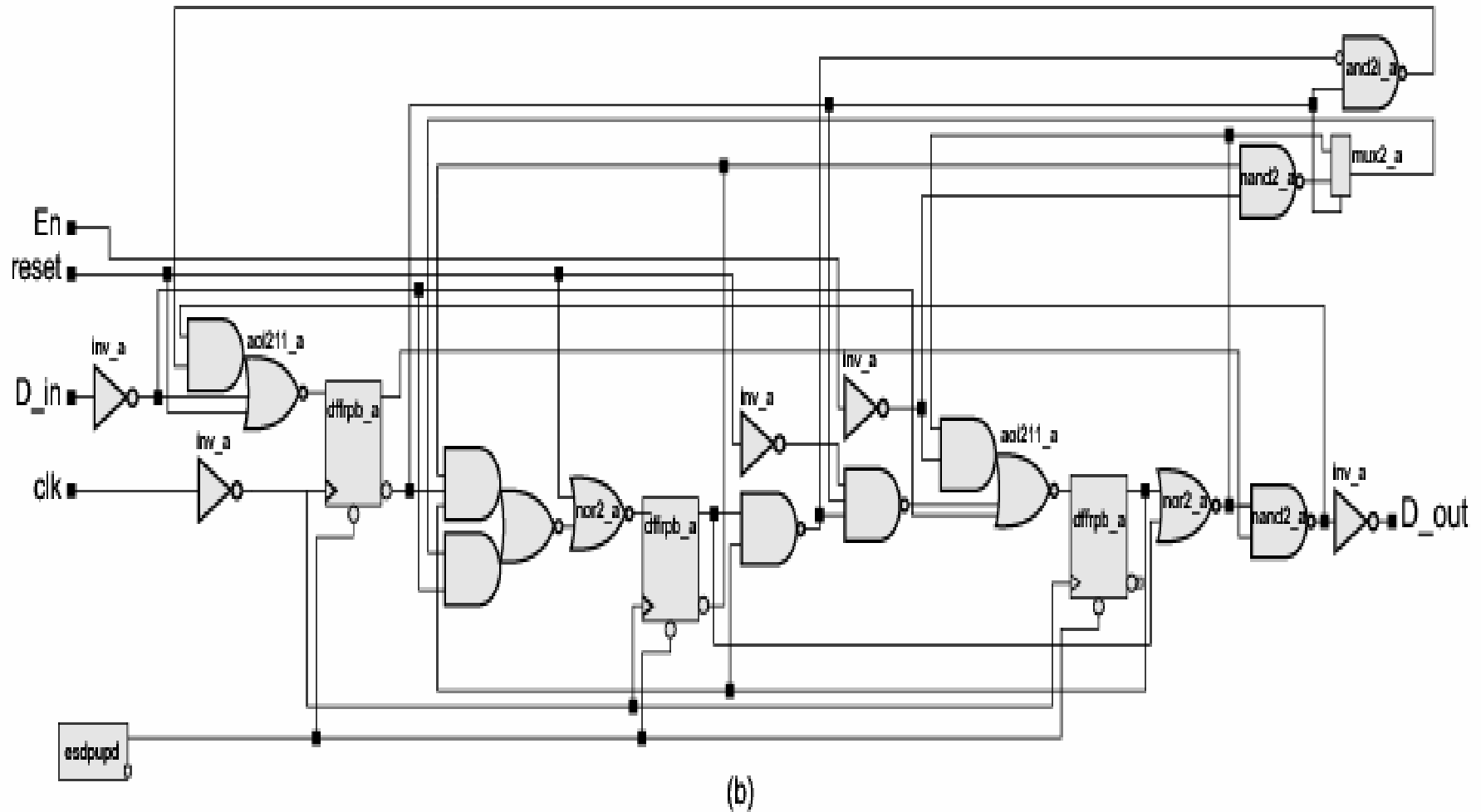



# Testbench

```
module t_Seq_Rec_3_1s ();  
    reg D_in_NRZ,D_in_RZ,En,clk,reset;  
    wire Mealy_NRZ;  
    wire Mealy_RZ;  
    wire Moore_NRZ;  
    wire Moore_RZ;  
    Seq_Rec_3_1s_Mealy M0 (Mealy_NRZ,D_in_NRZ,En,clk,reset);  
    Seq_Rec_3_1s_Mealy M1 (Mealy_RZ,D_in_RZ,En,clk,reset);  
    Seq_Rec_3_1s_Moore M2 (Moore_NRZ,D_in_NRZ,En,clk,reset);  
    Seq_Rec_3_1s_Moore M3 (Moore_RZ,D_in_RZ,En,clk,reset);  
    initial #275 $finish;  
    initial begin #5 reset=1; #1 reset=0; end  
    initial begin clk=0; forever #10 clk=~clk; end  
    initial begin  
        #5 En=1;  
        #50 En=0; end
```



**initial**

**fork**

**begin** #10 D\_in\_NRZ=0; #25 D\_in\_NRZ=1; #80 D\_in\_NRZ=0; **end**

**begin** #135 D\_in\_NRZ=1; #40 D\_in\_NRZ=0; **end**

**begin** #195 D\_in\_NRZ=1'bx; #60 D\_in\_NRZ=0; **end**

**join**

**initial**

**fork**

#10 D\_in\_RZ=0;

#35 D\_in\_RZ=1; #45 D\_in\_RZ=0;

#55 D\_in\_RZ=1; #65 D\_in\_RZ=0;

#75 D\_in\_RZ=1; #85 D\_in\_RZ=0;

#95 D\_in\_RZ=1; #105 D\_in\_RZ=0;

#35 D\_in\_RZ=1; #145 D\_in\_RZ=0;

#135 D\_in\_RZ=1; #45 D\_in\_RZ=0;

#155 D\_in\_RZ=1; #165 D\_in\_RZ=0;

#195 D\_in\_RZ=1'bx; #250 D\_in\_RZ=0;

**join**

**endmodule**



# fork

- Groups statements into **a parallel block**, so that they are **executed concurrently**.

- **fork [ : Label [ Declarations... ] ]**


**Statements...**

**Join**

- Declaration = {either} Register Parameter Event
- **Not synthesizable.**




# Simulation

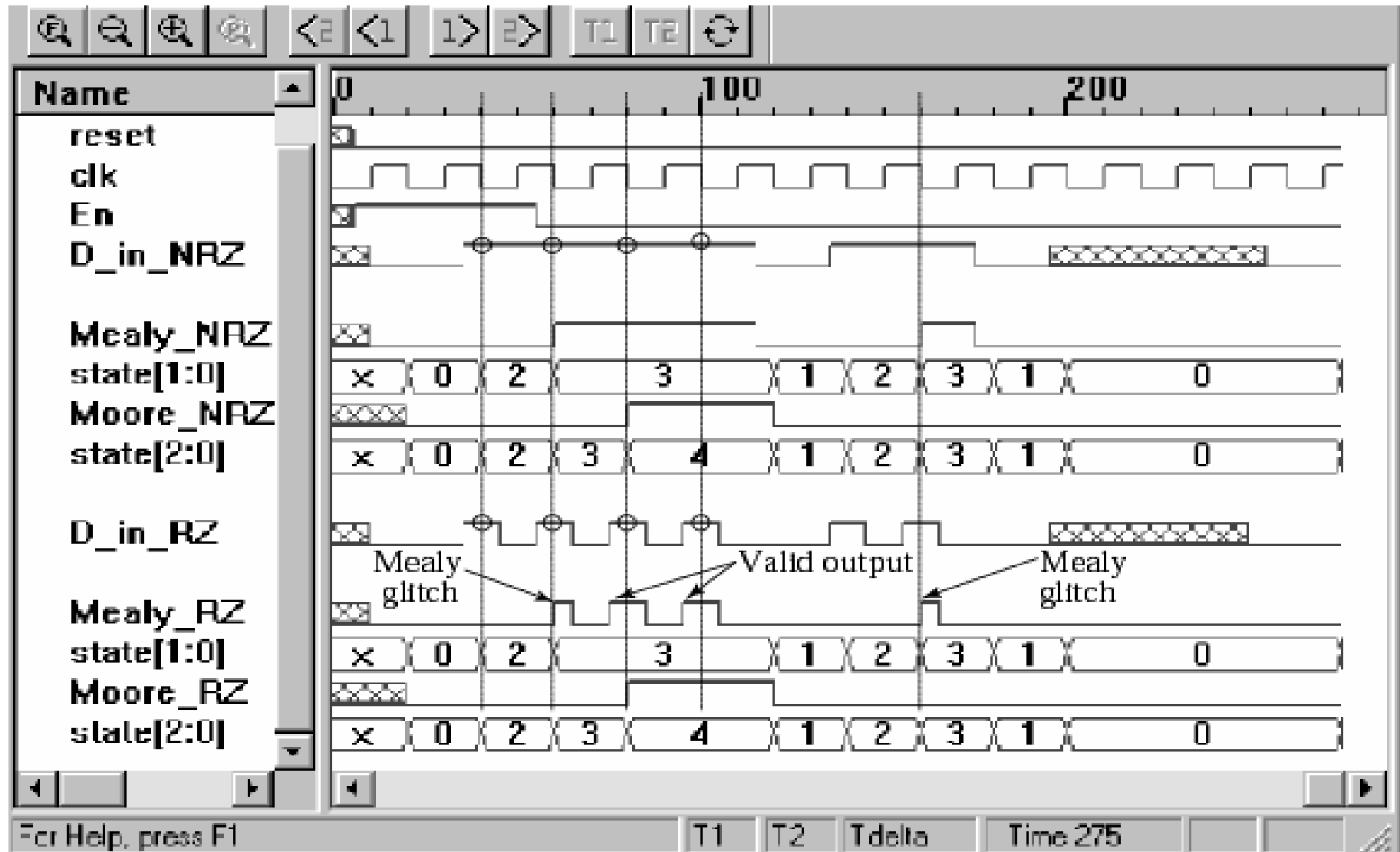





# Simulation result

 




# Alternative approach for Mealy-type

```
module Seq_Rec_3_1s_Mealy_Shft_Reg (D_out, D_in, En,  
    clk, reset);  
    output D_out;  
    input D_in, En;  
    input clk, reset;  
    parameter Empty=2'b00;  
    reg [1:0] Data;  
    always @ (negedge clk)  
    if (reset==1) Data<=Empty;  
        else if (En==1) Data<={D_in, Data[1]};  
    assign D_out=((Data==2'b11)&&(D_in==1)); // mealy_output  
endmodule
```


 
# Mealy sequence recognizers for detecting three successive 1s in a serial bit stream






# Alternative approach for Moore-type

```
module Seq_Rec_3_1s_Moore_Shft_Reg (D_out, D_in, En, clk,  
    reset);  
    output D_out;  
    input D_in, En;  
    input clk, reset;  
    parameter Empty=2'b00;  
    reg [2:0] Data;  
  
    always @ (negedge clk)  
    if (reset==1) Data<=Empty; else if (En==1)  
        Data<={D_in, Data[2:1]};  
    assign D_out=((Data==3'b111);    // Moore output  
endmodule
```



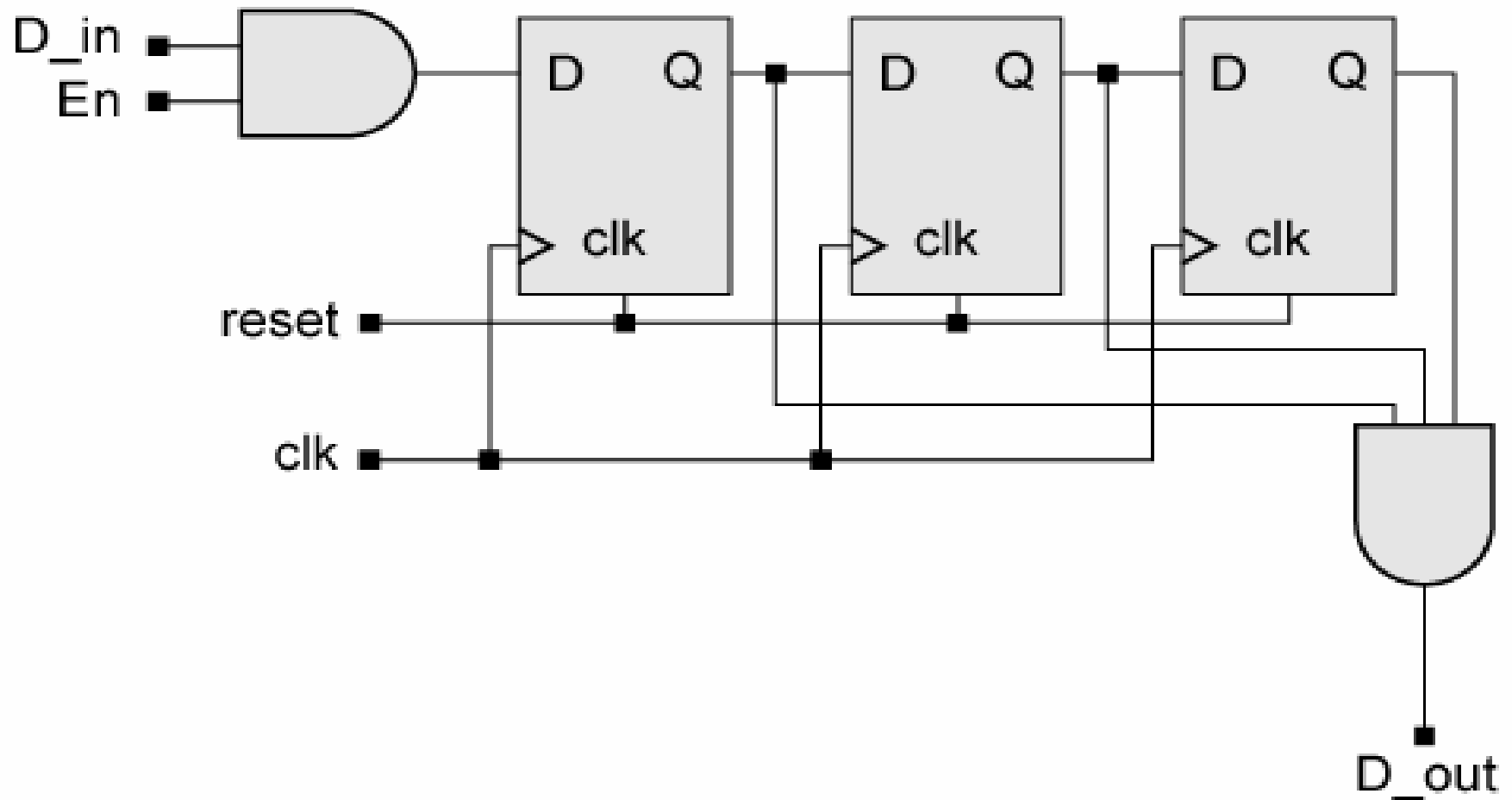
# Moore sequence recognizers for detecting three successive 1s in a serial bit stream






# Synthesis circuit

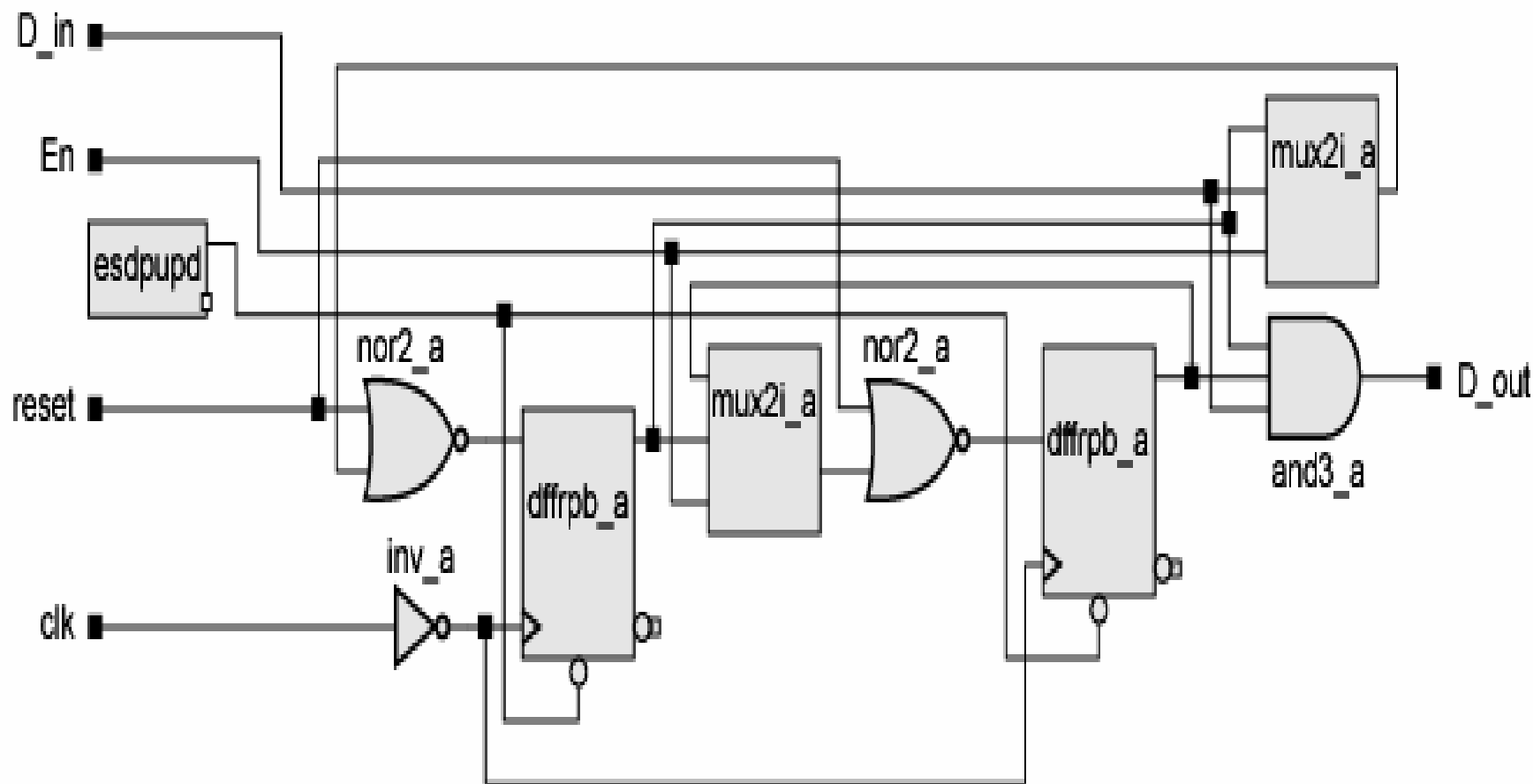

(a)





# Synthesis circuit

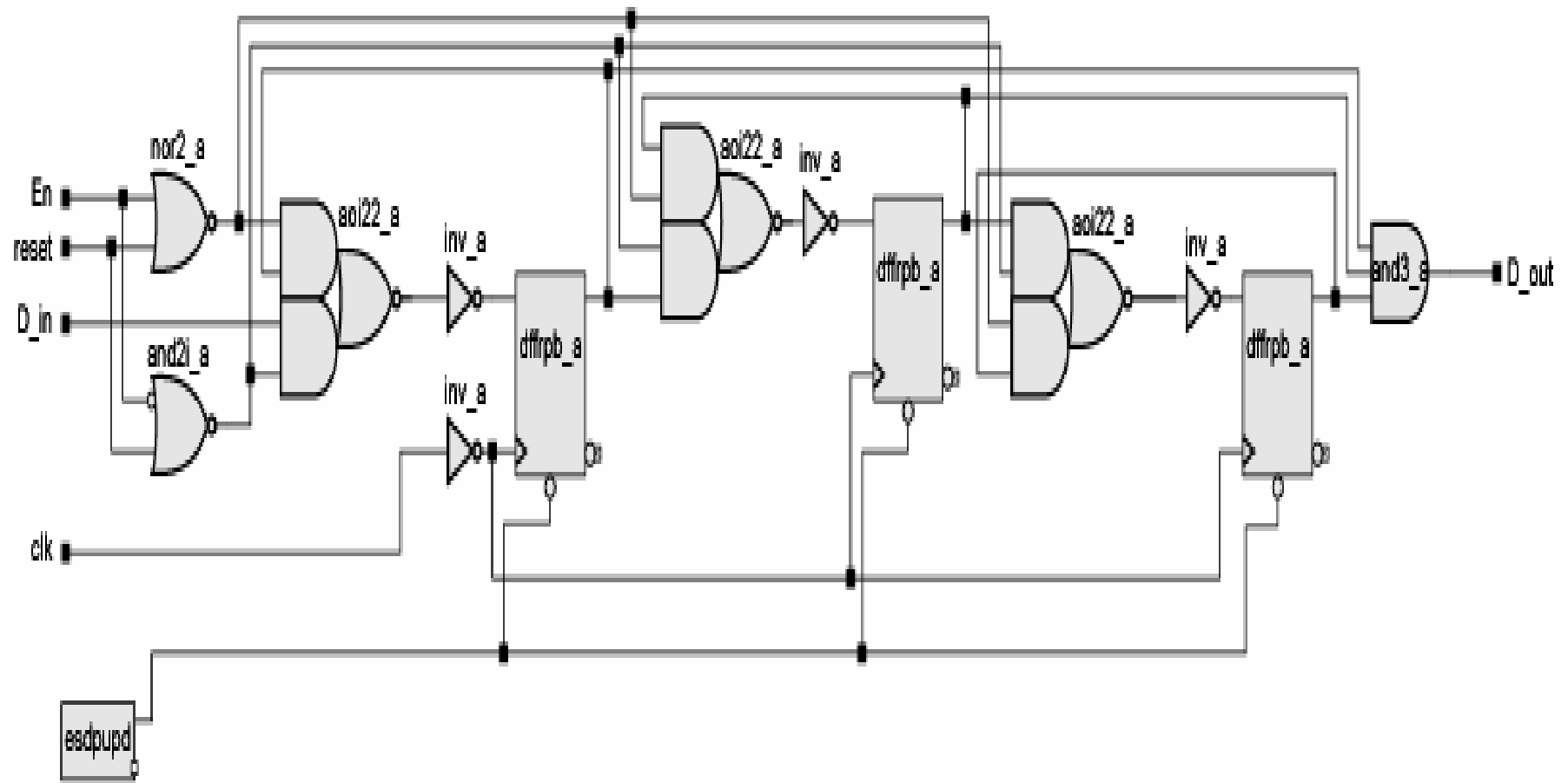

(b)



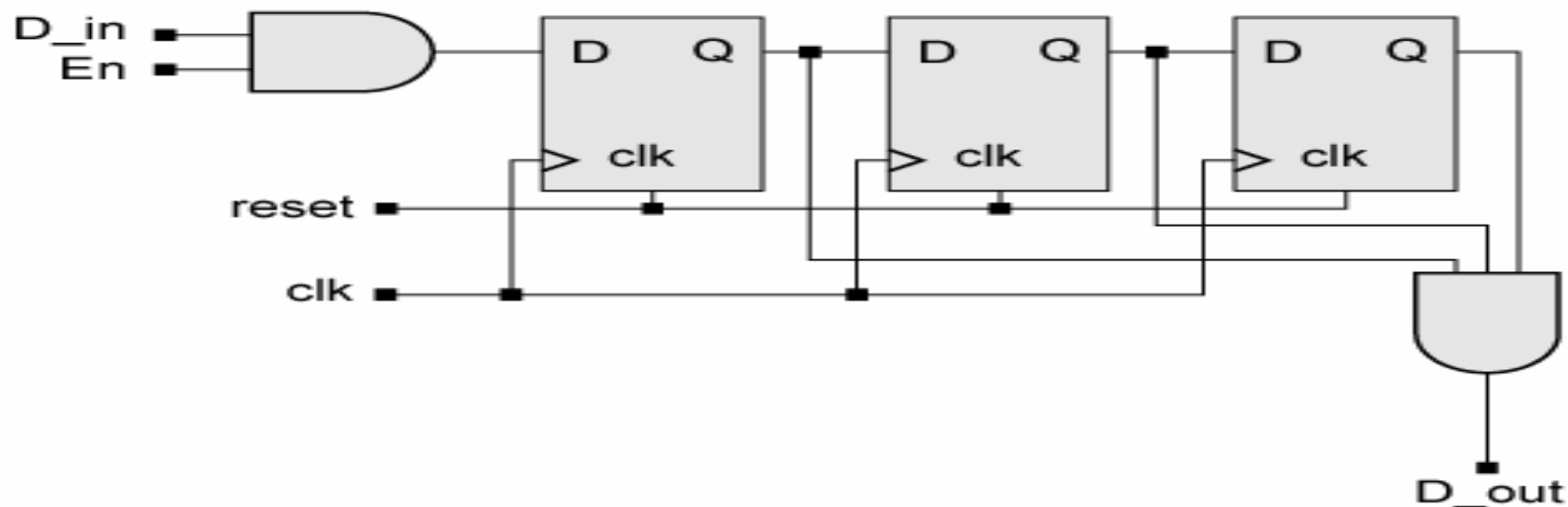 
# The difference of Mealy, Moore sequence recognizers







# Simulation result

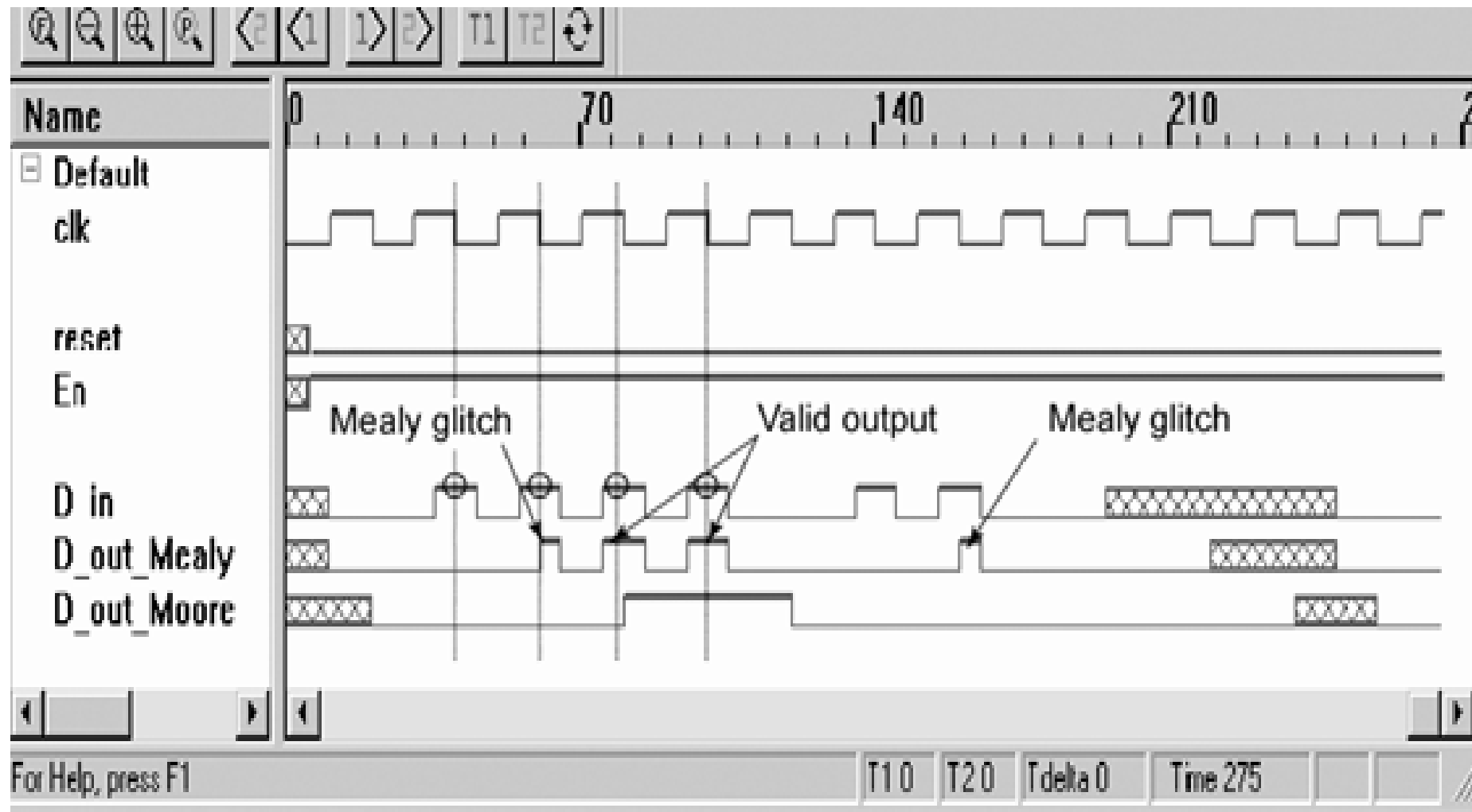




## 6.7 Registered logic

- Variables whose values are assigned synchronously with a clock signal are said to be registered
- **Registered signals are updated at the active edges of the clock** and are stable (i.e., they cannot glitch)
- The outputs of a Moore-type state machine are not registered, but they **cannot glitch** with changes at the machine's input


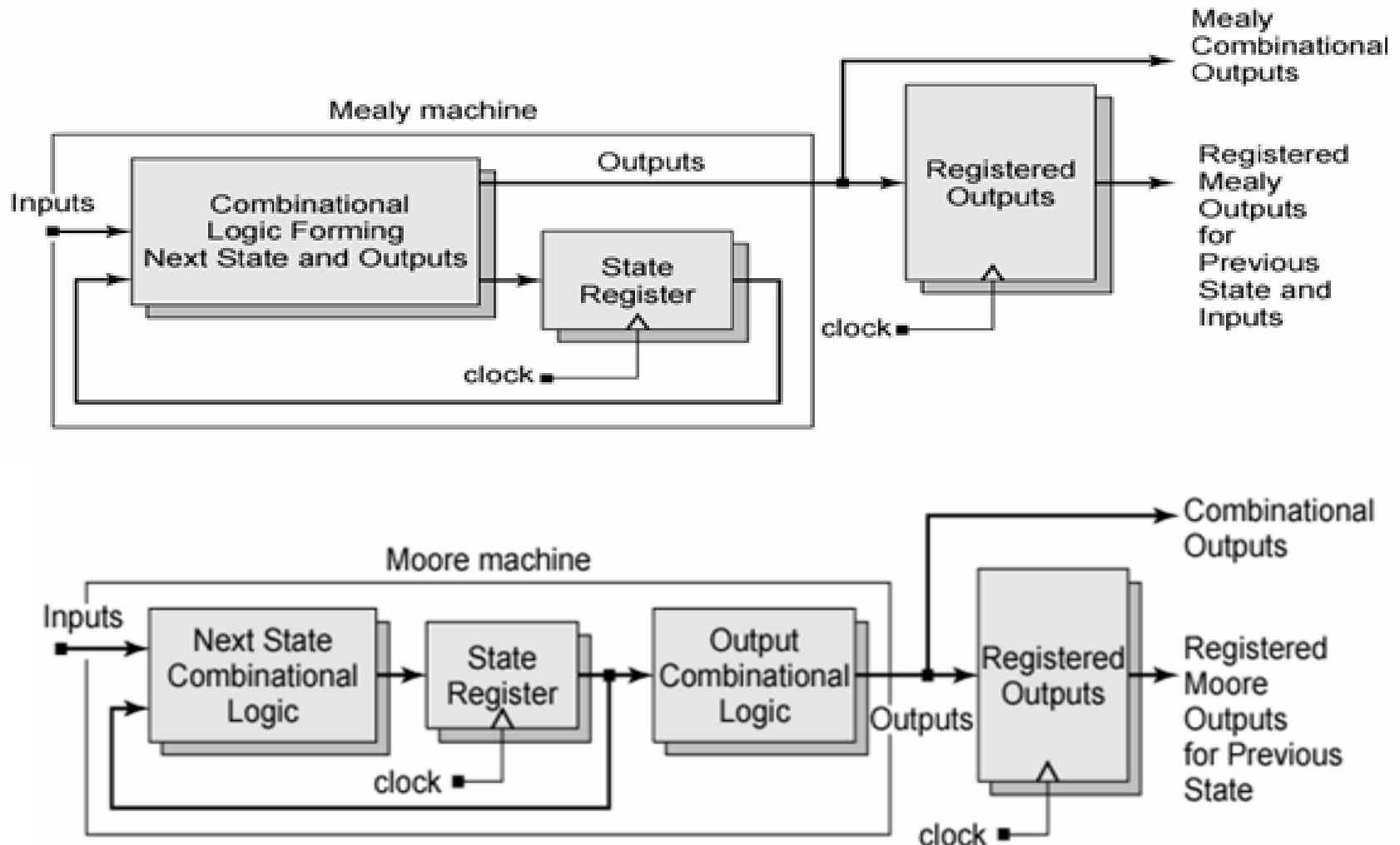
# Registered outputs in a Mealy,moore machine



(b)




## Example 6.27

```
module mux_reg (y,a,b,c,d,select,clock);  
  output [7:0] y;  
  input [7:0] a,b,c,d;  
  input [1:0] select;  
  input clock;  
  reg y;  
  always @ (posedge clock)  
    case (select)  
      0: y<=a;    // non-blocking  
      1: y<=b;  
      2: y<=c;  
      3: y<=d;  
      default: y<=8'bx;  
    endcase  
endmodule
```




# Example 6.27

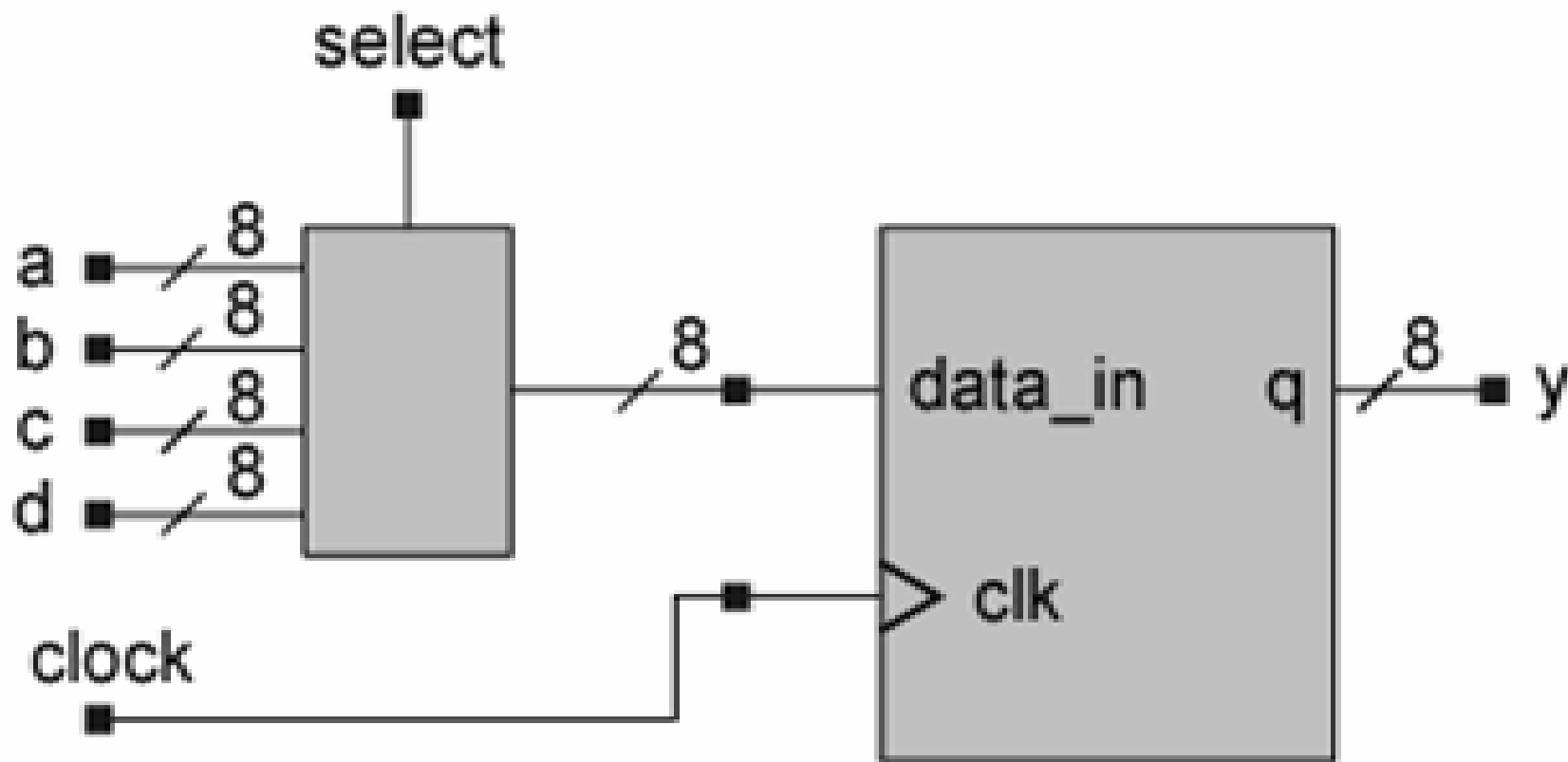

(a)



# Synthesized circuit

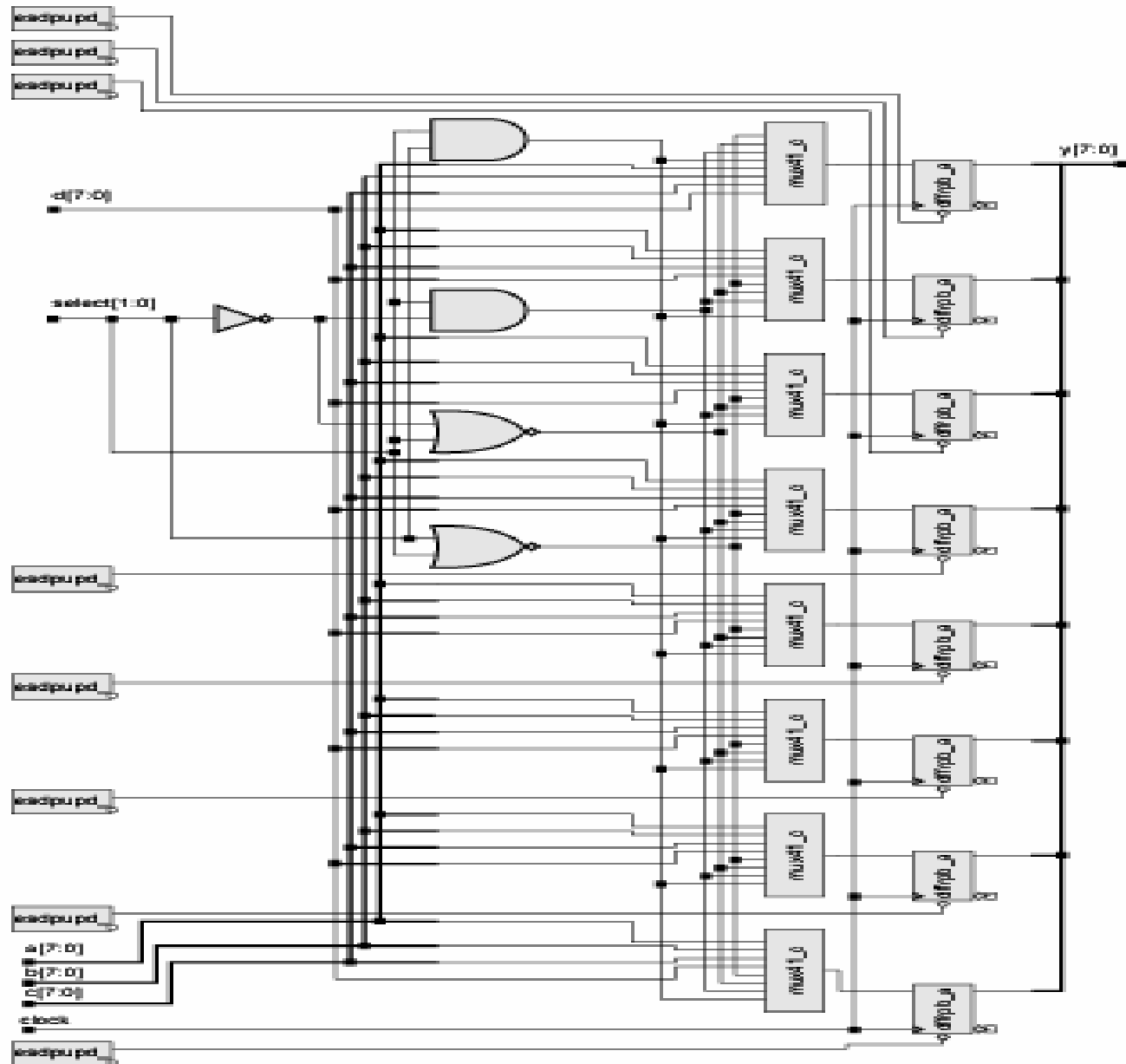



## Ex 6.28 Registered output of sequence recognizers

```
module Seq_Rec_3_1s_Mealy (D_out, D_in, En, clk, reset);  
    output D_out;  
    input D_in, En;  
    input clk, reset;  
    parameter S_idle=0; // Binary code  
    parameter S_0=1;  
    parameter S_1=2;  
    parameter S_2=3;  
    reg [1:0] state, next_state;  
    reg D_out_reg;  
    always @ (negedge clk)  
        if (reset==1) state<=S_idle,D_out_reg<=0;  
        else  
            begin state<=next_state;  
                D_out_reg<= ((state==S_2)&&(next_state==S_2)&& (D_in==1));  
            end  
end
```



**always @** (state **or** D\_in) **begin**

**case** (state)

S\_idle: **if** ((En==1)&&(D\_in==1)) next\_state=S\_1;

**else**

**if** ((En==1)&&(D\_in==0)) next\_state=S\_0;

**else**

next\_state=S\_idle;

S\_0: **if** (D\_in==0) next\_state=S\_0; **else**

**if** (D\_in==1) next\_state=S\_1;

**else**

next\_state=S\_idle;

S\_1: **if** (D\_in==0) next\_state=S\_0; **else**

**if** (D\_in==1) next\_state=S\_2;

**else**

next\_state=S\_idle;

S\_2,S\_3: **if** (D\_in==0) next\_state=S\_0; **else**

**if** (D\_in==1) next\_state=S\_3;

**else**

next\_state=S\_idle;

**default:**

next\_state=S\_idle;

**endcase**

**end**

**assign** D\_out=D\_out\_reg; // Mealy output

**endmodule**





# Moore-type sequence recognizer

```
module Seq_Rec_3_1s_Moore (D_out, D_in, En, clk, reset);  
  output D_out;  
  input D_in, En;  
  input clk, reset;  
  parameter S_idle=0; // Binary code  
  parameter S_0=1;  
  parameter S_1=2;  
  parameter S_2=3;  
  reg [1:0] state, next_state;  
  reg D_out_reg;  
  always @ (negedge clk)  
    if (reset==1) begin state<=S_idle; D_out_reg<=0; end  
    else  
      begin  
        state<=next_state; D_out_reg<=(next_state==S_3);  
      end
```




```
always @ (state or D_in) begin
    case (state)
        S_idle: if ((En==1)&&(D_in==1)) next_state=S_1; else
                if ((En==1)&&(D_in==0)) next_state=S_0;
                else                                next_state=S_idle;
        S_0:    if (D_in==0) next_state=S_0; else
                if (D_in==1) next_state=S_1;
                else                                next_state=S_idle;
        S_1:    if (D_in==0) next_state=S_0; else
                if (D_in==1) next_state=S_2;
                else                                next_state=S_idle;
        S_2,S_3: if (D_in==0) next_state=S_0; else
                if (D_in==1) next_state=S_3;
                else                                next_state=S_idle;
        default:                                next_state=S_idle;
    endcase
end

assign D_out=D_out_reg;    // Moore output
endmodule
```



# Simulation result

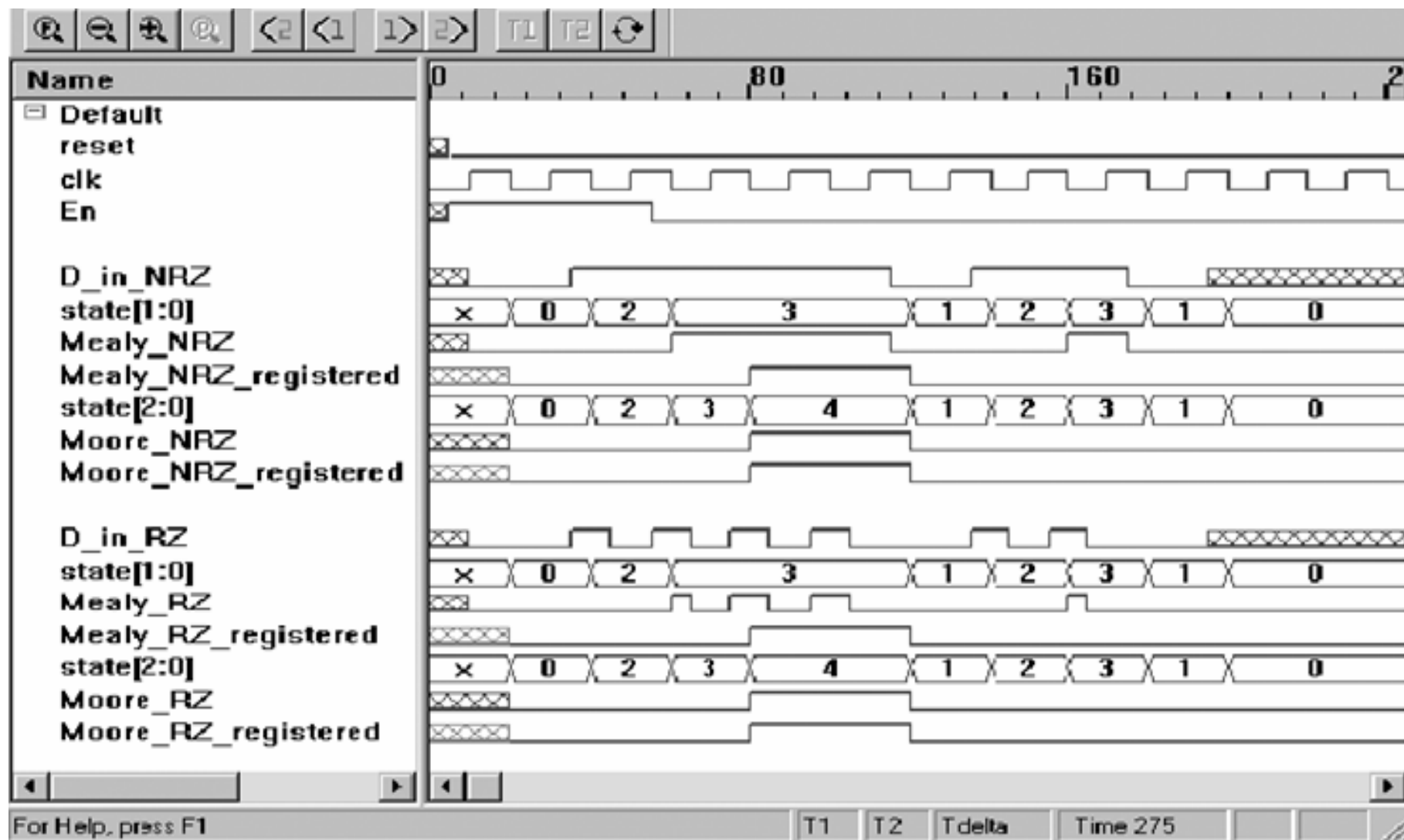



## 6.8 State encoding

- A set of flip-flops represent the states of the machine and a unique binary code be assigned to each state
- **Assigning a code to the states of a machine is called state assignment (state encoding)**
- **State encoding determines the number of flip-flops**



# General guideline of state assignment

- If two states have the same next state for a given input, give them logically adjacent state assignments,
- Assign logically adjacent state codes to states that have the same output for a given input.



# Commonly used state-assignment codes

#	Binary	One-Hot	Gray	Johnson
0	0000	0000000000000001	0000	00000000
1	0001	0000000000000010	0001	00000001
2	0010	0000000000000100	0011	00000011
3	0011	0000000000001000	0010	00000111
4	0100	0000000000010000	0110	00001111
5	0101	0000000000100000	0111	00011111
6	0110	0000000001000000	0101	00111111
7	0111	0000000010000000	0100	01111111
8	1000	0000000100000000	1100	11111111
9	1001	0000001000000000	1101	11111110
10	1010	0000010000000000	1111	11111100
11	1011	0000100000000000	1110	11111000
12	1100	0001000000000000	1010	11110000
13	1101	0010000000000000	1011	11100000
14	1110	0100000000000000	1001	11000000
15	1111	1000000000000000	1000	10000000



# Number of state assignment

- The number of flip-flops must be sufficient to represent the number of states as a binary number
- A state machine with  $N$  states will require at least  $\log_2 N$  flip-flops



## 6.9 Synthesis of implicit state machines, registers, and counters

- An implicit state machine **has one or more clock-synchronized event-control expressions in a behavior**
- Multiple event-control expressions of an implicit FSM will **be synchronized to the same edge of the same clock**





## 6.9.1 Implicit state machines

- **The state is defined implicitly by the evolution of activity within a cyclic behavior**
- May contain multiple clock-synchronized event-control expressions within the same behavior
- Being a more general style of design than explicit FSMs
- **limitation:** each state may be entered from only one other state



# The multiple event-control expressions separate the activity of the behavior into distinct clock cycles of the machine

```
always @ (posedge clk)    // Synchronized event before first  
                           // assignment
```

```
begin
```

```
reg_a<=reg_b;    // Executes in first clock cycle
```

```
reg_c<=reg_d;    // Executes in first clock cycle
```

```
@ (posedge clk)    // Begins second clock cycle
```

```
begin
```

```
reg_g<=reg_f;    // Executes in second clock cycle
```

```
reg_m<=reg_r;    // Executes in second clock cycle
```

```
end
```

```
end
```



## 6.9.2 Synthesis of counters

- Synthesize a variety of counters and shift registers as single-cycle implicit state machines

### Ex 6.29 a 4-bit ripple counter


1. can be implemented with **T-type flip-flops**
- 2. has limited practical application**
3. the output count is also **subject to glitches during the transitions**



```
module ripple_counter (count, toggle, clock, reset,);
output [3: 0]    count;
input  toggle, clock, reset;
reg    [3: 0]    count;
wire    c0, c1, c2;
    assign c0 = count[0];
    assign c1 = count[1];
    assign c2 = count[2];
    always @ (posedge reset or posedge clock)
        if (reset == 1'b1) count[0] <= 1'b0; else
            if (toggle == 1'b1) count[0] <= ~count[0];
    always @ (posedge reset or negedge c0)
        if (reset == 1'b1) count[1] <= 1'b0; else
            if (toggle == 1'b1) count[1] <= ~count[1];
    always @ (posedge reset or negedge c1)
        if (reset == 1'b1) count[2] <= 1'b0; else
            if (toggle == 1'b1) count[2] <= ~count[2];
    always @ (posedge reset or negedge c2)
        if (reset == 1'b1) count[3] <= 1'b0; else
            if (toggle == 1'b1) count[3] <= ~count[3];
endmodule
```




# Structure of a 4-bit ripple counter

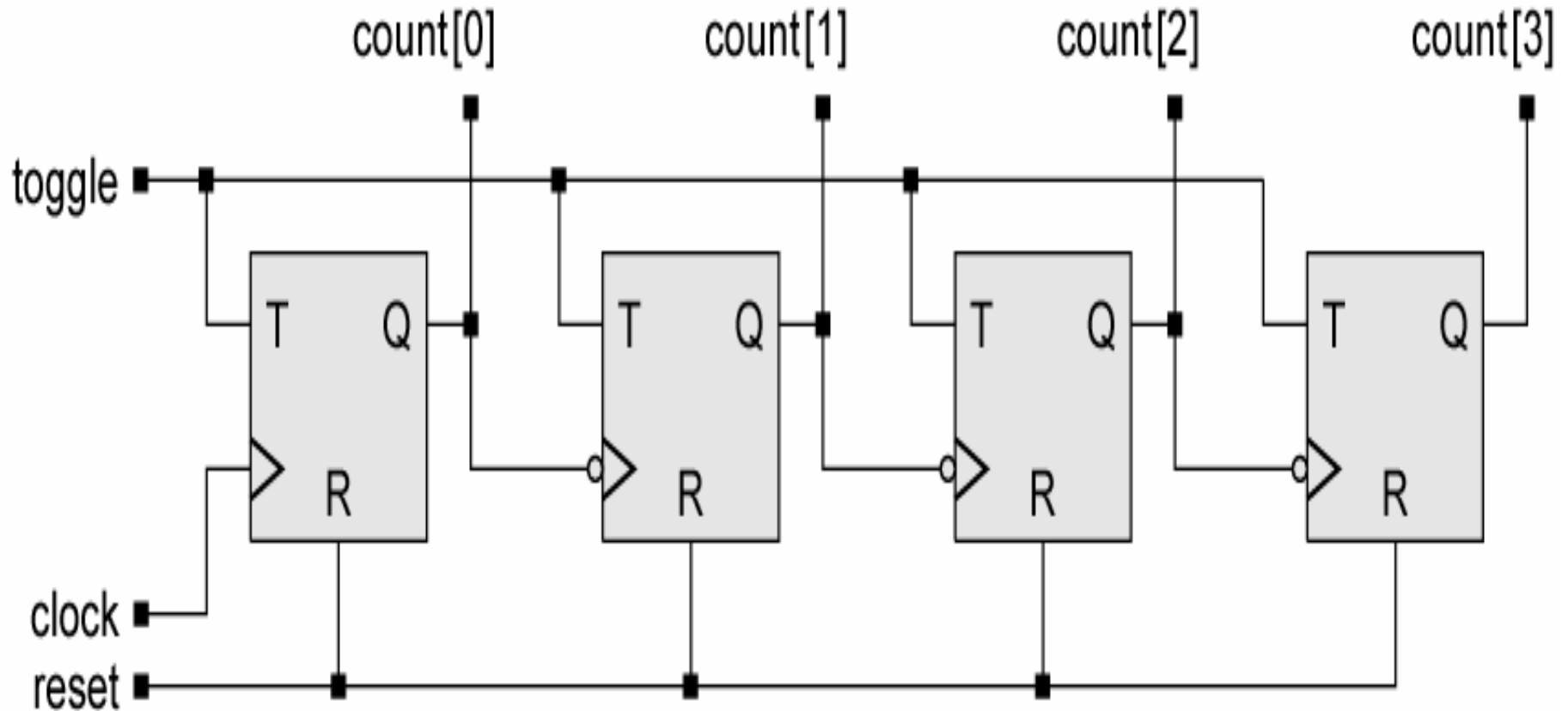


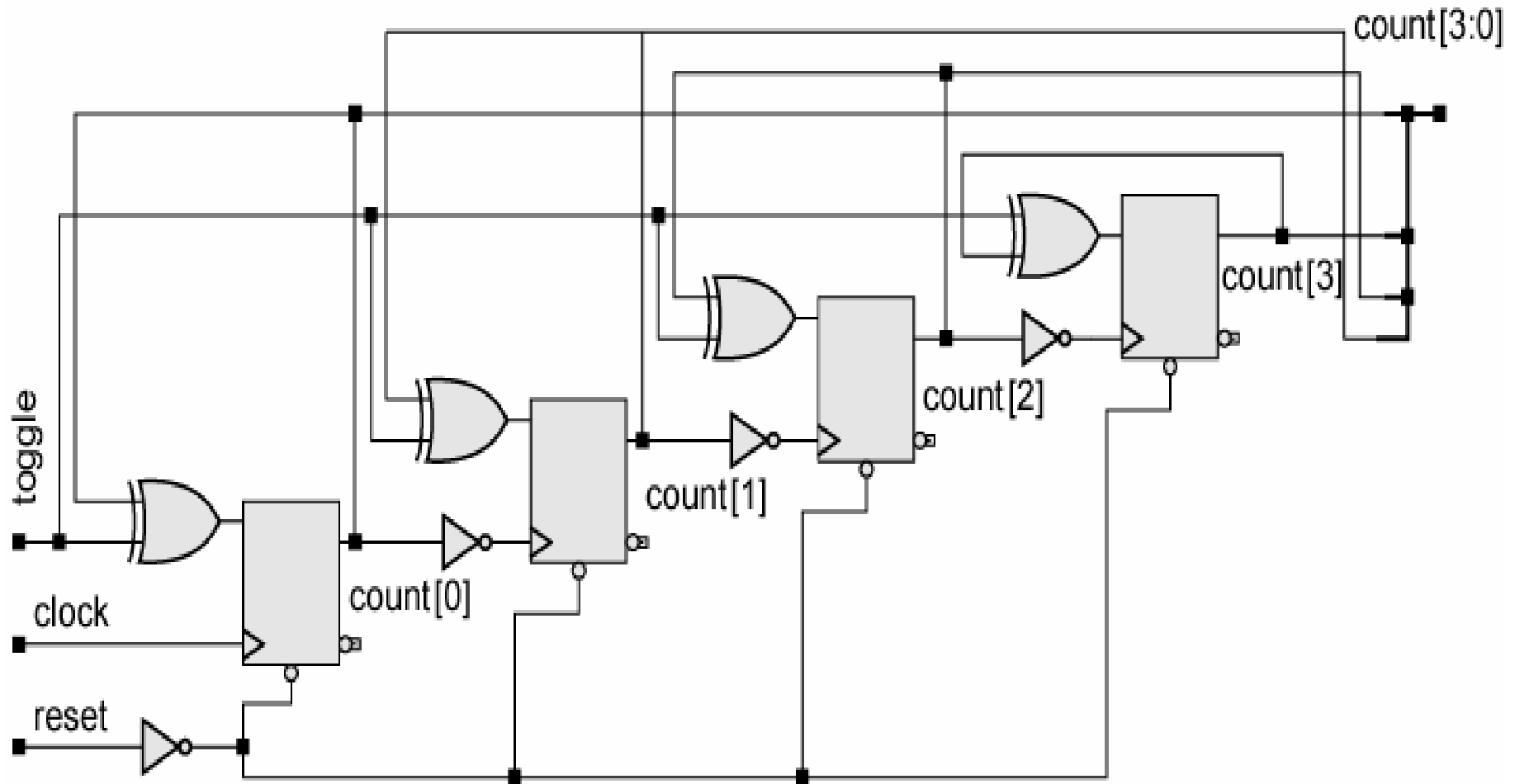
# Synthesized circuit for 4-bit ripple counter





## 6.9.3 Synthesis of registers

- Storage elements in a sequential machine can be implemented with flip-flops or with latches, depending on the clocking scheme used by the machine



## Ex 6.31: Shift register with combinational logic forming the register variable


```
module shifter_1 (sig_d, new_signal, Data_in, clock, reset);  
  output sig_d, new_signal;  
  input Data_in, clock, reset;  
  reg sig_a, sig_b, sig_c, sig_d, new_signal;  
  always @ (posedge reset or posedge clock)  
    begin if (reset==1'b1)  
      begin  
        sig_a<=0;  
        sig_b<=0;  
        sig_c<=0;  
        sig_d<=0;  
      end else  
        begin  
          sig_a<=Data_in;  
          sig_b<=sig_a;  
          sig_c<=sig_b;  
          sig_d<=sig_c;  
          new_signal<=(~sig_a) & sig_b;  
        end  
      end  
    end  
endmodule
```

How many flip-flops?





# Generic structure

 




# Example 6.32

```
module shifter_2 (sig_d, new_signal, Data_in, clock, reset);  
output sig_d, new_signal;  
input Data_in, clock, reset;  
reg sig_a, sig_b, sig_c, sig_d, new_signal;  
always @ (posedge reset or posedge clock)  
  begin if (reset==1'b1)  
    begin  
      sig_a<=0;  
      sig_b<=0;  
      sig_c<=0;  
      sig_d<=0;  
    end  
  else begin  
    sig_a<=shift_input;  
    sig_b<=sig_a;  
    sig_c<=sig_b;  
    sig_d<=sig_c;  
  end  
end  
assign new_signal<=(~sig_a) & sig_b;  
endmodule
```

How many flip-flops?



 In shifter\_2, new\_signal is formed **outside of the behavior in a continuous assignment**, and is synthesized as the combinational logic





## Ex 6.33 Accumulator-1

```
module Add_Accum_1 (accum, overflow, data,  
    enable, clk, reset_b);  
    output [3:0] accum;  
    output overflow;  
    input [3:0] data;  
    input enable, clk, reset_b;  
    reg accum, overflow;  
    always @ (posedge clk or negedge reset_b)  
        if (reset_b==0)  
            begin accum<=0; overflow<=0; end  
        else if (enable) {overflow, accum} <=accum+data;  
            //concatenate the carry and sum into one  
endmodule
```




# Accumulator-2

```
module Add_Accum_2
    (accum, overflow, data, enable, clk, reset_b);
output [3:0] accum;
output overflow;
input [3:0] data;
input enable, clk, reset_b;
reg overflow;
wire [3:0] sum;
assign {overflow, sum}=accum+data;
    //concatenate the carry and sum into one
always @ (posedge clk or negedge reset_b)
    if (reset_b==0) begin accum<=0;
    else if (enable) accum<=sum;
endmodule
```

ACC 1-2's  
difference ?




# Simulation result

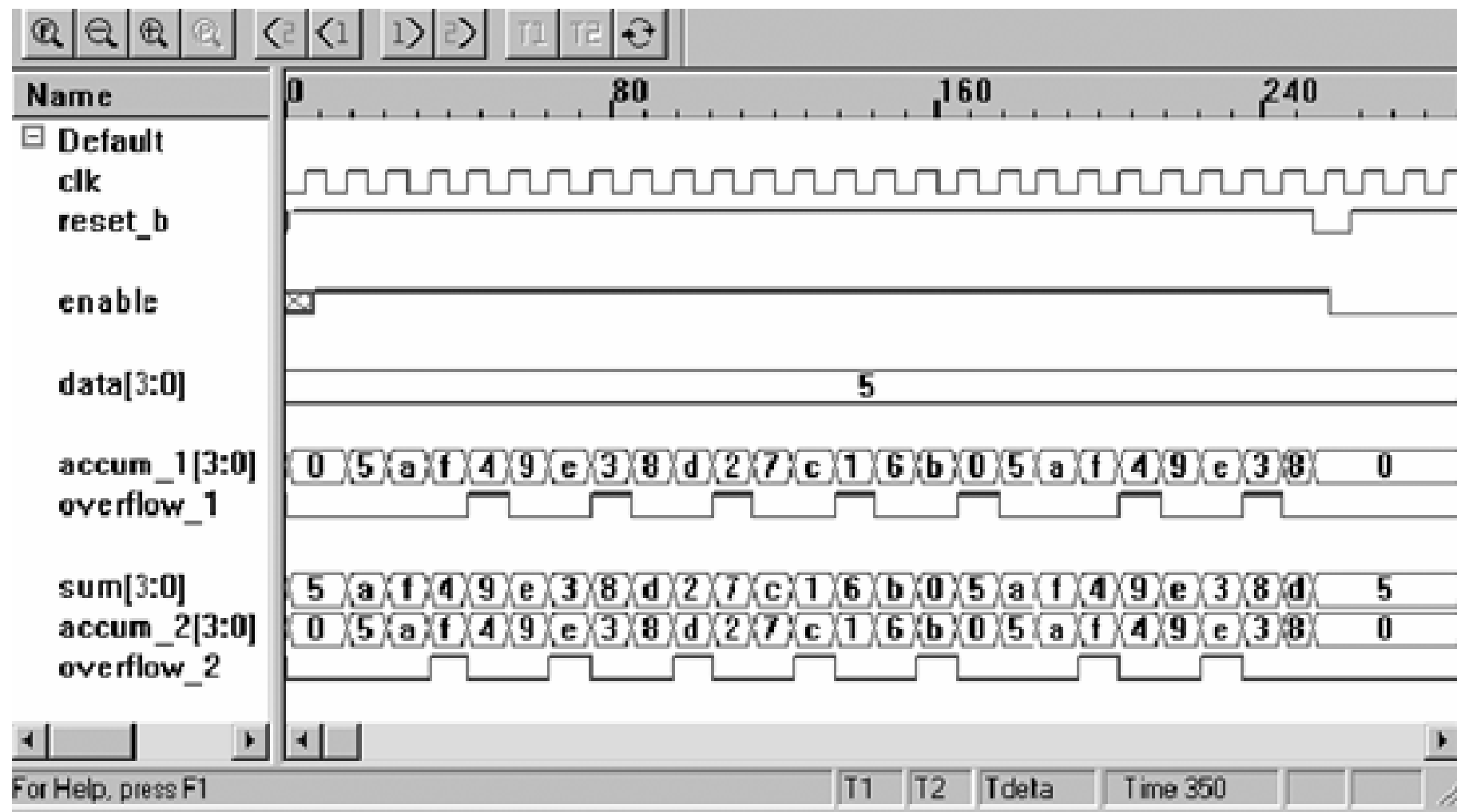

(a)



# Synthesis circuit

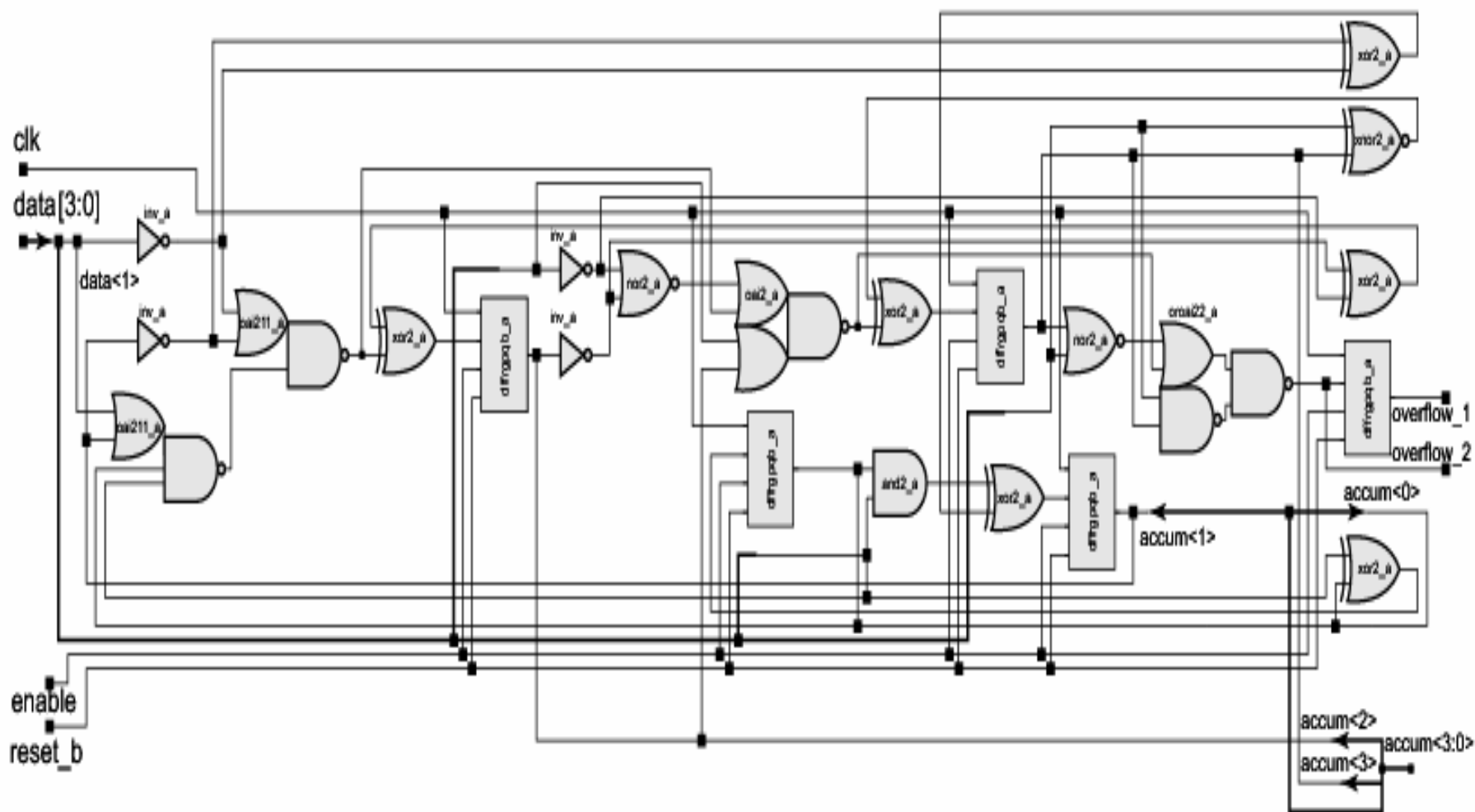



## 6.10 Resets

- Every sequential module in a design should have a reset signal.
- Otherwise, the initial state of the machine and its operation cannot be controlled
- **If an initial state cannot be assigned, the machine cannot be tested for manufacturing defects**





## 6.11 Synthesis of gated clocks and clock enables

- Designers **avoid using gated clocks**
- Low-power designs deliberately disable clocks **to reduce or eliminate power wasted** by useless switching of transistors
- **Improperly gated clocks can cause the clock signal to violate a flip-flop's constraint on the minimum width of the clock pulse**



# The recommended way to write a Verilog description that synthesizes a gated clock


```
module best_gated_clock
    (clock, reset_, data_gate, data, Q);
input clock, reset_, data, data_gate;
output Q;
reg Q;
always @ (posedge clock or negedge reset_)
    if (reset_==0) Q<=0;
    else if (data_gate) Q<=data;
                                     // infers storage
endmodule
```



# Synthesis of Gated Clocks

always @ (posedge clk)

if (enable == 1) q\_out <= Data\_in;

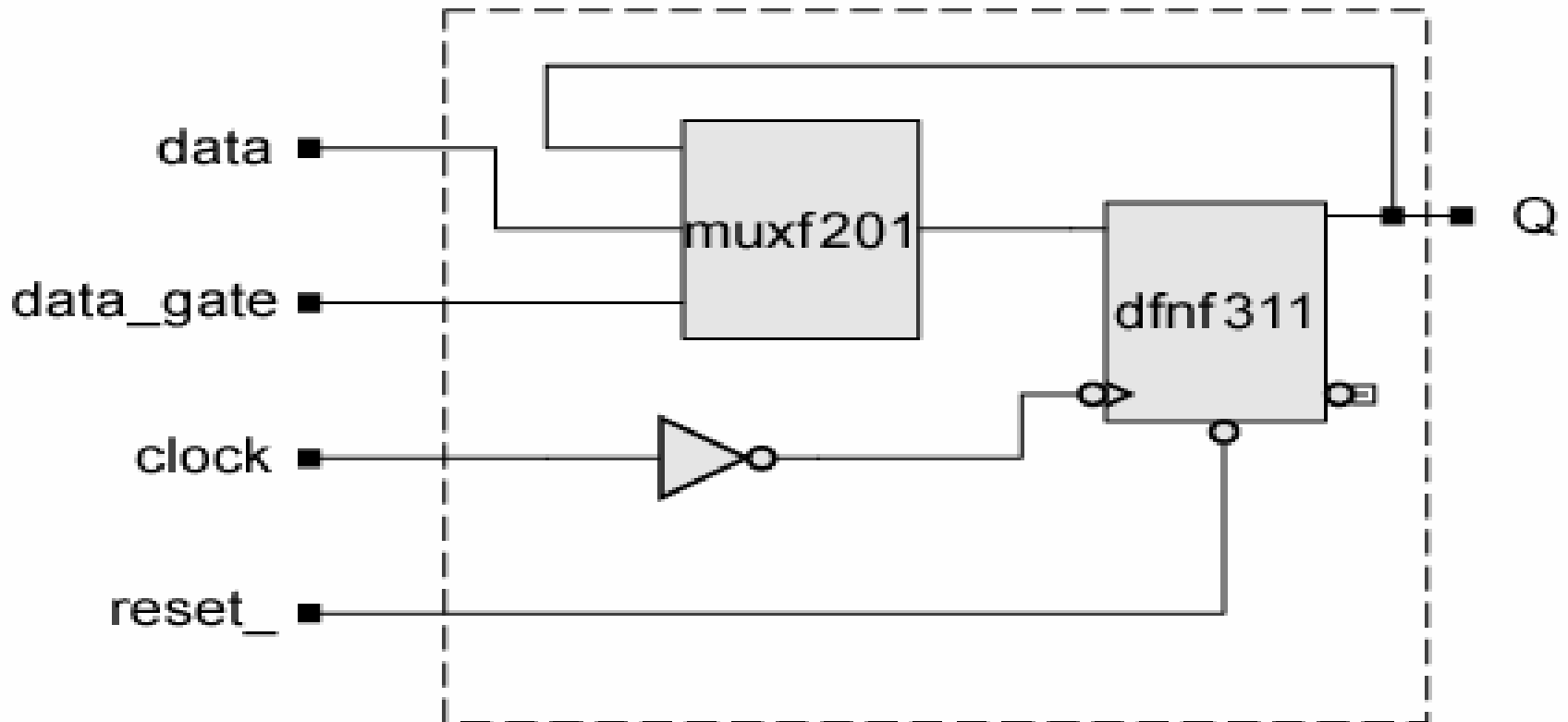



## 6.12 Anticipating the results of synthesis

- The results of synthesis should not be taken **at face value**.
- It is advisable to anticipate what the synthesis process will produce and then examine the results against those expectations
- The section will cover some of **the basic rules that will help the designer anticipate the results of synthesis and write Verilog descriptions** that infer the desired results



## 6.12.1 Synthesis of data types

- Nets that are primary inputs or outputs will be retained in the design
- **Internal nets may be eliminated** by the action of the synthesis tool
- **Integers are stored as 32-bit data objects**
- Use sized numbers (e.g., 8'b0110\_1110) to reduce the size of the register required to hold a parameter
- **x or z have no hardware counterpart**



## 6.12.2 Operator grouping

- All Verilog operators may be used in expressions forming a binary or Boolean value
- Some operators may be treated in a special way by the technology mapper
- **+, -, <, >, = may be mapped directly to a library element**
- Otherwise, the synthesis tool will convert the operator into an equivalent set of Boolean equations
- **Some operators must be restricted for successful synthesis**



# Restricted operators

- **Shift operators (<<,>>) are synthesizable, when the shift is by a constant number of bits**
- The reduction, bitwise, and logical connective operators are each equivalent to operations performed by a logic gate  
(& ~& | ~| ^ ~^ ^~ reduction (~^ and ^~ are equivalent))
- **The conditional operator (?...:) synthesizes into library muxes or into gates that implement the functionality of a mux**
- When an expression has multiple operators, the architecture of the synthesized result will reflect the parsing of the compiler and the precedence of the operators



## Ex 6.35 Operator group



```
module operator_group (sum1, sum2, a, b, c, d);  
    output [4:0] sum1, sum2;  
    input [3:0] a, b, c, d;  
  
    assign sum1=a+b+c+d;  
    assign sum2=(a+b)+(c+d);  
endmodule
```





For speed, sum2 will be approximately 30% faster.

  For low power, input d forming sum1 could be used for the signal that changes more frequently.





## 6.12.3 Expression substitution

- Synthesis tools perform expression substitution to determine the outcome of a sequence of procedural (blocking) assignments in a behavior
- If it is necessary for procedural assignments to be used, be aware that expression substitution will affect the result



## Example 6.36

```
module multiple_reg_assign
```

```
    (data_out1, data_out2, data_a, data_b, data_c, data_d, sel, clk);
```

```
    output [4:0] data_out1, data_out2;
```

```
    input [3:0] data_a, data_b, data_c, data_d;
```

```
    input sel, clk;
```

```
    reg data_out1, data_out2;
```

```
    always @ (posedge clk)
```

```
    begin
```

```
        data_out1=data_a+data_b;
```

```
        data_out2=data_out1+data_c;
```


```
        if (sel==1'b0) data_out1=data_out2+data_d;
```

```
    end
```

```
endmodule
```




# Dataflow structure

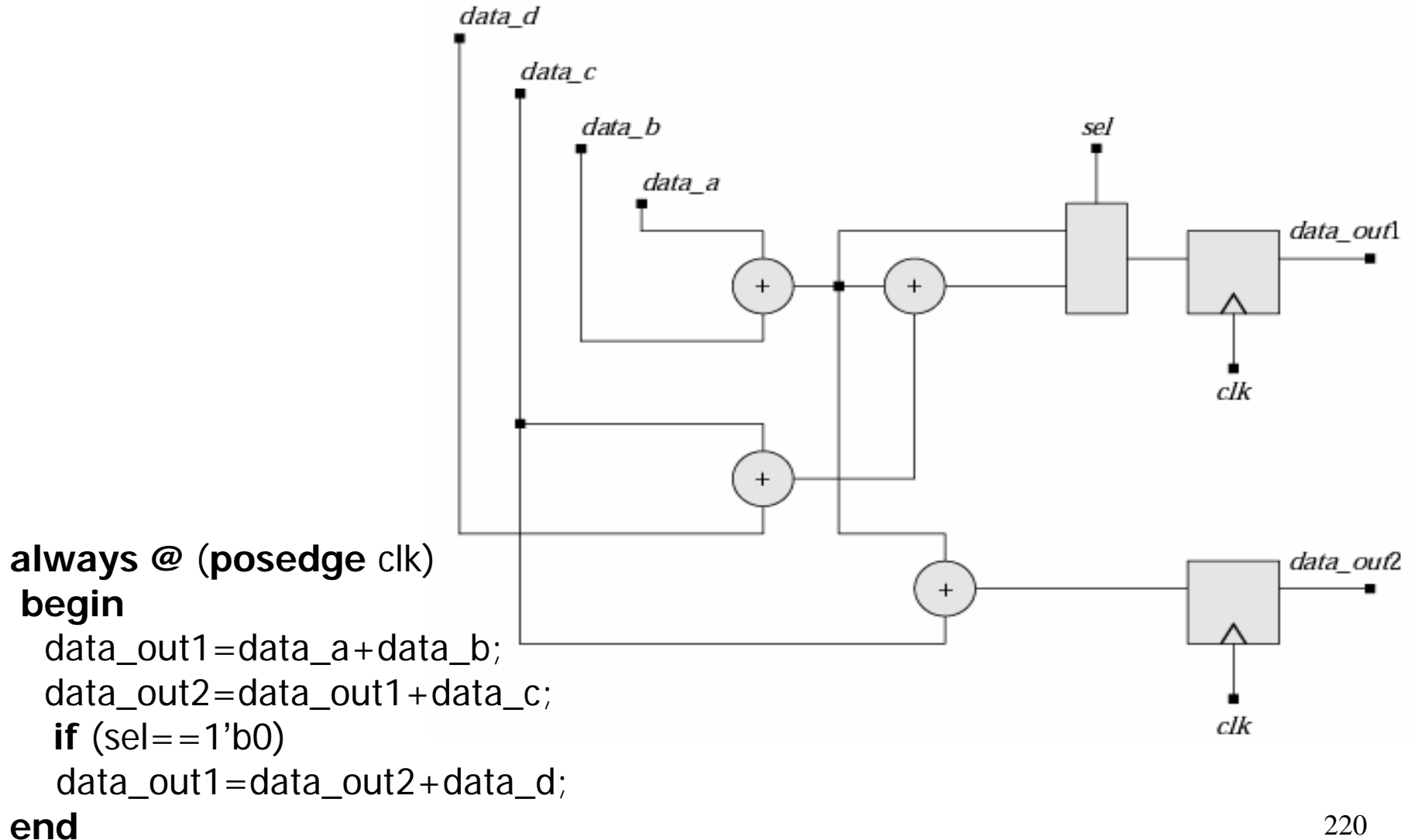



# Synthesize to the circuit

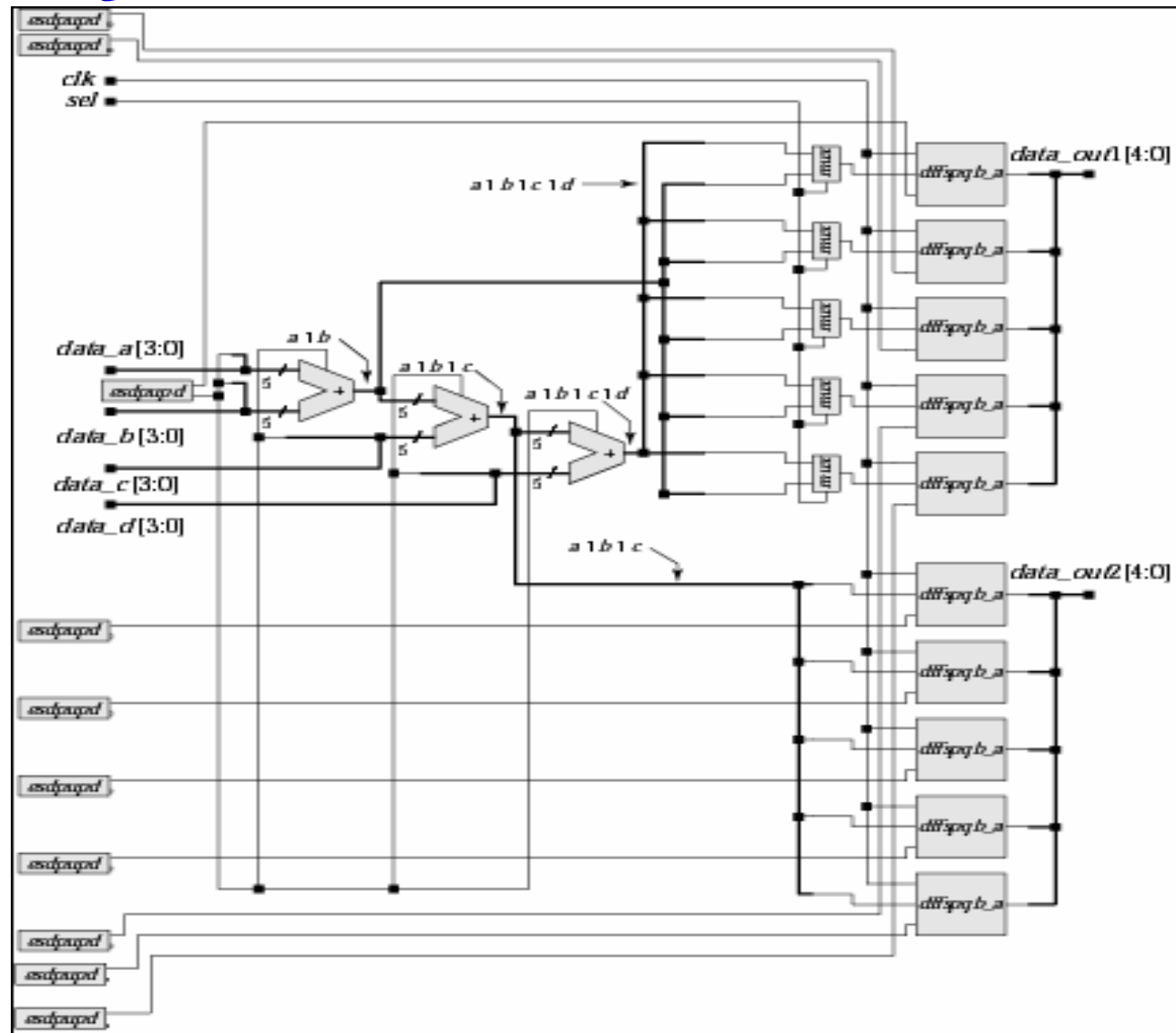



```
module expression_sub
(data_out1, data_out2, data_a, data_b, data_c,
  data_d, sel, clk);
  output [4:0] data_out1, data_out2;
  input [3:0] data_a, data_b, data_c, data_d;
  input sel, clk;
  reg [4:0] data_out1, data_out2;
  always @ (posedge clk)
  begin
    data_out2=data_a+data_b+data_c;
    if (sel==1'b0)
      data_out1=data_a+data_b+data_c+data_d;
    else
      data_out1=data_a+data_b;
    end
  endmodule
```



# a recommended style which implements equivalent logic **with the nonblocking operator**

```
module expression_sub_nb
    (data_out1nb, data_out2nb, data_a, data_b, data_c, data_d, sel, clk);
output [4:0] data_out1nb, data_out2nb;
input [3:0] data_a, data_b, data_c, data_d;
input sel, clk;
reg [4:0] data_out1, data_out2;
always @ (posedge clk)
    begin
        data_out2nb<=data_a+data_b+data_c;
        if (sel==1'b0)
            data_out1nb<=data_a+data_b+data_c+data_d;
        else
            data_out1nb<=data_a+data_b;
        end
    endmodule
```




## 6.13 Synthesis of loops

- A loop is ***data-independent (static)***, if the number of its iterations can be determined by the compiler before simulation
- A loop is **data-dependent** if the number of iterations depends on some variable during operation
- A data-dependent loop may have a **dependency on embedded timing controls**





# Possible loop structures

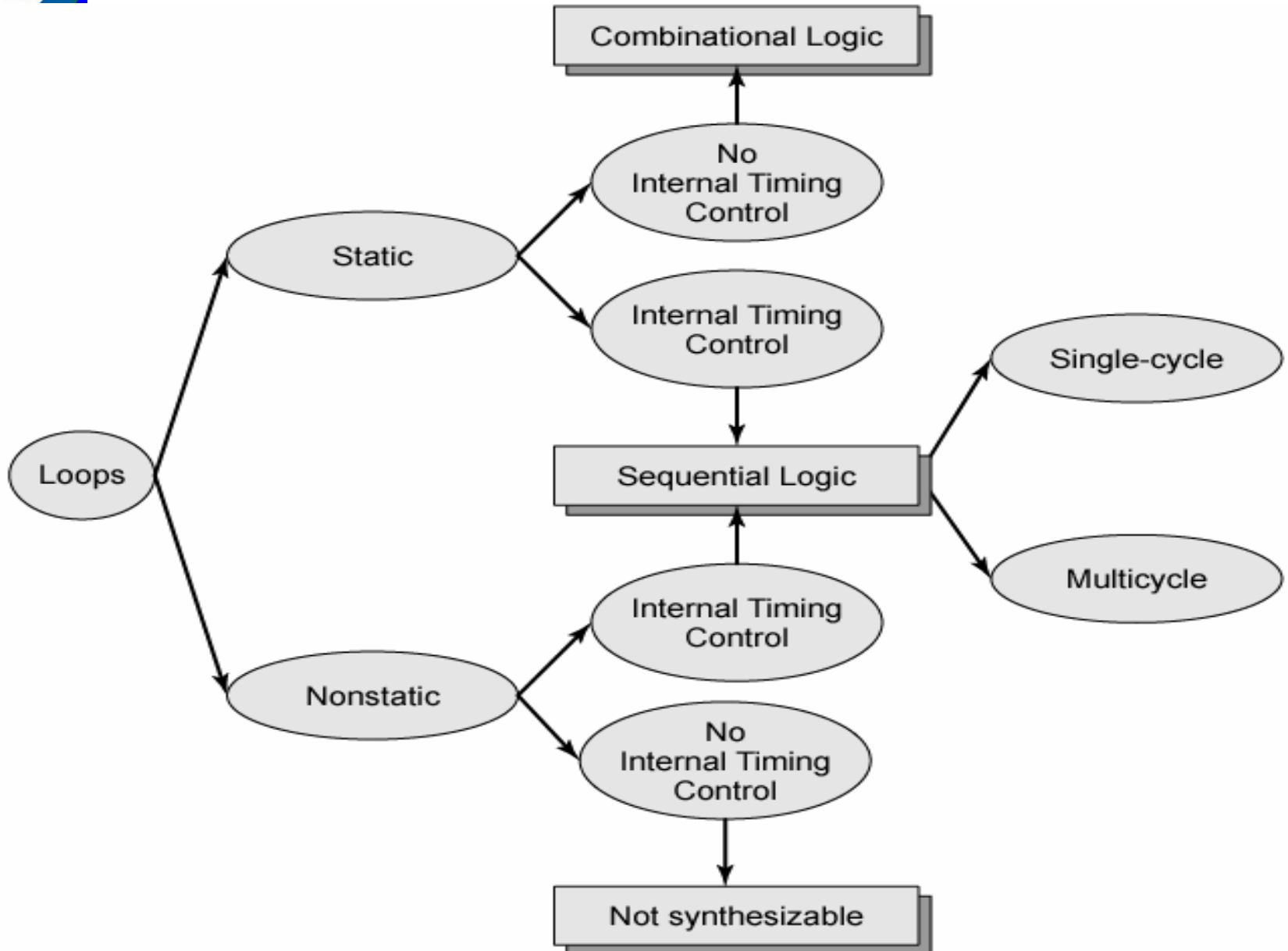



# In principle

- Static loops can be synthesized using *repeat*, *for*, *while*, and *forever* loop constructs
- A given **vendor** might choose to confine the descriptive style of a static loop to a particular construct
- Non-static loops that do not have internal timing controls cannot be synthesized



## 6.13.1 Static loops without embedded timing controls

- If a loop has **no internal timing controls and no data dependencies**, its computational activity is implicitly **combinational**
- The iterative computational sequence has a non-iterative counterpart obtained by unrolling the loop



## Example 6.37

```
module for_and_loop_comb (out, a, b);
```

```
    output [3:0] out;
```

```
    input [3:0] a, b;
```

```
    reg [2:0] i;
```

```
    reg [3:0] out;
```

```
    wire [3:0] a, b;
```

```
    always @ (a or b)
```


```
        begin
```

```
            for (i=0;i<=3;i=i+1)
```

```
                out[i]=a[i] & b[i];
```

```
        end
```

```
endmodule
```

 




# The unrolled loop is equivalent to:

**always @ (a or b)**

**begin**

**for (i=0;i<=3;i=i+1) out[i]=a[i] & b[i];**

**end**

 

**out[0]=a[0] & b[0];**

**out[1]=a[1] & b[1];**

**out[2]=a[2] & b[2];**

**out[3]=a[3] & b[3];**



# ***For* loop and *repeat* loop**

- A ***for*** loop with static range is equivalent to a ***repeat*** loop with the same range
- **Some tools support only the *for* loop**



## Example 6.38

```
module count_ones_a (bit_count, data, clk, reset);  
  parameter data_width=4;  
  parameter count_width=3;  
  output [count_width-1:0] bit_count;  
  input [data_width-1:0] data;  
  input clk, reset;  
  reg [count_width-1:0] count, bit_count, index;  
  reg [data_width-1:0] temp;  
  always @ (posedge clk)  
    if (reset) begin count=0; bit_count=0; end  
    else begin  
      count=0; bit_count=0; temp=data;  
      for (index = 0; index < data_width; index = index + 1)  
        begin count=count+temp[0]; temp=temp >>1; end  
      bit_count=count;  
    end  
endmodule
```



## 6.13.2 Static loops with embedded timing controls

- If a static loop has an embedded edge-sensitive event-control expression, **the computational activity of the loop is synchronized and distributed over one or more cycles of the clock**
- As a result, **the behavior is that of an implicit state machine** in which each iteration of the loop occurs after a clock edge





## Ex 6.39

```
module count_ones_b0 (bit_count, data, clk, reset);  
    parameter data_width = 4;  
    parameter count_width = 3;  
    output [count_width-1: 0] bit_count;  
    input [data_width-1: 0] data;  
    input clk, reset;  
    reg [count_width-1: 0] count, bit_count;  
    reg [data_width-1: 0] temp;  
    integer index;  
    always begin: wrapper_for_synthesis  
        @ (posedge clk) begin: machine  
            if (reset) begin bit_count = 0; disable machine; end  
            else
```



```
count = 0; bit_count = 0; index = 0; temp = data;
forever @ (posedge clk)
  if (reset) begin bit_count = 0; disable machine; end
  else if (index < data_width-1)
    begin
      count = count + temp[0];
      temp = temp >> 1;
      index = index + 1;
    end
  else begin //index=3,no shift
    bit_count = count + temp[0];
    disable machine;
  end

end // machine
end // wrapper_for_synthesis
endmodule
```



# Alternative approach-1

```
module count_ones_b1 (bit_count, data, clk, reset);  
  parameter data_width=4;  
  parameter count_width=3;  
  output [count_width-1:0] bit_count;  
  input [data_width-1:0] data;  
  input clk, reset;  
  reg [count_width-1:0] count, bit_count, index;  
  reg [data_width-1:0] temp;  
  integer index;  
  always begin: wrapper_for_synthesis  
    @ (posedge clk)  
      begin: machine
```



```
if (reset) begin bit_count=0; disable machine; end
else begin count=0; bit_count=0; index=0; temp=data;
    while (index<data_width-1) begin
        if (reset) begin bit_count=0; disable machine; end
        else if ((index<data_width) && (temp[0]))
            count=count+1;
            temp=temp>>1;
            index=index+1;
        @ (posedge clk)
    end
    if (reset) begin bit_count=0; disable machine; end
    else bit_count=count;
    disable machine;
end
end // machine
end // wrapper_for_synthesis
endmodule
```



## Alternative approach-2


```
module count_ones_b2 (bit_count, data, clk,  
    reset);  
  
    parameter data_width=4;  
    parameter count_width=3;  
    output [count_width-1:0] bit_count;  
    input [data_width-1:0] data;  
    input clk, reset;  
    reg [count_width-1:0] count, bit_count, index;  
    reg [data_width-1:0] temp;  
    integer index;  
    always begin: machine
```



```
for (index=0; index<=data_width; index=index+1)
  begin
    @ (posedge clk)
      if (reset) begin bit_count=0; disable machine; end
      else if (index==0) begin
        count=0; bit_count=0; index=0; temp=data; end
      else if (index<data_width) begin
        count=count+temp[0];
        temp=temp>>1; end
      else bit_count=count+temp[0];
    end
  end // machine
endmodule
```




# Simulation result (reset begin)

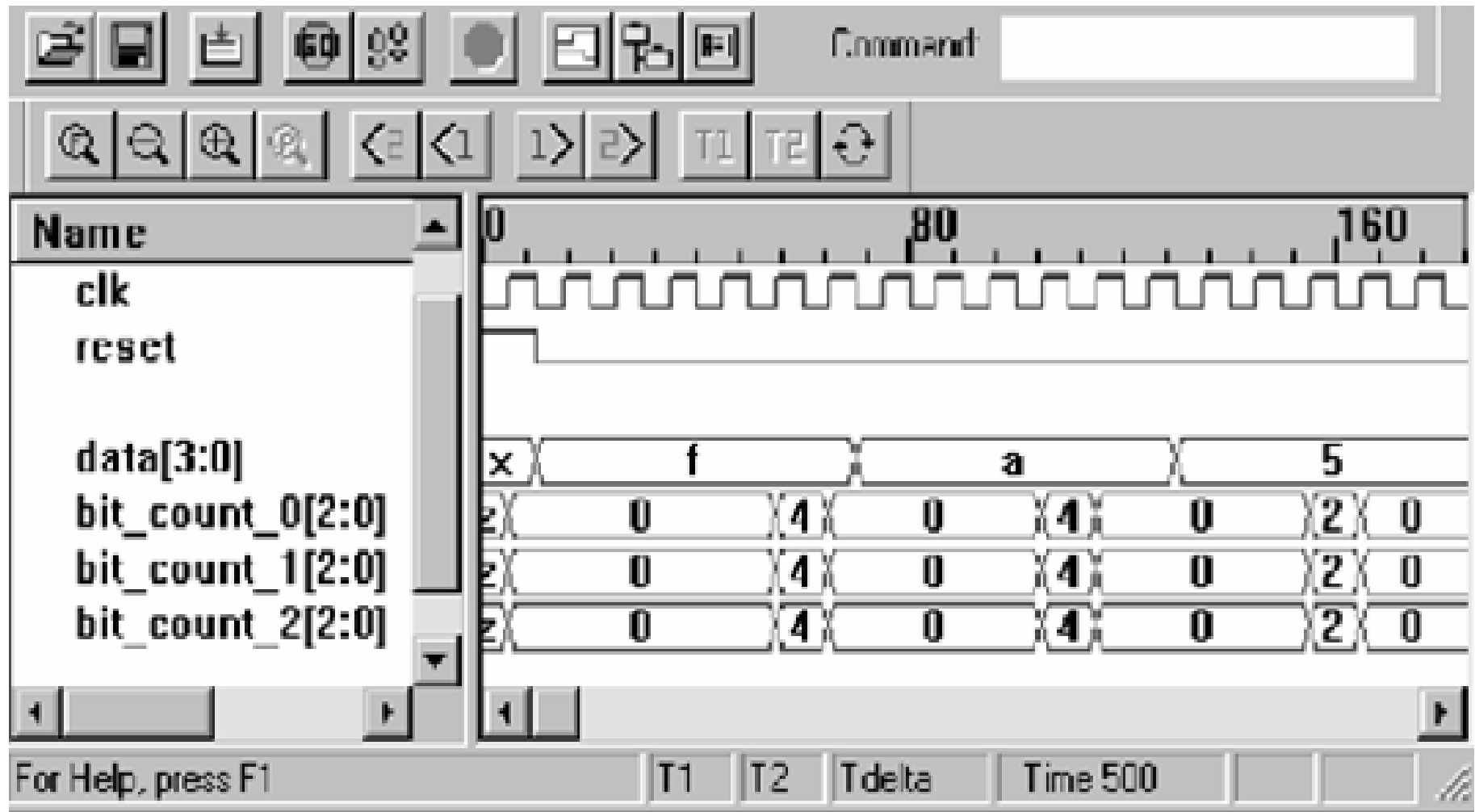

(a)



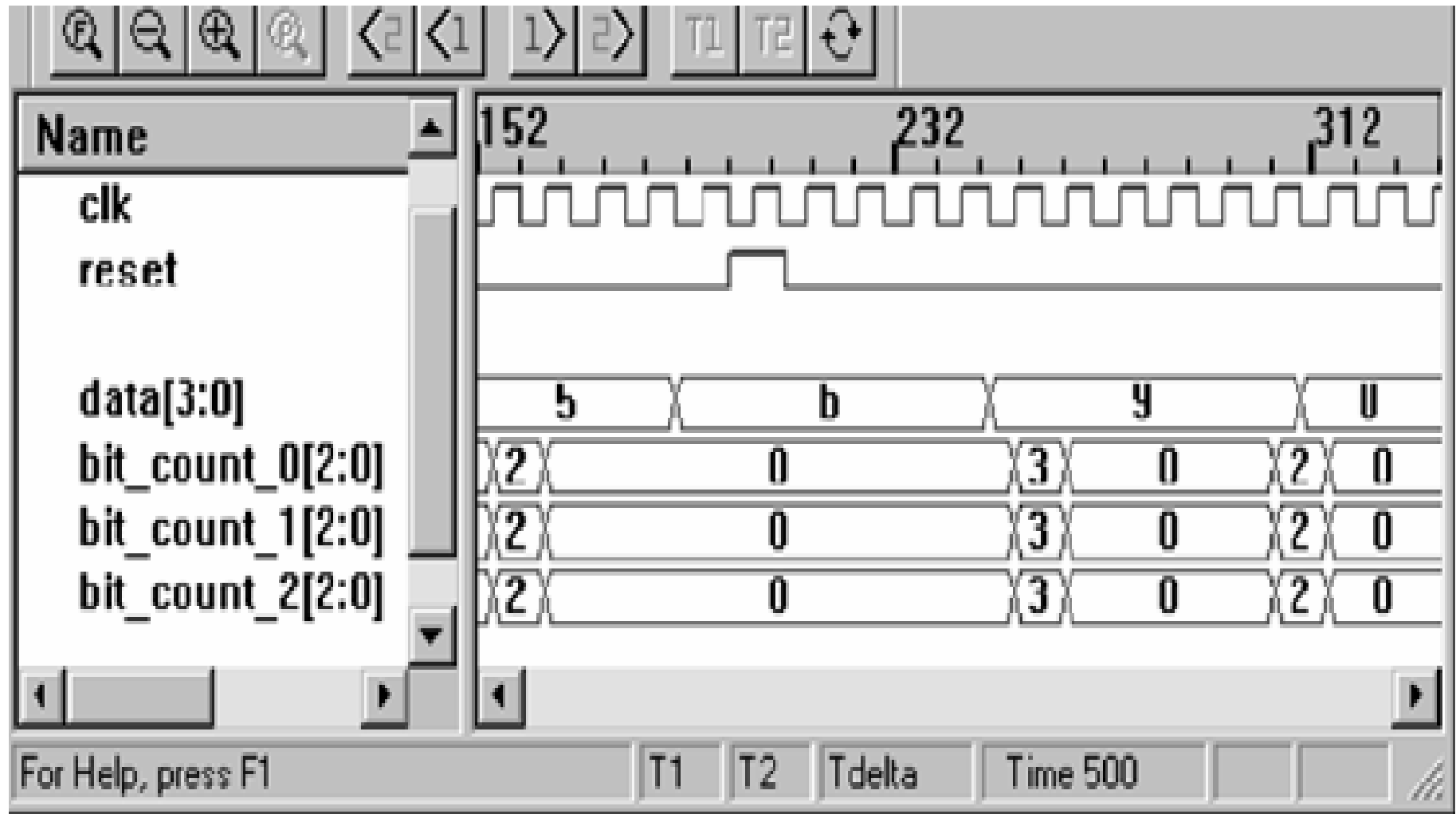
# Simulation result (reset at the random position)







# The synthesized circuit

 

(b)



## 6.13.3 Nonstatic loops without embedded timing controls

- **If the loop does not have embedded timing control, the behavior can be simulated, but it cannot be synthesized**
- Under the action of a simulator, the behavior is virtually sequential and can be simulated
- **But hardware cannot execute** the computation of the loop in a single cycle of the clock




# Example 6.40

```
module count_ones_c (bit_count, data, clk, reset);  
  parameter data_width=4;  
  parameter count_width=3;  
  output [count_width-1:0] bit_count;  
  input [data_width-1:0] data;  
  input clk, reset;  
  reg [count_width-1:0] count, bit_count, index;  
  reg [data_width-1:0] temp;  
  always @ (posedge clk)  
    if (reset) begin count=0; bit_count=0; end  
    else begin  
      count=0; temp=data;  
      for (index=0; | temp; index=index+1)  
        begin  
          if (temp[0]) count=count+1; temp=temp>>1;  
        end  
      bit_count=count;  
    end  
endmodule
```



# Simulation result

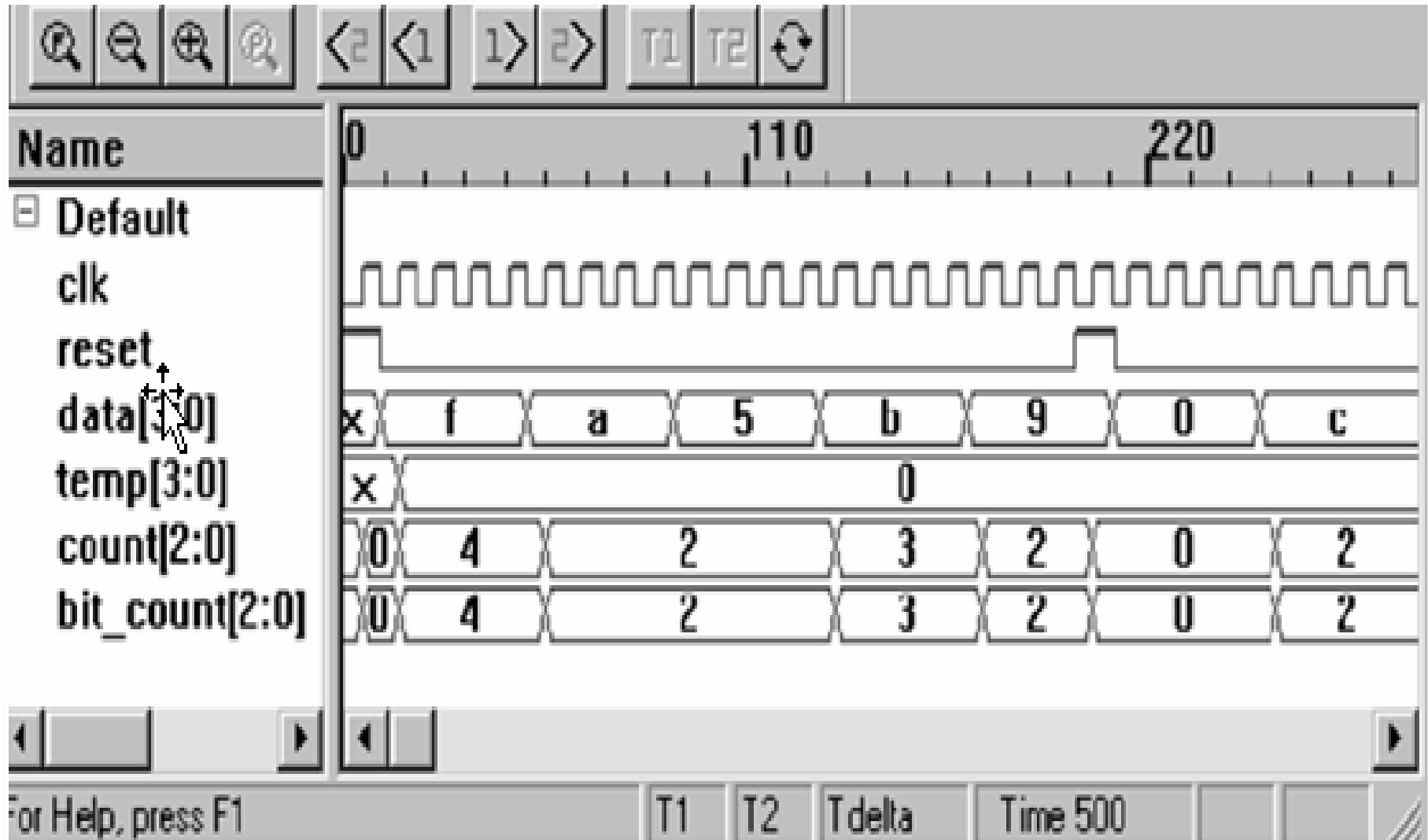



## 6.13.4 Nonstatic loops with embedded timing controls

- A nonstatic loop may implement a multicycle operation
- The data dependency alone is not a barrier to synthesis because the activity of the loop can be distributed over multiple cycles of the clock
- However, **the iterations of a non-static loop must be separated by a synchronizing edge-sensitive event control expression in order to be synthesized.**



## Example 6.41

```
module count_ones_d (bit_count, data, clk, reset);  
  parameter data_width=4;  
  parameter count_width=3;  
  output [count_width-1:0] bit_count;  
  input [data_width-1:0] data;  
  input clk, reset;  
  reg [count_width-1:0] count, bit_count, index;  
  reg [data_width-1:0] temp;  
  always begin: wrapper_for_synthesis  
    @ (posedge clk)  
    if (reset) begin count=0; bit_count=0; end
```



```
else begin: bit_counter
```

```
    count=0;
```

```
    temp=data;
```

```
    while (temp)
```

```
        @ (posedge clk)
```

```
            if (reset) begin count=2'b0;
```

```
                disable bit_counter; end
```

```
            else begin
```

```
                count=count+temp[0];
```

```
                temp=temp>>1;
```

```
            end
```

```
        @ (posedge clk)
```

```
            if (reset) begin count=0;
```

```
                disable bit_counter; end
```

```
            else bit_count=count;
```


```
    end    // bit_counter
```

```
end // wrapper_for_synthesis
```

```
endmodule
```



# Simulation result

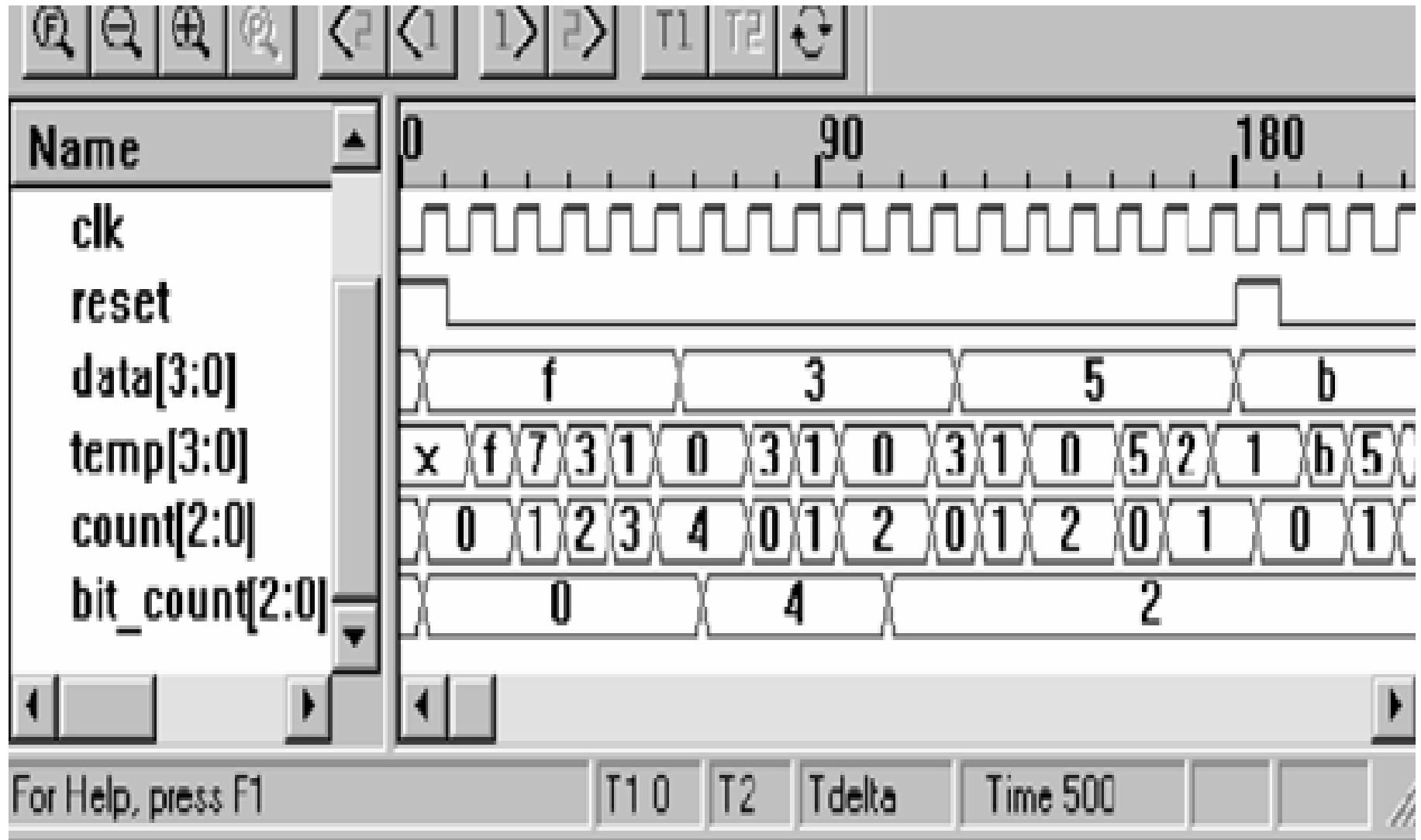





# Another version

```
module count_ones_SD (bit_count, done, data, start, clk, reset);  
  parameter data_width=4;  
  parameter count_width=3;  
  output [count_width-1:0] bit_count;  
  output done;  
  input [data_width-1:0] data;  
  input start, clk, reset;  
  reg [count_width-1:0] count, bit_count, index;  
  reg [data_width-1:0] temp;  
  reg done, start;  
  always@ (posedge clk) begin: bit_counter  
    if (reset) begin count=0; bit_count=0; done=0; end
```



**else if start** begin

done=0;

count=0;

bit\_count=0;

temp=data;

for (index=0; index<data\_width; index=index+1)

**@ (posedge clk)**

**if (reset) begin** count=0; bit\_count=0; done=0;

**disable** bit\_counter; **end**

**else begin**

count=count+temp[0];

temp=temp>>1; **end**

**@ (posedge clk)** // Required for final register transfer

**if (reset) begin** count=0; bit\_count=0; done=0;

**disable** bit\_counter; **end**

**else begin** bit\_count=count; done=1; **end** //output


**end**

**end**

**endmodule**



# Simulation result

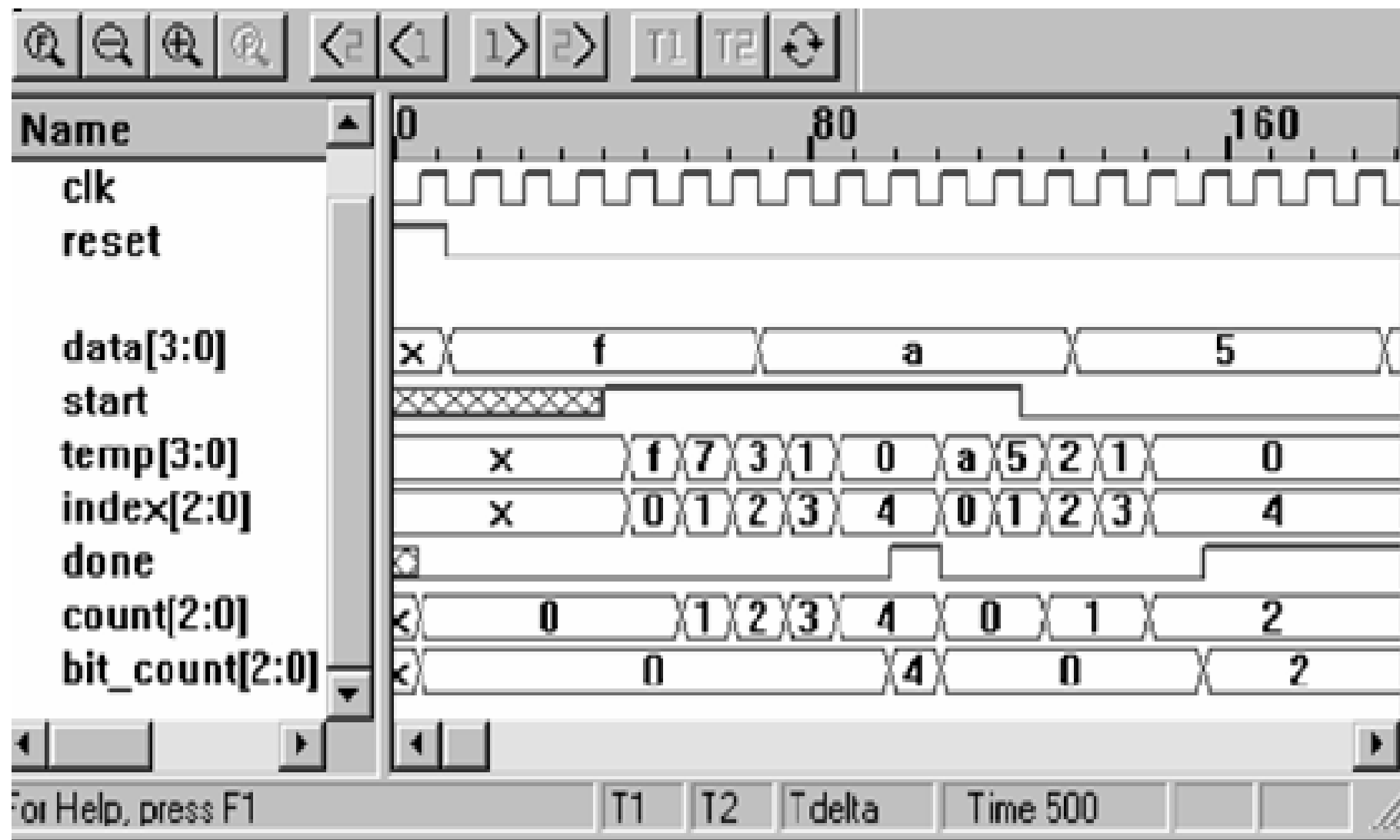




## 6.13.5 State-machine replacements for unsynthesizable loops

- Synthesis tools **do not support non-static loops** that do not have embedded timing controls
- Such machines are not directly synthesizable
- But their loop structures can be **replaced by equivalent synthesizable sequential behavior.**



## Ex 6.42 ASMD chart of count\_ones\_SM

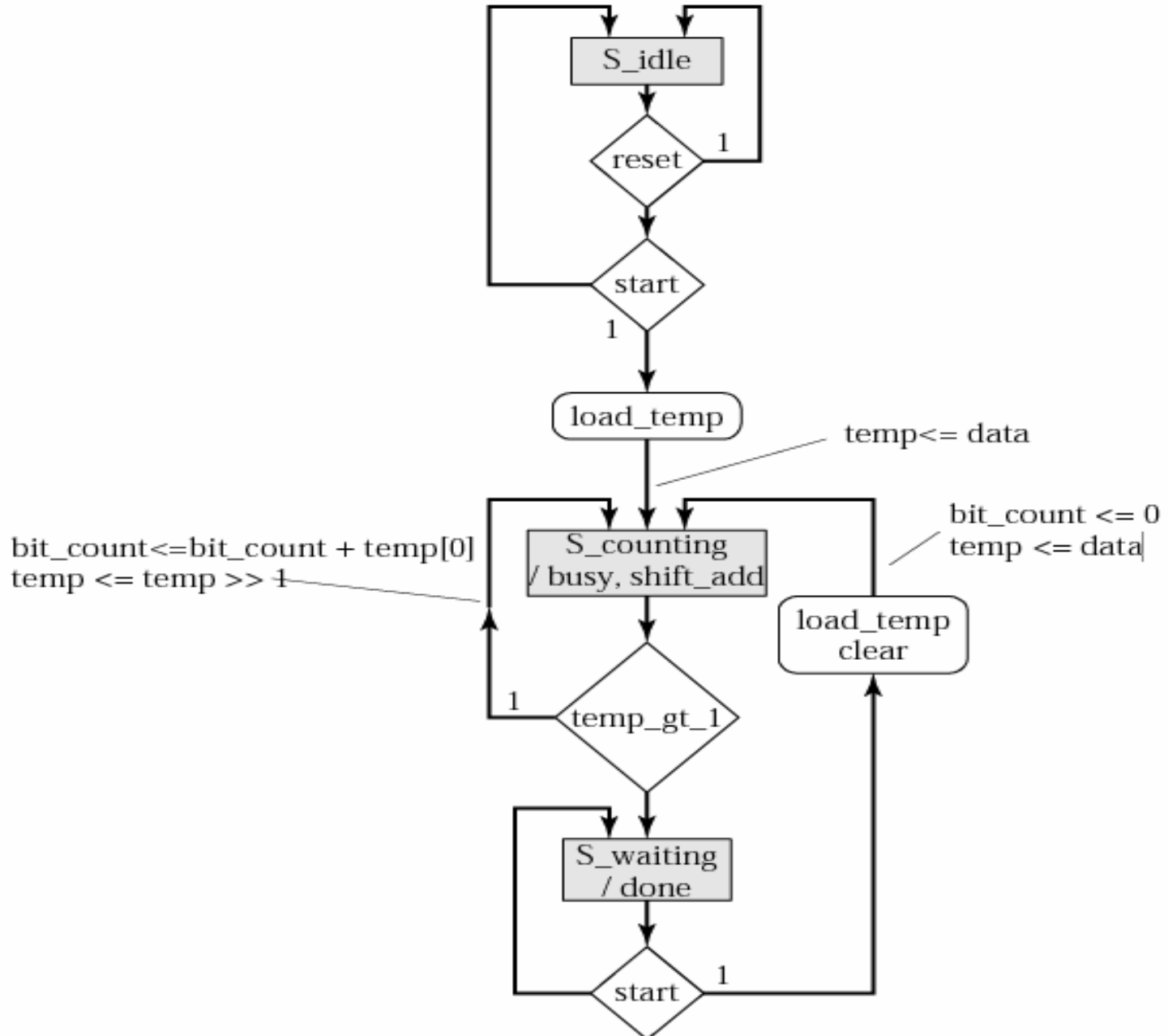



```
module count_ones_SM (bit_count, busy, done, data, start, clk,  
    reset);  
    parameter counter_size=3;  
    parameter word_size=4;  
    output [counter_size-1:0] bit_count;  
    output busy, done;  
    input [word_size-1:0] data;  
    input start, clk, reset;  
    wire load_temp, shift_add, clear;  
    wire temp_0, temp_gt_1;  
    controller M0 (load_temp, shift_add, clear, busy, done, start,  
        temp_gt_1, clk, reset);  
    datapath M1 (temp_gt_1, temp_0, data, load_temp, shift_add,  
        clk, reset);  
    bit_counter_unit M2 (bit_count, temp_0, clear, clk, reset);  
endmodule
```



```
module controller (load_temp, shift_add, clear, busy, done,  
    start, temp_gt_1, clk, reset);  
    parameter state_size=2;  
    parameter S_idle=0;  
    parameter S_counting=1;  
    parameter S_waiting=2;  
    output load_temp, shift_add, clear, busy, done;  
    input start, temp_gt_1, clk, reset;  
    reg bit_count;  
    reg [state_size-1:0] state, next_state;  
    reg load_temp, shift_add, busy, done, clear;  
    always @ (state or start or temp_gt_1)  
        begin  
            load_temp=0;  
            shift_add=0;  
            done=0;  
            busy=0;  
            clear=0;  
            next_state=S_idle;
```



```
case (state)
  S_idle: if (start) begin next_state=D_counting; load_temp=1;
           end
  S_counting: begin busy=1; if (temp_gt_1)
              begin next_state=S_counting; shift_add=1; end
              else begin next_state=S_waiting; shift_add=1; end
              end
  S_waiting: begin
             done=1;
             if (start) begin next_state=S_counting; load_temp=1;
                             clear=1; end
             else next_state=S_waiting; end
             default: begin clear=1; next_state=S_idle; end
endcase
end
always @ (posedge clk) // state transitions
  if (reset)
    state<=S_idle;
  else state<=next_state;
endmodule
```






```
module datapath (temp_gt_1, temp_0, data, load_temp,
  shift_add, clk, reset);
  parameter word_size=4;
  output temp_gt_1, temp_0;
  input [word_size-1:0] data;
  input load_temp, shift_add, clk, reset;
  reg [word_size-1:0] temp;
  wire temp_gt_1=(temp>1);
  wire temp_0=temp[0];
  always @ (posedge clk) // state ,loading, shifting
    if (reset) begin   temp<=0; end
    else begin
      if (load_temp) temp<=data;
      if (shift_add) begin temp<= temp >>1; end
    end
endmodule
```



```
module bit_counter_unit (bit_count, temp_0,  
    clear, clk, reset);  
    parameter counter_size=3;  
    output [counter_size-1:0] bit_count;  
    input temp_0;  
    input clear, clk, reset;  
    reg bit_count;  
    always @ (posedge clk)  
        if (reset || clear)  
            bit_count<=0;  
        else bit_count<=bit_count+temp_0;  
endmodule
```




# Simulation

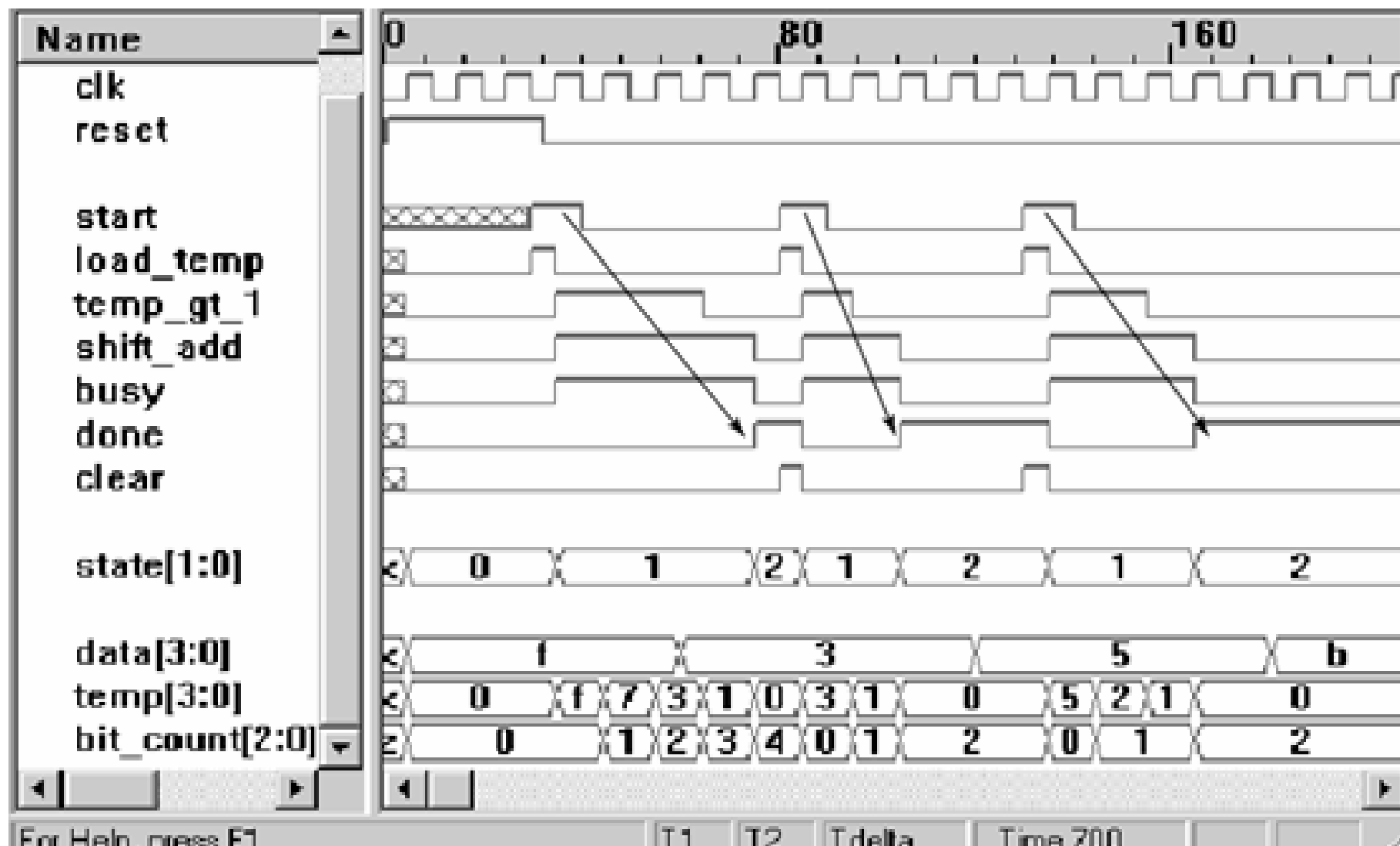





# Synthesis circuit of control unit

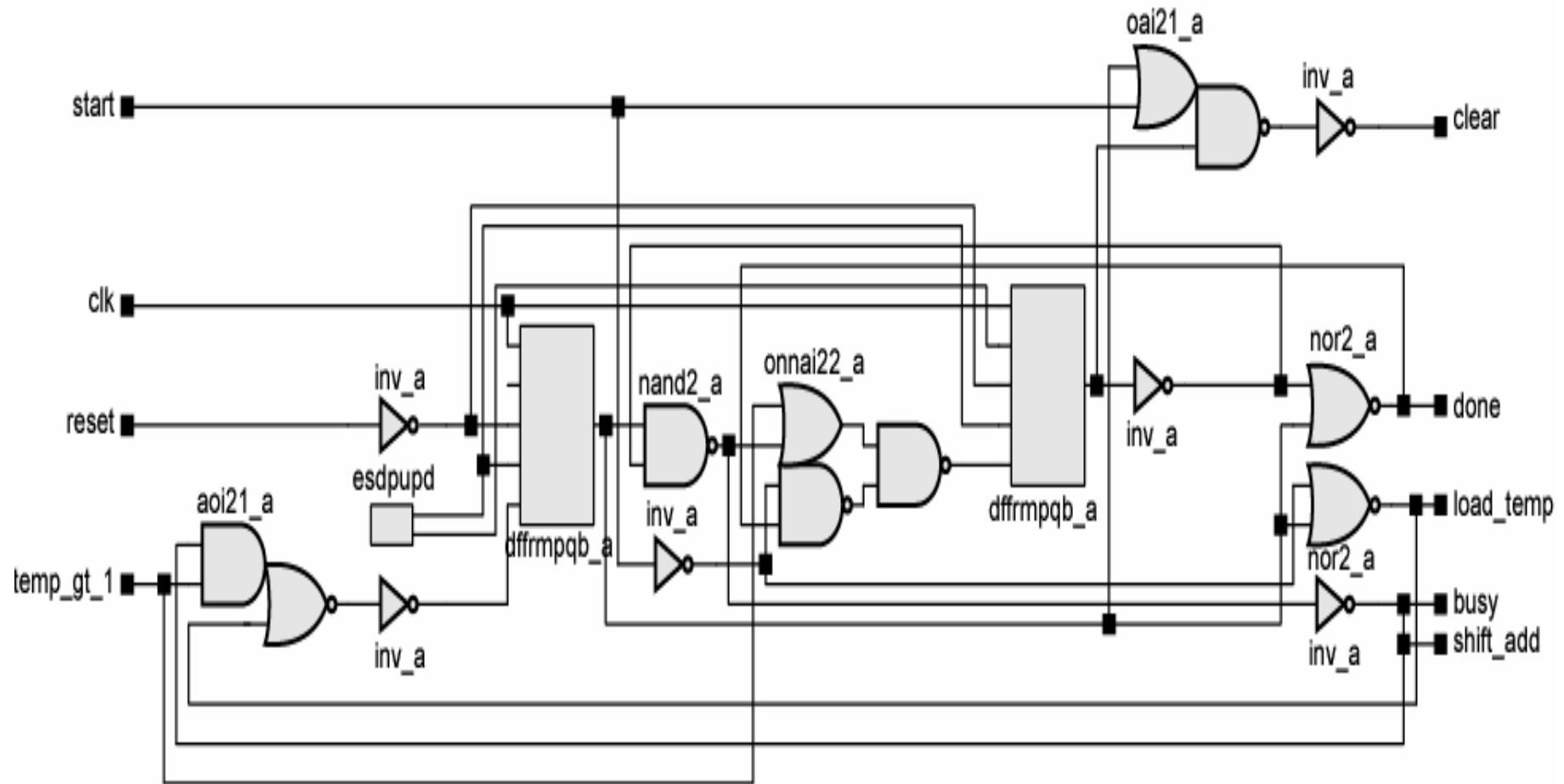

(b)



## 6.14 To avoid design traps

- In general, **avoid referencing the same variable in more than one cyclic (always) behavior.**
- When variables are referenced in more than one behavior, there can **be races in the software**, and the post-synthesis simulated behavior may not match the pre-synthesis behavior.
- Never assign value to the same variable in multiple behaviors.



## 6.15 Divide and conquer: partitioning a design

- VLSI circuits commonly contain more gates than a synthesis tool can accommodate
- It is standard practice **to partition such circuits hierarchically into small functional units**, which have a manageable complexity
- This partitioning is done **top-down, across one or more layers of hierarchy**
- Synthesis tools commonly synthesize circuits with about 10,000 to 100,000 gates, but beyond that the return diminishes as the run-time becomes large
- It is easier to modify the lower-level modules to make the design more amenable to synthesis, then to work with large modules.



# Partitioning a design

**partitioning is not done randomly, Skill and experience play a role**

- A design is partitioned along functional lines into smaller functional units:
- each with a common clock domain
- each of which is **to be verified separately**
- functionally related logic should be grouped within a partition
- **a module contain no more than one state machine**
- the partition of a design should group registers and their logic
- module boundaries are preserved in synthesis (i.e., optimized separately)





# Problems

- 6-20. Synthesize a circuit that will detect an illegal BCD-encoded word.
- 6-24. Under what conditions will a synthesis tool create combinational logic?
- 6-25. Under what conditions will a synthesis tool create a circuit that implements a transparent latch?
- 6-26. Under what conditions will a synthesis tool create an edge-triggered sequential circuit?
- 6-27. Discuss how to describe a synchronous reset condition using Verilog.




## problem 6-21


- Develop, verify (before and after synthesis), and synthesize a Verilog module that encapsulates the functionality shown in **Fig – P621 (a)**, where the outputs of the A/D converters are inputs to a module that interleaves the sample bytes, **with separate sub-modules** for the control unit, the mux, the demux, the parallel to serial converter, and the serial to parallel converter.
- Define additional interface signals as needed to complete the design.
- Model the multiplexer so that its outputs will be registered. Carefully document your work



# Fig – P621

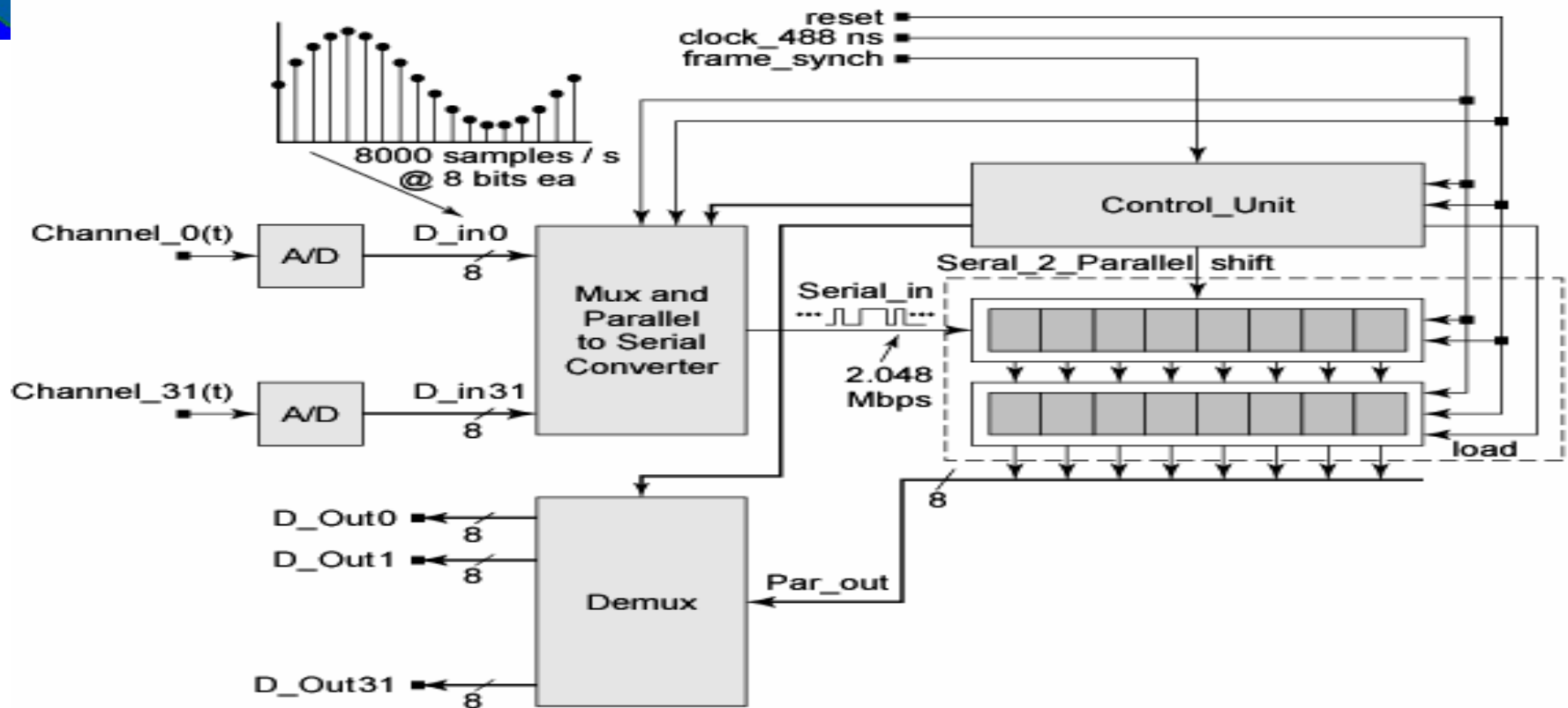

(a)

 

(b)



# 电话系统

## 公用电话交换网PSTN

(Public Switched Telephone Network)


- 端到端的数据传输率:  $10^4$  b/s
- 干线的数据传输率:  $10^{10}$  b/s
- 总体误码率:  $<10^{-5}$
- 通信干线采用光纤或微波数字传输系统

。

**优点:** 出错率低、可传输语音/数据/图像、速率高、成本低、维护容易




## 构成：本地回路、交换局、干线

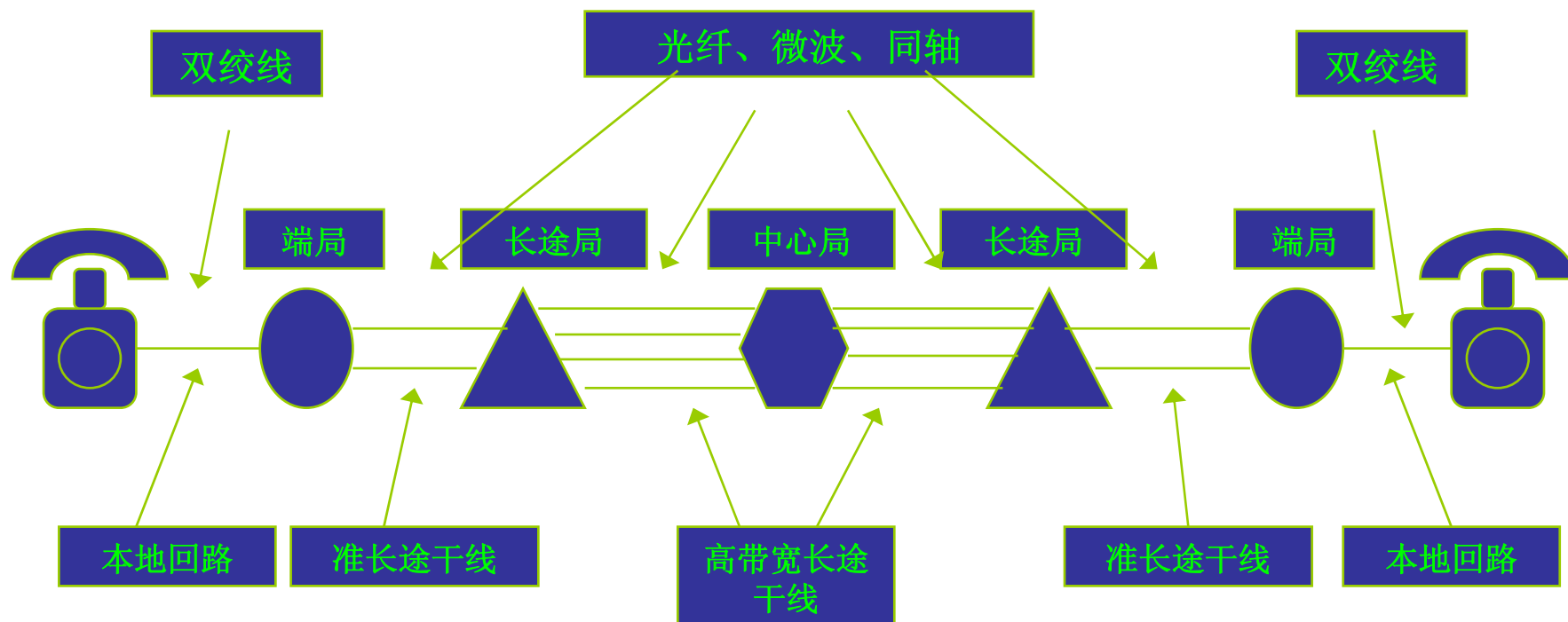


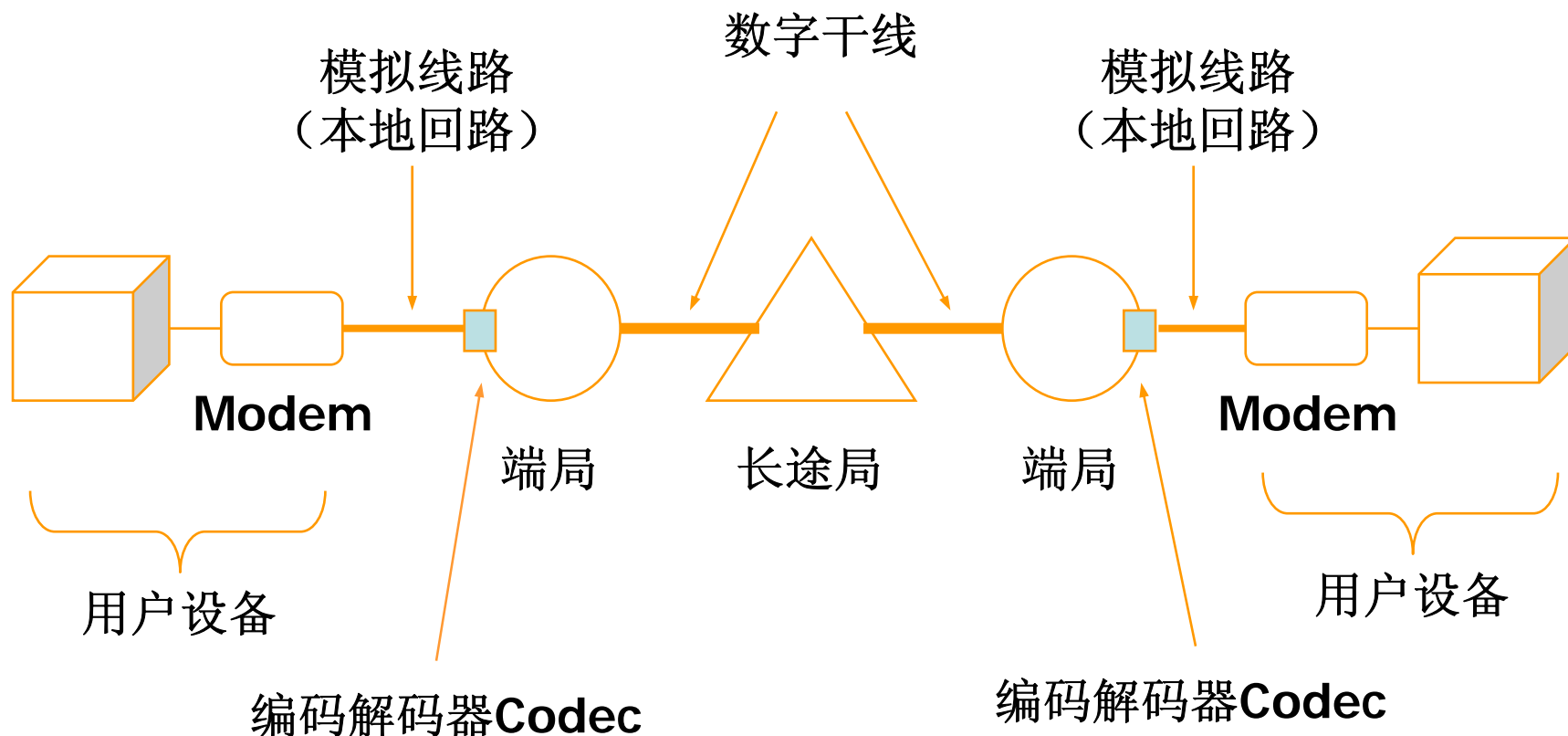
# 本地回路

- 绝大多数为模拟线路
- 计算机间传输：以模拟为主，信号要经过多次变换：**数字→模拟→数字→模拟→数字**





# 数据复用技术

- 复用——多路不同信号共享一个公共信道

为何要复用？


线路成本问题，能提高通信线路的利用率




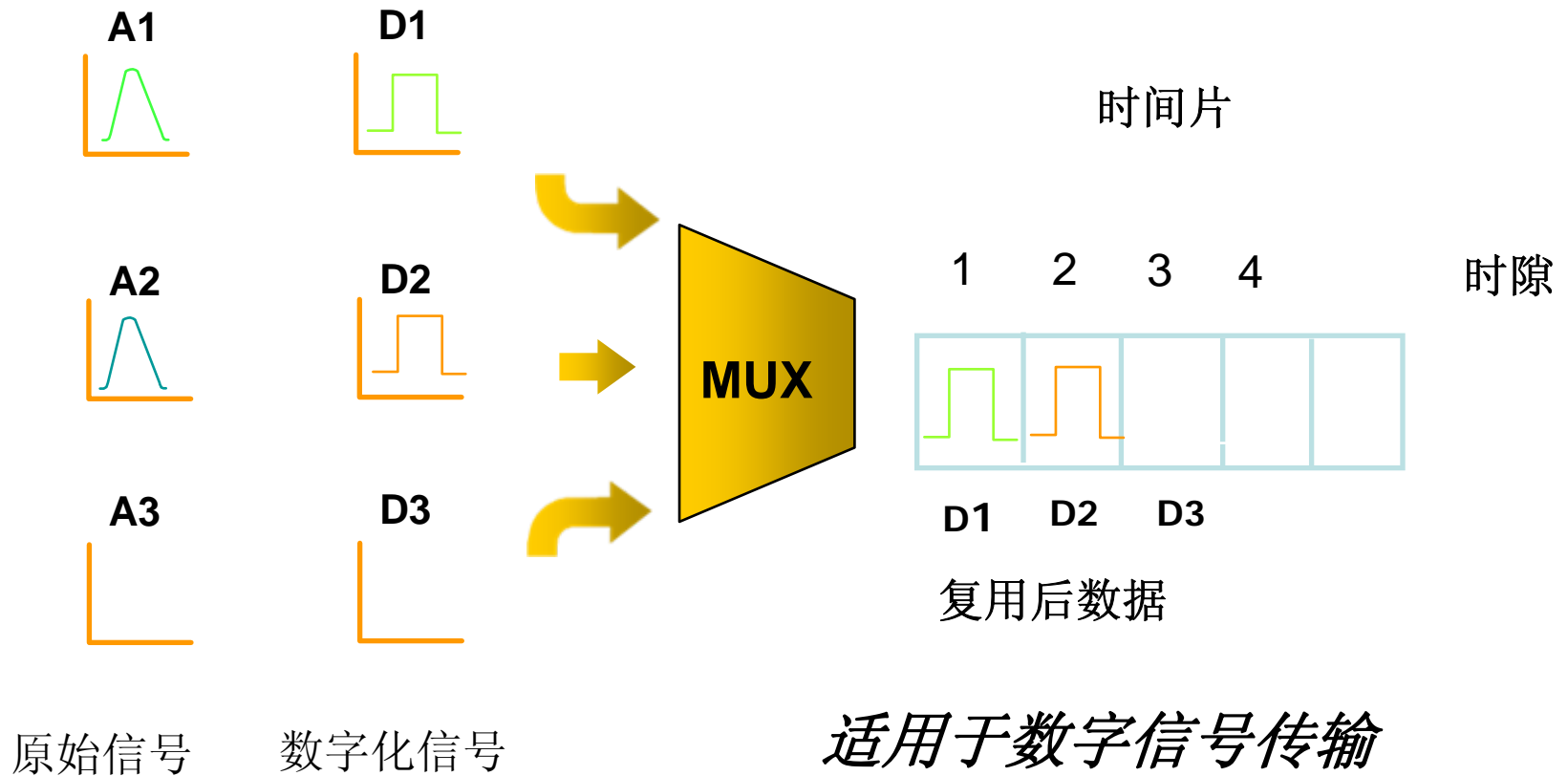
# Time Division Multiplexing

原理：把时间分割成小的时间片，每个时间片分为若干个通道（时隙），每个用户占用一个通道传输数据。







 
# Time Division Multiplexing

- 时分多路复用是将信道用于传输的时间划分为若干个时间片；
- 每个用户分得一个时间片；
- 在其占有的时间片内，用户使用通信信道的全部带宽。





# E1标准

每125 $\mu$ s为一个时间片，每时间片分为32个通道（供32个用户轮流使用）。

每通道占用125  $\mu$ s /32=3.90625  $\mu$ s

每通道一次传送8位二进制数据，即每个二进制位占用0.48828125  $\mu$ s，所以

$$\text{E1速率} = 1/0.48828125 = 2.048 \text{ Mb/s}$$

也可以这样计算**E1速率**

$$\text{E1速率} = (32 \times 8 \text{ bit}) / 125 \mu\text{s} = 2.048 \text{ Mb/s}$$



# 时分复用（TDM）原理

① 
$$T_s = \frac{1}{f_s} = 125 \text{ } \mu\text{S}$$

$$T_c = T_s / K = 125 \div 32 = 3.9 \text{ } \mu\text{S}$$

② 
$$f_B = nKf_s = 8 \times 32 \times 8000 = 2048 \text{ Kb} / \text{s}$$


③ 
$$B_{\min} = f_B / 2 = 1024 \text{ KHZ}$$

④ 平均每路电话占用带宽：

$$1024\text{KHZ} \div 32 = 32\text{KHZ}$$





# 时分多路复用

 




# MUX/DEMUX

 

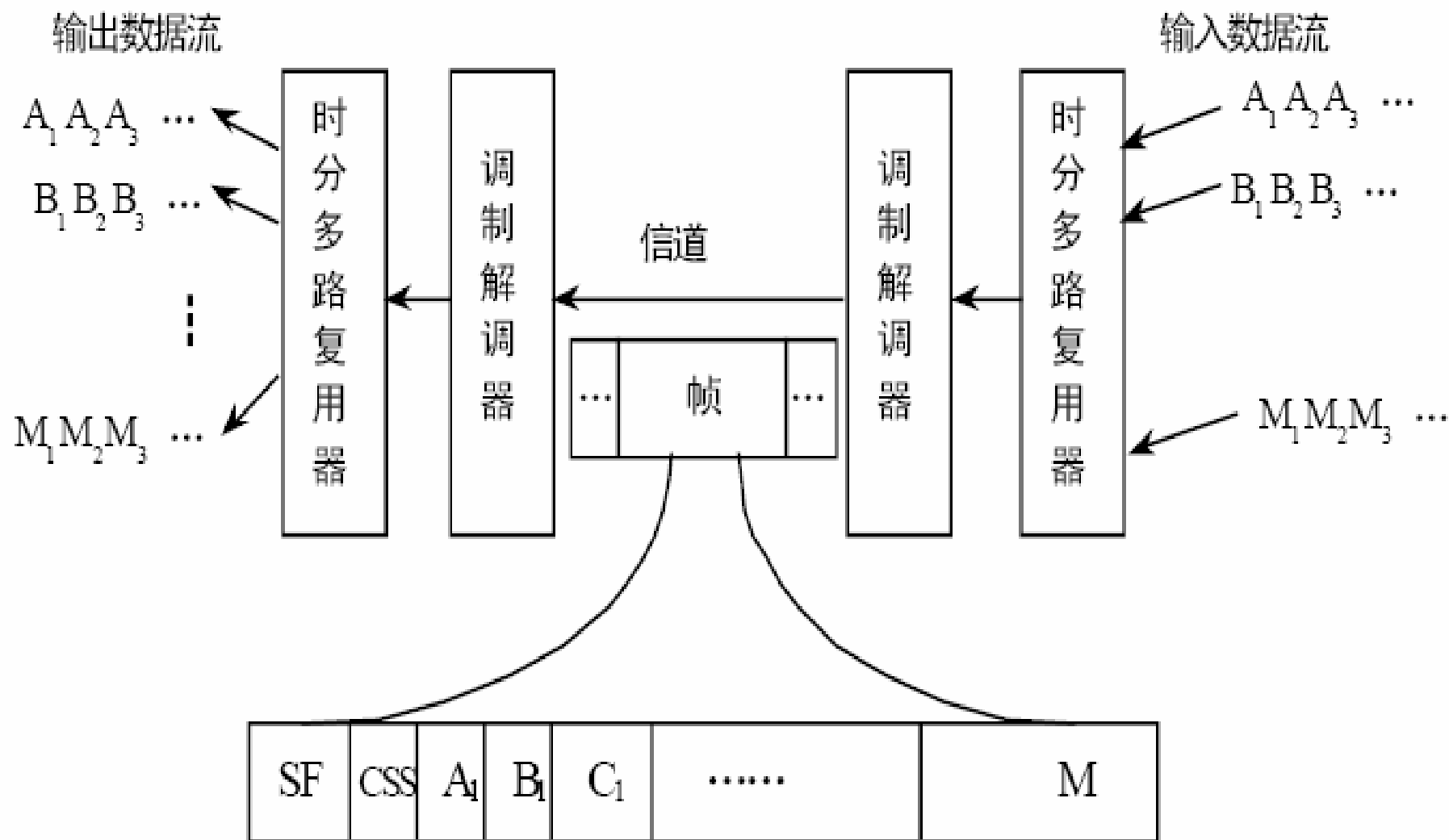



# Multiplexing Process

 



# Demultiplexing process

