




# Chapter 7

## Design and Synthesis of Datapath Controllers



# RTL design of the digital system

## RT Level Design

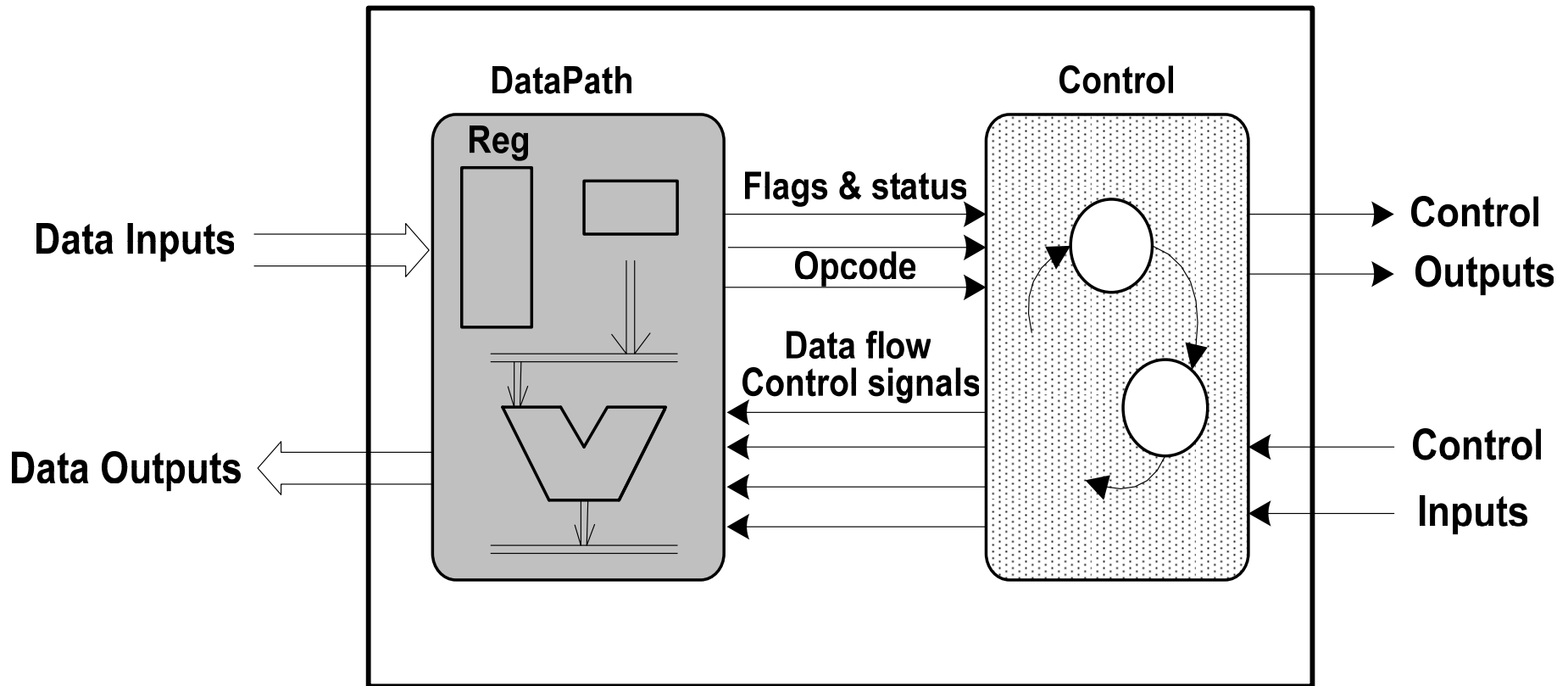



# Datapath & Controller

- The datapath portion of the circuit is the portion that **transforms the input signals into the corresponding output signals.**
- The controller is the portion that **governs the flow of the input signals through the various components comprising the datapath.**



# Control-dominated & Data-dominated systems

- **Control-dominated systems** are reactive systems, responding to external events
- **Data-dominated systems** are shaped by the requirements of **high-throughput data computation and transport**, as in telecommunications and signal processing
- **Sequential machines** are commonly classified and **partitioned into datapath units and control units**



# Data-dominated systems

- Most datapaths include **arithmetic units**, such as **arithmetic and logic units (ALUs)**, **adders**, **multipliers**, **shifters**, and **digital signal processors**
- Datapath units are **characterized by repetitive operations on different sets of data**, as in **signal processing**, **image processing**, and **multimedia**




# Control units

- Architectures that are dominated by control units will **generally have a significant amount of random (irregular) logic, together with some regular structures**, like **multiplexers** for steering signals, and **comparators**


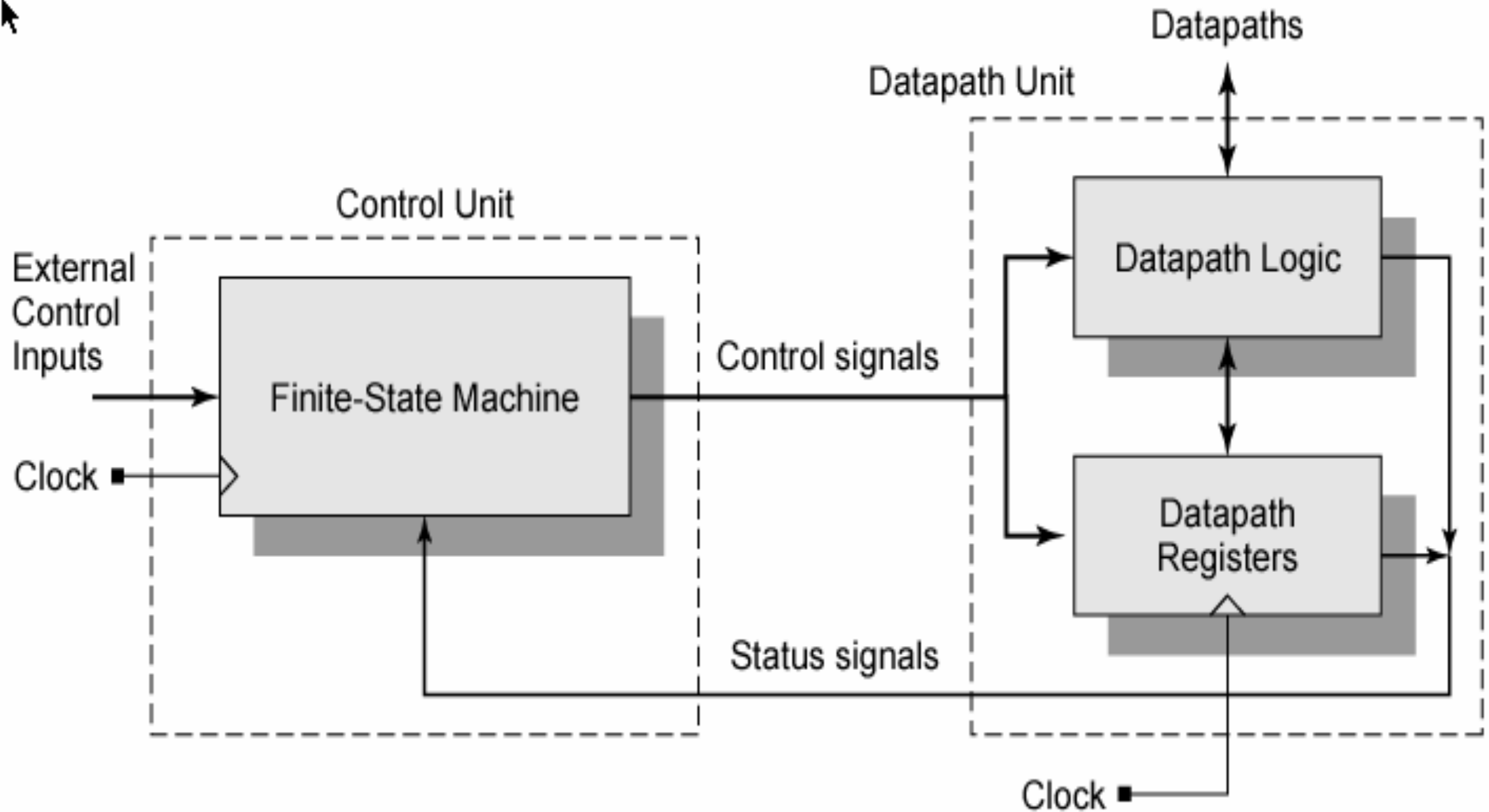
# State-machine controller for a datapath






# 7.1 Partitioned sequential machines

- Partitioning a sequential machine into **a datapath and a controller** clarifies the architecture and simplifies the design of the system
- The process by which the machine is designed is said to be **application-driven**
- Ultimately, **the FSM that controls the datapath.**




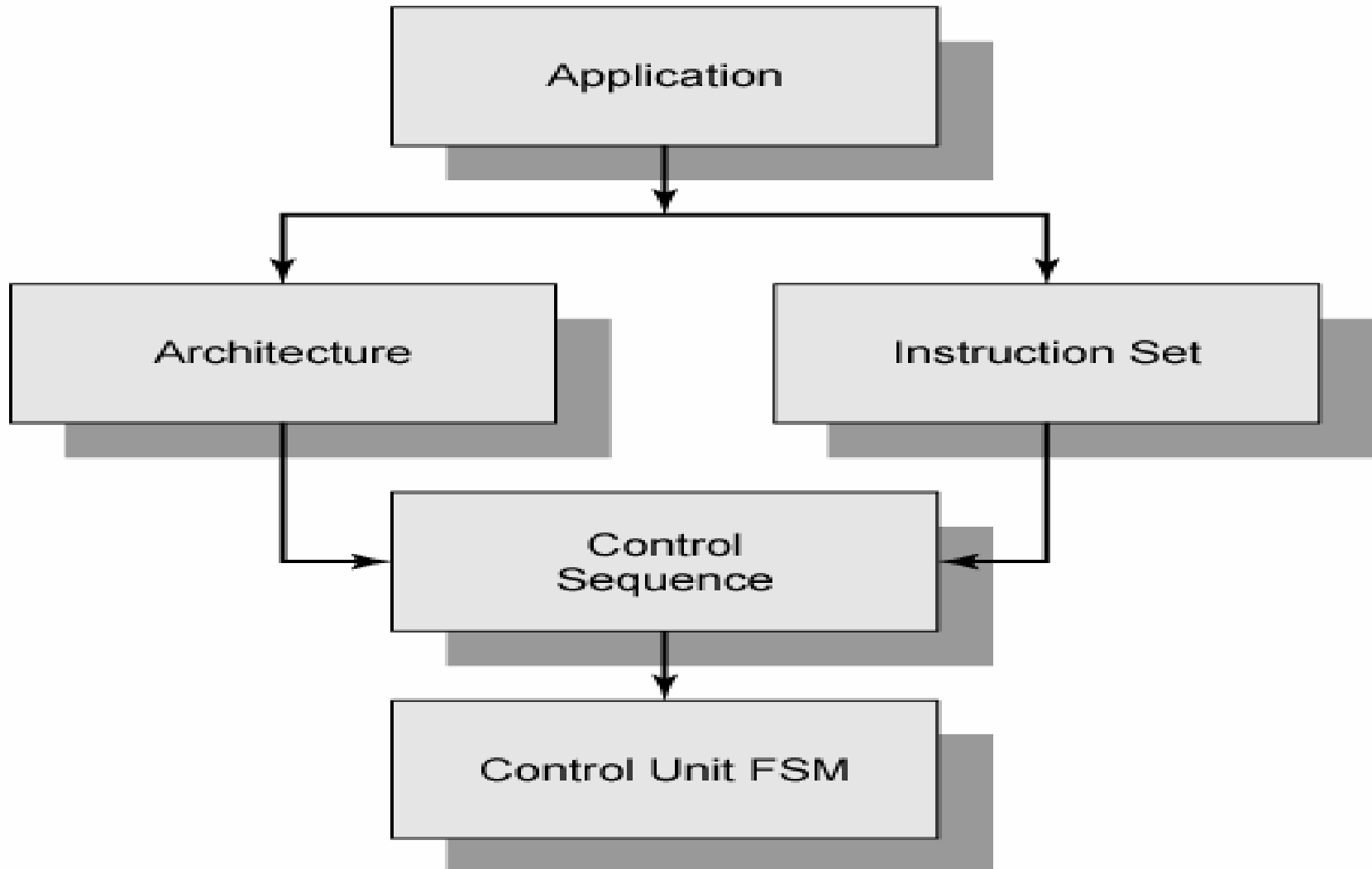
# The sequence of steps in an application-driven design process






## 7.2 Design example: binary counter

- A synchronous 4-bit binary counter ,it is incremented by a count of 1 at each active edge of the clock
- To describe the counter **by an implicit state machine**
- Binary\_Counter\_Imp, executing a register transfer operation ( $\text{count} \leq \text{count} + 1$ ) conditionally, in every clock cycle, depending on enable, and then synthesize a hardware realization directly
- To partition the machine into an architecture of separate datapath and control units


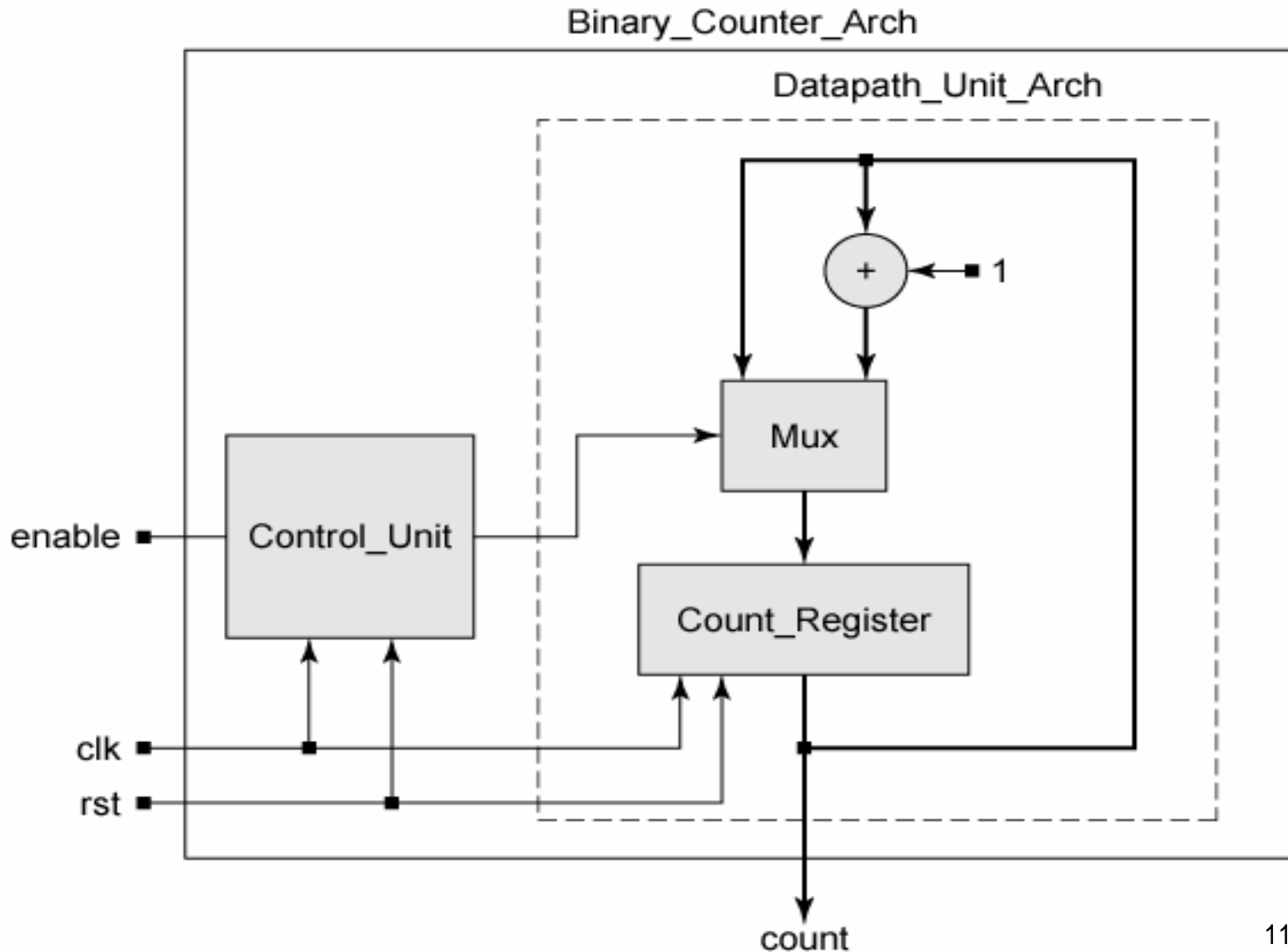
# The architecture of separate datapath and control units






# The functional elements

- (1) a 4-bit register to hold count
- (2) a mux that steers either count or the sum of count and 1 to the input of the register
- (3) a 4-bit adder to increment count
- The signal **enable** must be asserted for counting to occur, and the signal **rst** overrides all activity and drives count to a value  $0000_2$



# The simplified STG of the machine

 




# Another view of the binary counter

- Another view of the binary counter **is based on the counter's activity**
- The machine **described by the ASM chart** in Figure 7-5, **Binary\_Counter\_ASM**, **has one state, S\_running.**
- At every clock, enable is tested and a transition is made back to S\_running;
- If enable is asserted, a conditional register operation that increments the counter is executed concurrently with the state transition



**Figure 7-5 The binary counter:  
based on the counter's activity**

 




# A third method

- The designing of binary counter partitions the machine into a control unit and a datapath unit, but **designs a RTL behavioral model for the datapath unit, rather than a structural model**
- This style separates the design of the control unit from the design (and synthesis) of the datapath unit and simplifies the description of the datapath unit
- **It separates the unit that determines what happens from the unit that determines when it happens.**




 
# A third method – ASMD (enable\_DP linking the controller to the datapath)





# Example 7.1

```
module Binary_Counter_Part_RTL (count, enable, clk, rst);  
  parameter      size=4;  
  output [size-1:0] count;  
  input          enable;  
  input          clk, rst;  
  wire          enable_DP;  
  Control_Unit M0 (enable_DP, enable, clk, rst);  
  Datapath_Unit M1 (count, enable_DP, clk, rst);  
endmodule
```


```
module Control_Unit (enable_DP, enable, clk, rst);  
  output enable_DP;  
  input enable;  
  input clk, rst;           // not needed  
  wire enable_DP=enable;    // pass through  
endmodule
```



```
module Datapath_Unit (count, enable, clk, rst);  
    parameter          size=4;  
    output [size-1:0]  count;  
    input              enable;  
    input              clk, rst;  
    reg                count;  
    wire [size-1:0]    next_count;  
    always @ (posedge clk)  
        if (rst==1) count<=0;  
        else if (enable==1) count<=next_count(count);  
  
    function [size-1:0] next_count;  
    input [size-1:0] count;  
    begin  
        next_count=count+1;  
    end  
endfunction  
endmodule
```



# Simulation result

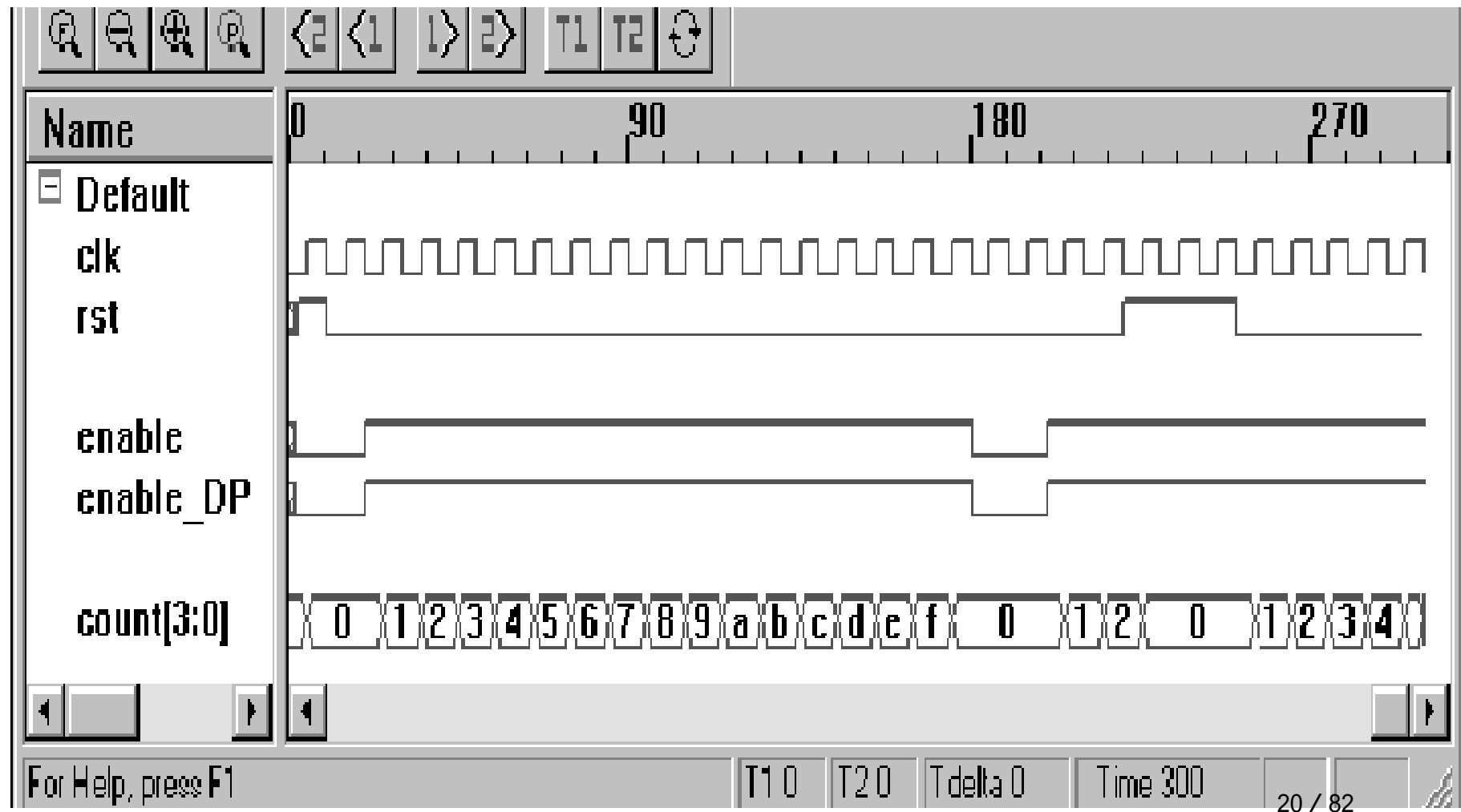




# A counter which increments its count every third clock cycle:

**Only change the control unit**

```
module Control_Unit_by_3 (enable_DP, enable, clk, rst);  
    output          enable_DP;  
    inputenable;  
    inputclk, rst;          // Not needed  
    reg enable_DP;  
    always begin: Cycle_by_3  
        @ (posedge clk) enable_DP <= 0;  
        if ((rst == 1) || (enable != 1)) disable Cycle_by_3; else  
            @ (posedge clk)  
                if ((rst == 1) || (enable != 1)) disable Cycle_by_3;  
                else  
                    @ (posedge clk)  
                        if ((rst == 1) || (enable != 1))  
                            disable Cycle_by_3;  
                        else  
                            enable_DP <= 1;  
                    end // Cycle_by_3  
    endmodule
```




# Simulation result

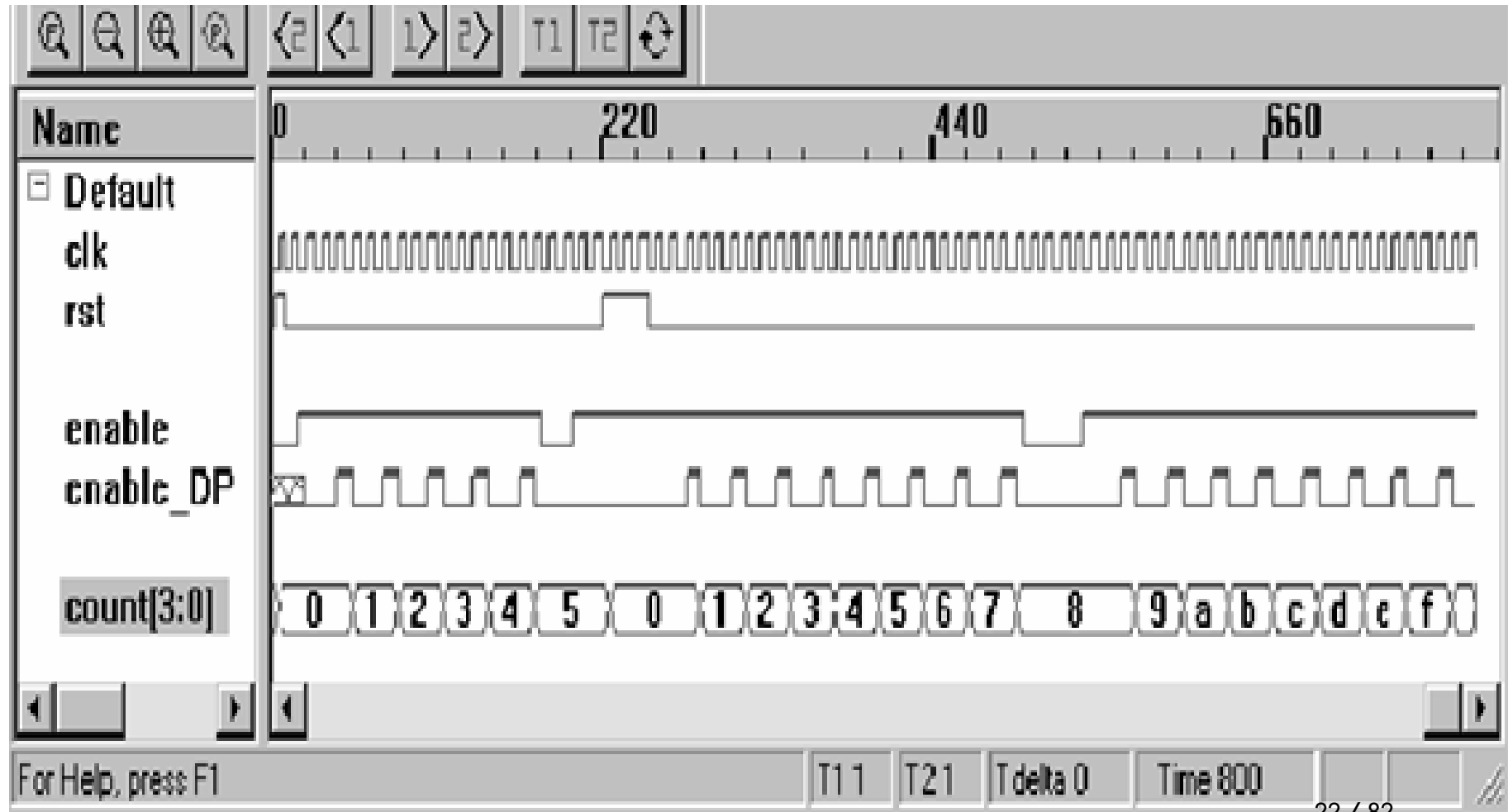



# The synthesis results

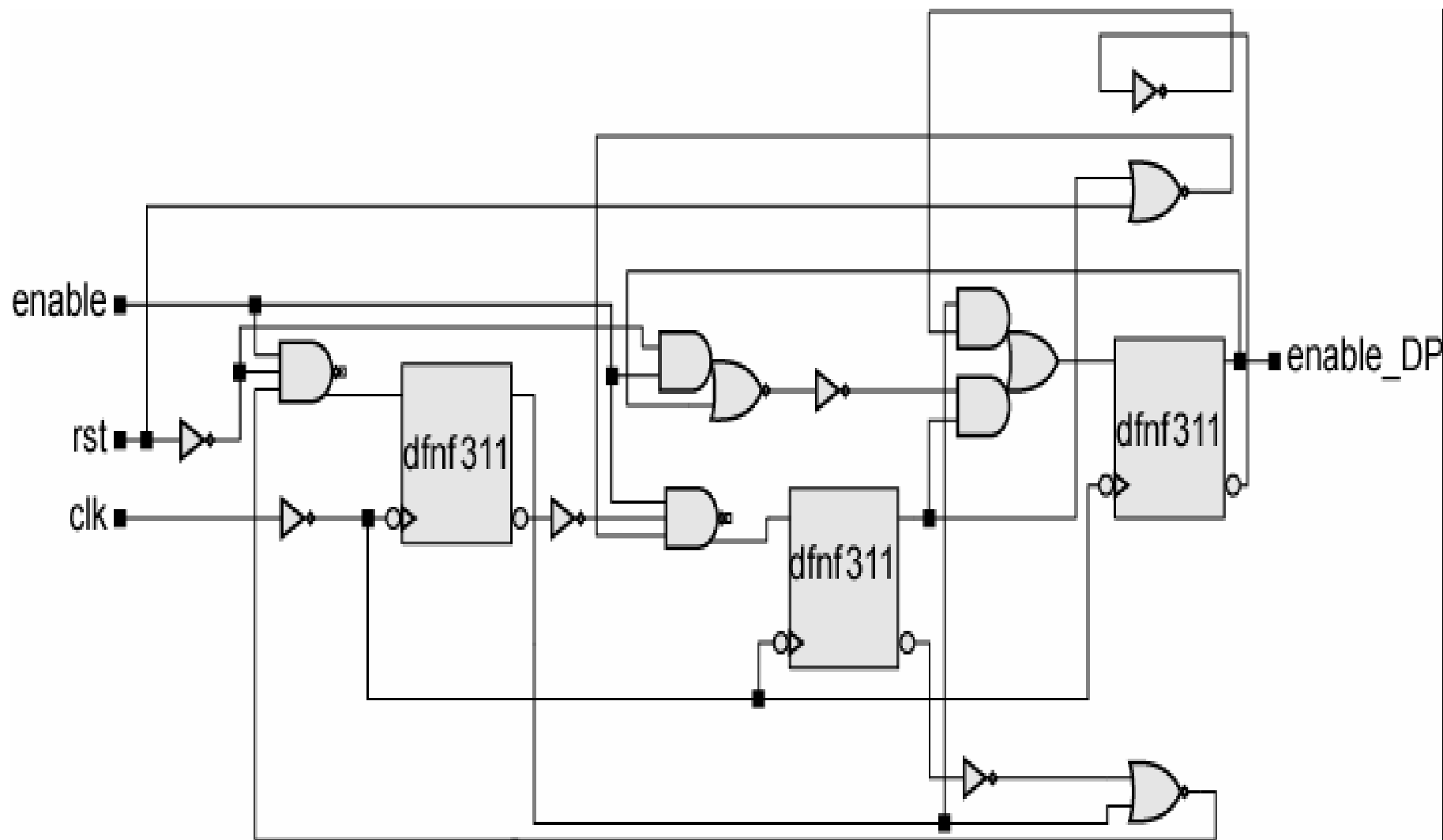



## 7.3 RISC Architecture

- **Architectures of Microprocessors**
  - Random logic
  - Micro Code
  - Pipeline
- **Instruction Sets**
  - Reduced instruction-set computers (RISC)
  - Complicated instruction-set computers (CISC)





# RISC Architecture

- **Reduced instruction-set computers (RISC)** are designed to have **a small set of instructions that execute in short clock cycles**, with a small number of cycles per instruction
- RISC machines are optimized to achieve efficient pipelining of their instruction streams



# RISC Architecture

- Reduced Instruction Set Computer
  - Contains limited instruction set
  - Remove the complexity of micro-memory
  - Programs may be longer
- Examples:  
Power PC series, IBM,  
Motorola, ARM...




# The machine consists of the functional units

- **a processor, a controller, and memory**
- Program instructions and data are stored in memory
- In program-directed operation, instructions are fetched synchronously from memory, decoded, and executed to:
  - (1) operate on data within the arithmetic and logic unit (ALU)
  - (2) change the contents of storage registers
  - (3) change the contents of the program counter (PC), instruction register (IR) and the address register (ADD\_R)
  - (4) change the contents of memory
  - (5) retrieve data and instructions from memory, and
  - (6) control the movement of data on the system busses


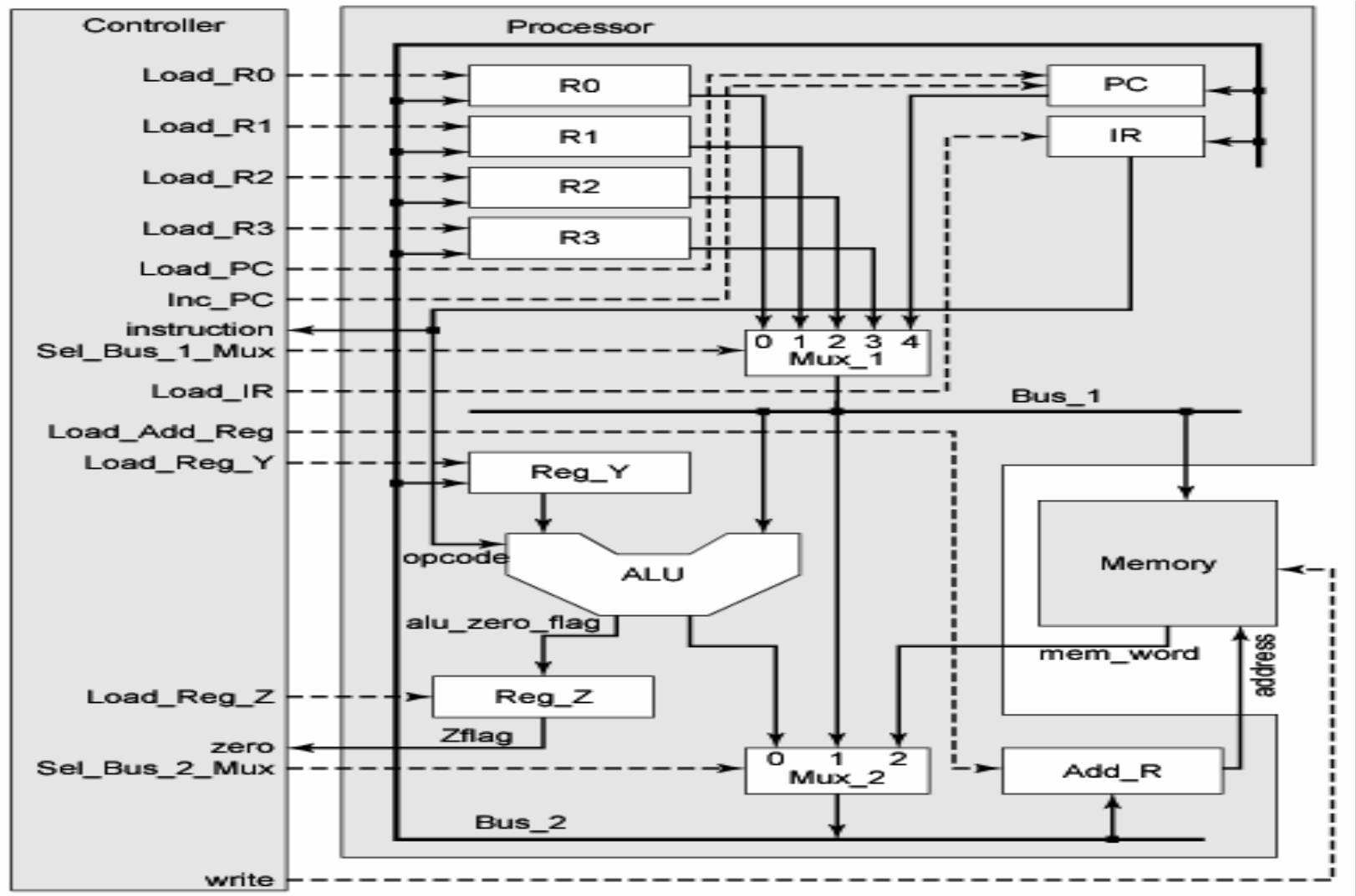
# A stored-program RISC-architecture machine





# A stored-program RISC-architecture machine


## Processor includes :

registers, datapaths, control lines, and an ALU ,...

- **ALU** : two operand datapaths, and its instruction set      Instruction Action
- **Controller**: steer data to the proper destination, according to the instruction being executed ,fetch, decode, and execute
- **Instruction Set** : long or short depending on




## 7.4 CPU Design and Test

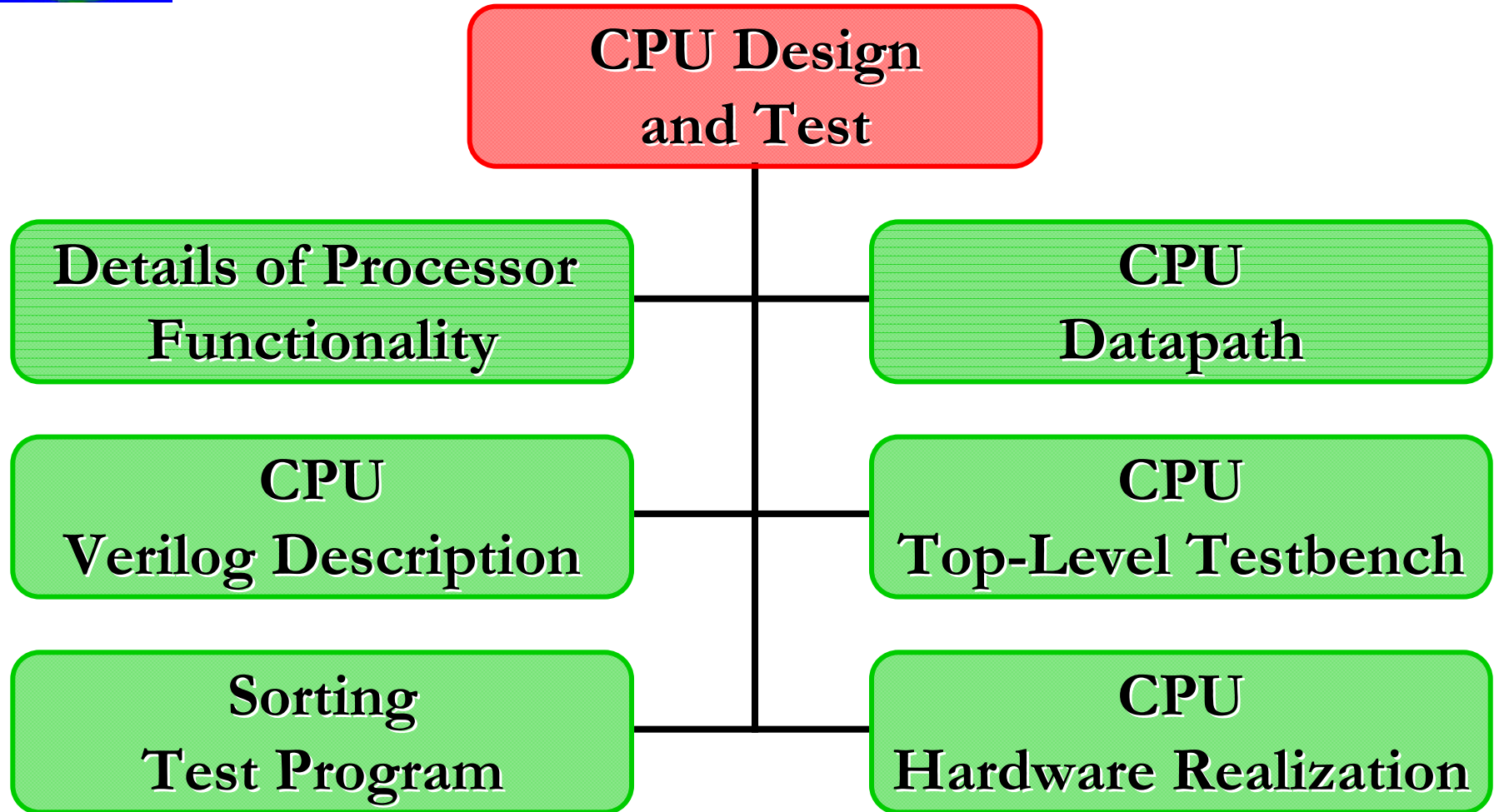




# von Neumann Computer Model

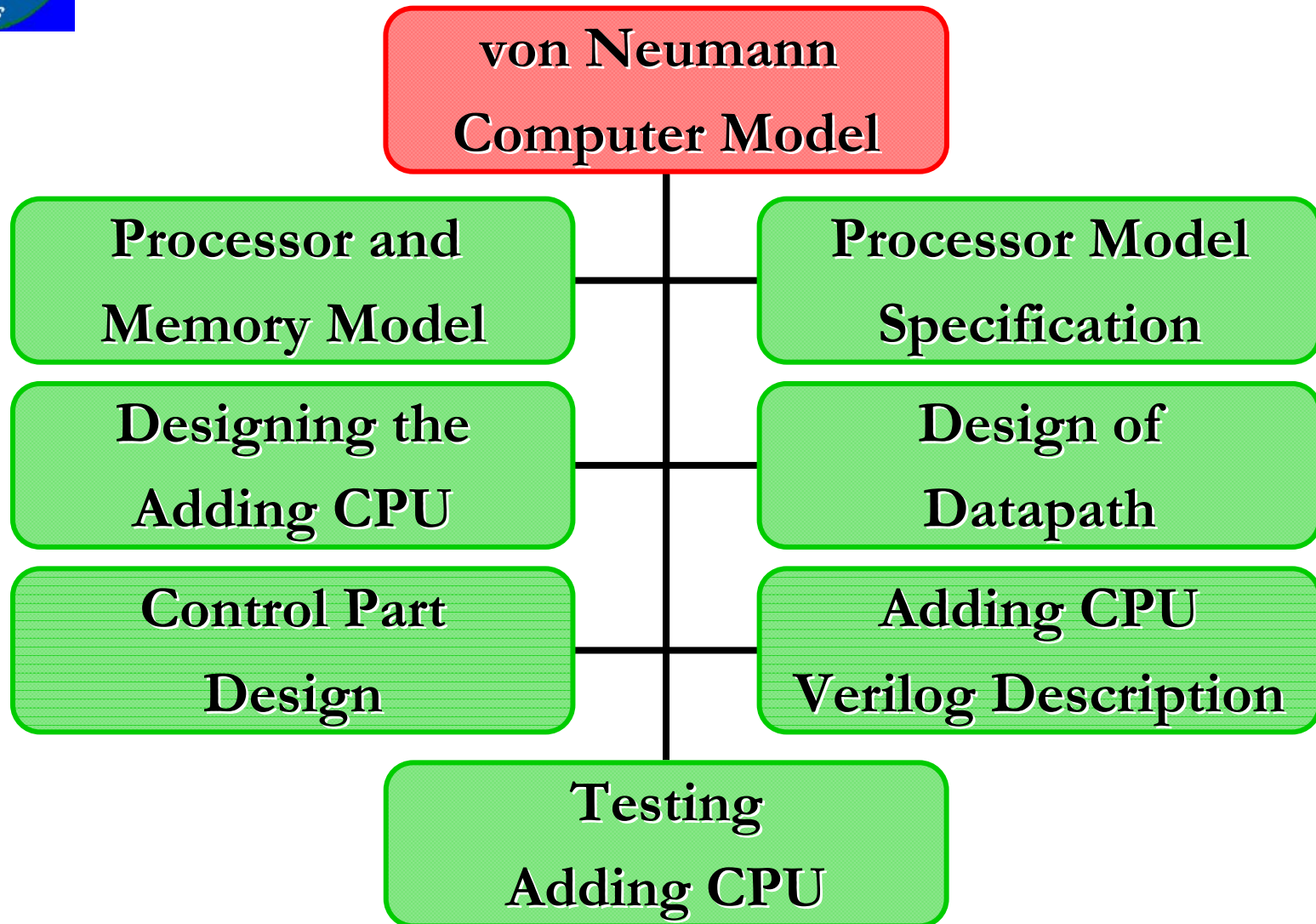



# Processor and Memory Model

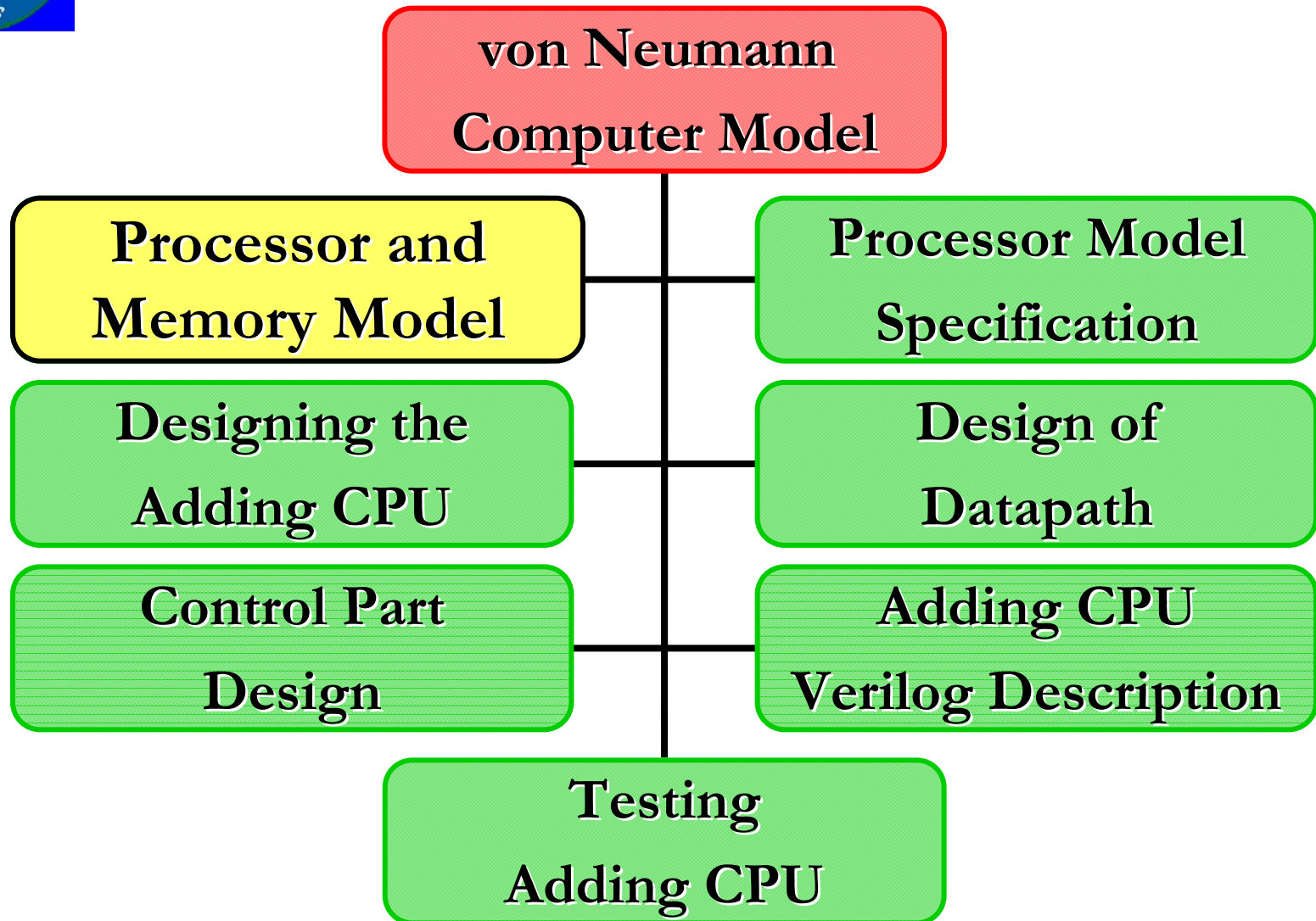






# Processor and Memory Model

## von Neumann Process Model

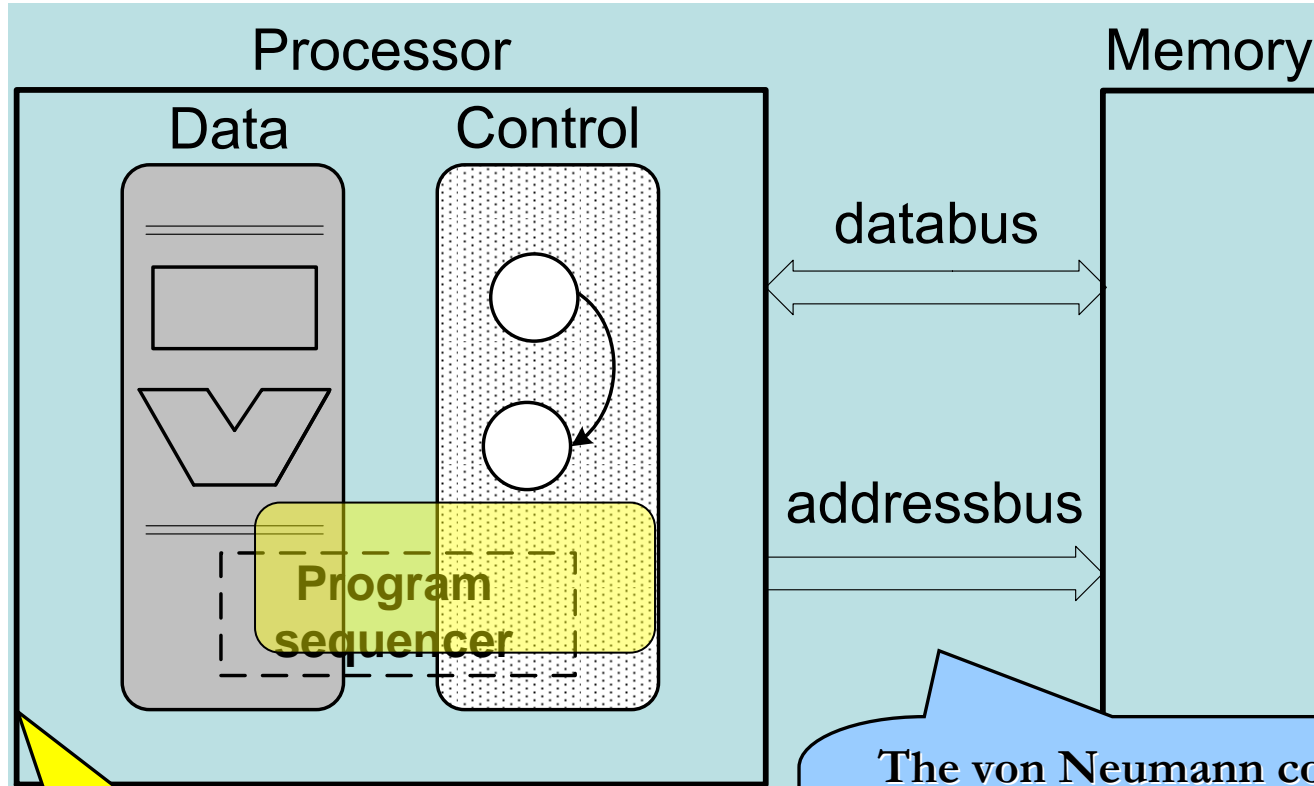


Using a sequencer, the processor fetches instructions from its memory.

The von Neumann computer model is based on a processor using instructions and data from a single memory.




# Processor Model Description

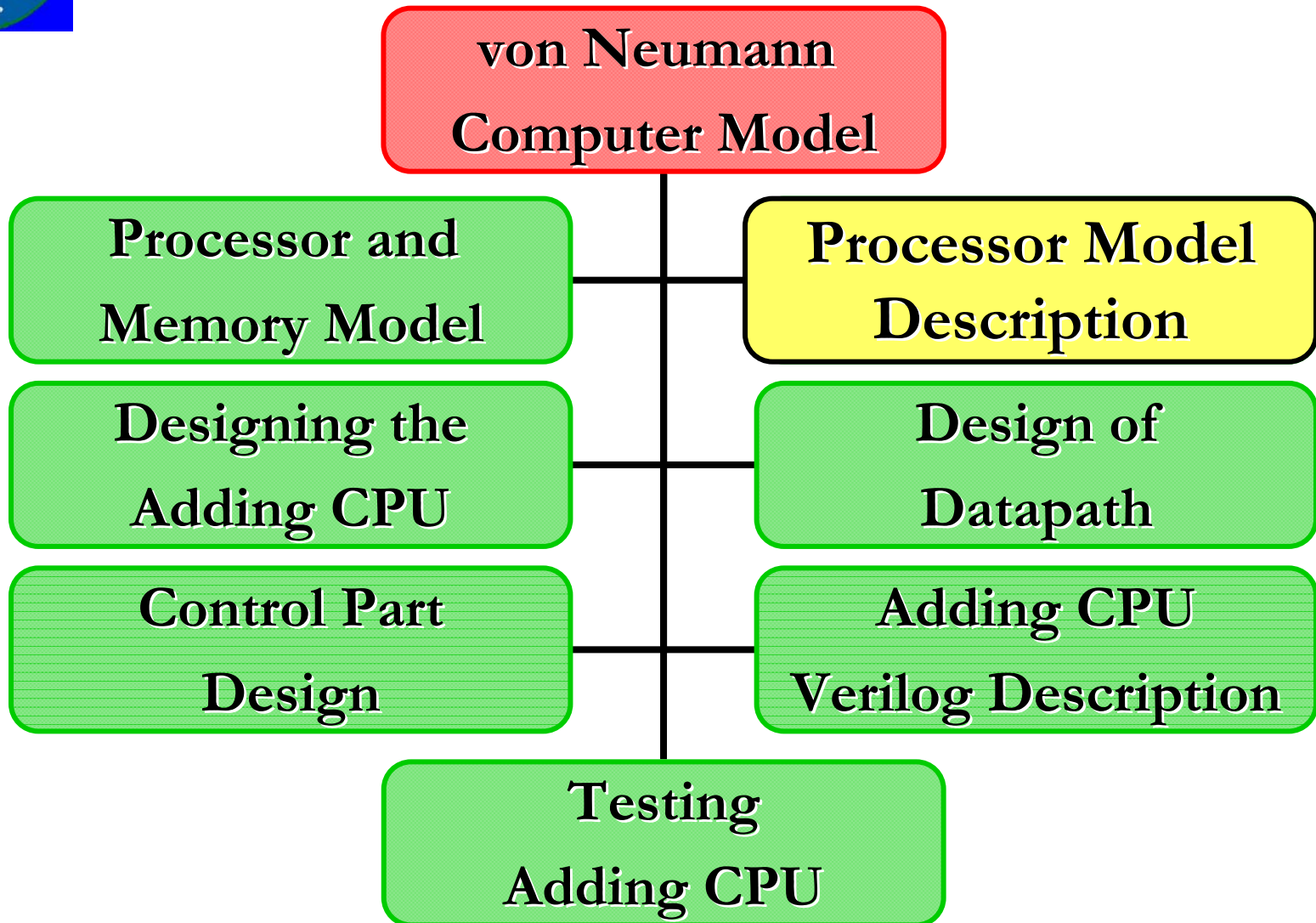




# Processor Model Description

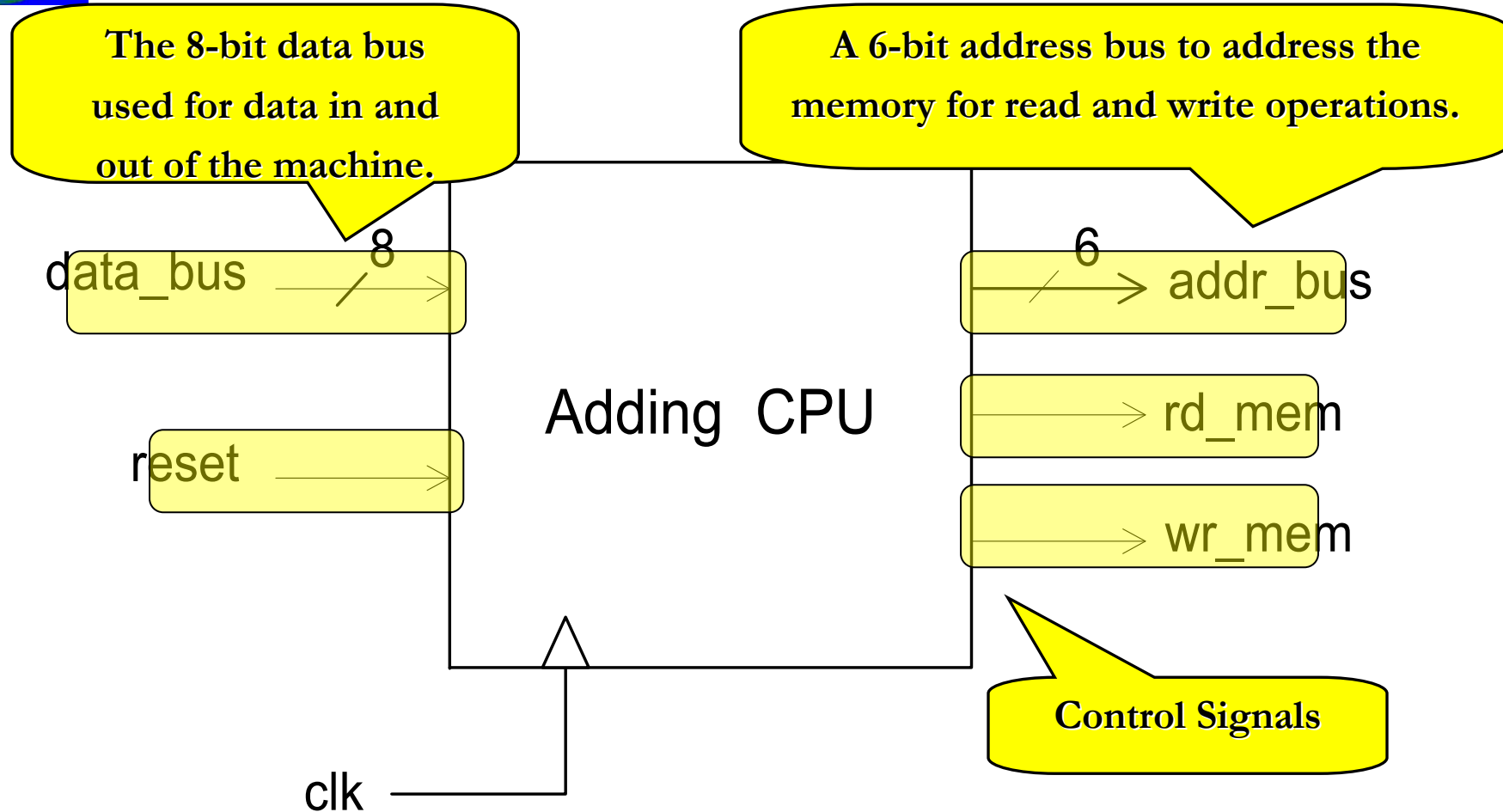

## ■ Interface of the Adding CPU Example




# Processor Model Description

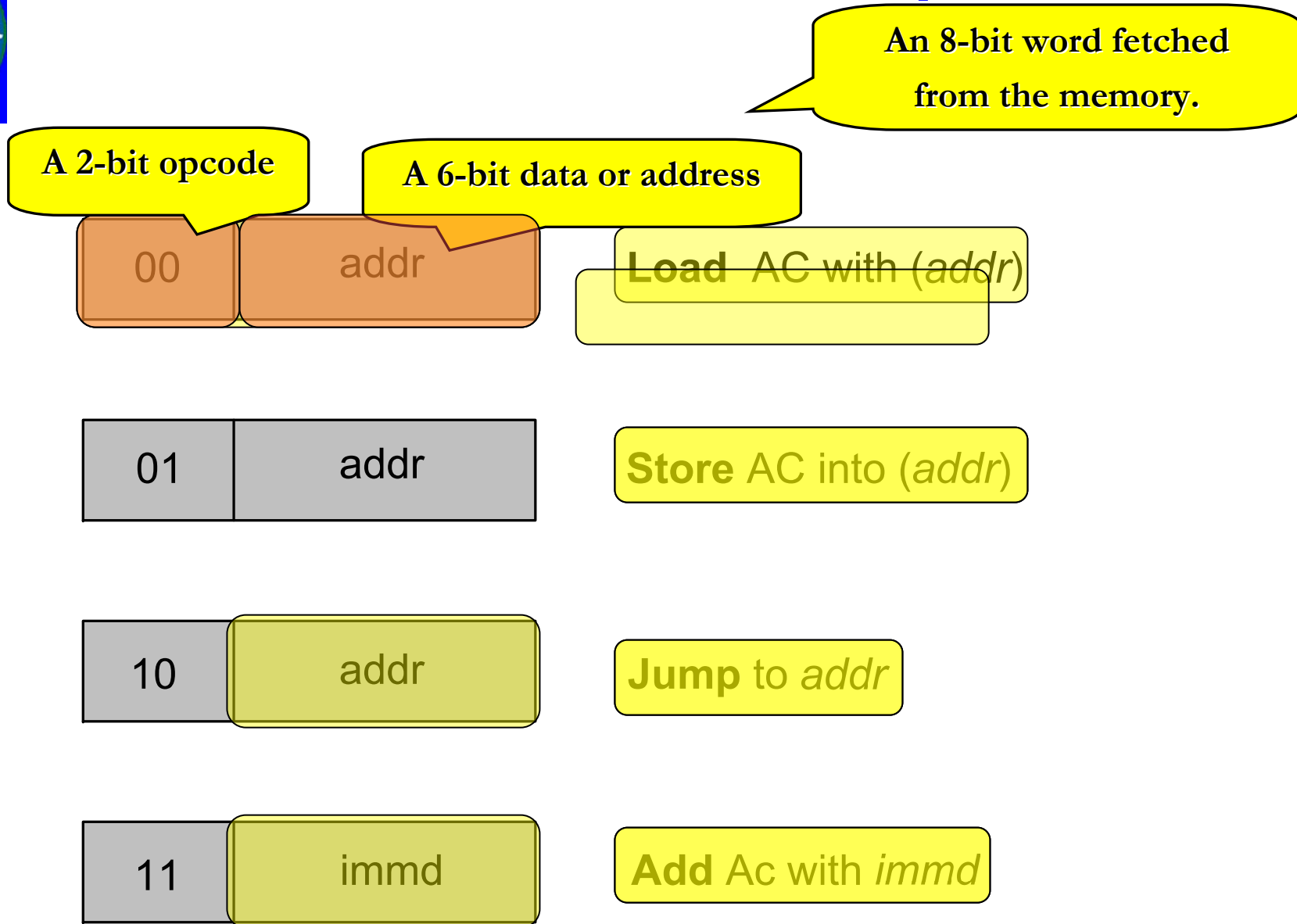

## ■ Instruction Format



# Designing the Adding CPU

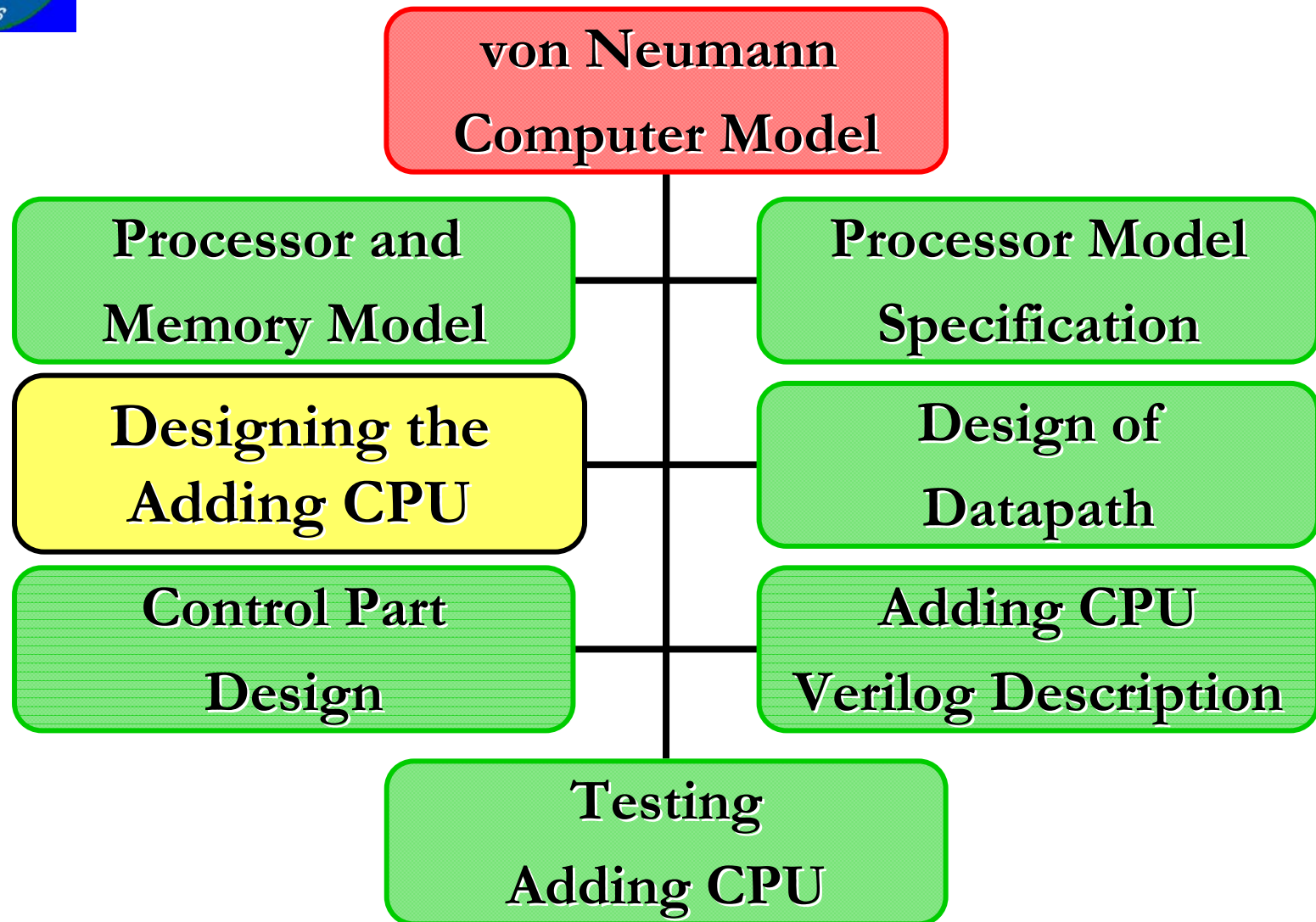




# Designing the Adding CPU

- The first step in the design of our adding machine:
  - Decide on its **data and control partitioning**
  - Decide what goes into its data part and what behavior is expected from its controller
- **The datapath of the design has:**
  - The *AC* register for keeping data to operate on
  - The *PC* register to keep track of the address being fetched
  - An adder unit to perform the addition
  - An instruction register (*IR*) for storing the most recent instruction fetched
- **The controller part** is a state machine that **looks at the opcode** of the instruction in *IR* and **decides** on how data is to be routed.




# Design of Datapath

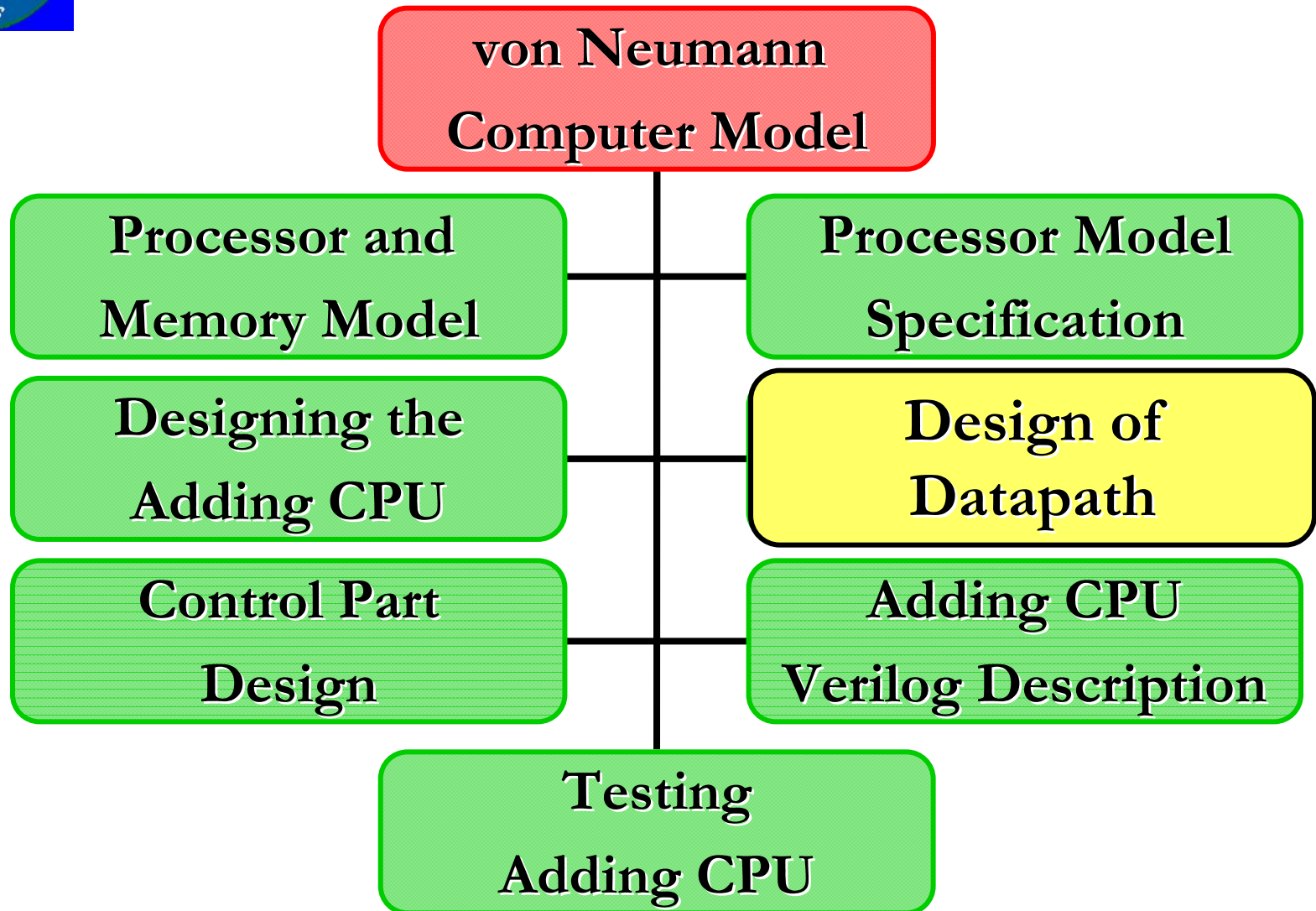



# Design of Datapath

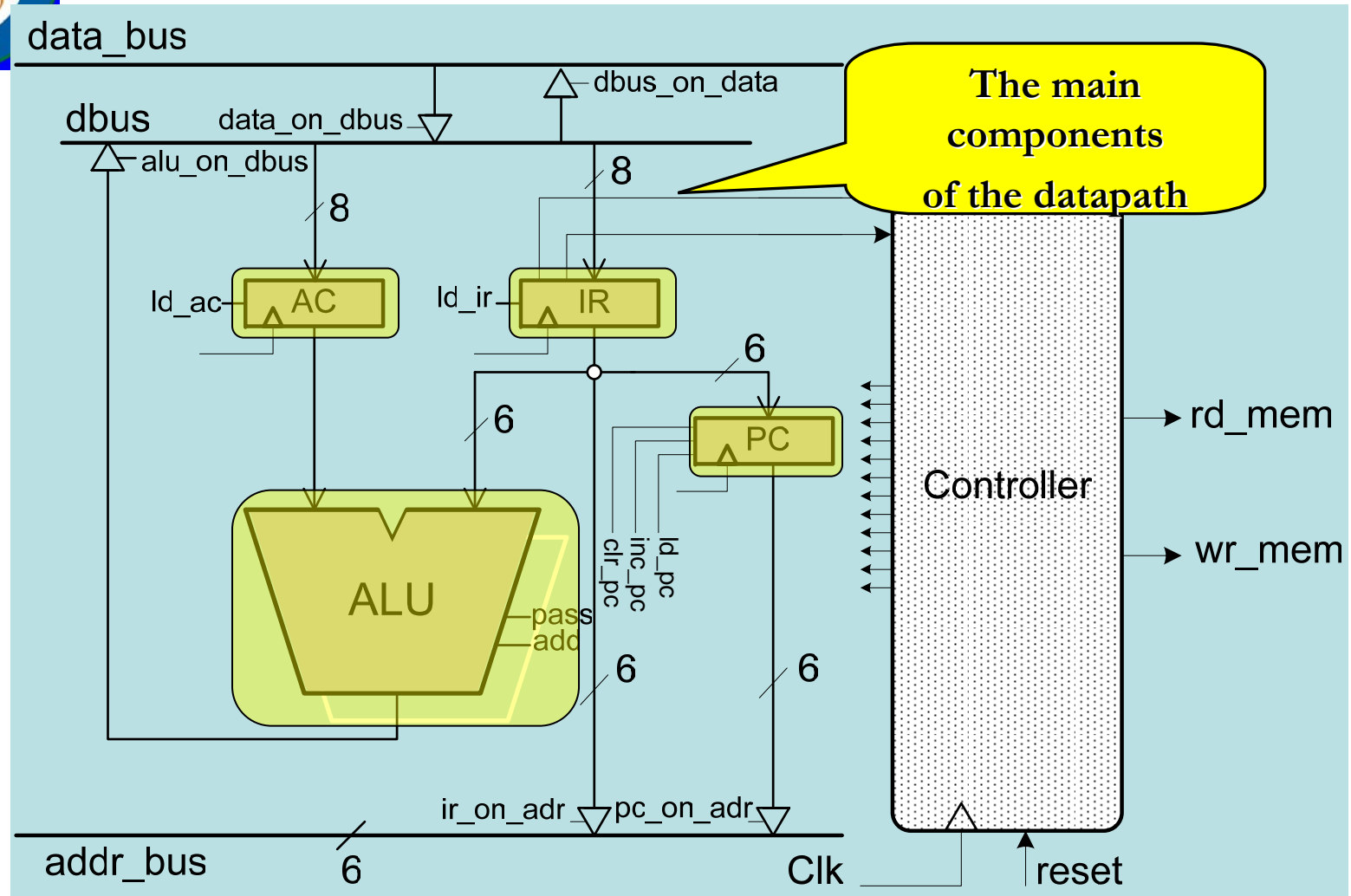


## ■ Architectural Design of our Adding Machine






# Design of Datapath

The Datapath

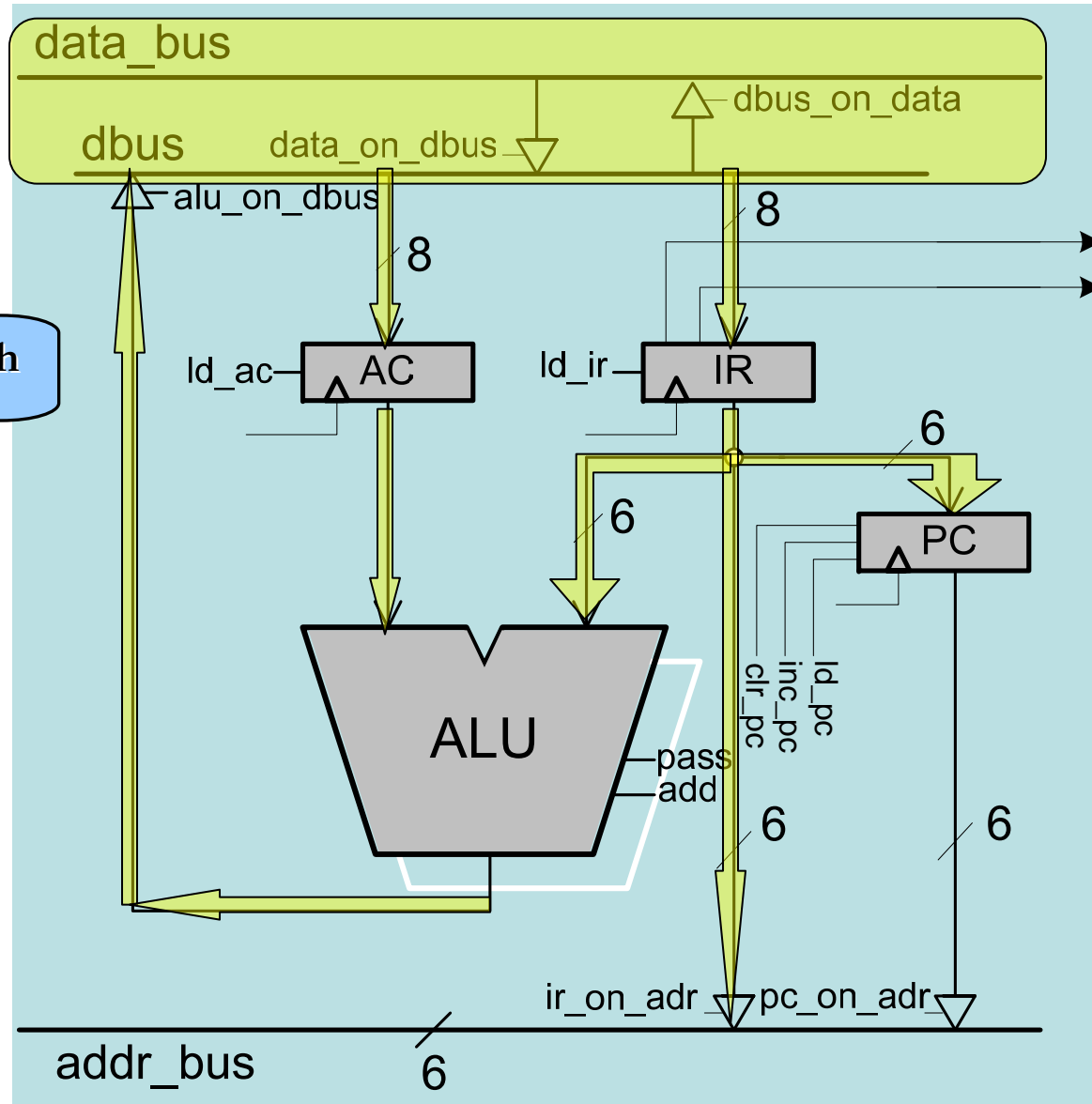




# Control Part Design

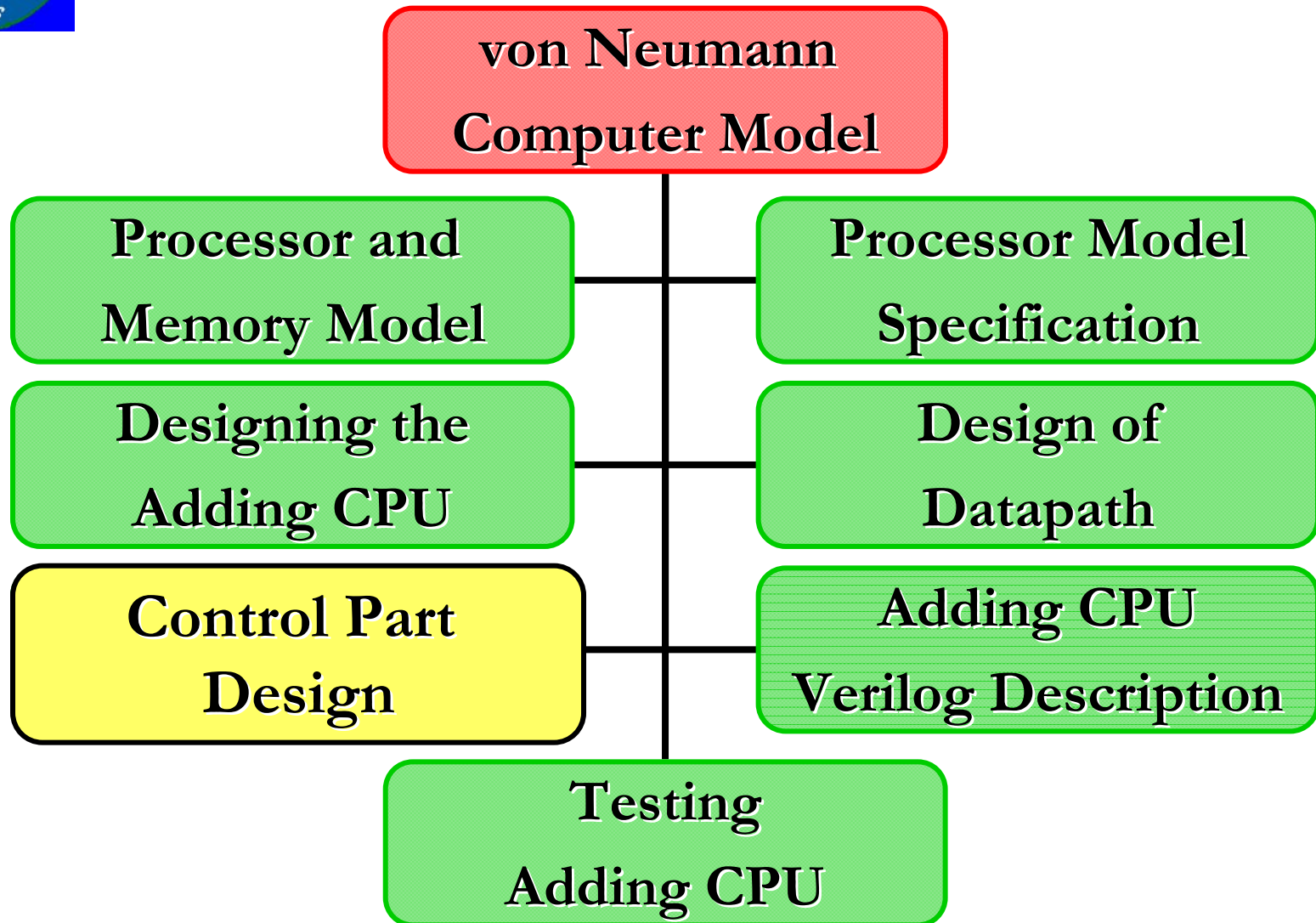

# Control Part Design

As the machine cycles through these states, various control signals are issued.

The controller has 4 states.

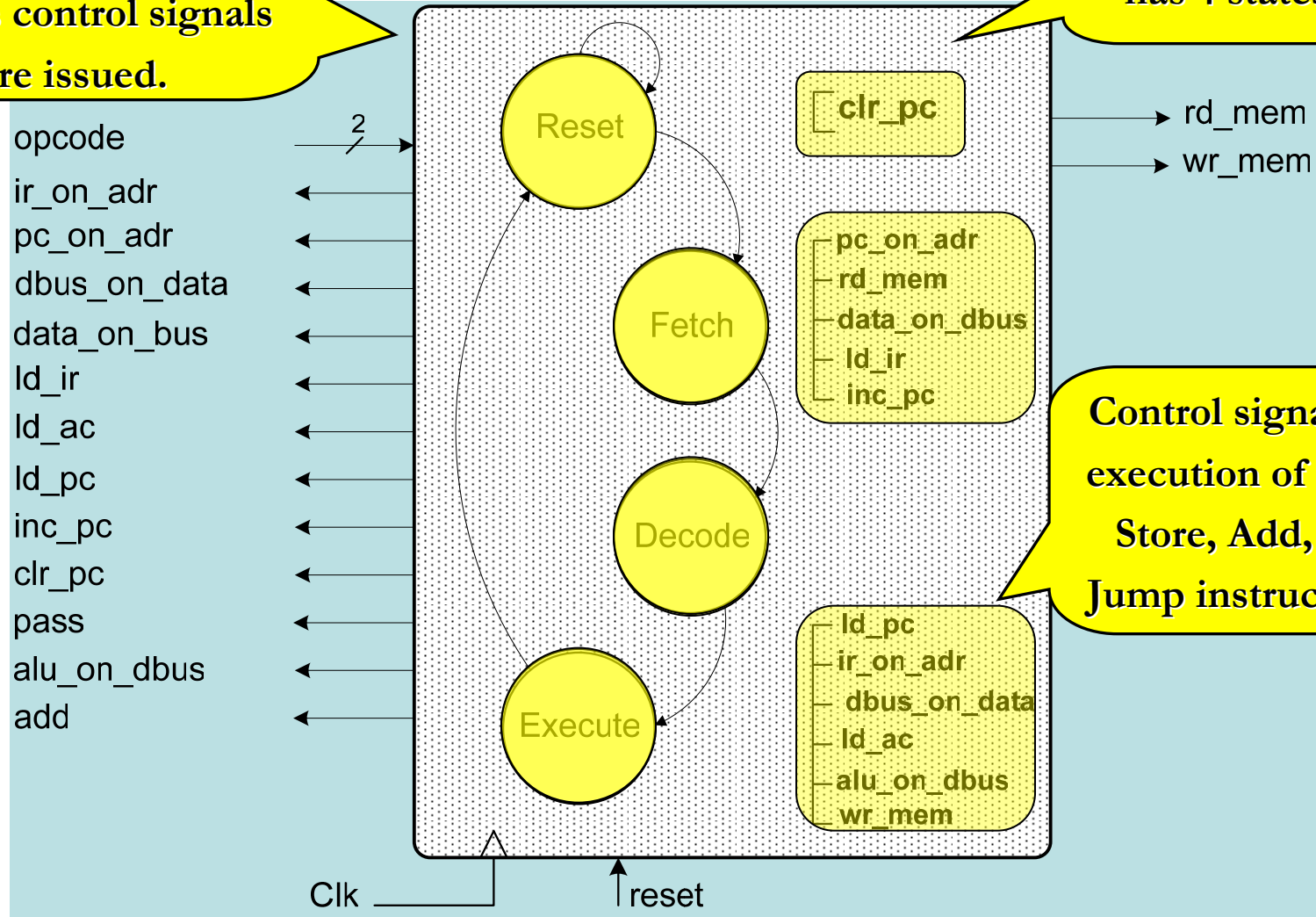


Control signals for execution of Load, Store, Add, and Jump instructions.

## Controller of adding CPU



# Adding CPU Verilog Description

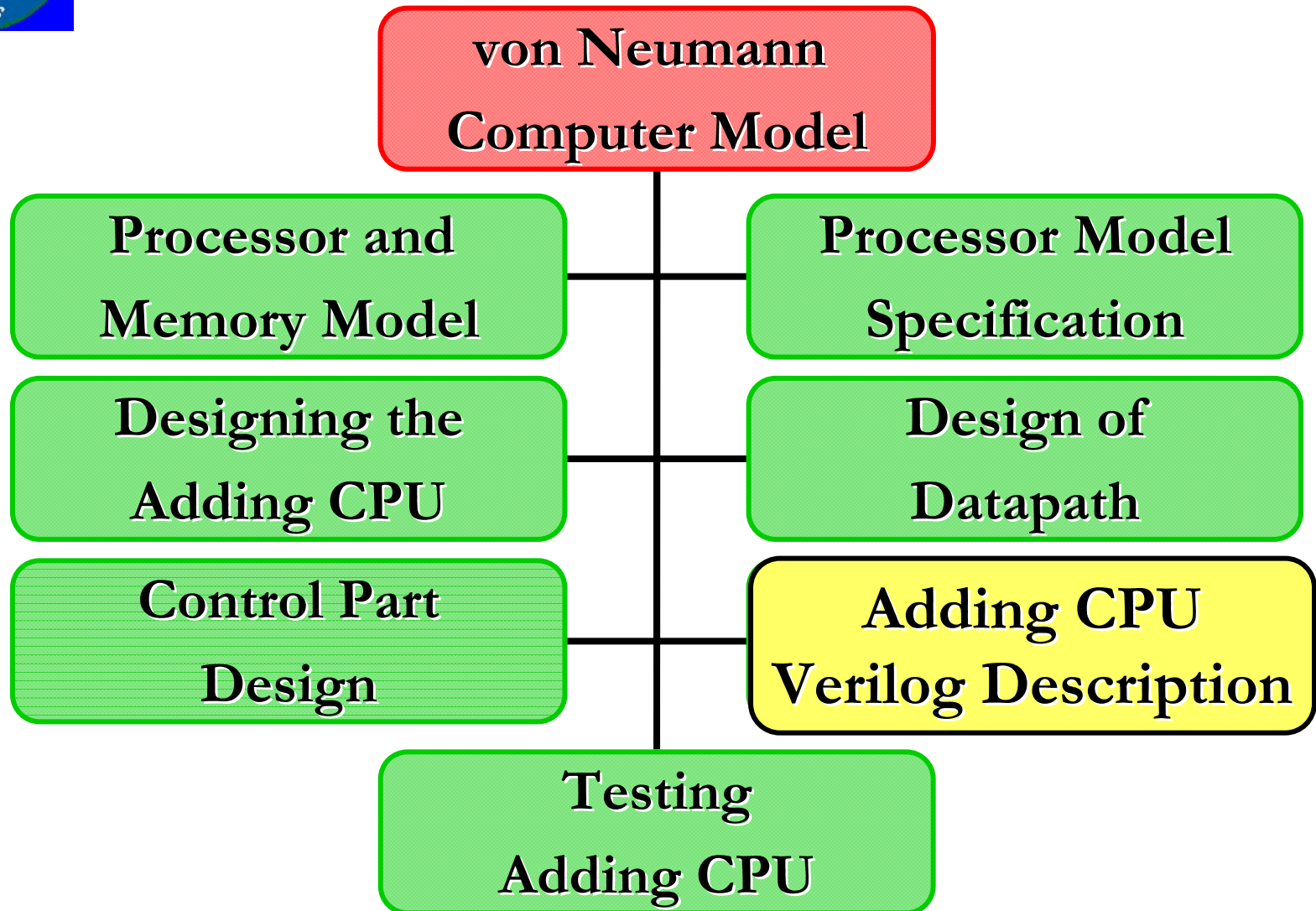




# Adding CPU Verilog Description

- Developing the complete Verilog code of our adding machine by:
  - Describing components of the datapath
  - Forming the Verilog code of the datapath by instantiating and wiring these components
  - Describing the controller using a state machine coding style
  - At the end, wiring datapath and controller in a top-level Verilog module



# Adding CPU Verilog Description

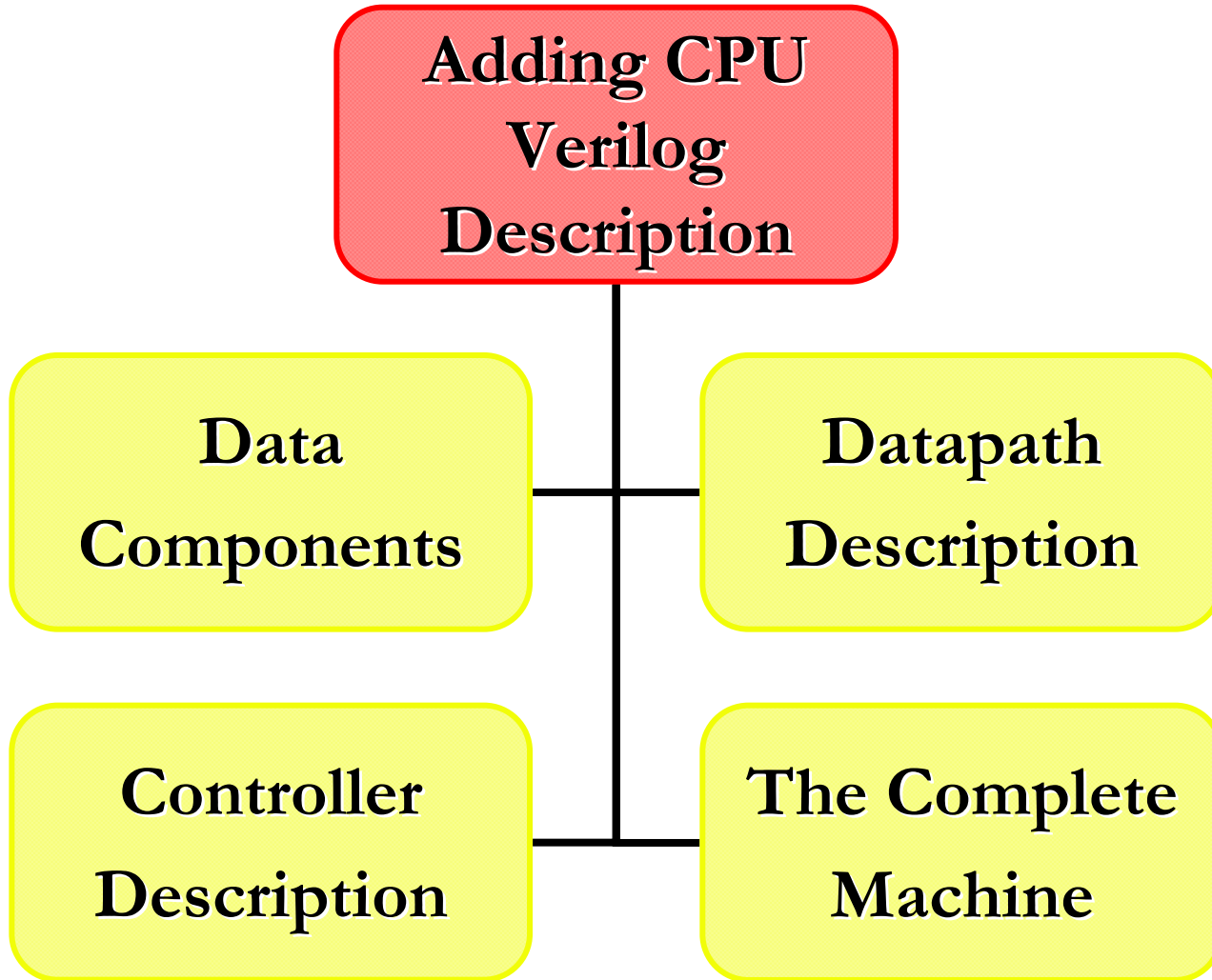




# Datapath Components of Adding Machine

```
module AC ( input [7:0] data_in, input load, clk,
            output reg [7:0] data_out );
    always @( posedge clk )
        if( load ) data_out <= data_in;
endmodule
//
//
module PC ( input [5:0] data_in, input load, inc, clr, clk,
            output reg [5:0] data_out );
    always @( posedge clk )
        if( clr ) data_out <= 6'b000_000;
        else if( load ) data_out <= data_in;
        else if( inc ) data_out <= data_out + 1;
endmodule
//
//
module IR ( input [7:0] data_in, input load, clk,
            output reg [7:0] data_out );
    always @( posedge clk )
        if ( load ) data_out <= data_in;
endmodule
//
//
module ALU ( input [7:0] a, b, input pass, add,
            output reg[7:0] alu_out );
    always @(a or b or pass or add)
        if (pass) alu_out = a;
        else if (add) alu_out = a + b;
        else alu_out = 0;
endmodule
```




# Testing Adding CPU

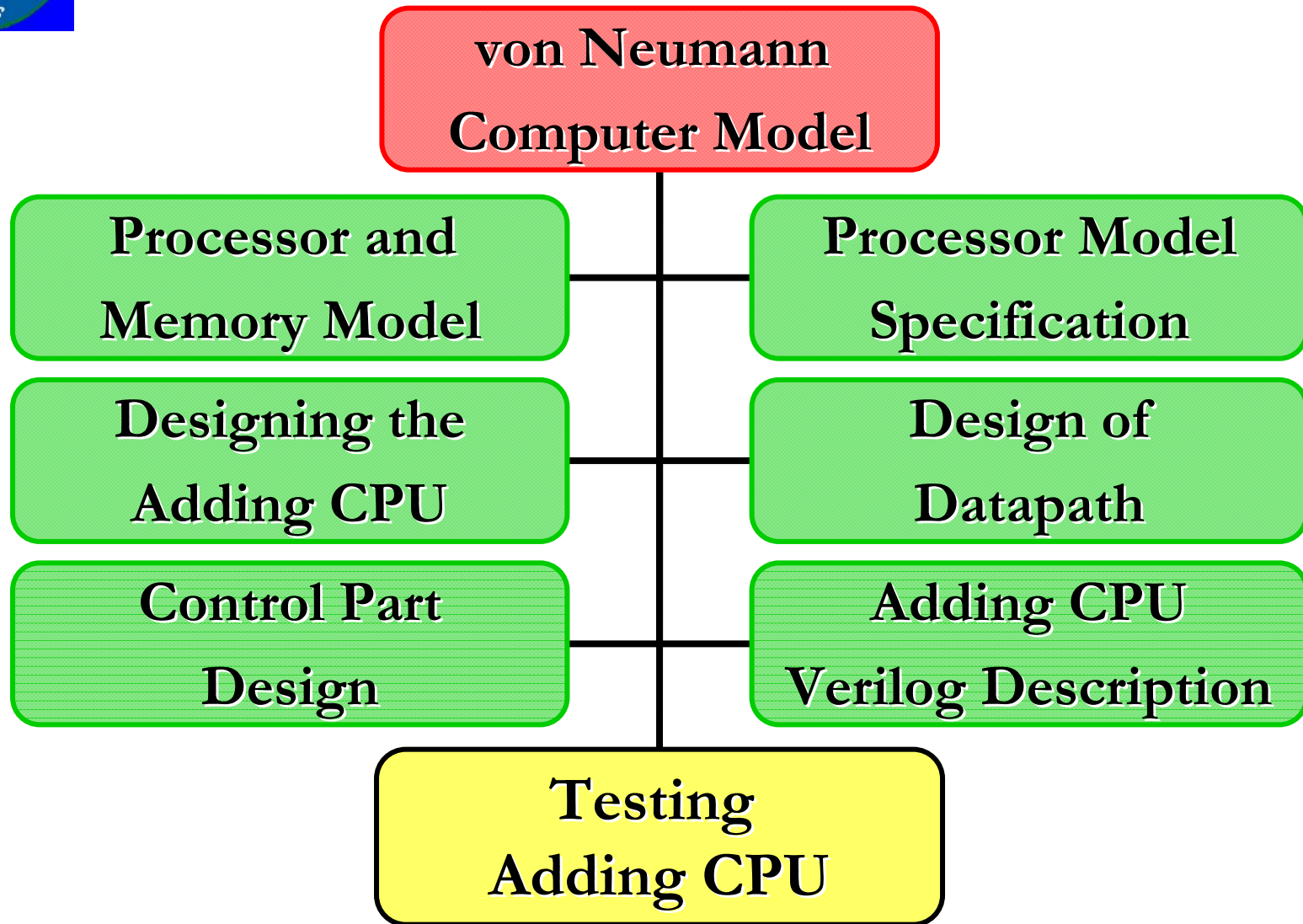




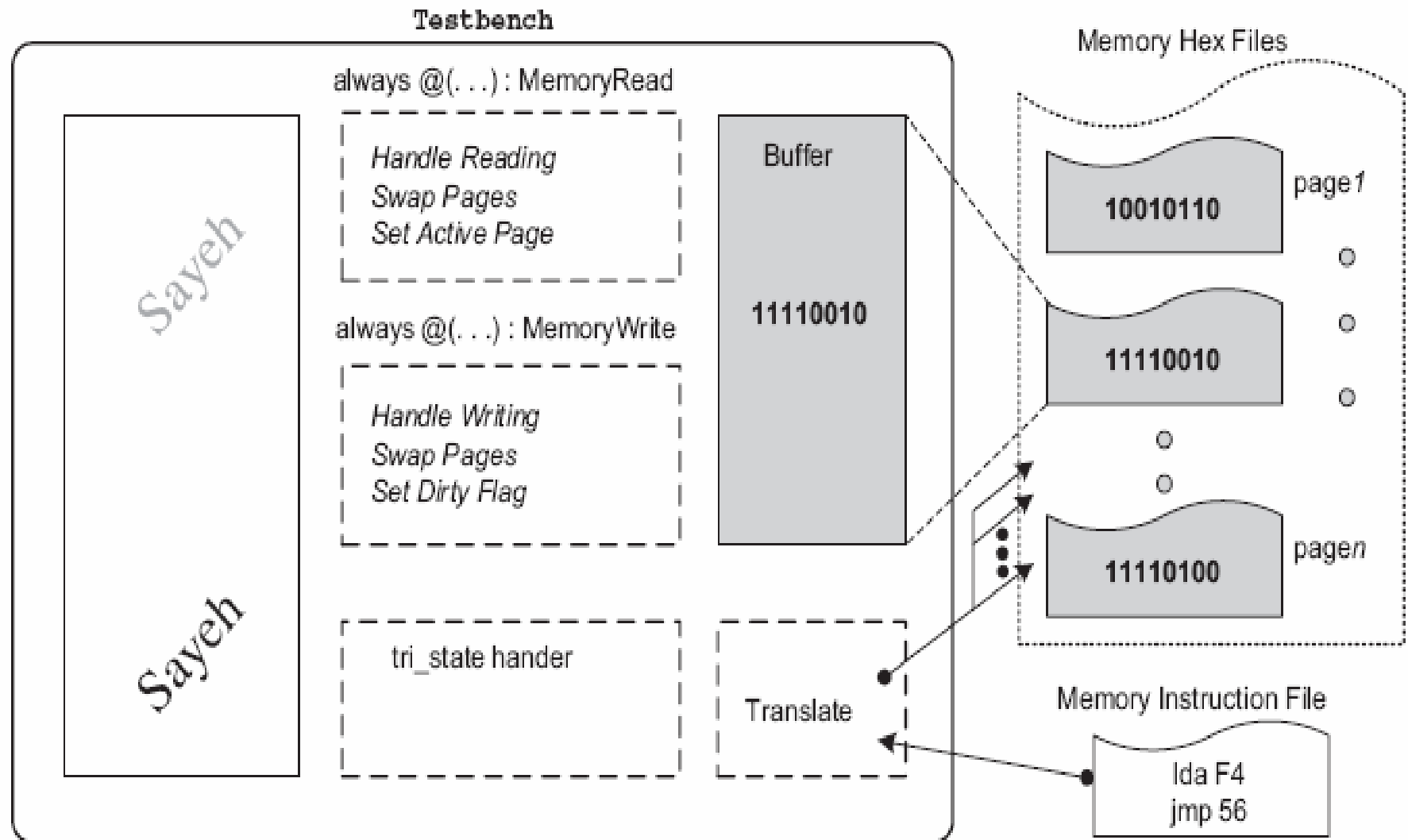
# Graphical Representation of CPU Testbench





# CPU test

- Instruction translation.
- Memory read procedure.
- Memory write procedure.
- Sorting test program
- CPU hardware realization




## 7.5 Design examples

- **USB2.0 interface IP CORE**
- **Wireless Sensor Network node controller**




# 1. USB2.0 IP CORE

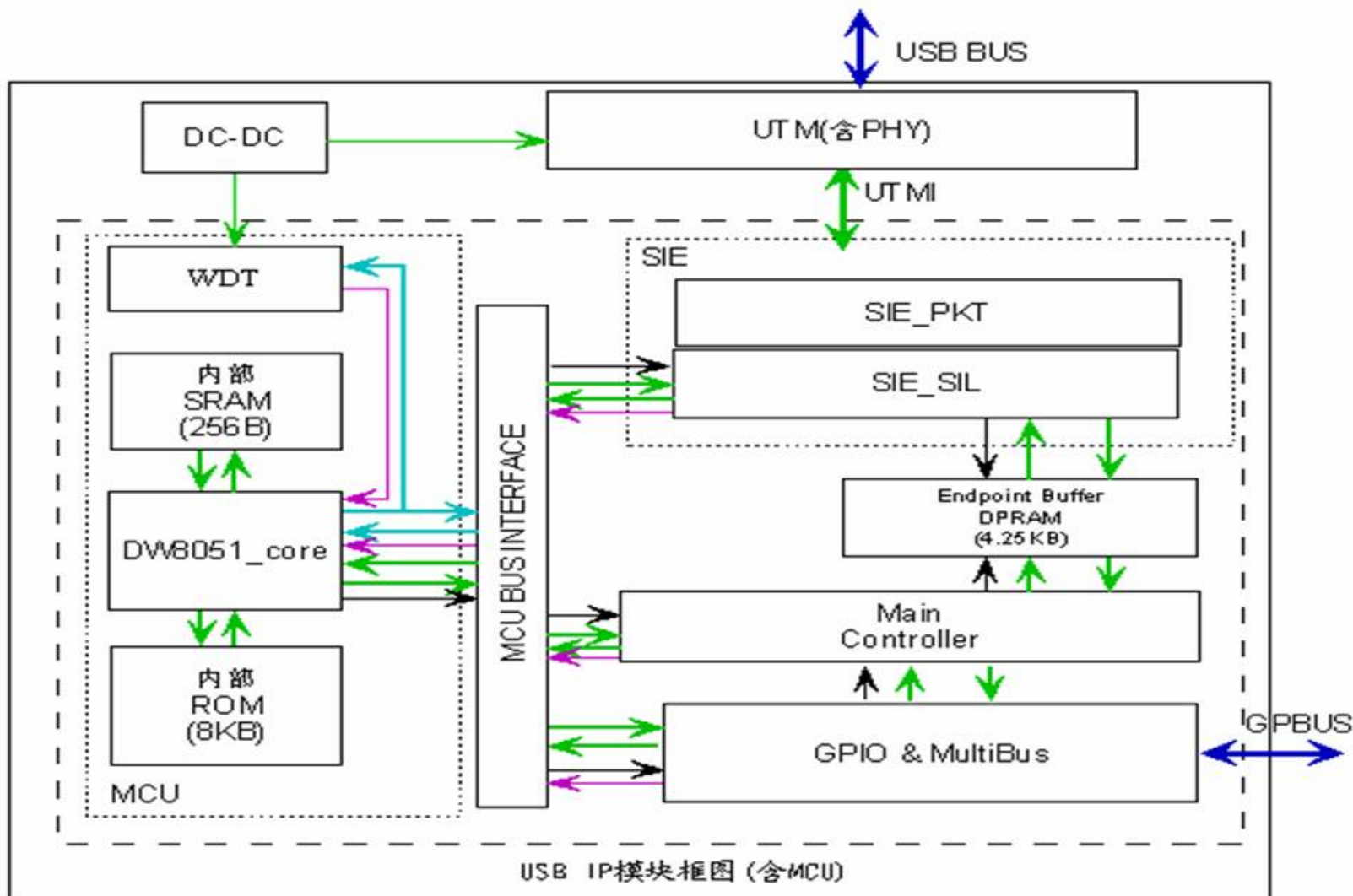




# 8051 CPU CORE

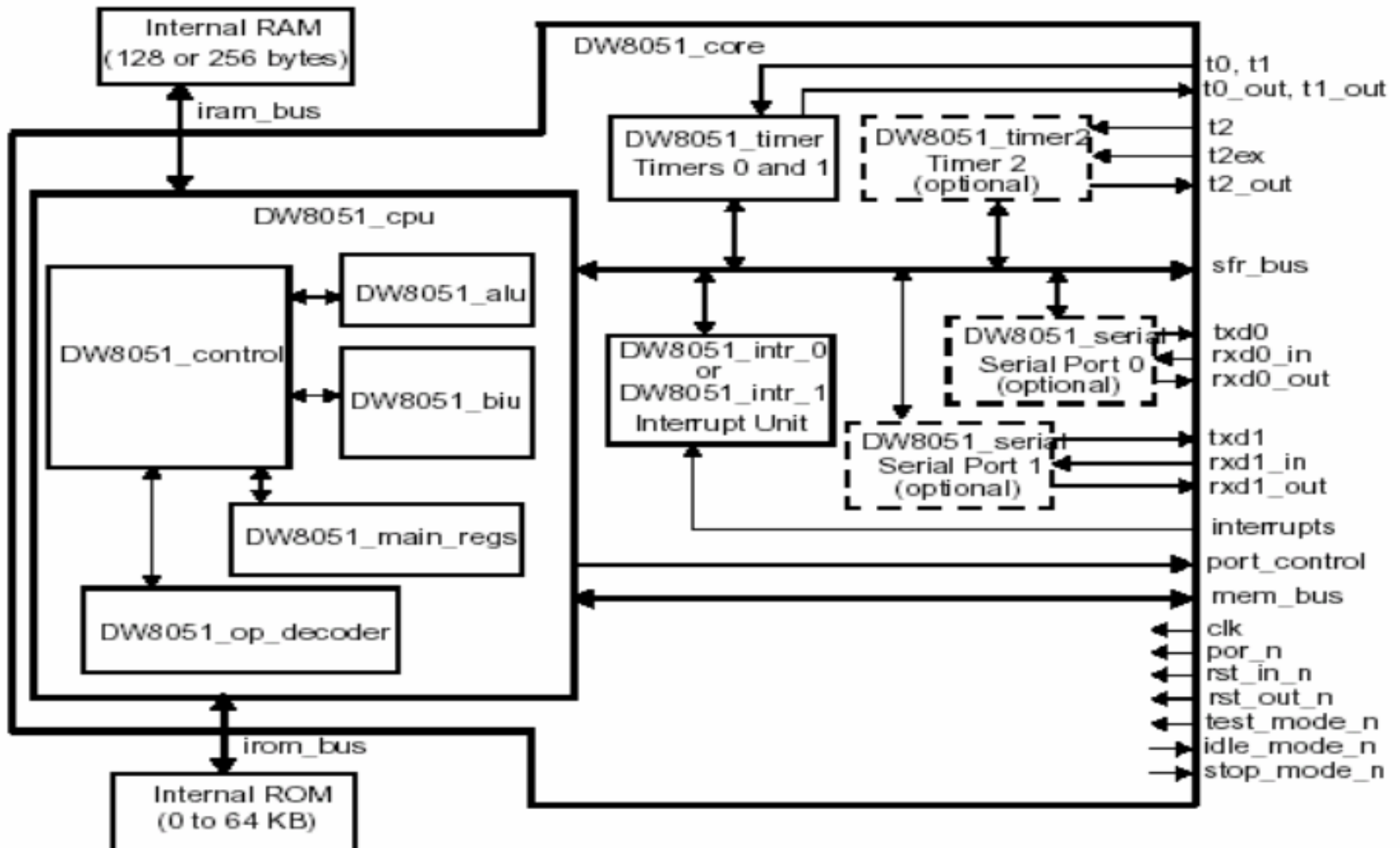



# The Demo of USB2.0 IP CORE

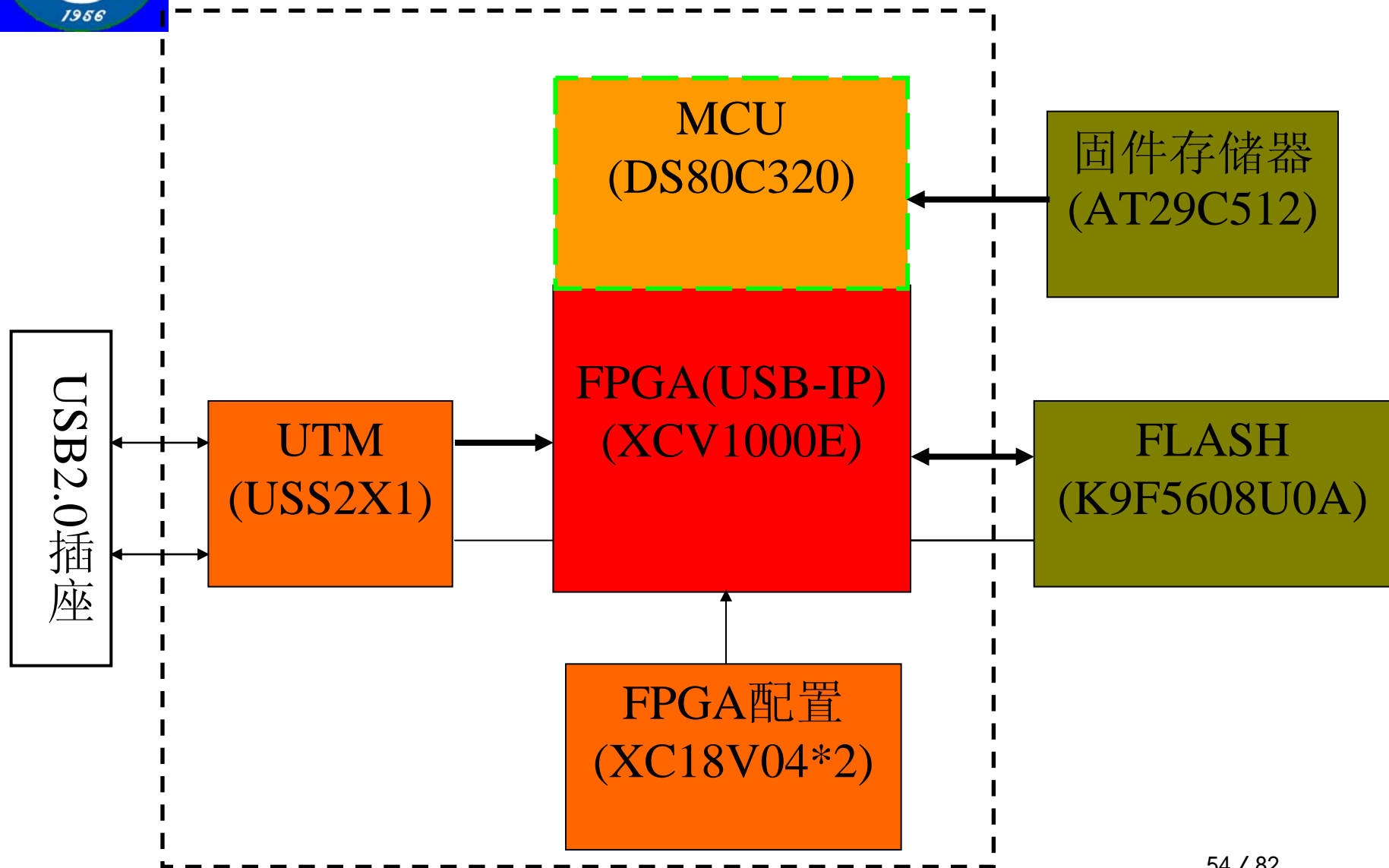






# USB2.0 DEMO Baesd on FPGA






# USB2.0 DEMO Baesd on ASIC

 





# USB2.0 interface chip(ASIC)

 



## 2. Low power MCU design for Wireless Sensor Network

 


图1 无线传感器网络体系结构图



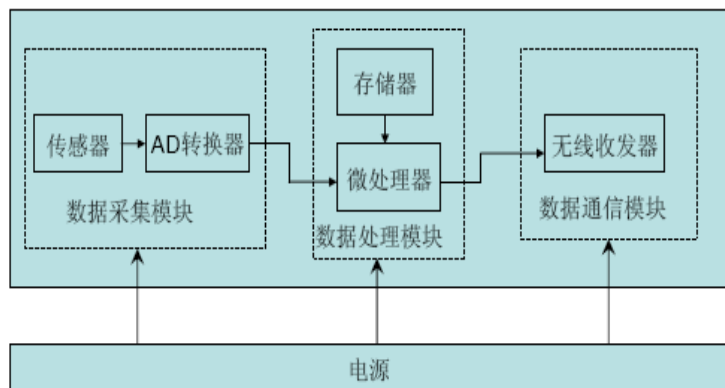


图2 节点的组成结构图

 

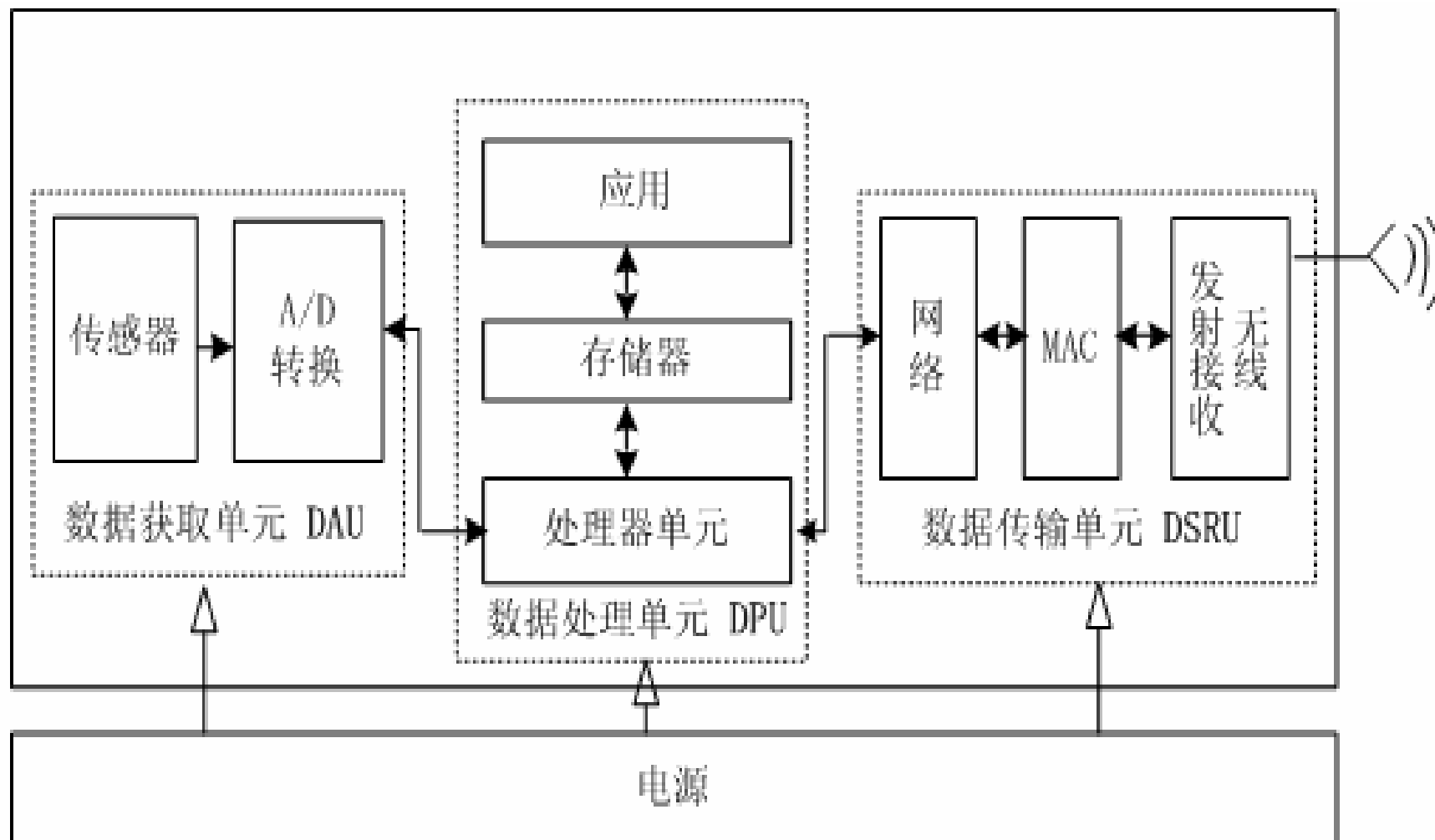


# The Node Controller of Wireless Sensor Network







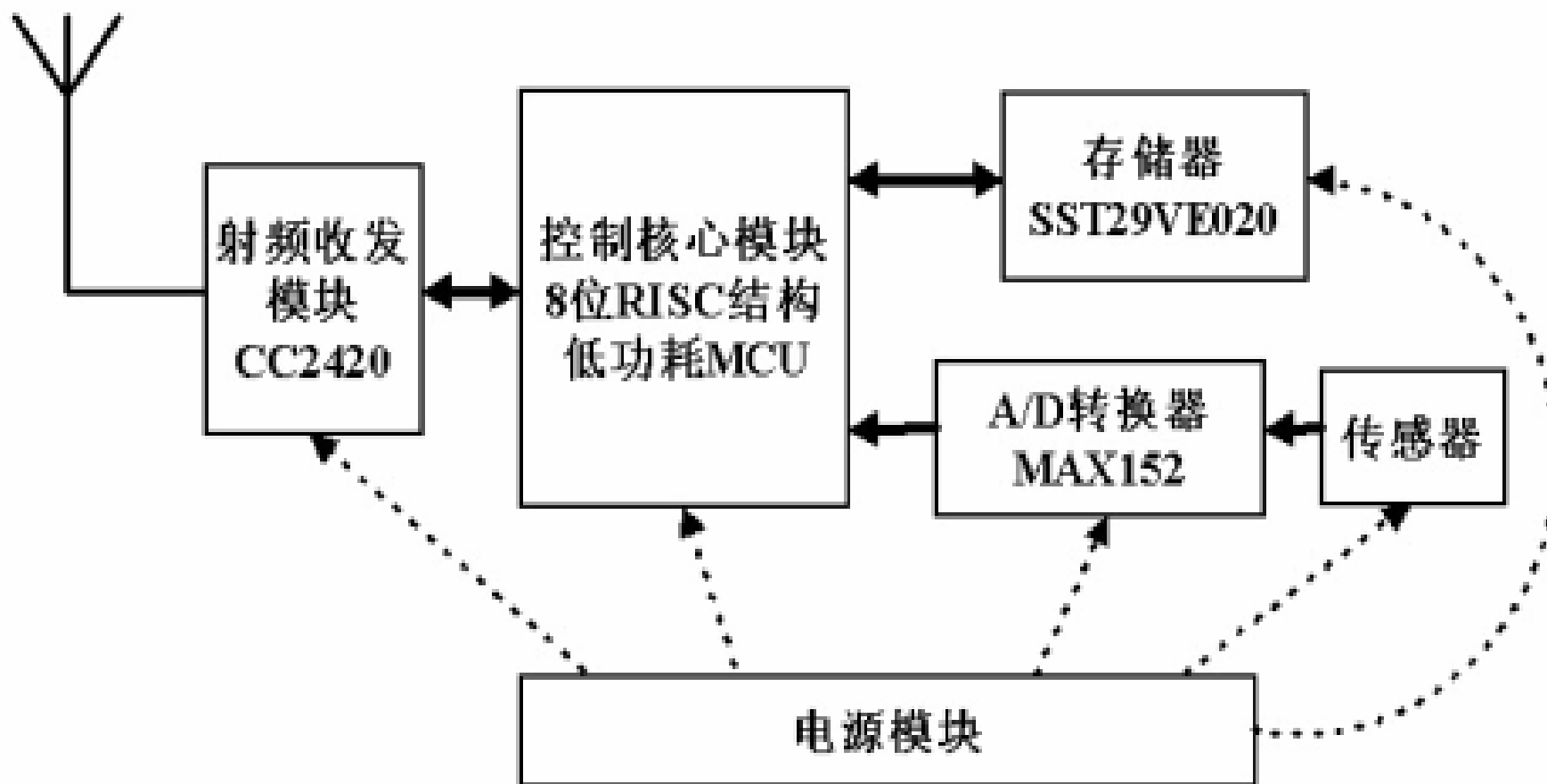
# The Node Hardware Architecture of Wireless Sensor Network




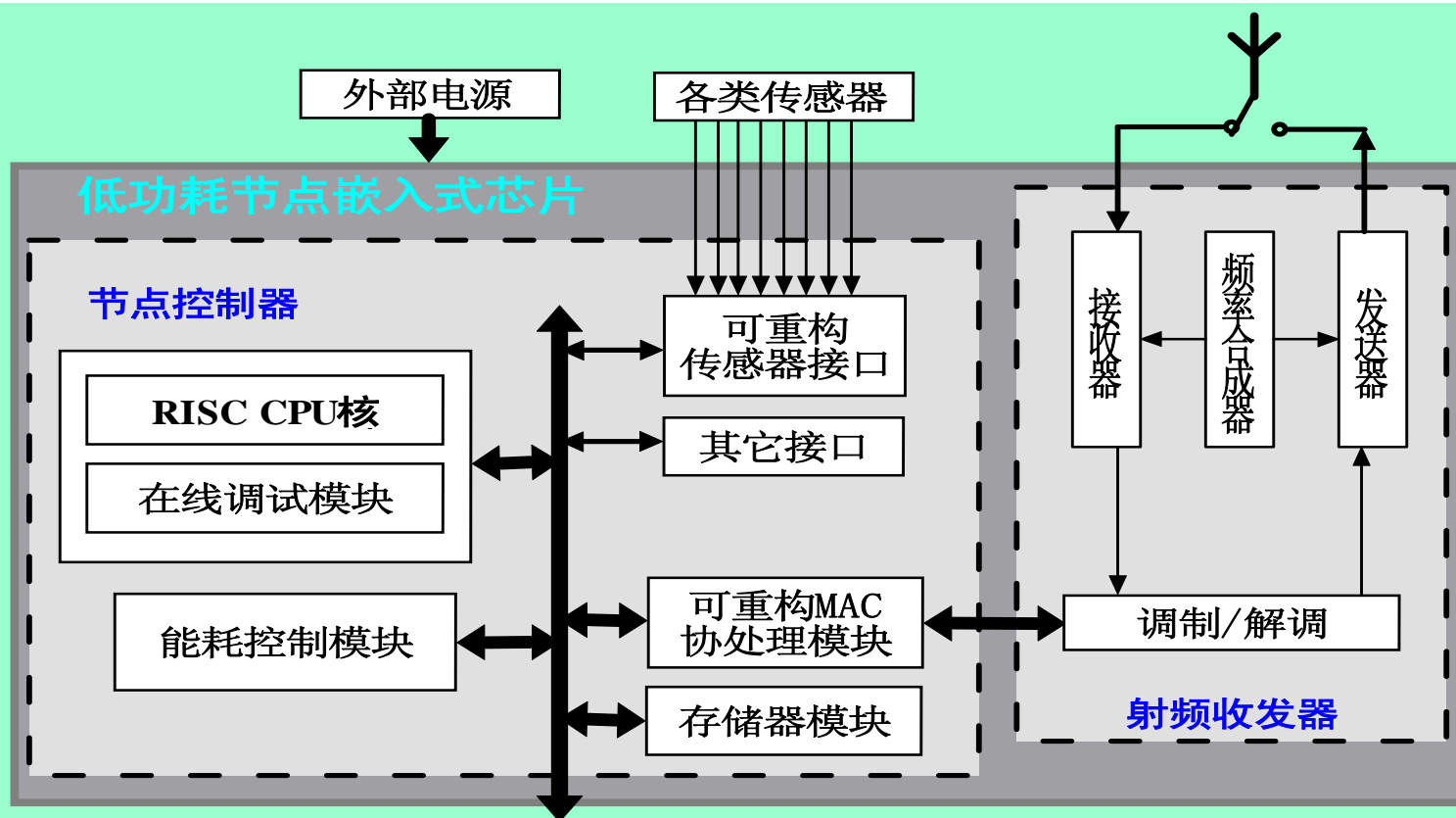
# The Node Controller of Wireless Sensor Network



(1) WSN节点系统架构及其关键技术


(2) WSN节点芯片设计与测试验证

(3) 芯片软硬件集成调试环境

(4) MAC及组网协议及WSN典型应用验证系统




# Low power MCU design

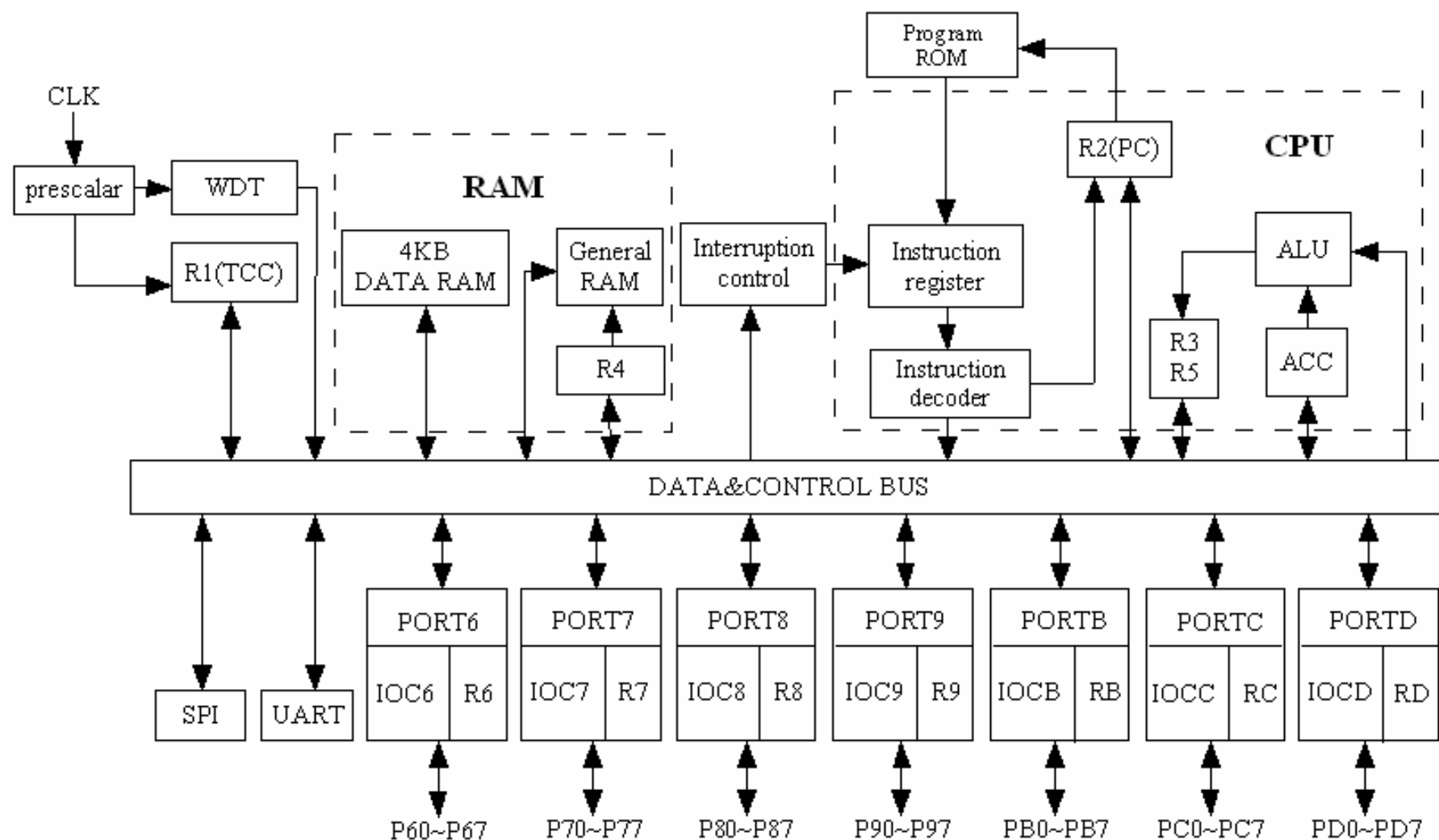




# The Memory Organization

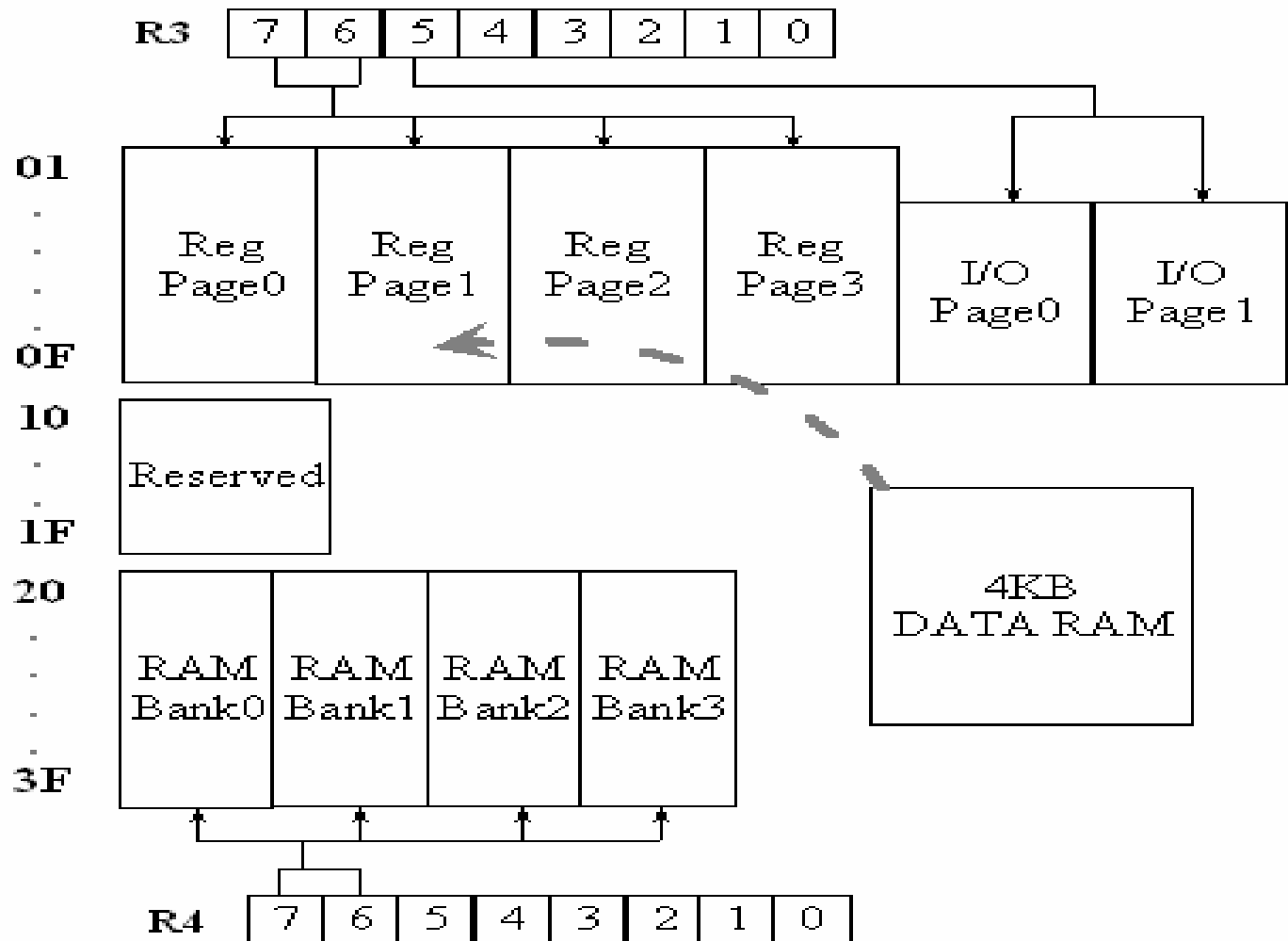



# The Program Counter

 






# The Function Module Registers Sets

Address	Register Page0	Register Page1	Register Page2	Register Page3	I/O Register Page0	I/O Register Page1
01	R1 TCC Buffer	R1 Real Int Flag1	R1 Real Int Flag2	R1 UART Rec Buf		
02						
03						
04			R4 UART Control1	R4 UART Control2		
05		R5 Counter Setting	R5 CNT1 low 8 bit			
06	R6 Port6 I/O Data		R6 CNT1 high 8 bit		IOC6 Port6 I/O Cntl	
07	R7 Port7 I/O Data		R7 CNT2 Data	R7 SPI Control	IOC7 Port7 I/O Cntl	
08	R8 Port8 I/O Data			R8 SPIData Buf	IOC8 Port8 I/O Cntl	
09	R9 Port9 I/O Data				IOC9 Port9 I/O Cntl	
0A						
0B	RB PortB I/O Data				IOCB PortB I/O Cntl	
0C	RC PortC I/O Data	RC DRAM Data Buf			IOCC PortC I/O Cntl	IOCC Port6 Pull High
0D	RD PortD I/O Data	RD DRAM addlow			IOCD PortD I/O Cntl	IOCD Port7 Pull High
0E	RE Int Flag1	RE DRAM addhigh		RE UART Trans Buf	IOCE Int Mask1	
0F	RF Int Flag2				IOCF Int Mask2	





# The Interrupt System

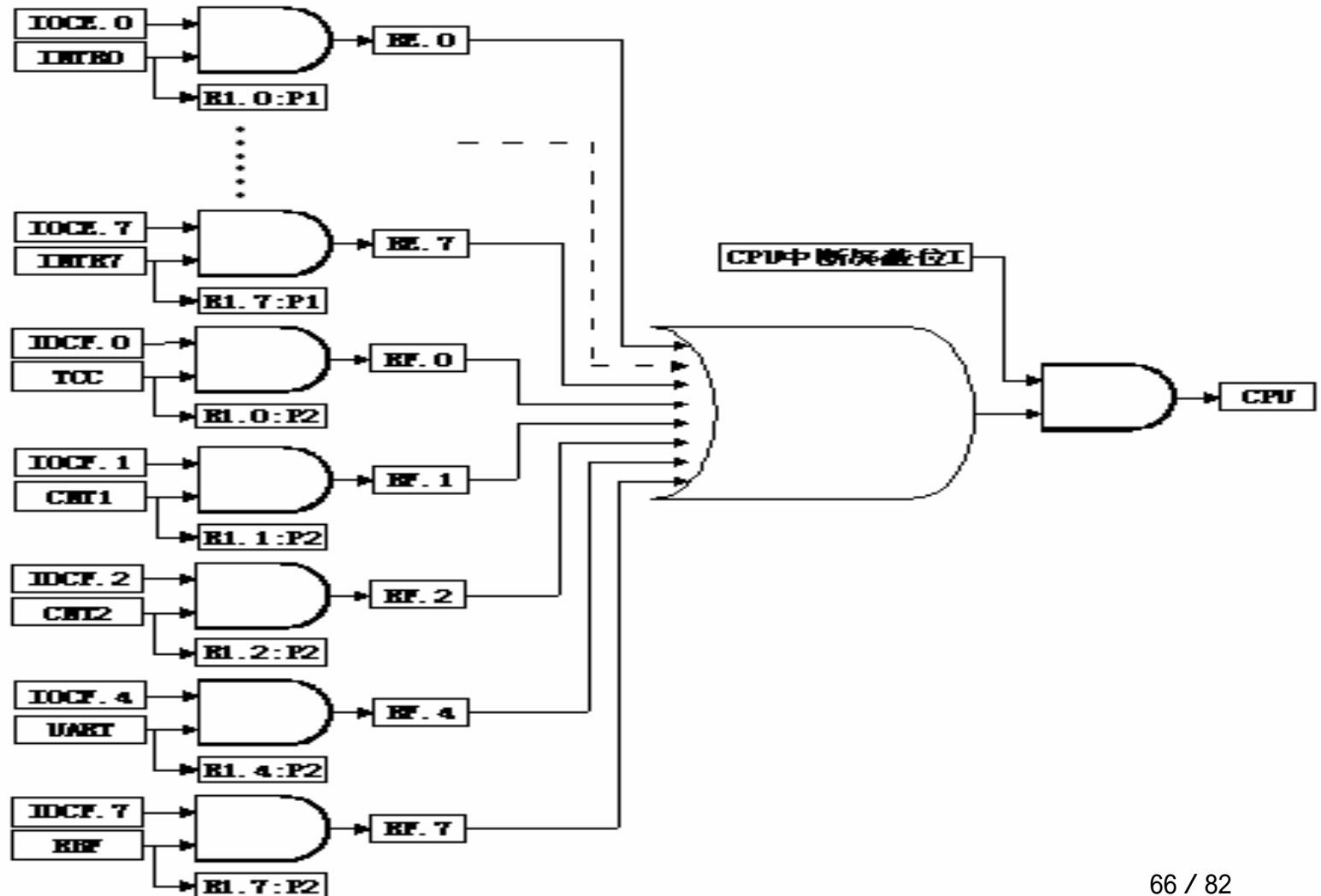



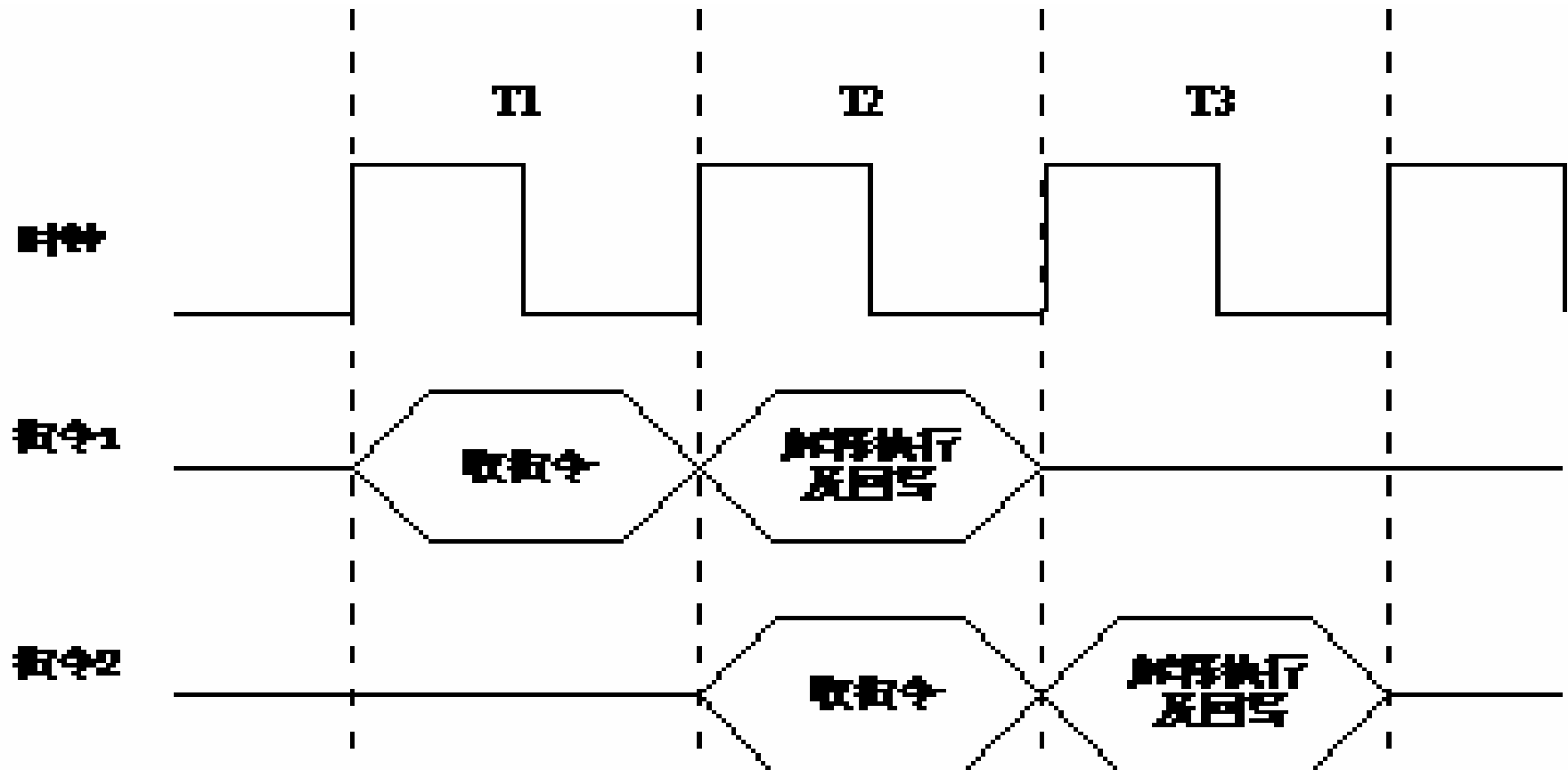
# Execution of the single cycle instruction



 




# The WDT & TCC

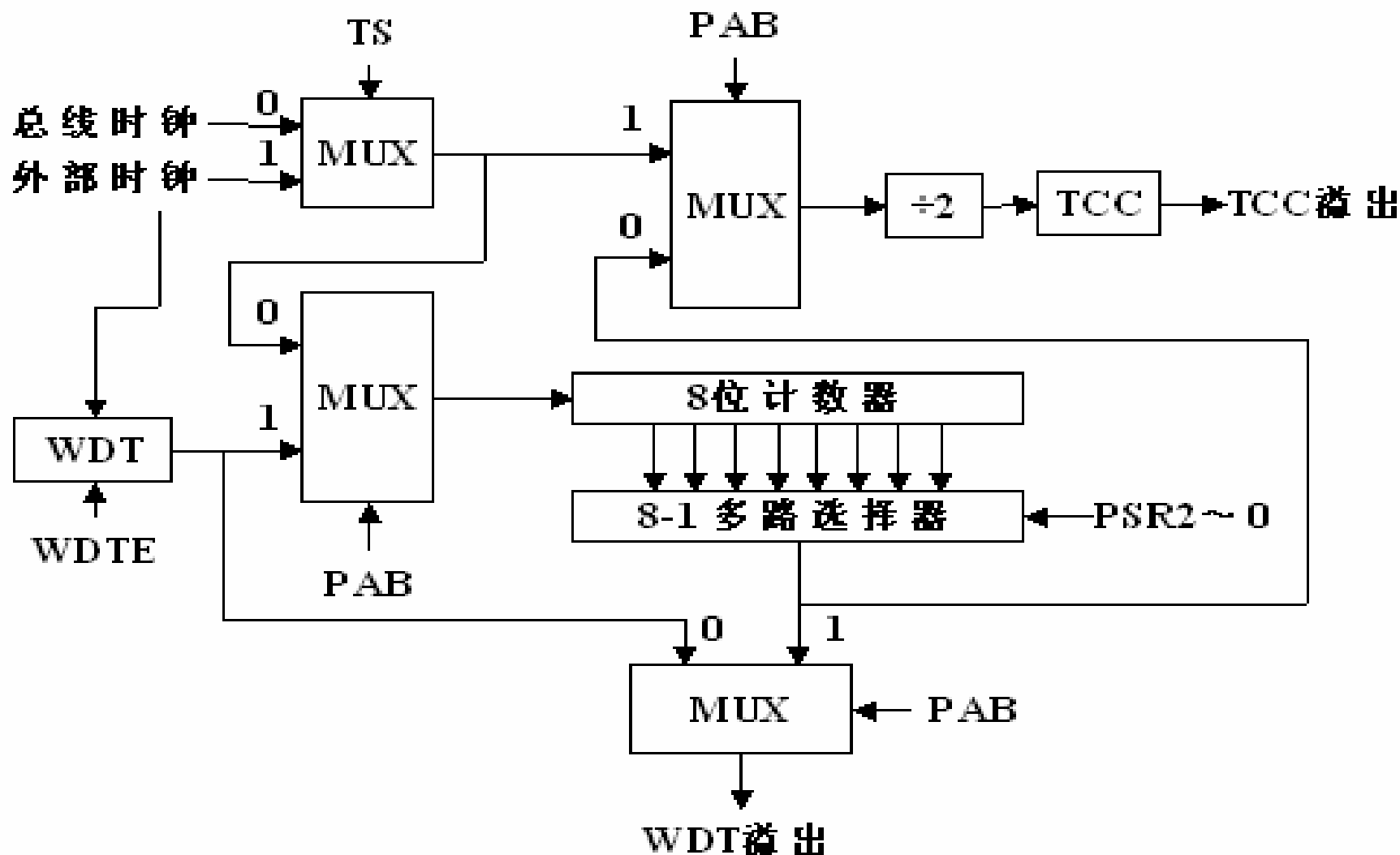




# The Timer and Counter

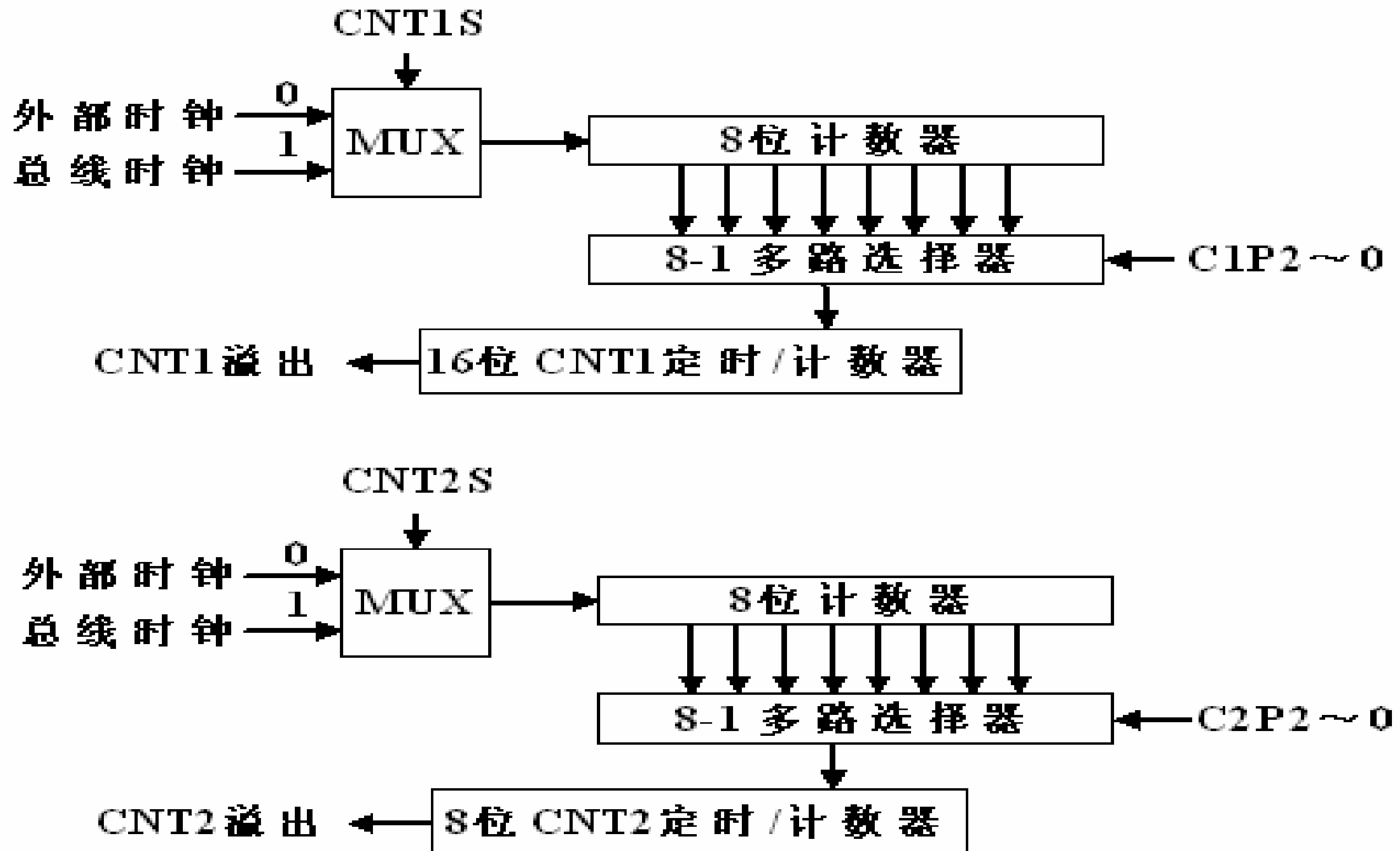




# The SPI

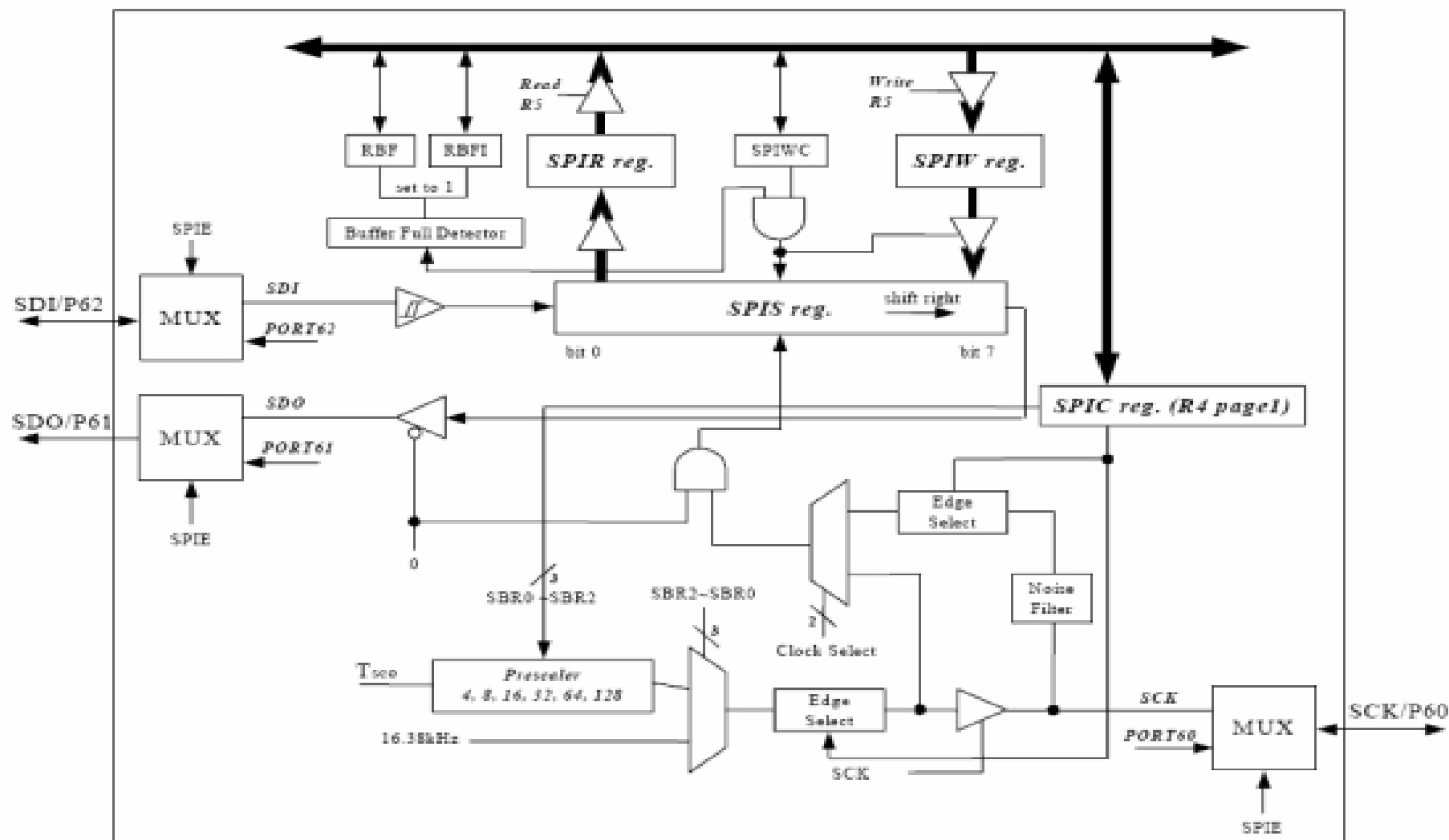




# The UART


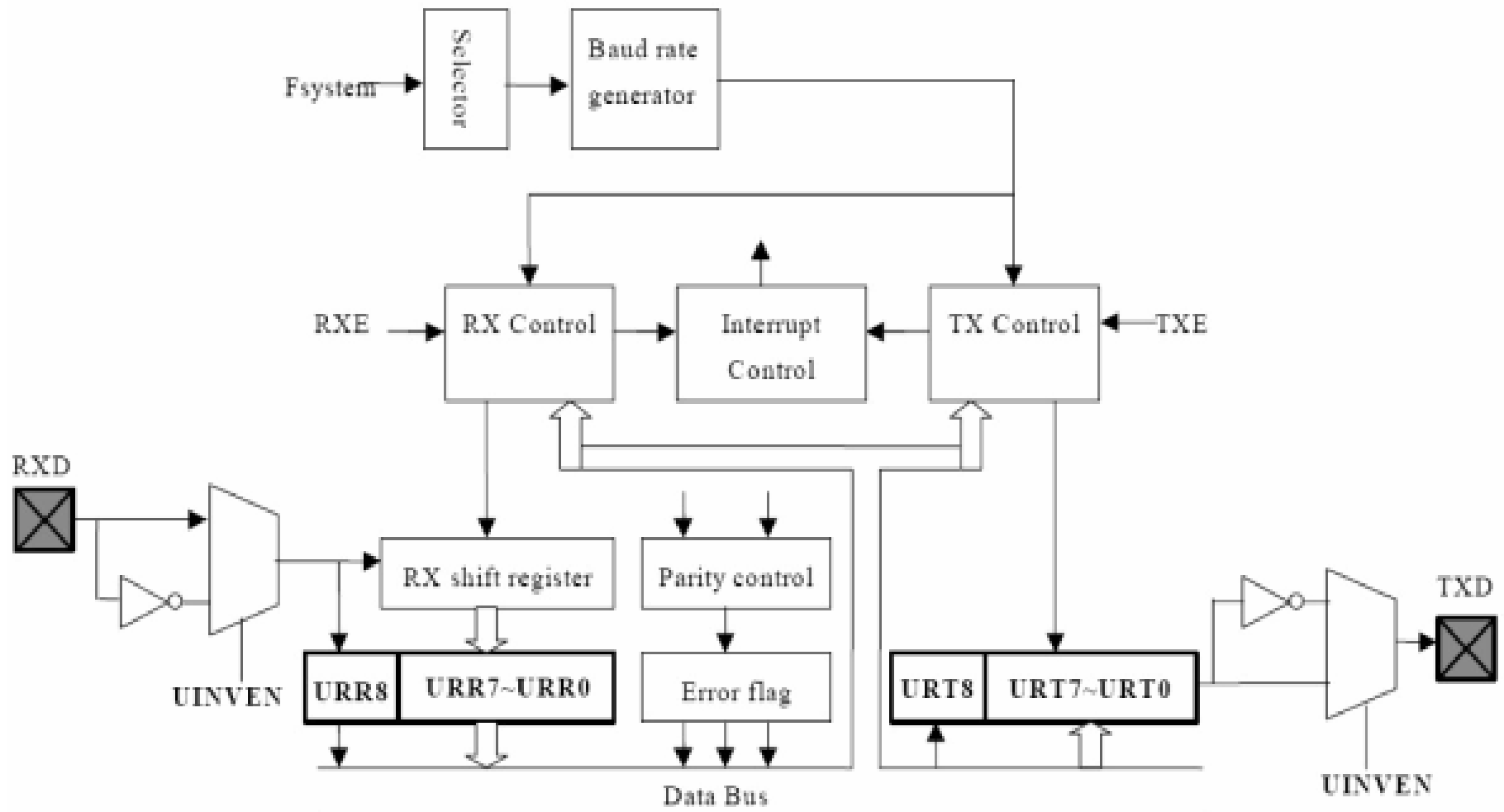








# The Architecture of I/O Ports

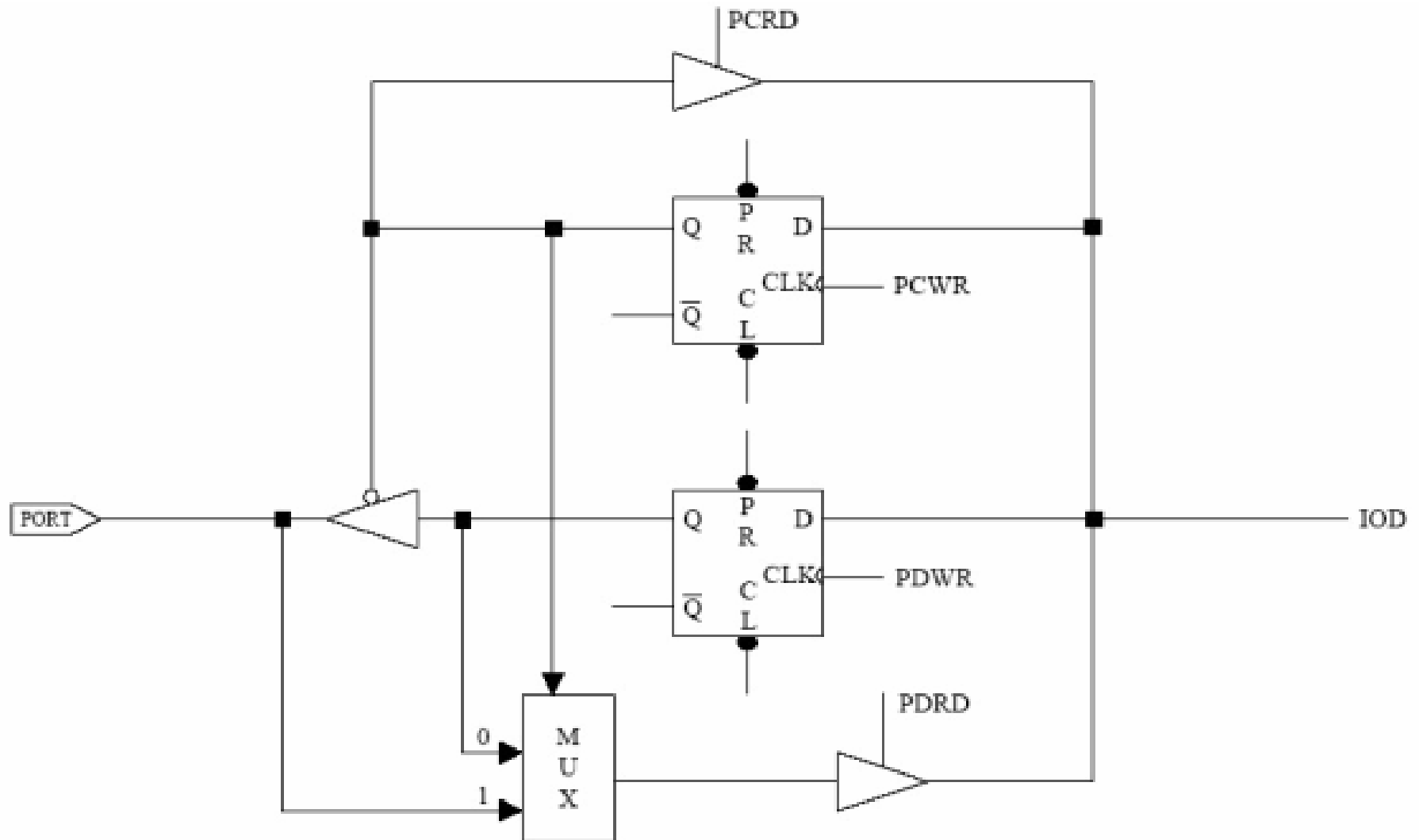

  


  
# Wireless Sensor Network node controller








# Wireless Sensor Network node controller




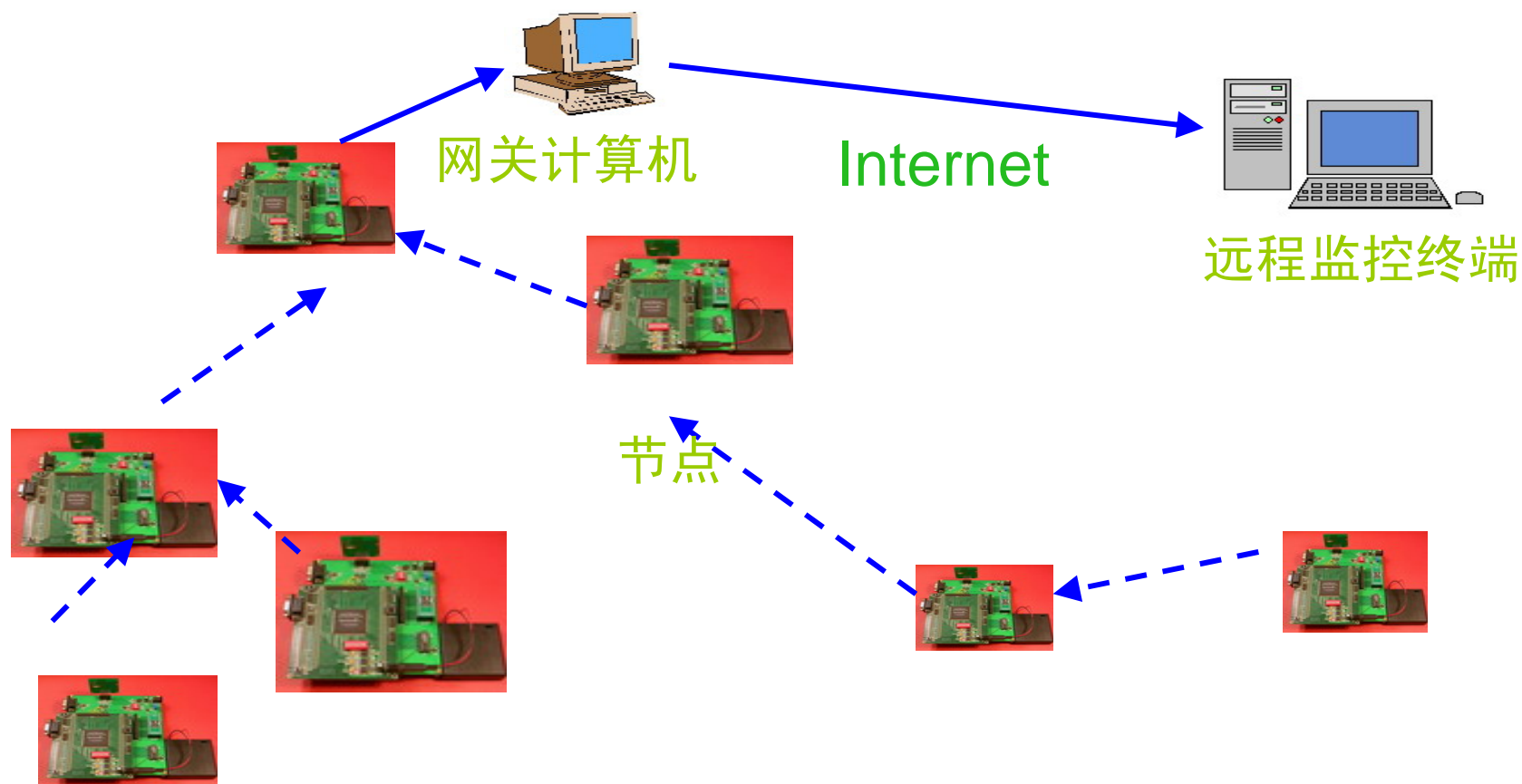
# The Node Controller Demo of Wireless Sensor Network






# Problem

- 7-1 Develop, verify, and synthesize **Johnson\_Counter\_ASM**, a Verilog behavioral module of based on a direct implementation of the ASM chart in Figure 7.5.
- Hint: Use a Verilog function to described next\_count.




# Figure 7.5

 




# Ring Counter

 

IF A B C D = 1 0 0 0 At S t a r t:

 






# Johnson Counter (Switch-Tail)


- A Johnson counter is also a shift register with feedback.

Assuming the initial state ABC is 000 we get the timing diagram shown:

 - The state must be initialized to operate correctly. Use logic to assure this.



IF ABCD = 000 At Start:

 



# Problem

- **7-18**

- Describe the differences between the circuits that will be synthesized from the following Verilog cyclic behaviors:
- `always @ (a or b or c or d) y = a + b + c + d;`
- `always @ (a or b or c or d) y = (a + b) + (c + d);`