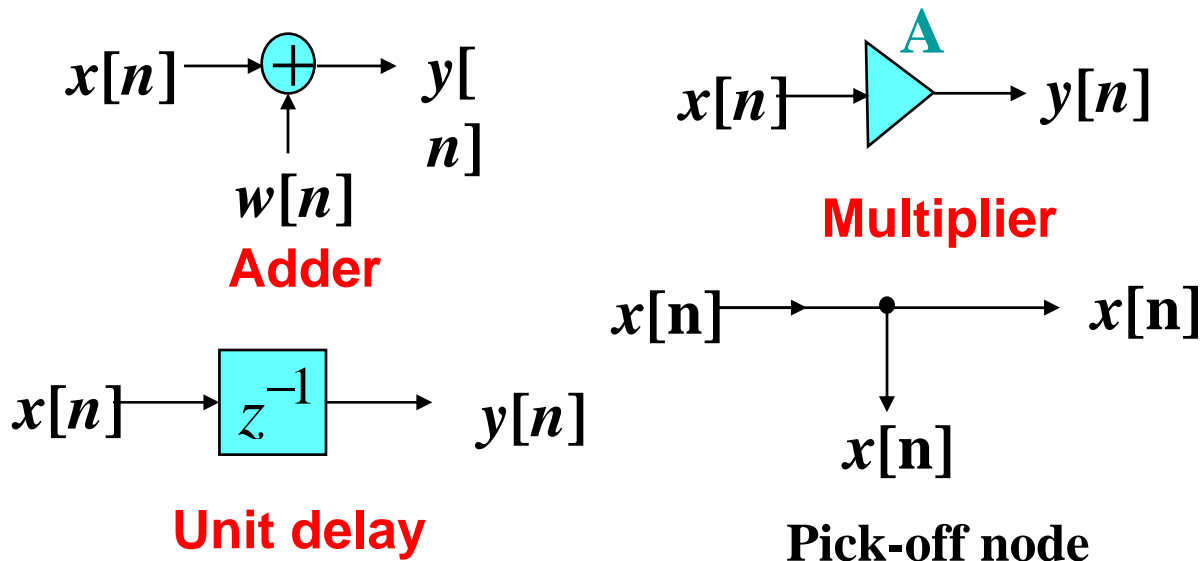




Chapter 10 Architectures for Arithmetic Processors

- Many algorithms require **repeated execution of arithmetic operations**, so **it is important that they be implemented efficiently**
- Examining **algorithms and architectures** for implementing addition, subtraction, multiplication, and division of **fixed-point numbers**





10.1 Number Representation

A binary number system has **two symbols and a radix of 2.**

Ex: an n-bit unsigned binary number is

represented as $B = b_{n-1}b_{n-2} \dots b_1b_0$, $b_i \in \{0,1\}$

- A **binary number** can be expressed as a weighted sum of ascending and descending powers of 2:

with **decimal value** $B_{10} = \sum_{i=-m}^{i=n-1} b_i 2^i$



Signed numbers

There are three common formats for signed numbers:

- Signed magnitude
- 1s complement
- 2s complement




10.1.1 Signed Magnitude Representation of Negative Integers

- The MSB of a word is the encoded sign bit:
0 representing a positive value;
1 representing a negative value.
- 0 has two representations:
+0: 0000_0000
-0: 1000_0000



Fig. 10-1 The numbers wheel of 8 bit signed-magnitude numbers

 



10.1.2 Ones Complement Representation of Negative Integers


- $-B$ denotes the 1s complement of an n -bit binary number B :

$$B + (-B) = 2^n - 1$$

- Positive numbers are represented in a 1s complement system in the same way they do in a signed-magnitude system
- But **negative 1s complement numbers are represented differently, in a 1s complement format**



1s complement numbers

 



10.1.3 Twos Complement Representation of Positive and Negative Integers


- The 2s complement of an n -bit binary integer is defined as:

$$B^* = 2^n - B$$

or: $B + B^* = 2^n = 0 \bmod n$



2s complement numbers

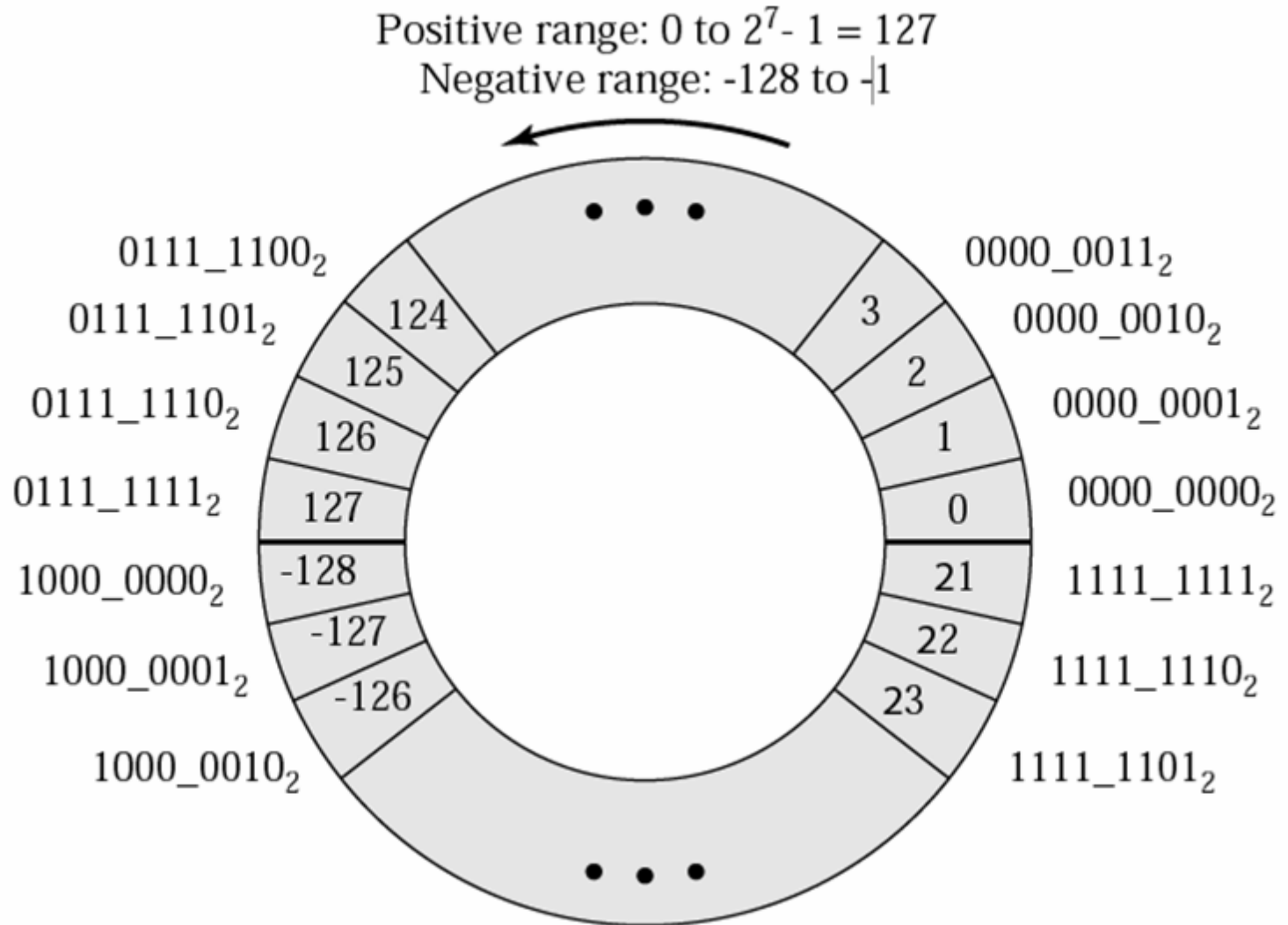



10.2 Functional Units for Addition and Subtraction

- Addition and subtraction are implemented in all arithmetic processors
- There are several alternatives that provide a tradeoff between hardware cost and performance




10.2.1 Ripple-Carry Adder

- A 16-bit ripple-carry adder can be formed by cascading four 4-bit ripple-carry adders in a chain
- The carry generated by a unit is passed to the carry input port of its neighbor, beginning with the least significant bit




Ripple-Carry Adder

 



Ripple Carry Adder

 



Alternative architecture to form the outputs quickly

- If the word length of the processor using the adder is large, it might be necessary to use an alternative architecture **to form the outputs quickly enough to satisfy timing constraints**
- **Pipelining the dataflow is one alternative**, but it introduces latency and requires hardware to implement the pipeline registers
- **Another alternative is to consider other algorithms for addition**, among those that are used are :
 - the carry look-ahead algorithm**
 - the carry select algorithm**
 - the carry-save algorithm**



10.2.2 Carry Look-Ahead Adder

- The algorithm is based on the observation that **the value of the carry** into any stage of a multicell adder **depends on only the data bits of the previous stages and the carry into the first stage**
- This relationship can be exploited to improve the speed of the adder **by using additional logic to implement the carry**, rather than waiting for the value to propagate through the cells of the adder




Generate a Carry & Propagate a carry

- A given cell is said **to generate a carry** if both of the cell's data bits are 1
- A cell is said **to propagate a carry** if either of the cell's data bits could combine with the carry into the cell to cause a carry out to the next stage of the adder



Full-Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate



Carry Look-Ahead Adders

-- Basic Idea

Recall that

$$\begin{aligned}c_i &= a_i b_i + a_i c_{i-1} + b_i c_{i-1} \\&= a_i b_i + a_i b_i c_{i-1} + a_i b_i' c_{i-1} + a_i' b_i c_{i-1} + a_i' b_i c_{i-1} \\&= a_i b_i + a_i b_i' c_{i-1} + a_i' b_i c_{i-1} \\&= a_i b_i + (a_i b_i' + a_i' b_i) c_{i-1} \\&= a_i b_i + (a_i \oplus b_i) c_{i-1}\end{aligned}$$

Let $g_i = a_i b_i$ [carry generate]

$p_i = a_i \oplus b_i$ [carry propagate]

Then $c_i = g_i + p_i c_{i-1}$

$s_i = p_i \oplus c_{i-1}$



Carry Look-Ahead Adders

-- Three-Bit Example

$$c_0 = g_0$$

$$s_0 = p_0$$

$$c_1 = g_1 + p_1 c_0$$

$$= g_1 + p_1 g_0$$

$$s_1 = p_1 \oplus c_0$$

$$c_2 = g_2 + p_2 c_1$$

$$= g_2 + p_2 (g_1 + p_1 g_0)$$




$$= g_2 + p_2 g_1 + p_2 p_1 g_0$$

$$s_2 = p_2 \oplus c_1$$

$$g_i = a_i b_i,$$
$$p_i = a_i \oplus b_i$$



Carry Look-Ahead Adder Design

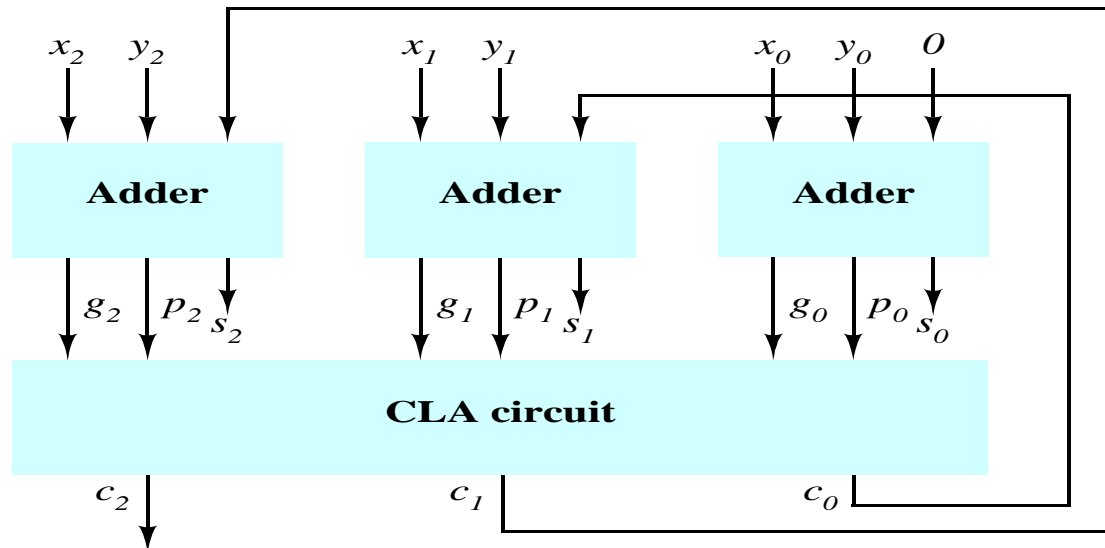  



Carry Look-Ahead Adder

$$C_0=0, \quad C_{i+1} = a_i b_i + a_i C_i + b_i C_i = a_i b_i + (a_i + b_i) C_i$$

Suppose : $g_i = a_i b_i$, $q_i = a_i + b_i$

Then:

$$\begin{aligned} C_{i+1} &= g_i + p_i C_i \\ &= g_i + p_i (g_{i-1} + p_{i-1} C_{i-1}) \\ &= g_i + p_i (g_{i-1} + (p_{i-1} (g_{i-2} + p_{i-2} C_{i-2}))) \\ &\quad \dots \\ &= g_i + p_i (g_{i-1} + p_{i-1} (g_{i-2} + p_{i-2} (\dots (g_0 + p_0 C_0) \dots))) \\ &= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \dots + p_i p_{i-1} \dots p_1 p_0 + p_1 g_0 + p_i p_{i-1} \dots p_1 p_0 C_0 \end{aligned}$$

g_i, p_i depend on: a_i, b_i

C_{i+1} depends on : $a_i, a_{i-1} \dots a_0, b_i, b_{i-1} \dots b_0$, c_0




Carry Look-Ahead Adder

- The sum and the carry-out bits of each cell can be expressed in terms of the data bits of that cell and of the previous cells, and **the carry into only the first cell of the adder chain.**
- So there is ***no need to wait for a carry bit to propagate through the adder to a particular cell***




Fig 10-6 Schematic for arithmetic implementation of
 
$$C_{i+1} = a_i \& b_i + (a_i \oplus b_i) \& c_i$$






Gate level circuit-carry look adder

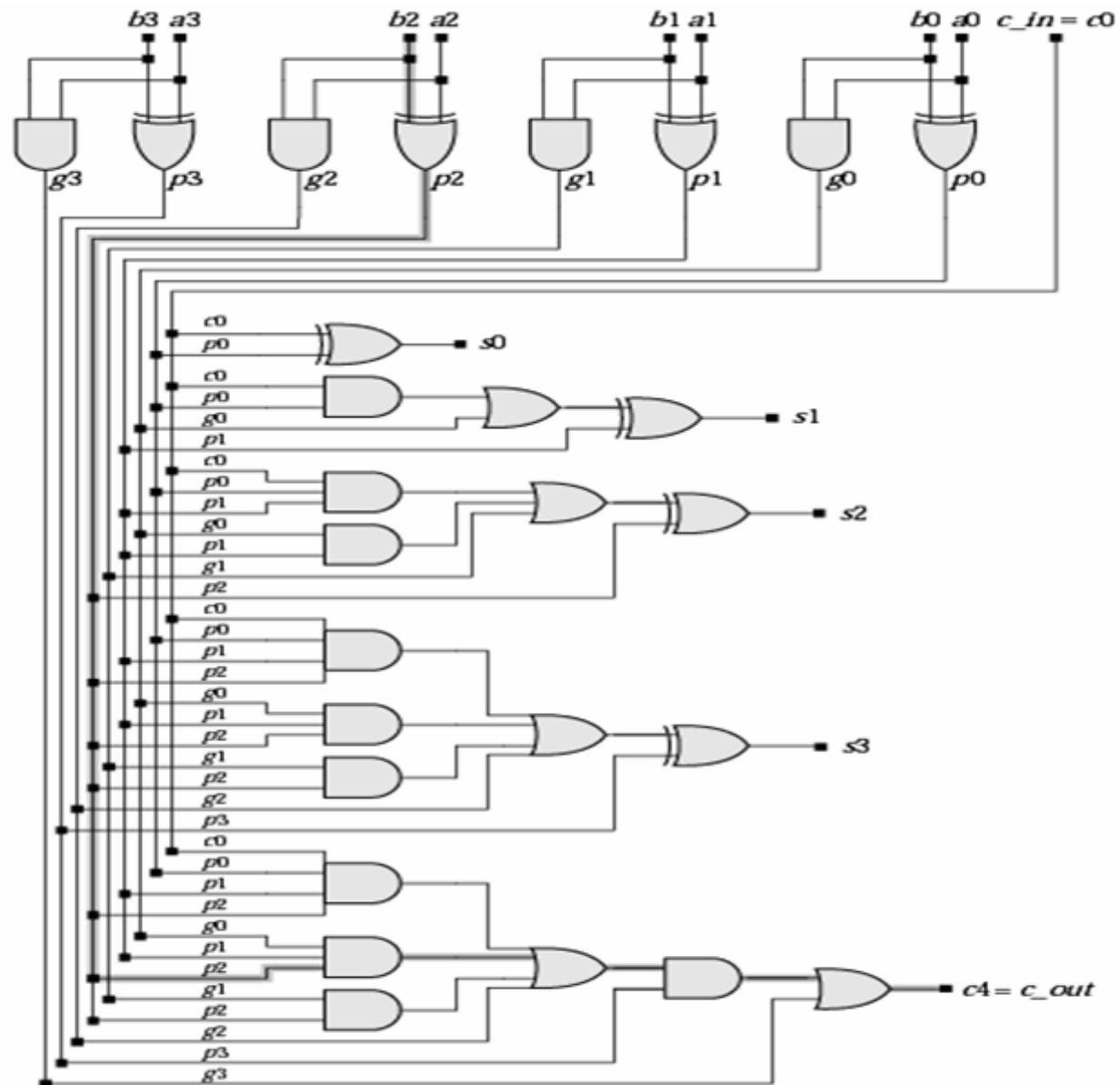



Gate level circuit- ripple-carry adder

 

(b)



The propagate and generate recursive algorithm for a four-bit adder

```
module Add_prop_gen (sum, c_out, a, b, c_in);  
    output    [3: 0]  sum;  
    output    c_out;  
    input     [3: 0]  a, b;  
    input     c_in;  
    reg       [3: 0]  carrychain;  
    integer    i;  
    wire      [3: 0]  g = a & b;  
    //carry generate, continuous assignment, bitwise and  
    wire      [3: 0]  p = a ^ b;  
    //carry propagate, continuous assignment, bitwise xor
```



```
always @ (a or b or c_in or p or g)  
begin: carry_generation  
integer i;  
carrychain[0] = g[0] + (p[0] & c_in);  
for(i = 1;i<= 3;i = i + 1)  
begin //  $C_{i+1} = a_i \& b_i + (a_i \oplus b_i) \& c_i$   
carrychain[i] = g[i] | (p[i] & carrychain[i-1]);  
end  
end  
wire [4:0] shiftedcarry = {carrychain, c_in};  
//concatenation  
wire [3:0] sum = p ^ shiftedcarry;  
//summation  
wire c_out = shiftedcarry[4];  
endmodule
```




Hardware subtraction units

- Hardware units usually implement subtraction **by adding the 1s complement of the subtrahend to the minuend, and then adding 1 to the result**
- This can be implemented with the architecture shown in Figure 10-9
- One adder unit can be used for addition or subtraction, depending on the value of the signal select



Fig 10-9 Architecture for a combined 4-bit datapath adder and subtractor unit

 



10.2.3 Overflow and Underflow

- Occurs when assigning a value that is too large (overflow) or too small (underflow) to be held in a variable
- Overflow occurs under two conditions:
 - (1) when adding two positive numbers produces a sum that exceeds the largest positive number that can be represented in the word length of the unit
 - (2) when adding two negative numbers produces a sum that is positive
- Arithmetic units include logic for underflow and overflow detection



10.3 Functional Units for Multiplication

- Multiplication can be **implemented with a combinational circuit or by a sequential circuit.**
- A combinational circuit require **more silicon area, but operate faster.**
- Sequential circuit require **less silicon area, but takes several clock cycles.**
- To discuss the differences between them and their own characters



10.3.1 Combinational (Parallel) Binary Multiplier

$$A \times B = \sum_{i=0}^{m-1} A_i 2^i \sum_{j=0}^{n-1} B_j 2^j$$

And we know:

$$\begin{aligned} & (a_1 + a_2 + \cdots + a_m)(b_1 + b_2 + \cdots + b_n) \\ &= a_1 b_1 + a_1 b_2 + \cdots + a_1 b_n \\ &+ a_2 b_1 + a_2 b_2 + \cdots + a_2 b_n + \cdots + a_m b_n \end{aligned}$$

So:

$$A \times B = \sum_{i=0}^{m-1} \sum_{j=0}^{n-1} A_i B_j 2^{i+j}$$



The result can be written as a sum of weighted powers of 2:

$$A \times B = \sum_{k=0}^{m+n-1} P_k 2^k$$

Generally

we complement multiplier **by adding shifted copies of the multiplicand.**




The Binary Multiplication

				1	0	1	0	1	0		Multiplicand
x						1	0	1	1		Multiplier
<hr/>											
				1	0	1	0	1	0		Partial products
						1	0	1	0	1	
				0	0	0	0	0	0		Partial products
+		1	0	1	0	1	0				
<hr/>											
		1	1	1	0	0	1	1	1	0	Result



Fig 9-10 Formation of a product by columnwise adding shifted copies of the multiplicand

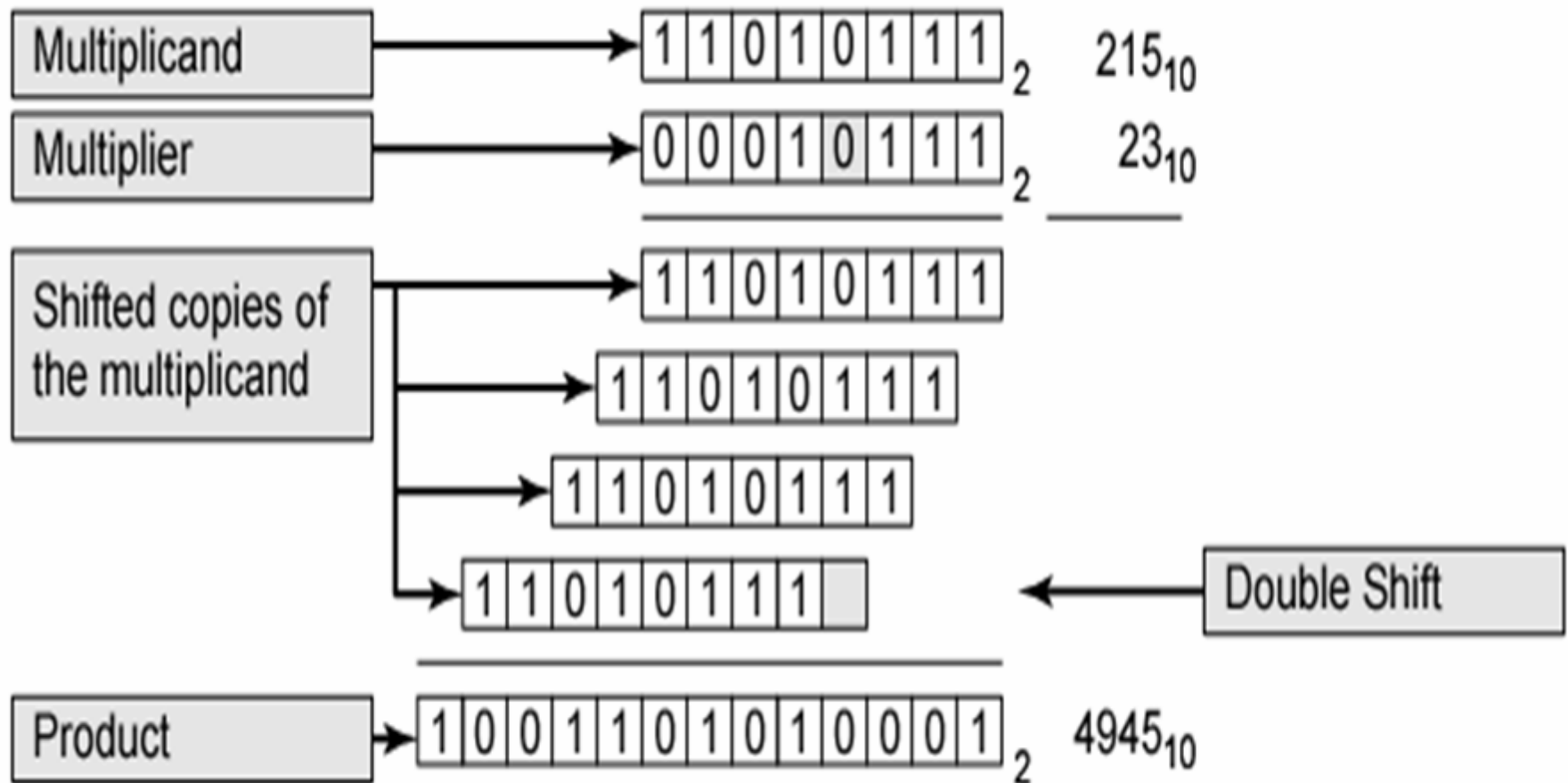



The process works manually

- The process shown in Figure 10-10 works manually, and a combinational circuit can be developed to implement the product, **with binary multiplication formed by an AND gate**
- **An ordinary adder operates on only two words at a time**, so a more attractive scheme that forms a sequence of row sums by adding a single copy of the multiplicand to an accumulated product will be presented here



Fig 9-11 Alternative sequential process forming the product of a pair of binary words by accumulating partial sums

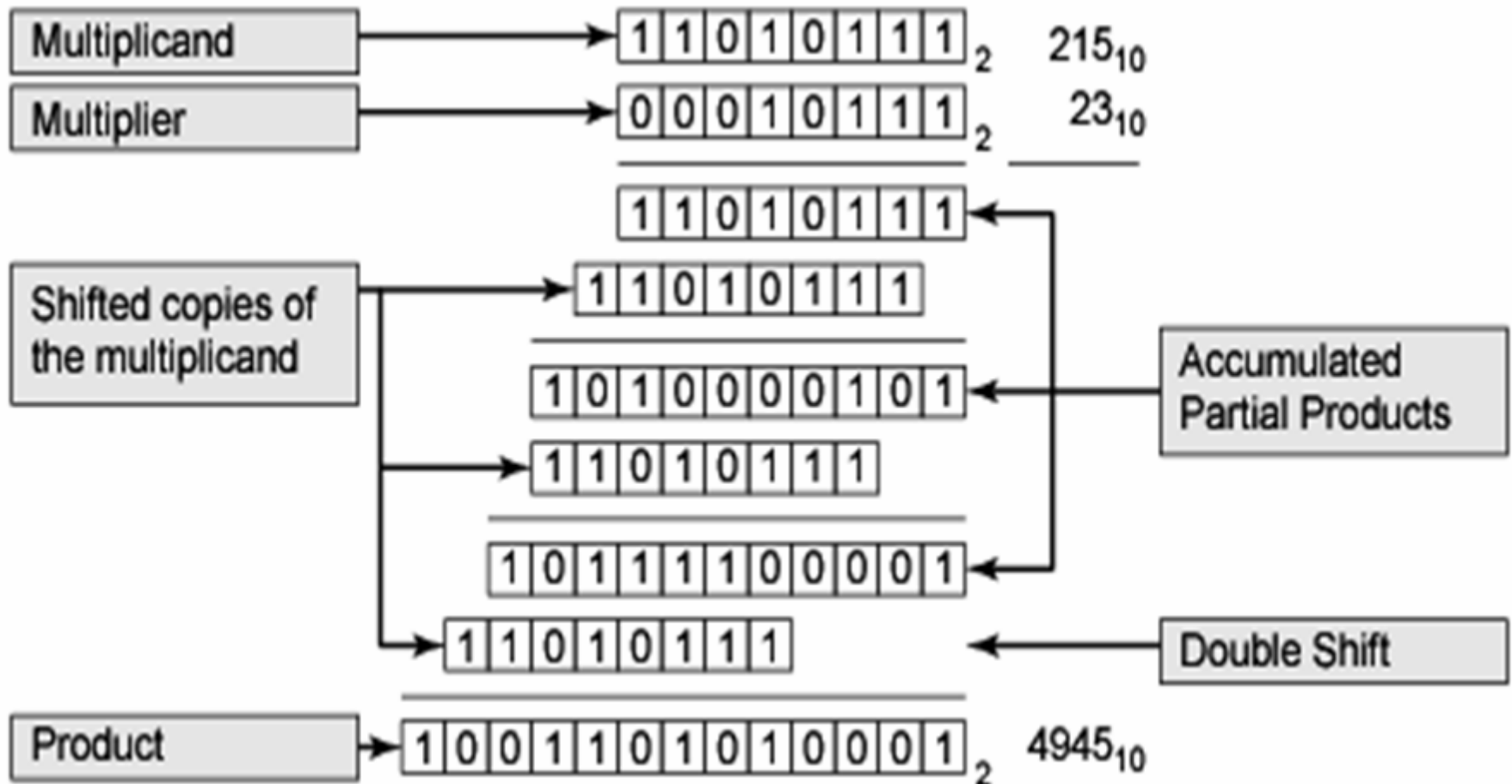


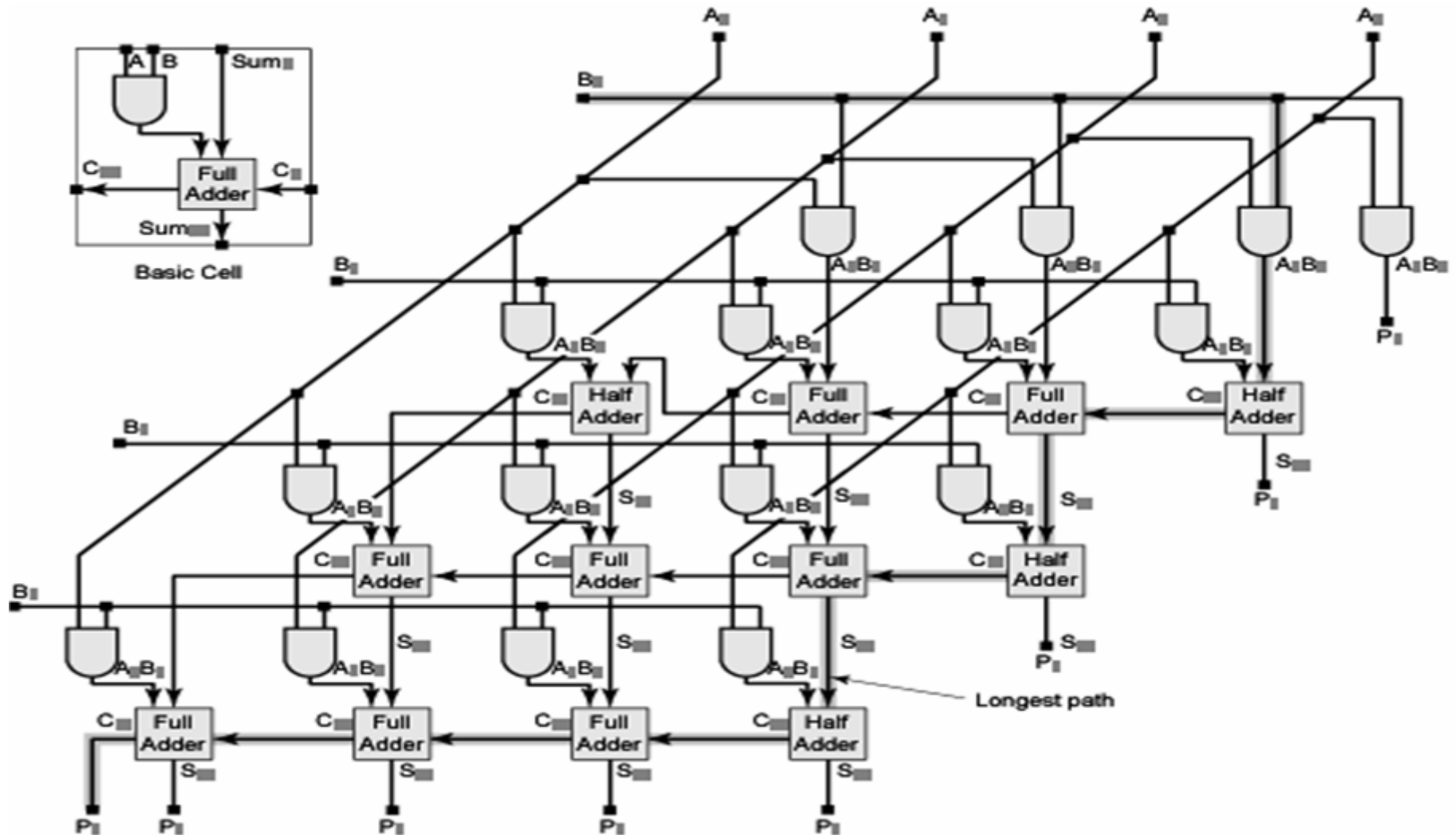


Fig 10-12 steps in the multiplication of unsigned 4-bit binary words

				A3 B3	A2 B2	A1 B1	A0 B0	Multiplicand Multiplier
				A ₃ B ₀ A ₂ B ₁ C ₁₁	A ₂ B ₀ A ₁ B ₁ C ₁₀	A ₁ B ₀ A ₀ B ₁	A ₀ B ₀ S ₀₀	Partial Product 0 Partial Product 1 1st Row Carries
				S ₁₃ A ₃ B ₂ C ₂₂	S ₁₂ A ₂ B ₂ A ₁ B ₂ C ₂₀	S ₁₁ A ₀ B ₂	S ₁₀	1st Row Sums Partial Product 2 2nd Row Carries
				S ₂₃ A ₃ B ₃ C ₃₁	S ₂₂ A ₂ B ₃ A ₁ B ₃ C ₃₀	S ₂₁ A ₀ B ₃	S ₂₀	2nd Row Sums Partial Product 3 3rd Row Carries
C ₃₃	S ₃₃	S ₃₂	S ₃₁	S ₃₀				3rd Row Sums
P ₇	P ₆	P ₅	P ₄	P ₃	P ₂	P ₁	P ₀	Final Product
2 ⁷	2 ⁶	2 ⁵	2 ⁴	2 ³	2 ²	2 ¹	2 ⁰	Weight



An array structure of glue logic ,half adder ,and full adder for a 4-bit binary





The Array Multiplier


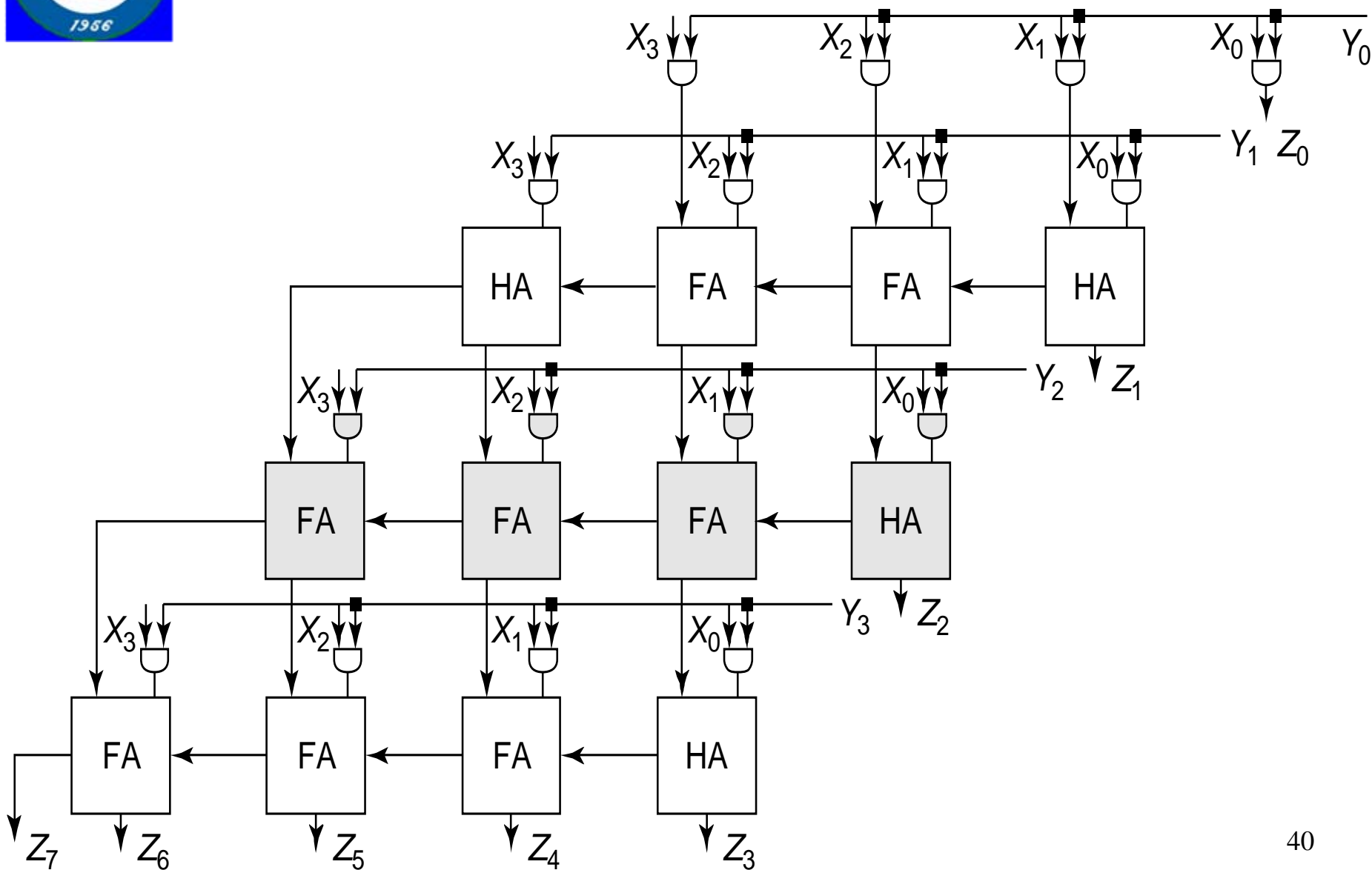


 

Fig 1-14 A systolic array structure for a 4-bit binary multiplier





The tradeoff for area and performance

- Both the carry and sum paths of the adders affect the longest path, and **balanced delays through them are desirable**
- The area of the device is relatively large, compared to other realizations, such as the sequential multipliers that will be considered
- But **the extra area is the price of the superior performance of the combinational multiplier.**




10.3.2 Sequential Binary Multiplier

- If area is an important consideration, it can be reduced at the expense of performance by scheduling the sub-operations of the multiplier to execute in successive clock cycles
- **The advantages of sequential multiplier:**
 - ① Compact, need fewer adders
 - ② Amenable to pipelining
 - ③ The silicon area dose not grow significantly with the word length
 - ④ The number of clock cycles grow in a linear manner, rather than exponentially



Fig 10-15 Interface signal of a sequential 8-bit binary multiplier

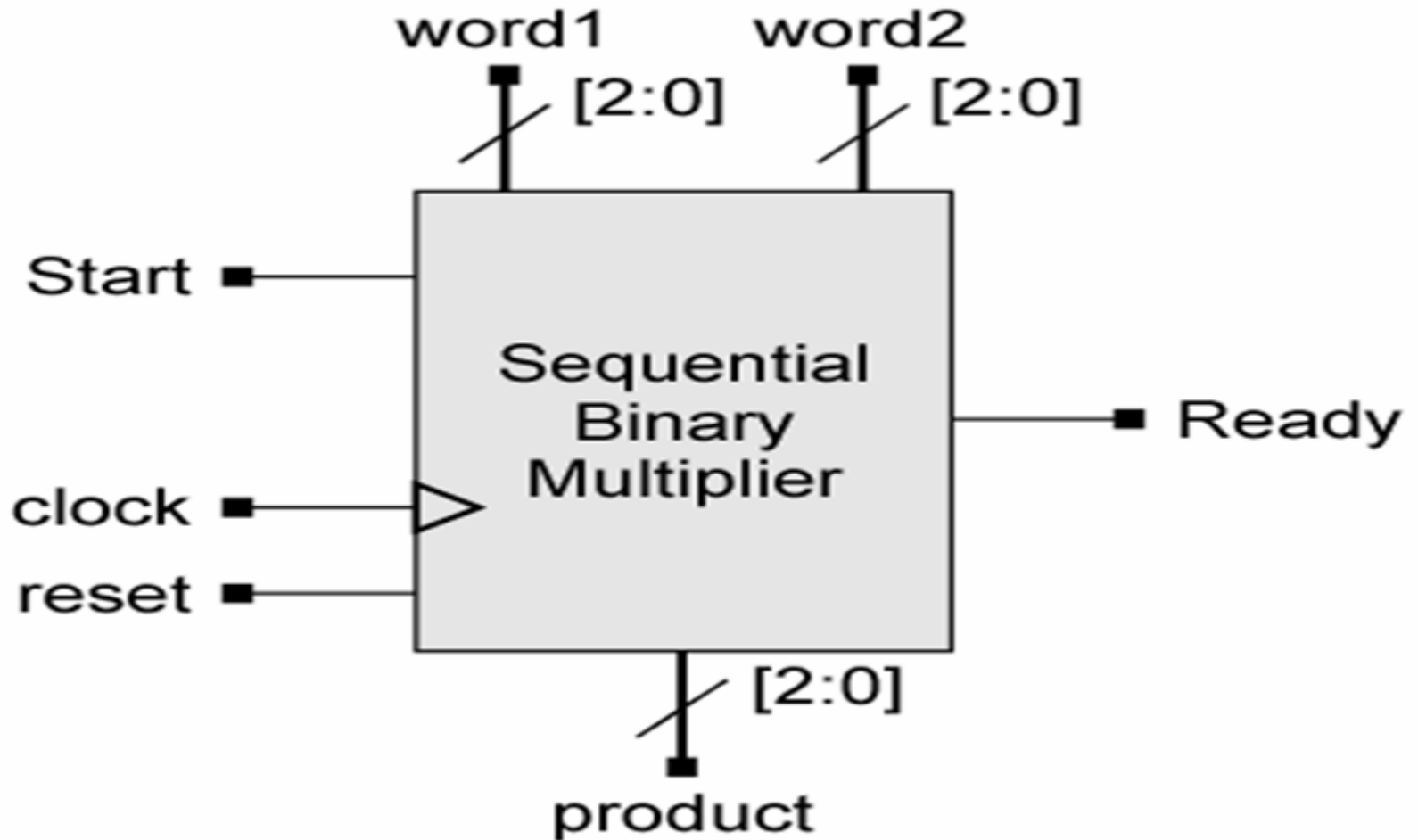




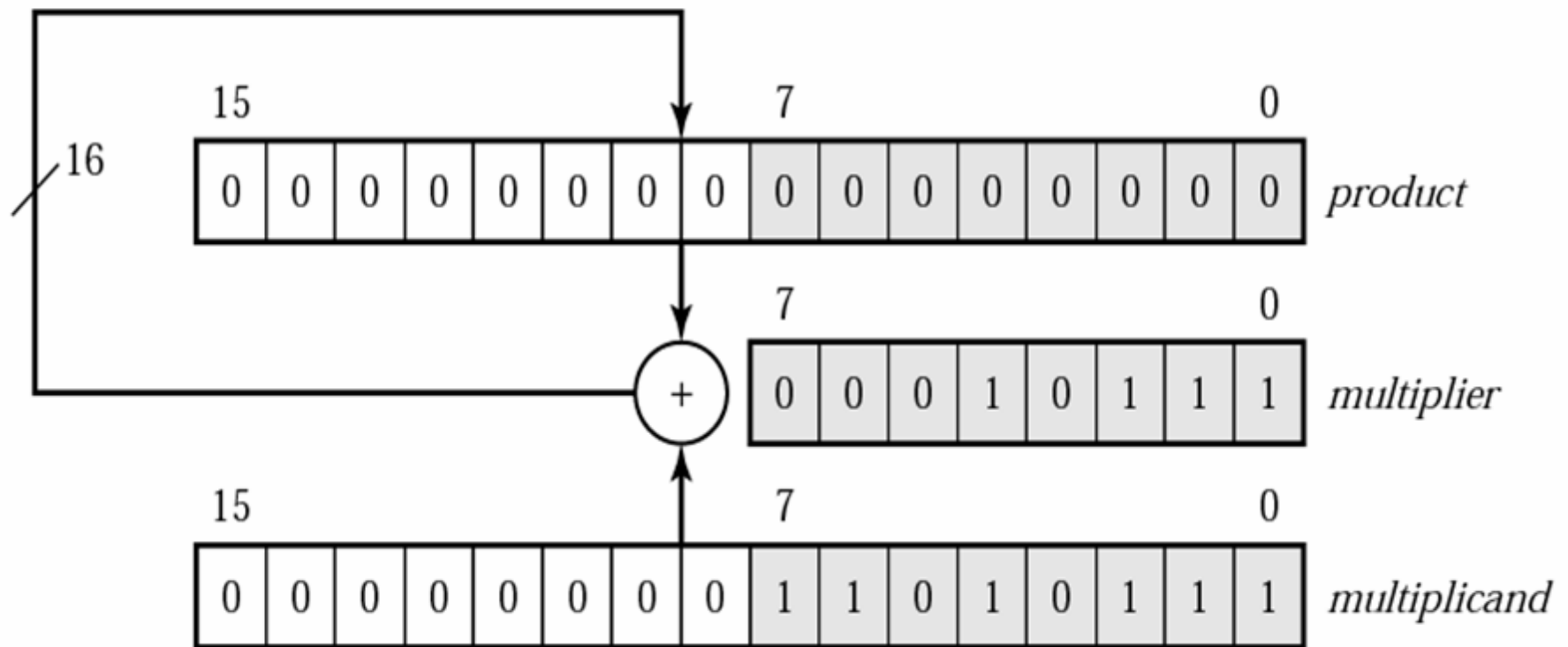10.3.3 Sequential Multiplier Design: Hierarchical Decomposition

- The method for designing a sequential binary multiplier has **two main steps**:
 - (1) **choose a datapath architecture** and
 - (2) **design a state machine to control the datapath**
- For a given datapath architecture, the state machine must generate the appropriate sequence of control signals to direct the movement of data to produce the desired product




Datapath architecture of a sequential 8-bit binary multiplier






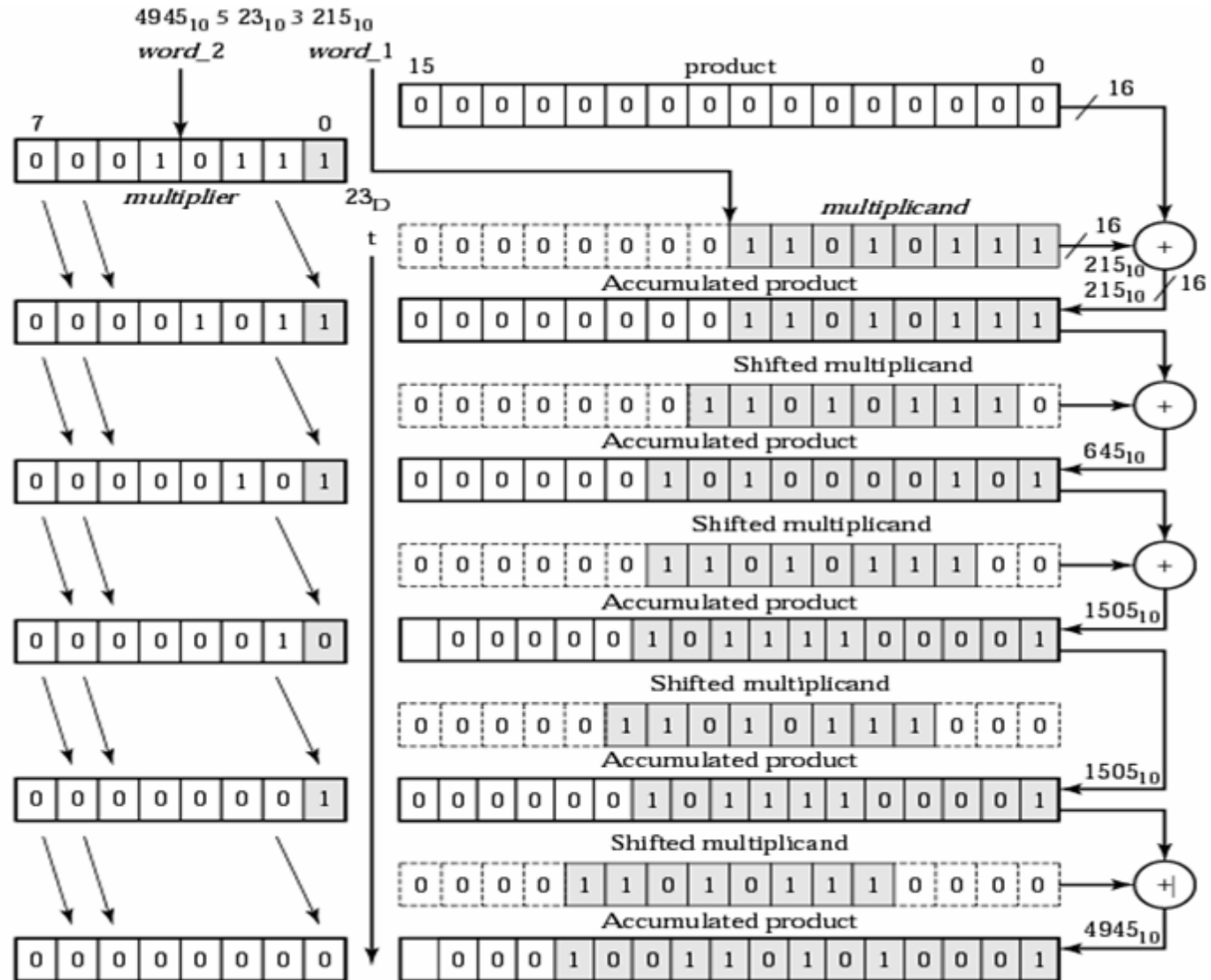Register transfers in an 8-bit sequential binary multiplier





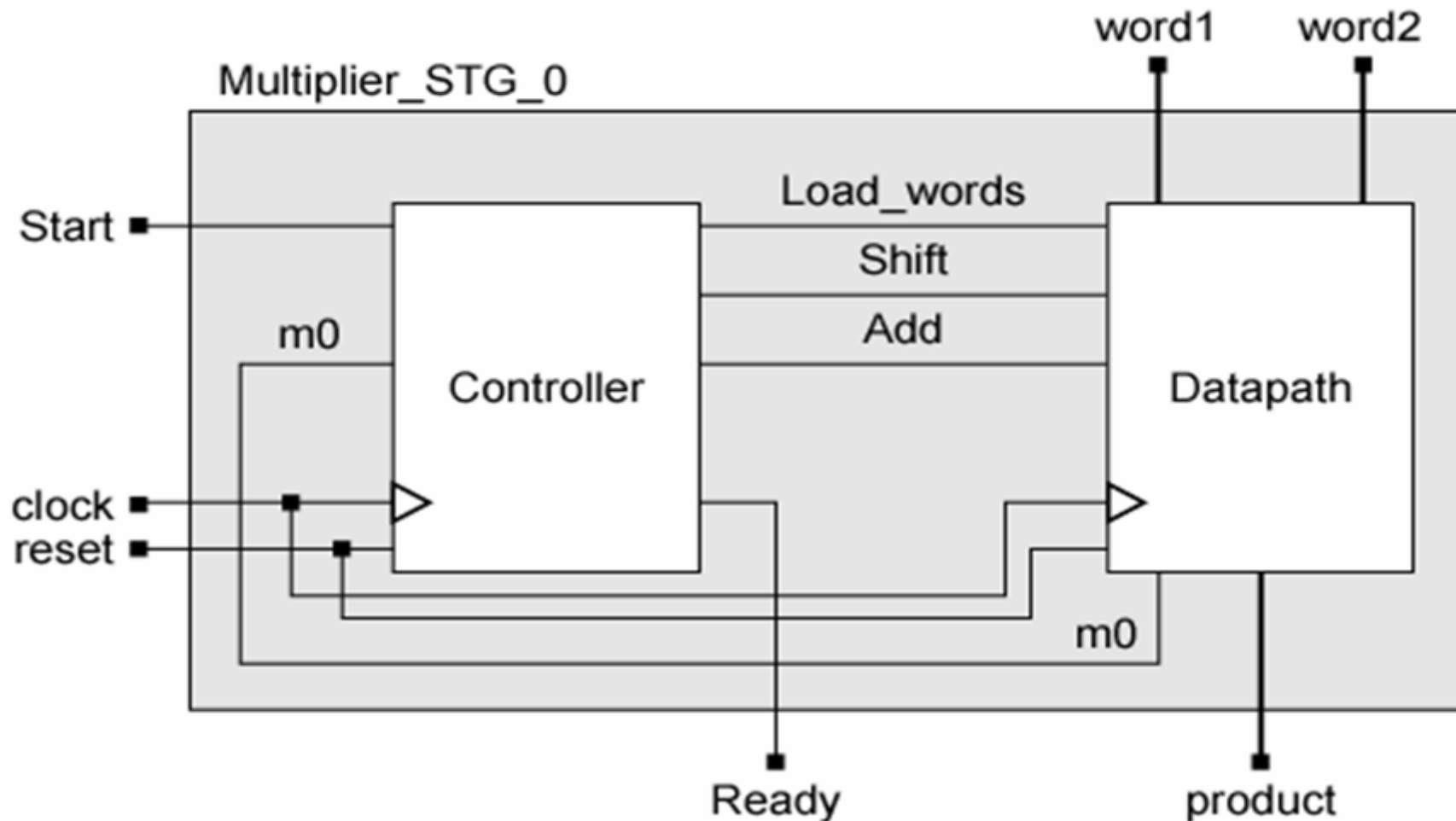Structure units of a partitioned sequential binary multiplier: The datapath and controller of the Verilog structural





10.3.4 STG-Based Controller Design

- Use state-transition graphs (STGs) to specify the state transitions of the controller
- Two kinds of design methods for controllers:
- STG-Based Controller Design
- ASMD-Based Sequential Binary Multiplier



Fig 10-19 Alternative STGs for a 4-bit sequential binary multiplier:

two versions of a STG for the controller, with different behavior in S_8


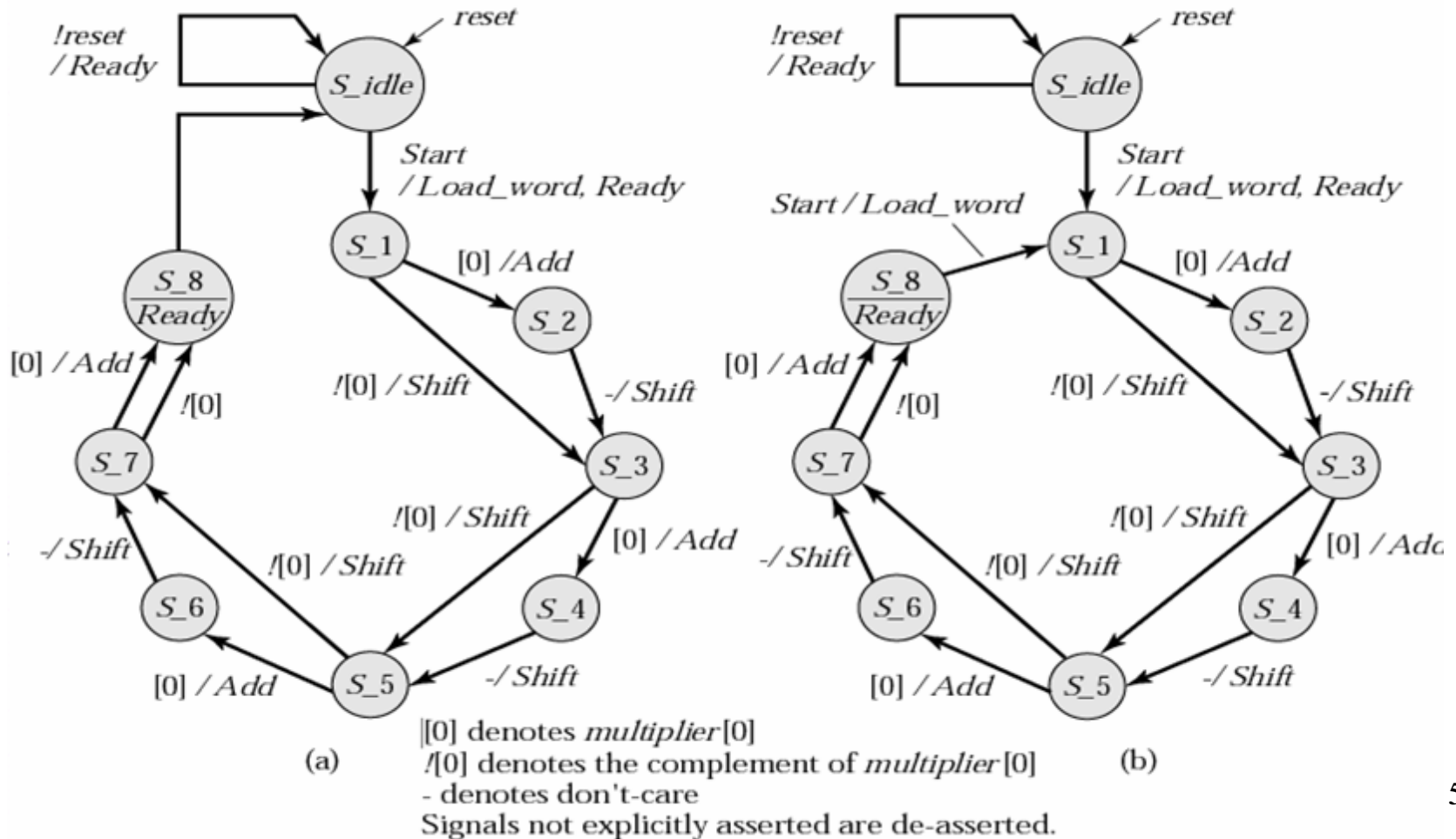


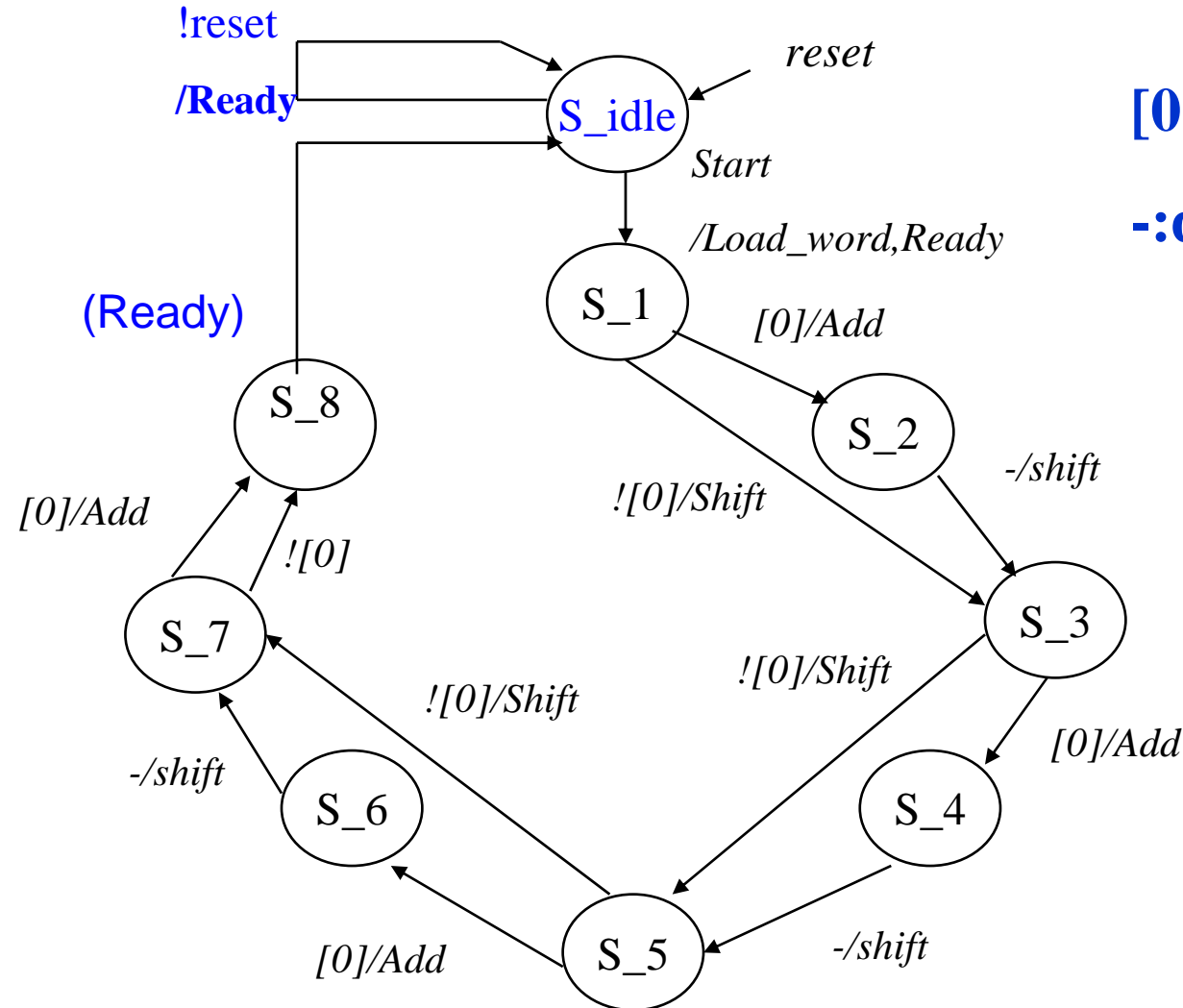

Fig 10-19(a) Machine return to S_idle upon completion



[0]: multiplier[0]

-:don't care



Example 10.1

- The Verilog **behavioral description of Multiplier_STG_0** is given, **along with a testbench** that contains an exhaustive **pattern generator** for word1 and word2, and **a comparator** that samples product and checks, while Done is asserted, whether product matches the expected value



```
module Multiplier_STG_0 ( product, Ready, word1,  
word2, Start, clock, reset);  
    parameter                                L_word = 4; // Datapath size  
    output      [2*L_word-1:0] product;  
    output      Ready;  
    input       [L_word-1:0] word1,word2;  
    input       Start,clock,reset;  
    wire        m0,load_words,Shift;
```

Datapath

```
    M1(product,m0,word1,word2,Load_words,Shift,Add,  
        clock,reset);
```

Controller

```
    2(Load_words,Shift,Add,Ready,m0,Start,clock,reset);  
endmodule
```



```
module Controller ( Load_words, Shift, Add
                    Start, clock, reset );
```

```
    Parameter          L_word=4; // Datapath si;
```

```
    Parameter          L_state=4;
```

```
    output              Load_words,Shift,Add,Ready;
```

```
    Input               m0,Start,clock,reset;
```

```
    reg    [L_state-1:0]    state,next_state;
```

```
    parameter             S_idle=0,S_1=1,S_2=2;
```


```
    parameter             S_3=3,S_4=4,S_5=5,S_6=6;
```

```
    parameter             S_7=7,S_8=8;
```

```
    reg                   Load_words,Shift,Add;
```

```
    wire
```

```
        Ready=((state==S_idle)&&!reset)||((state==S_8);
```

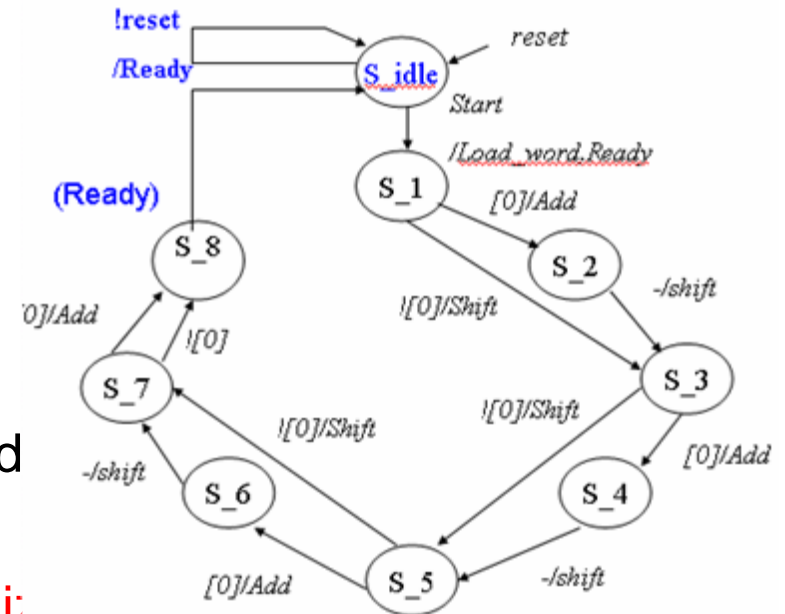



always @ (posedge clock or posedge reset)

if (reset) state <= S_idle; else state <= next_state;

always@ (state or Start or m0)

begin

Load_words=0;Shift=0;Add=0;

case(state)

S_idle: if(Start)

begin Load_words=1; next_state=S_1;**end**

else next_state=S_idle;

S_1: if(m0) **//m0=multiplier[0]**

begin Add=1; next_state=S_2;**end**

else

begin Shift=1;next_state=S_3; **end**

S_2: **begin** Shift=1; next_state=S_3; **end**

S_3: if(m0) **begin** Add=1; next_state=S_4; **end**

else **begin** Shift=1; next_state=S_5; **end**



```
S_5: if(m0) //m0=multiplier[0]
      begin  Add=1; next_state=S_6; end
      else
      begin  Shift=1; next_state=S_7; end
S_6:   begin  Shift=1; next_state=S_7; end
S_7:   if(m0)
      begin  Add=1; next_state=S_8; end
      else
      begin  Shift=1; next_state=S_8; end
S_8:   if(Start)
      begin Load_words=1;
           next_state=S_1; end
      else  next_state=S_8;
default: next_state=S_idle;
endcase
end
endmodule
```




```
module Datapath ( product, m0,  
    word1,word2, Load_words, Shift, Add, clock,  
    reset);  
    parameter    L_word=4;  
    output  [2*L_word-1:0]    product;  
    output                m0;  
    input  [L_word-1:0]    word1,word2;  
    Input  Load_words,Shift,Add,clock,reset;  
    reg [2*L_word-1:0]  product,multiplicand;  
    reg [L_word-1:0]    multiplier;  
    wire    m0=multiplier[0];
```



```
always@(posedge clock or posedge reset)
begin
    if(reset)
        begin multiplier<=0; multiplicand<=0;
            product<=0; end
    else if (Load_words)
        begin multiplicand<={4'b0,word1};
            multiplier<=word2; product<=0;end
    else if (Shift)
        begin multiplier<=multiplier>>1;
            multiplicand<=multiplicand<<1; end
    else if(Add)
        product<=product+multiplicand;
end
endmodule
```




10.3.5 Efficient STG-Based Sequential Binary Multiplier

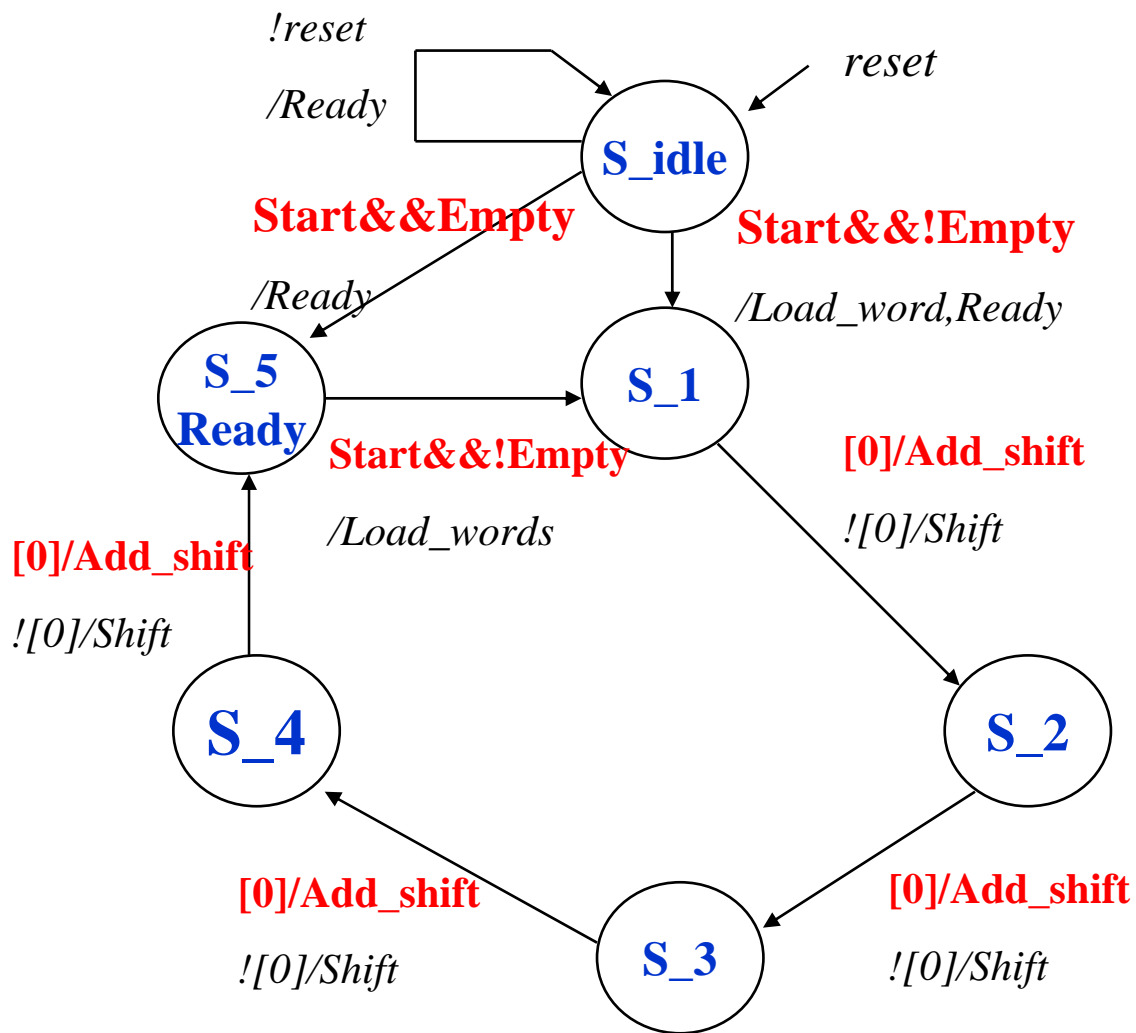- The sequential multiplier, Multiplier_STG_0, is **inefficient**, because it executes **the add and shift operations in separate clock cycles**
- If the architecture is modified **to direct the output of the adder** to the appropriate bits of the product register, **the operations can execute in the same cycle**

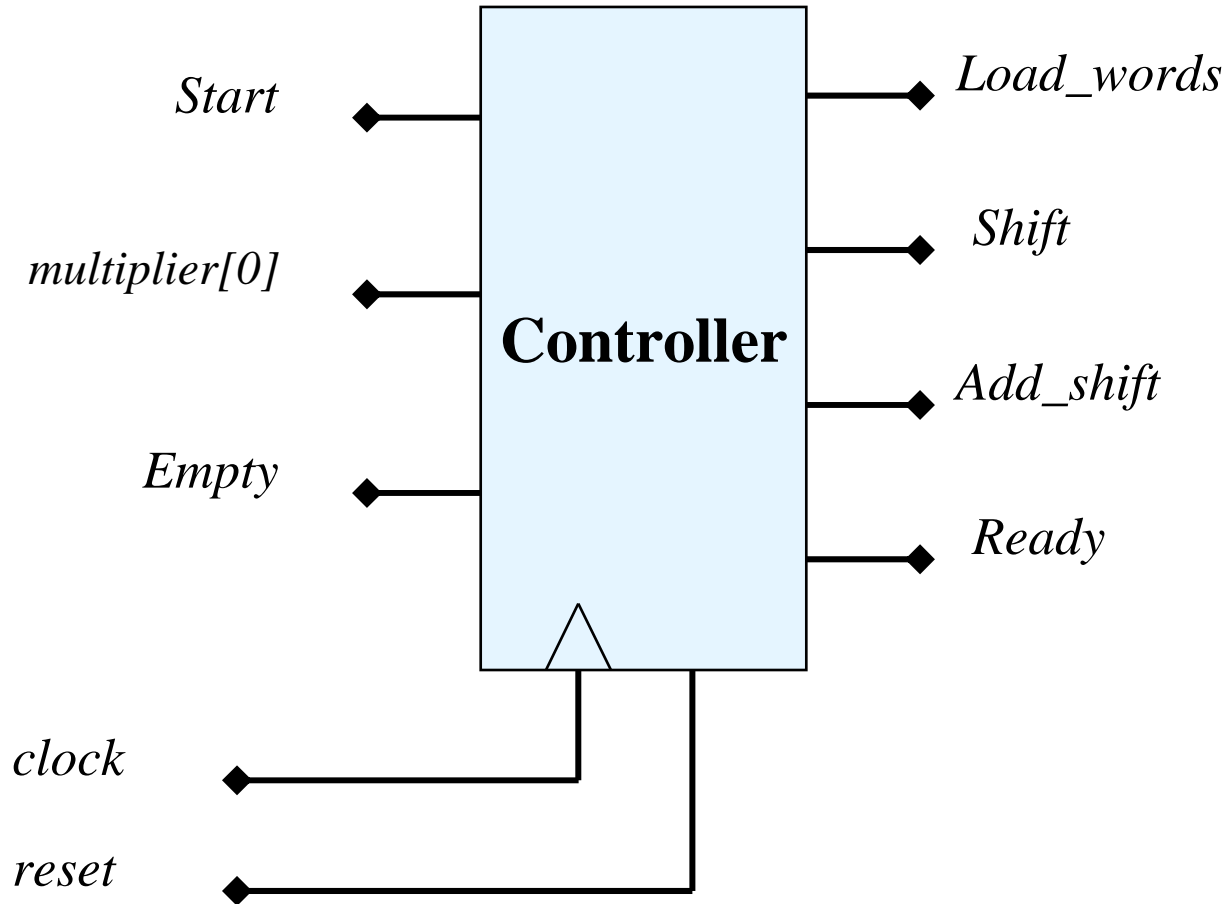


Figure 10-22 STG for the controller of an efficient sequential multiplier





STG and block diagram symbol for the controller of an efficient sequential multiplier





10.3.6 ASMD-Based Sequential Binary Multiplier

- STGs are convenient tools for designs that have only a few states, but **are cumbersome when the number of states is large**
- In STG-based design ,for longer words, additional code must be inserted for each new bit to handle additional state transitions.
- **ASMD charts facilitate scalable, portable, and re-usable designs.**


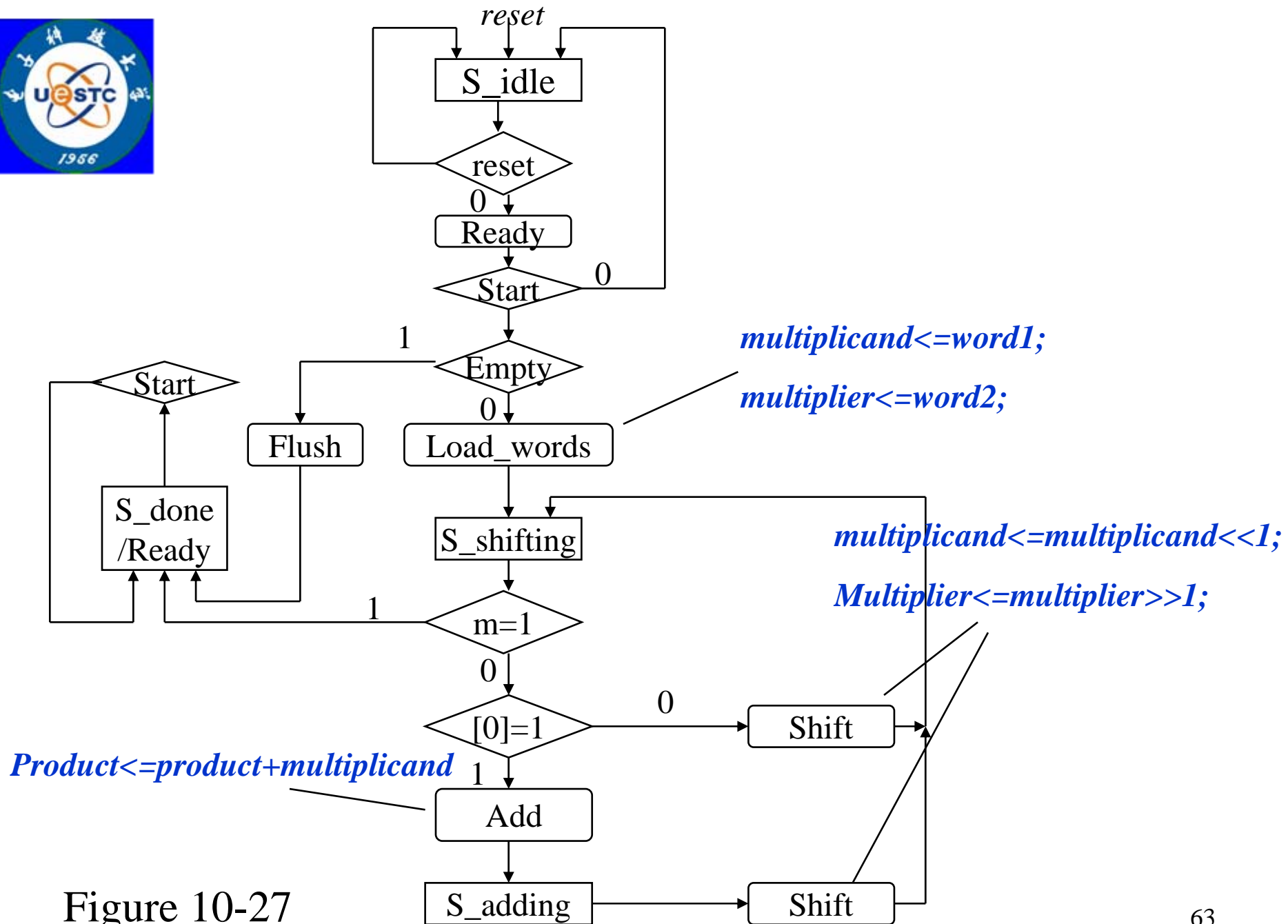


Figure 10-27

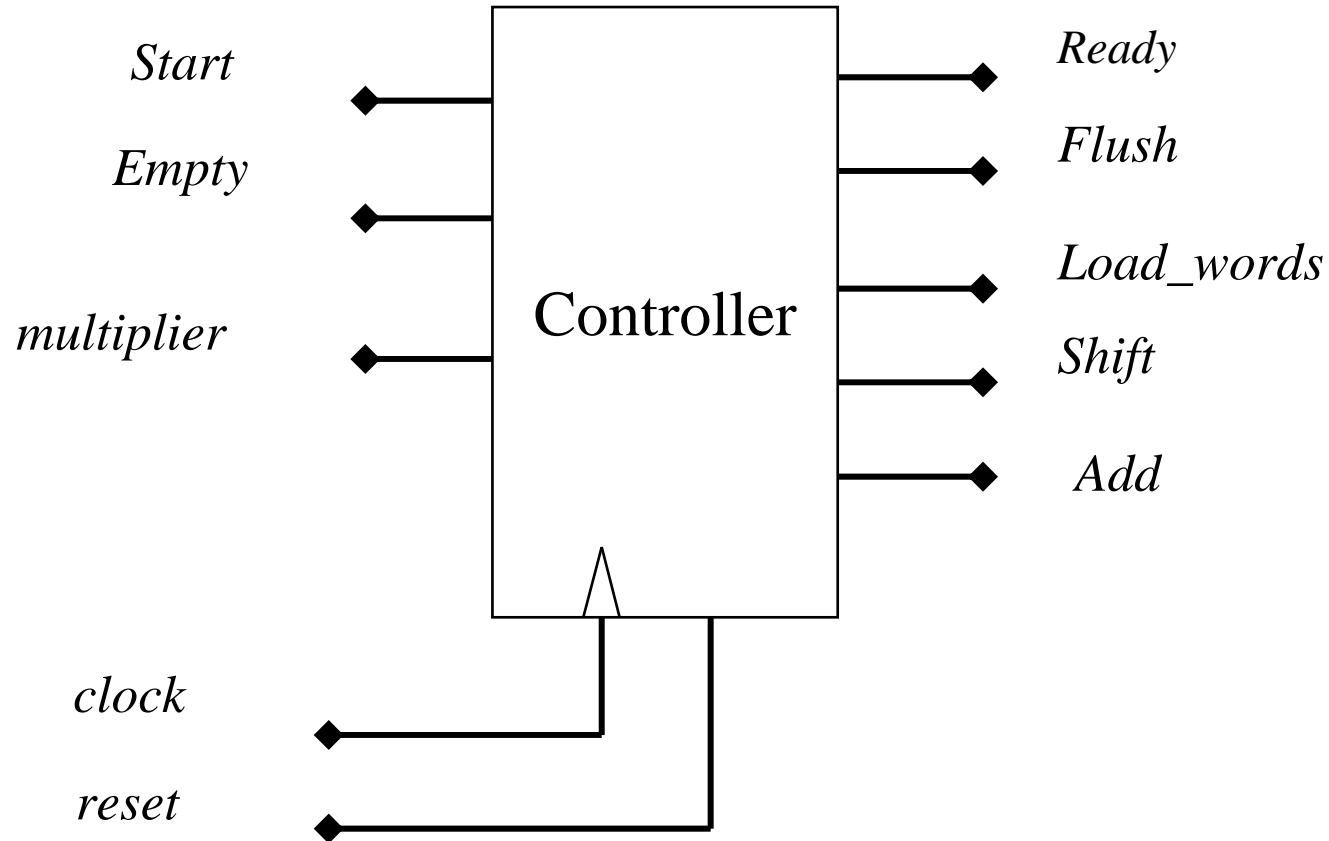

Start is decoded with higher priority than *Empty*






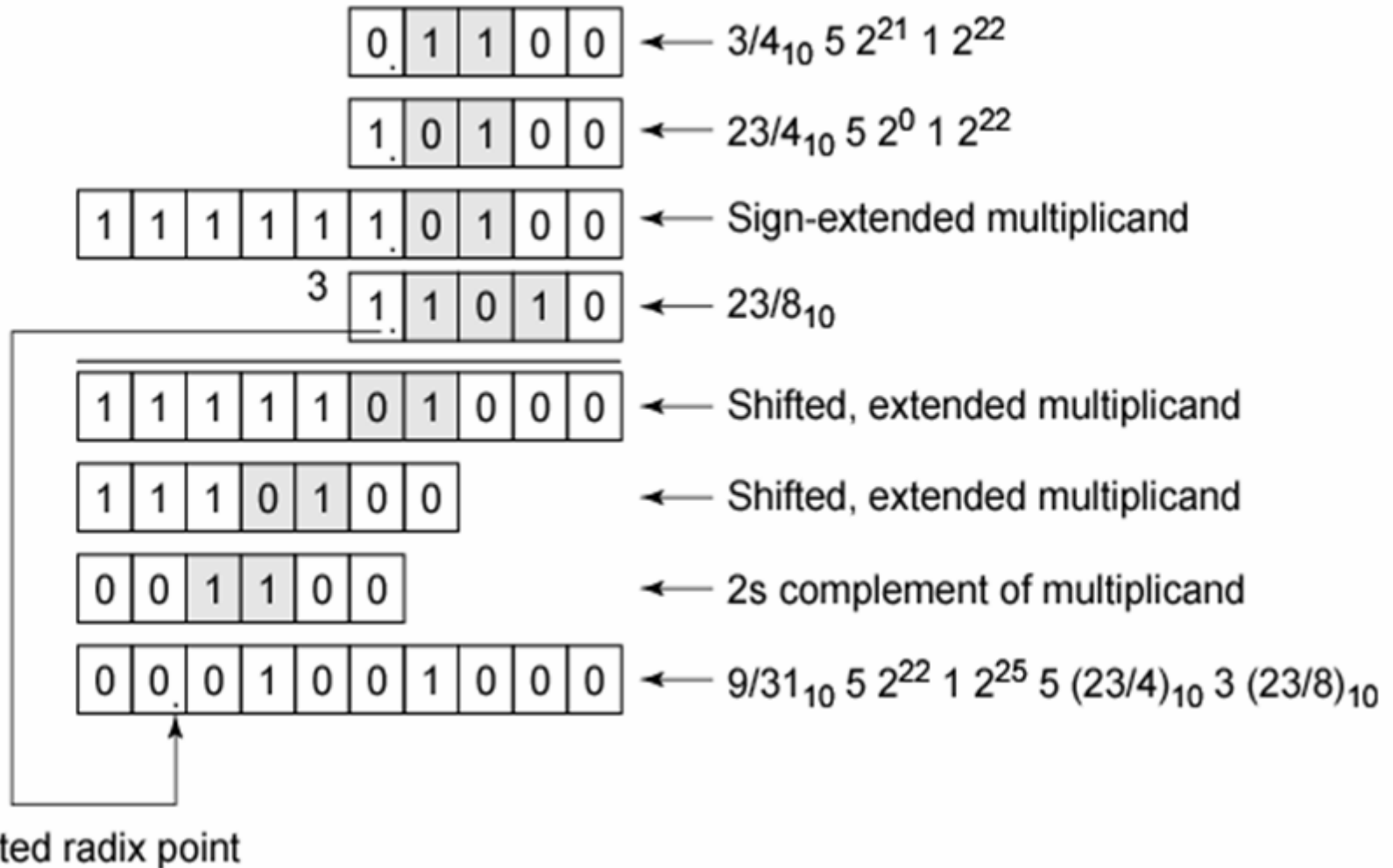10.6 Functional Units for Division

- Sequential multipliers use an add-and-shift algorithm to form the product of two words
- We will consider various architectures for sequential dividers that use a subtract-and-shift algorithm to form a quotient of two numbers.




A sequential algorithm for dividing two unsigned binary numbers





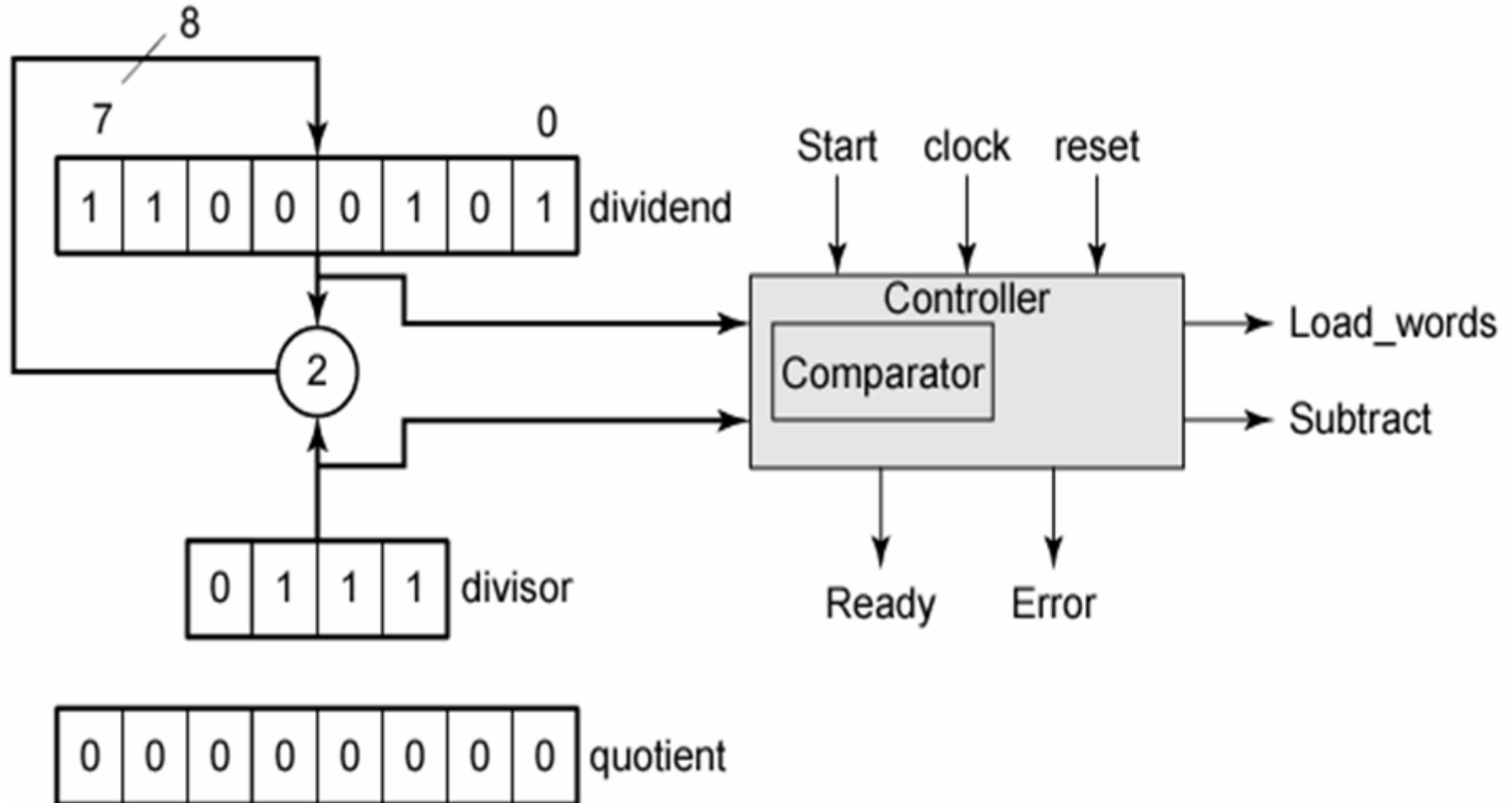Architecture of a simple binary divider unit





P10-1. The 4-bit multiplier shown in Figure 10-13 can be modified to exploit a 4-bit carry look-ahead adder instead of a ripple-carry adder. Compare the performance and area of the two models

